

**ELECTRICAL AND ELECTRONICS  
FOR DESIGN  
(SRSD 3092)  
Semester II 2019/2020**

**(INTRODUCTION)  
Week 1-1**

*Prepared by : DR NELIDYA MD YUSOFF*

# Lecturers

Lecturer	:	Dr Nelidya Md Yusoff / Dr Mohd Nabil Mukhtazaruddin
Room No.	:	Menara Razak
Telephone No.	:	03-21805265 / 03-21805266
E-mail	:	<a href="mailto:nelidya.kl@utm.my">nelidya.kl@utm.my</a> / <a href="mailto:mnabil.kl@utm.my">mnabil.kl@utm.my</a>

## Synopsis


This course introduces basic electrical and electronics for non-electrical students. The topic covers direct current (DC), alternating current (AC), basic semiconductor device such as PN Junction diodes, zener diode and bipolar transistor. Furthermore, it also covers the application of diode in series and parallel configuration, DC analysis for simple BJT circuit configuration.

# INTRODUCTION

- **Two credits** – 2 Hours/week
- **Timetable:** Wednesday – 2 hours (9 – 11 am)  
Bilik Kuliah 8, Level 14
- **Text Book:** Fundamentals of Electric Circuits by C.K.Alexander
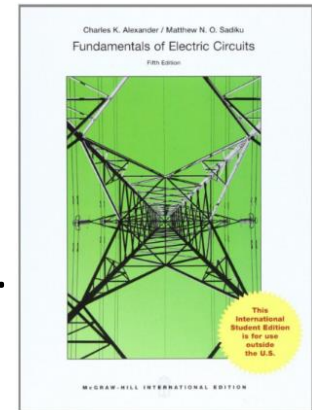
## References:

- Worked Example In Electrical Technology, B.L.Thejara.
- Electrical Technology, Seventh Edition, Hughes, Edward, Longman.
- Electrical Machinery, Ryff, Peter F, Prentice Hall.
- Schaum Outline Series, Electric Circuits, McGraw Hill.



# Course Outcome


No.	Course Learning Outcome	Programme Learning Outcome(s) Addressed	Assessment Methods	KPI
1.	Recognize the basic operations of electronic devices.	PO1	Q,T, ASG, F	0.5
2.	Analyse circuitry with diode and BJT component	PO1, PO3	Q,T, ASG, F	0.5
3.	Apply basic electrical circuit laws and methods in analysing DC and AC circuit	PO1, PO3	Q,T, ASG, F	0.5
4.	Familiarize with the concept and operation principle of the DC machine. Be able to calculate simple calculations determining parameters associated with DC machine.	PO1	Q, ASG, F	0.5



# Assessment


No	Assessment	Number	% each	% total	Week
1	Test	2	20	40	7 and 13
2	Assignment	2	5	10	4,9 and 12
3	Quizzes	4	2.5	10	3,6,11 and 15
4	Final Exam	1	40	40	
	Overall Total			100	

# Course Contents

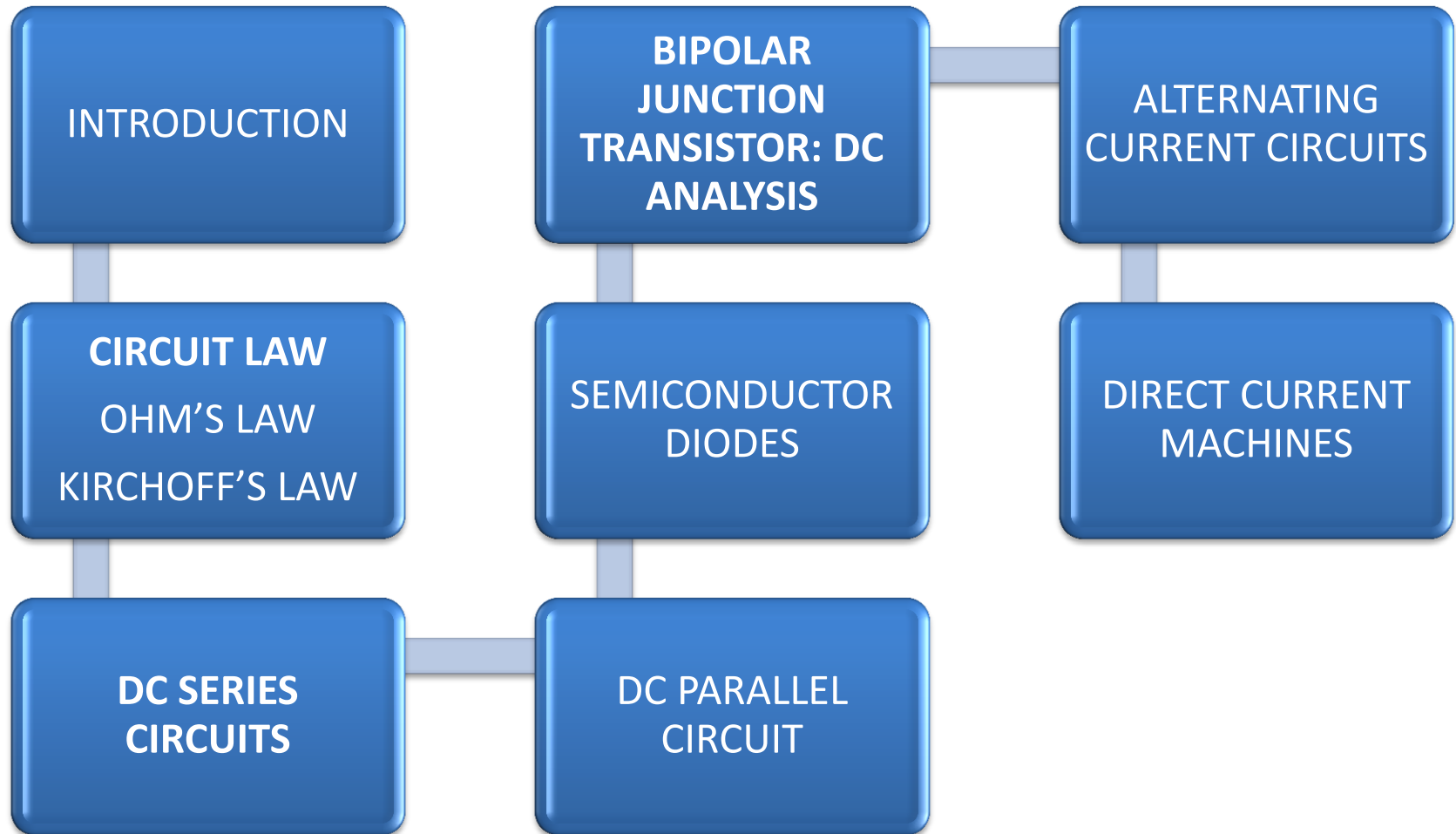

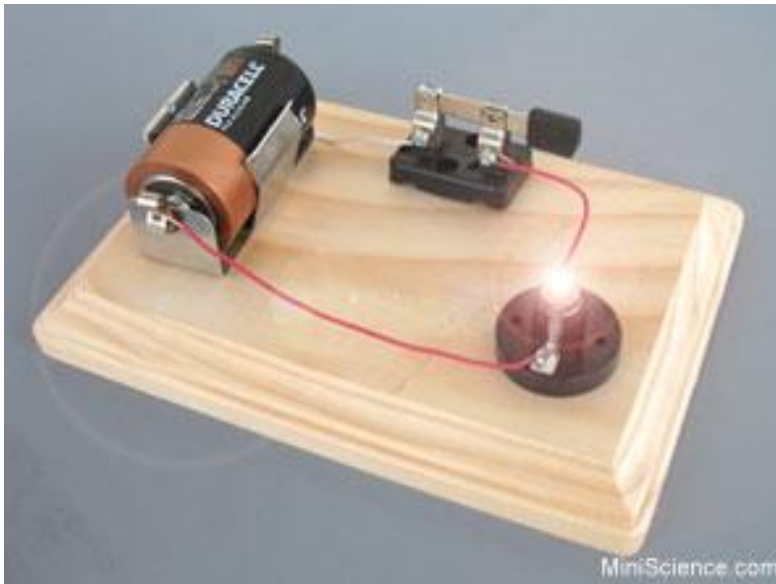
# BASIC CIRCUIT CONCEPTS

An **electric circuit** is formed by **interconnecting components** having **different electric properties**



Basic Electrical Circuit (Diagram)

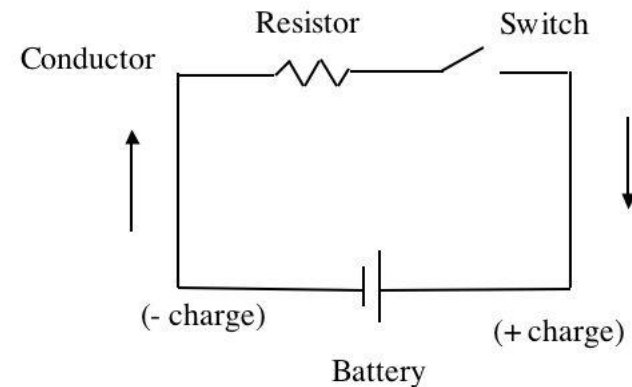

# Home Appliances




**ELECTRICAL AND ELECTRONICS  
FOR DESIGN  
(SRSD 3092)  
Semester II 2019/2020**

**(Basic Electric Circuit)  
Week 1-2**

*Prepared by : DR NELIDYA MD YUSOFF*

# What is a circuit?

Interconnection of electrical elements

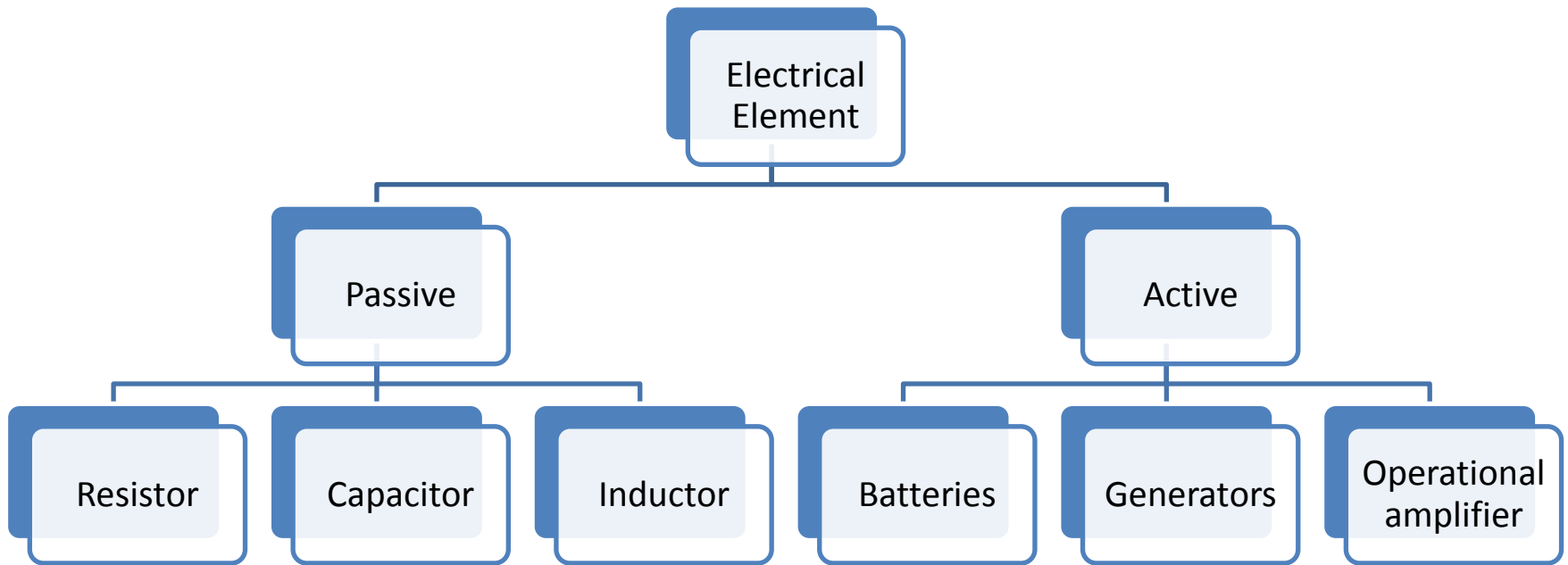

**Function: To transfer energy from one point to another**

# Passive and Active Elements

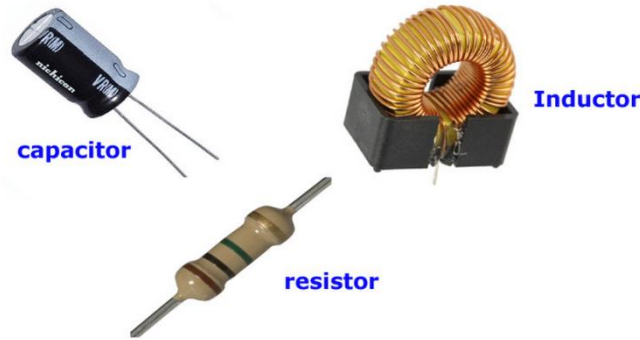


Figure: passive elements



**Passive Element**

Drop Energy (Take energy from circuit)

**Active Element**

Generate Energy

# Circuit Element Symbols


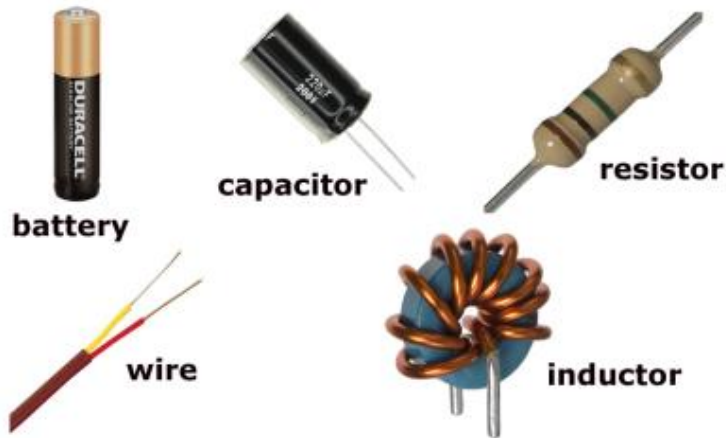



Figure: Some practical circuit element

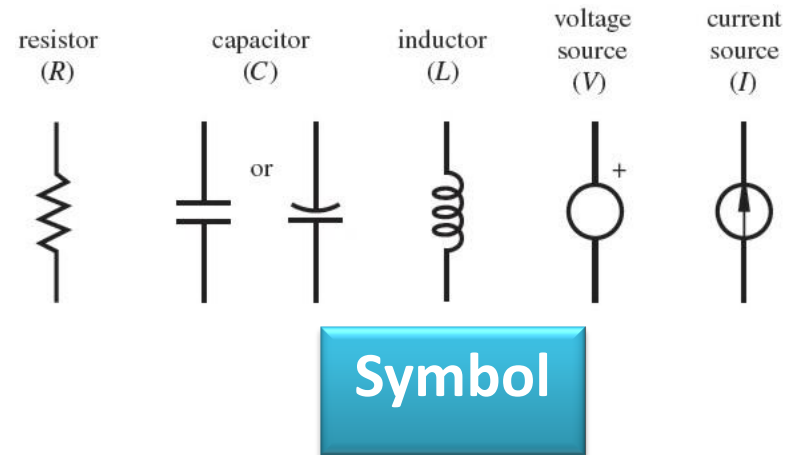



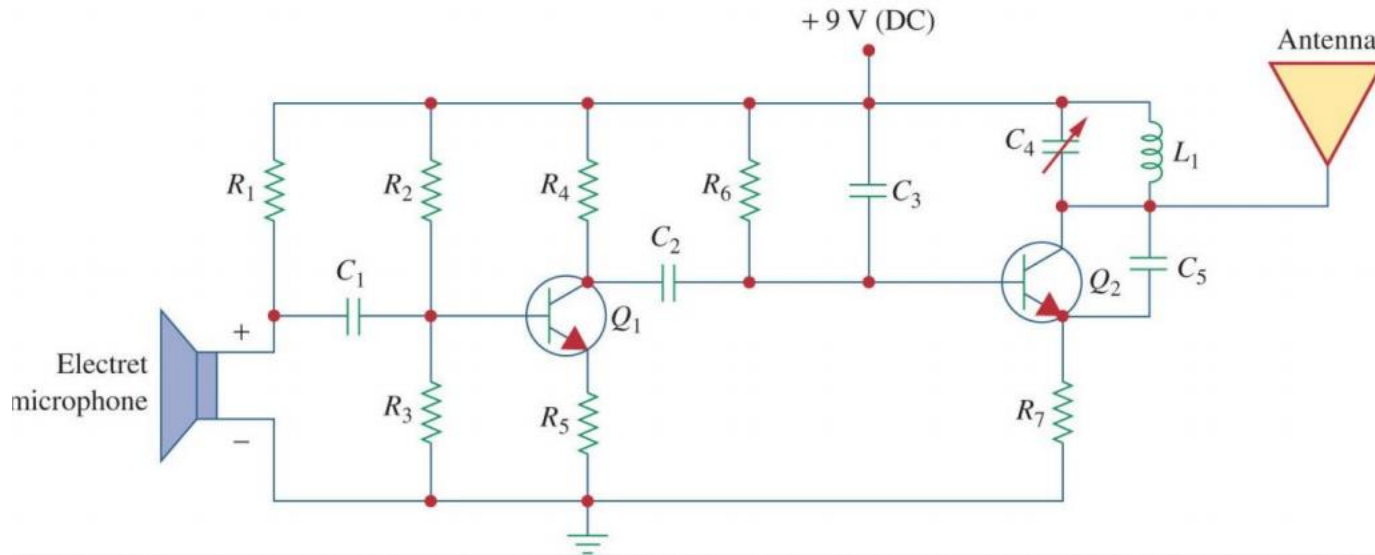
# Example of Electric Circuit

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



# Basic Circuit Concepts

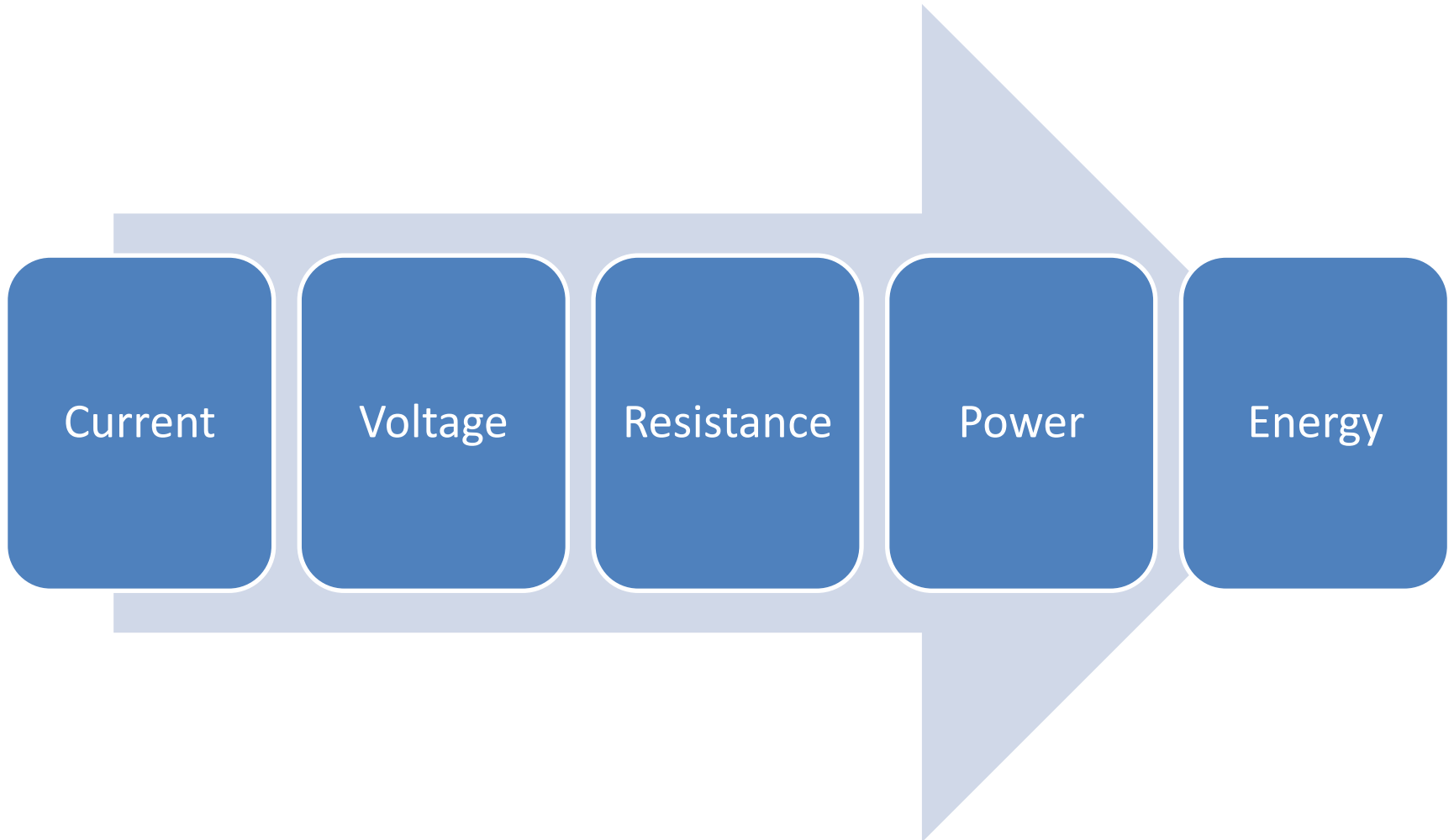

# Class Activity #1

## Numbered Head Together

Instruction:

Each group will get ONE topic

Discuss and present



Group	Topic
1	Current
2	Voltage
3	Resistance
4	Power

# Units

- When taking measurements, we must use units to quantify values

MEGA

KILO

MICRO

NANO

- Use International Systems of Units

+ measurement of length

**m**  
meter

+ measurement of mass

**kg**  
kilogram

measurement of pressure

**Pa**  
pascal

measurement of amount of substance

**mol**  
mole

measurement of force

**N**  
newton

+ measurement of Celsius temperature

**°C**  
degree Celsius

measurement of radioactivity



**Bq**  
becquerel

measurement of thermodynamic temperature

**K**  
kelvin

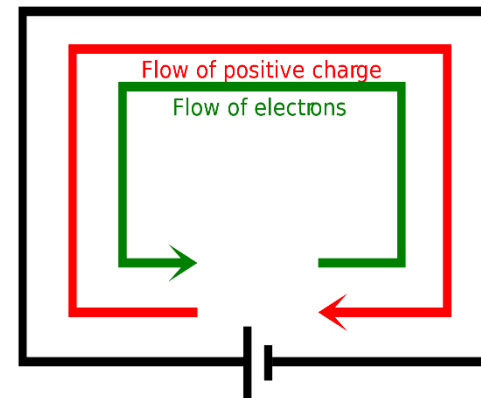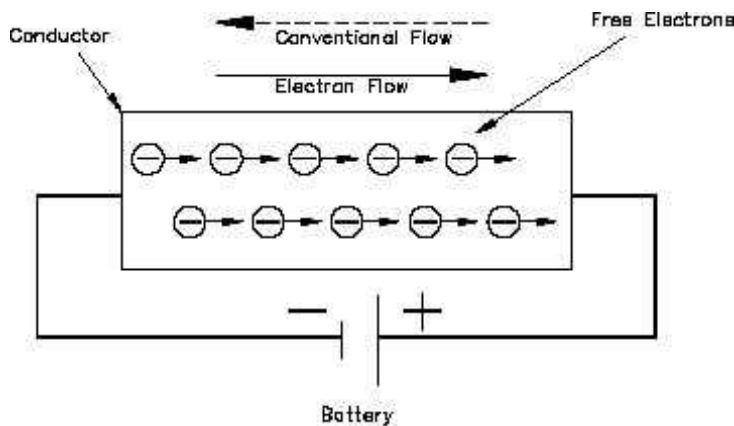
# CURRENT

- An **electric current** is a flow of **electric charge**. In **electric** circuits this charge is often carried by moving electrons in a wire. It can also be carried by ions in an electrolyte, or by both ions and electrons such as in a plasma.




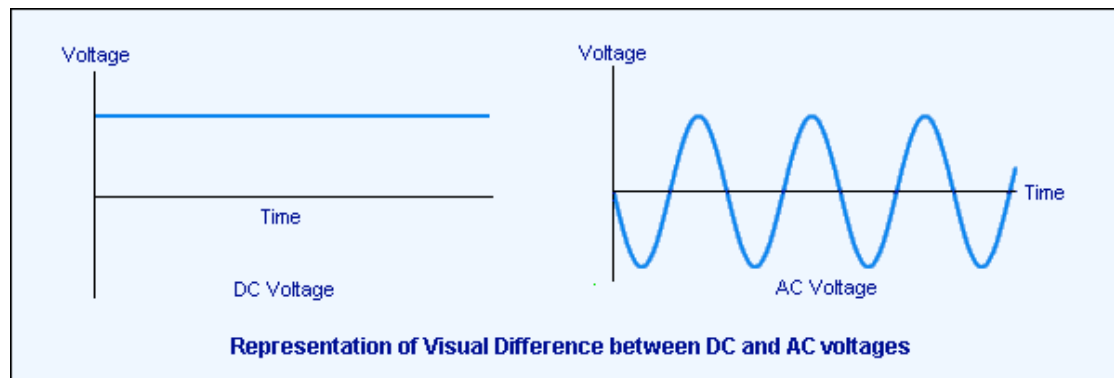
# Type of Currents

- **Two** types of current
- **Direct current (DC)** and **Alternating Current (AC)**
- DC: Common source – Battery
- AC: Common source – main power


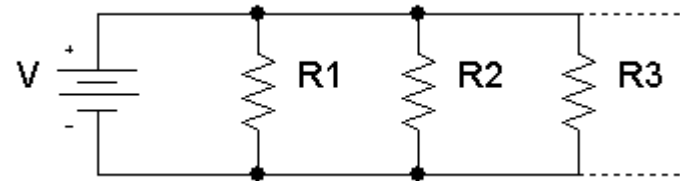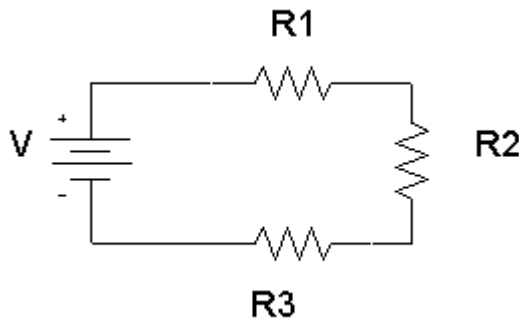
# RESISTANCE

- The electrical **resistance** of a circuit component or device is **defined** as the ratio of the voltage applied to the electric current which flows through it: If the **resistance** is constant over a considerable range of voltage, then Ohm's law,  $I = V/R$ , can be used to predict the behavior of the material.



# POWER

- The electric power in watts associated with a complete electric circuit or a circuit component represents the rate at which energy is converted from the electrical energy of the moving charges to some other form, e.g., heat, mechanical energy, or energy stored in electric fields or magnetic fields. For a resistor in a DC Circuit the power is given by the product of applied voltage and the electric current:

$$P = VI$$

where  $V$  = voltage

$I$  = current



# **ELECTRICAL AND ELECTRONICS FOR DESIGN (SRSD 3092) Semester II 2019/2020**

## **(Ohm's Law) Week 2-2**

*Prepared by : DR NELIDYA MD YUSOFF*

# Resistivity, R

- Materials tend to **resist** the flow of electricity through them.
- This property is called “**resistance**”
- The resistance of an object is a function of its length,  $l$ , and cross sectional area,  $A$ , and the material’s resistivity

$$R = \rho \frac{l}{A}$$

# Resistivity of Common Materials

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

**TABLE 2.1**

Resistivities of common materials.

Material	Resistivity ( $\Omega \cdot \text{m}$ )	Usage
Silver	$1.64 \times 10^{-8}$	Conductor
Copper	$1.72 \times 10^{-8}$	Conductor
Aluminum	$2.8 \times 10^{-8}$	Conductor
Gold	$2.45 \times 10^{-8}$	Conductor
Carbon	$4 \times 10^{-5}$	Semiconductor
Germanium	$47 \times 10^{-2}$	Semiconductor
Silicon	$6.4 \times 10^2$	Semiconductor
Paper	$10^{10}$	Insulator
Mica	$5 \times 10^{11}$	Insulator
Glass	$10^{12}$	Insulator
Teflon	$3 \times 10^{12}$	Insulator

# Resistors Colour Coding

**4 Band Resistor Color Coding**



COLOR	1ST BAND	2ND BAND	MULTIPLIER	TOLERANCE
BLACK	0	0	x1 $\Omega$	
BROWN	1	1	x10 $\Omega$	$\pm 1\%$
RED	2	2	x100 $\Omega$	$\pm 2\%$
ORANGE	3	3	x1000 $\Omega$	
YELLOW	4	4	x10000 $\Omega$	
GREEN	5	5	x100000 $\Omega$	$\pm 0.5\%$
BLUE	6	6	x1000000 $\Omega$	$\pm 0.25$
VIOLET	7	7	x10000000 $\Omega$	$\pm 0.10$
GREY	8	8		$\pm 0.05$
WHITE	9	9		
GOLD			0.1	$\pm 5\%$
SILVER			0.01	$\pm 10\%$



# Ohm's Law

The voltage,  $v$  across a resistor is directly proportional to the current,  $i$  flowing through the resistor.

$$V = IR$$


**Voltage [volts,  $v$ ] = current [amperes, A] x  
Resistance [ohms,  $\Omega$ ]**

# Ohm's Law

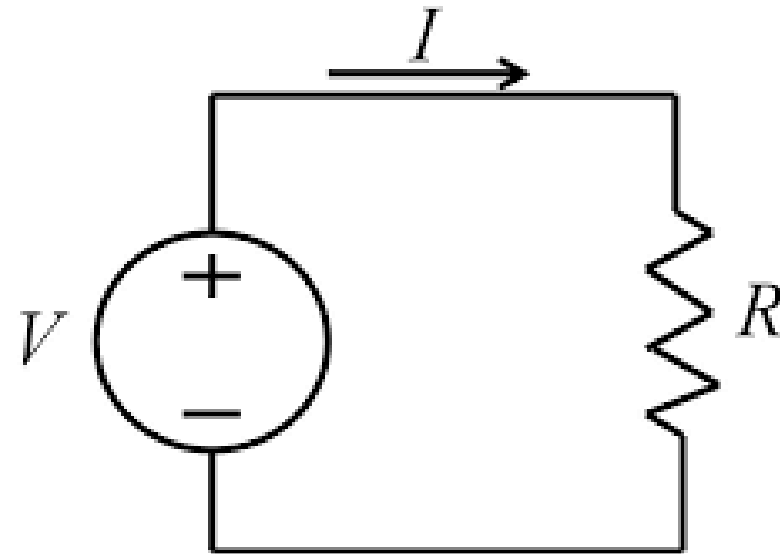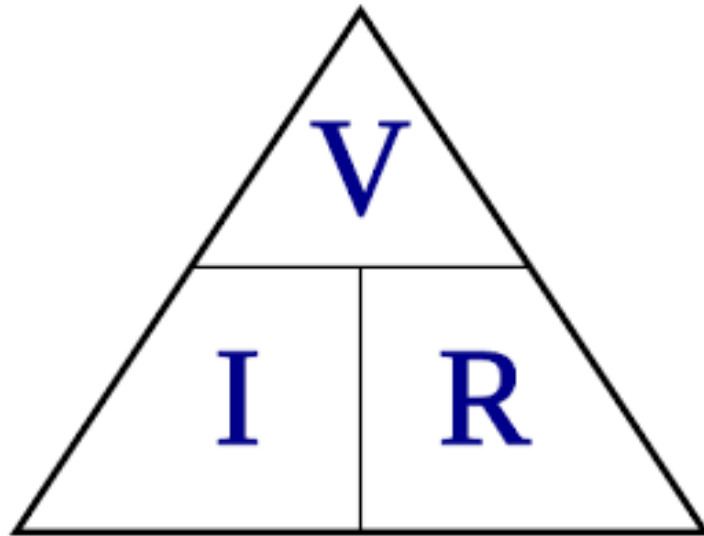


# Closed and Open Circuits

**Closed circuit**

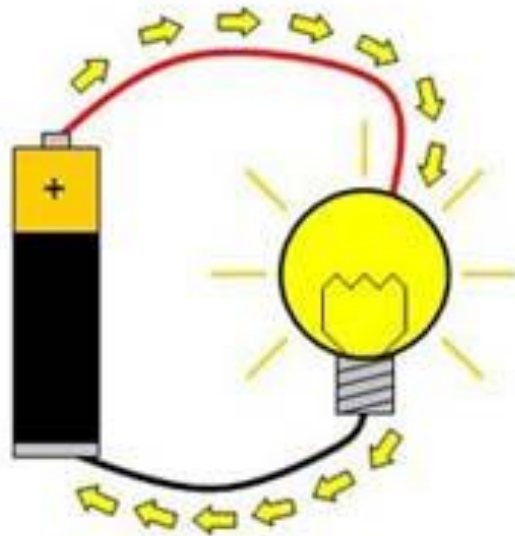


**Open circuit**

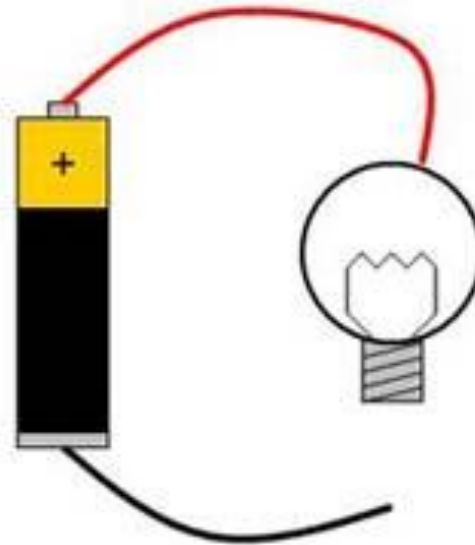

# Short Circuits

- Zero resistance
- Any current may flow through the short
- In practice this is a connecting wire

## Short circuit

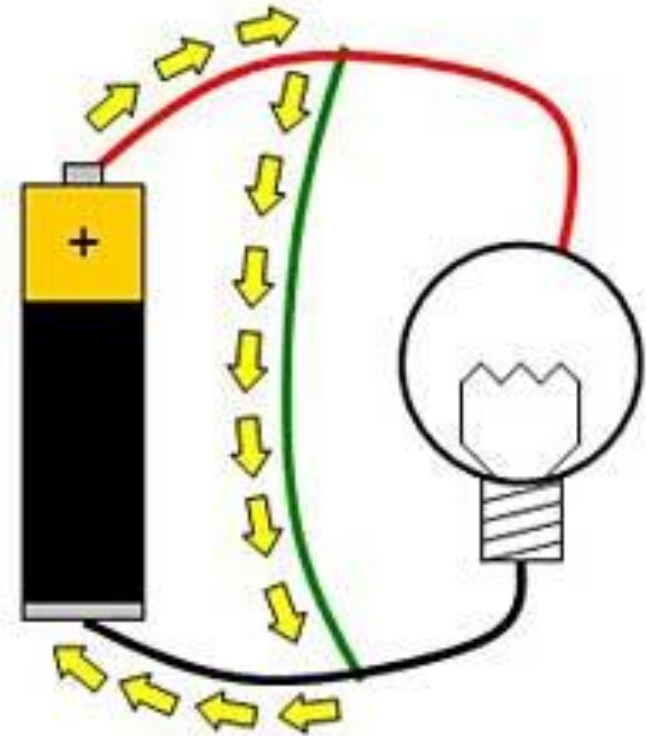



# Power Dissipation


- Running current through a resistor dissipates power.

$$p = vi = i^2 R = \frac{v^2}{R}$$

- The power dissipated is a non-linear function of current or voltage
- Power dissipated is always positive
- A resistor can never generate power

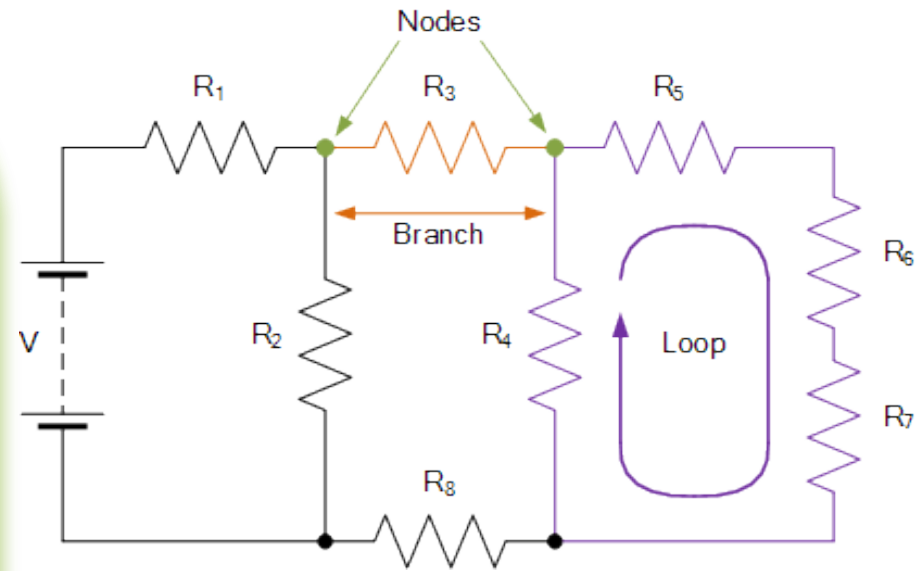
# Nodes, Branches and Loops

- **Branch:** a single element such as a voltage source or a resistor
- **Node:** The point of connection between two or more branches
- **Loop:** Any closed path in a circuit



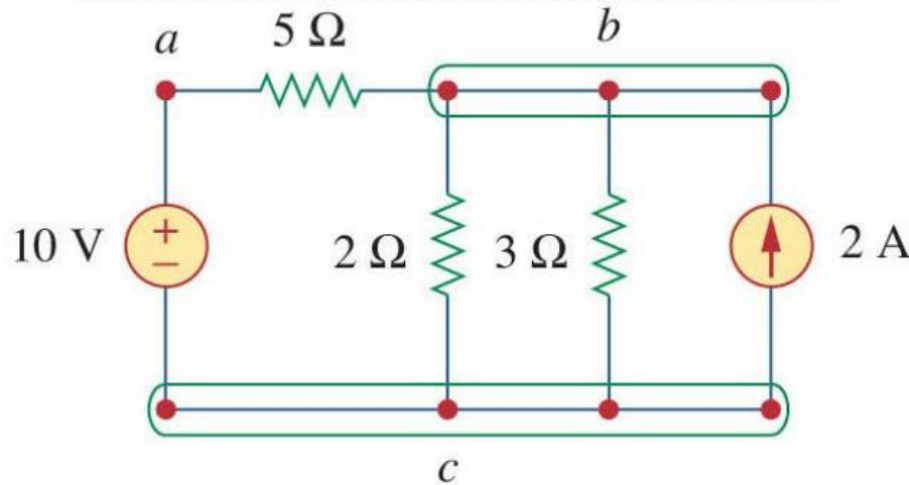
# Example of nodes, branches and Loops

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




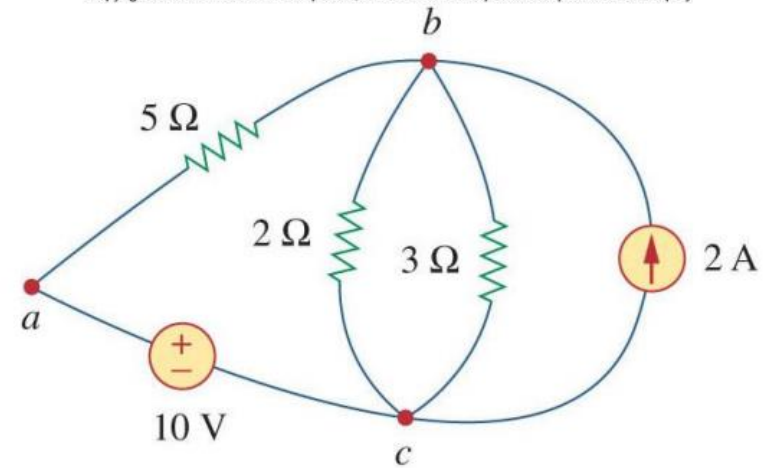
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



# Network Topology
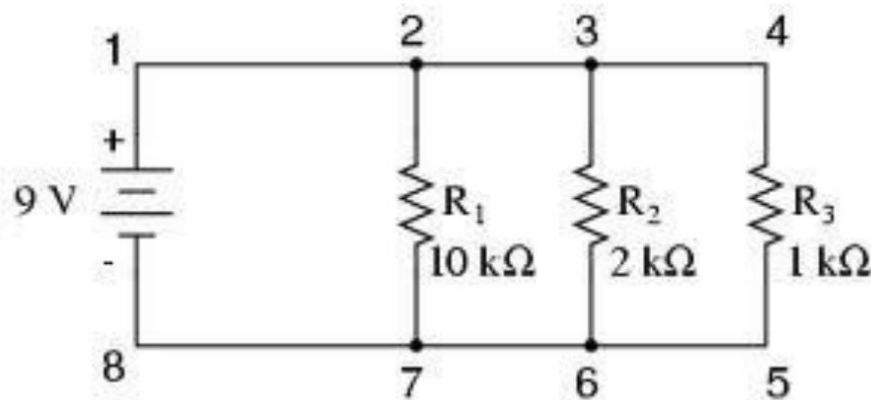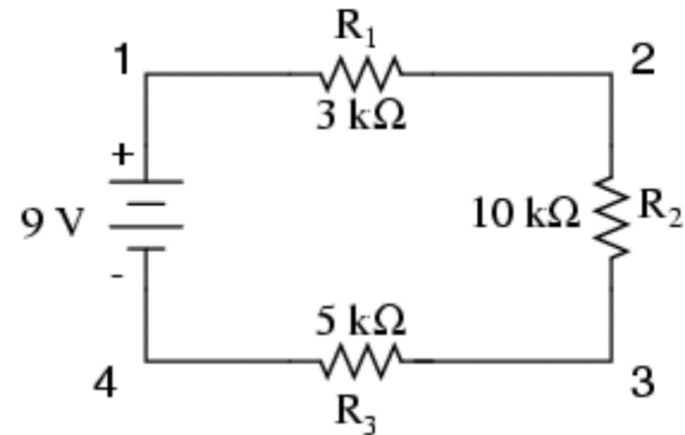
## Series:

- Share a single node
- Carry the same current




## Parallel:

- Connected to the same two nodes
- Same voltage
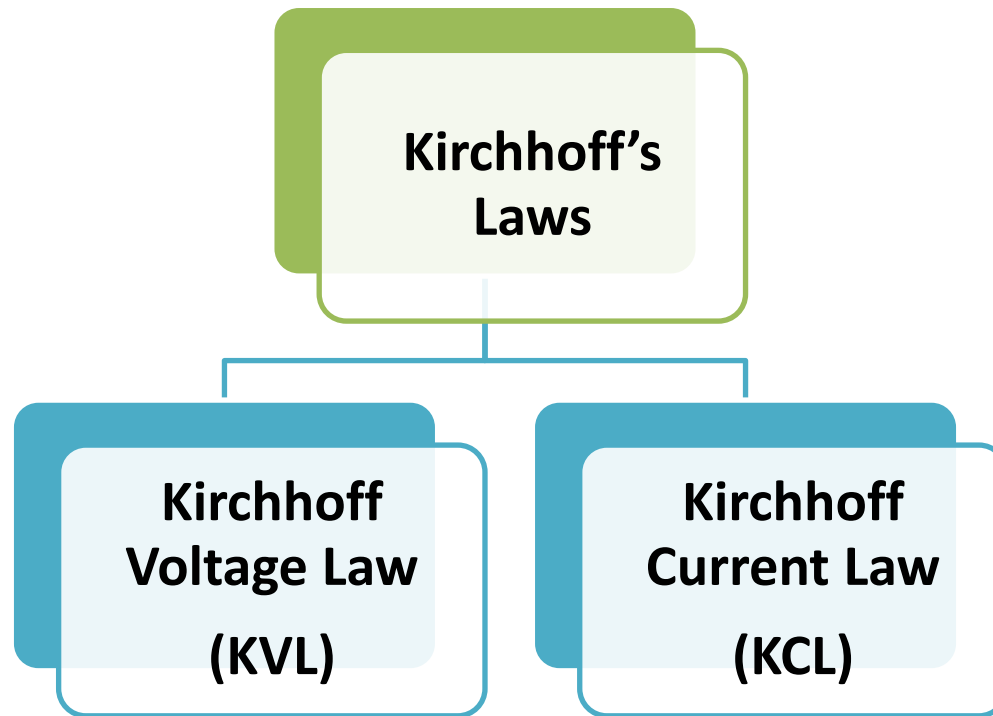
# Kirchhoff's Laws


- Ohm's law is not sufficient for circuit analysis
- Kirchhoff's laws complete the needed tools



# Kirchhoff Voltage Law (KVL)


- Kirchhoff's voltage law is based on **conservation of energy**
- It states that the algebraic **sum of voltages around a closed path (or loop) is zero.**
- It can be expressed as:

$$\sum_{m=1}^M v_m = 0$$

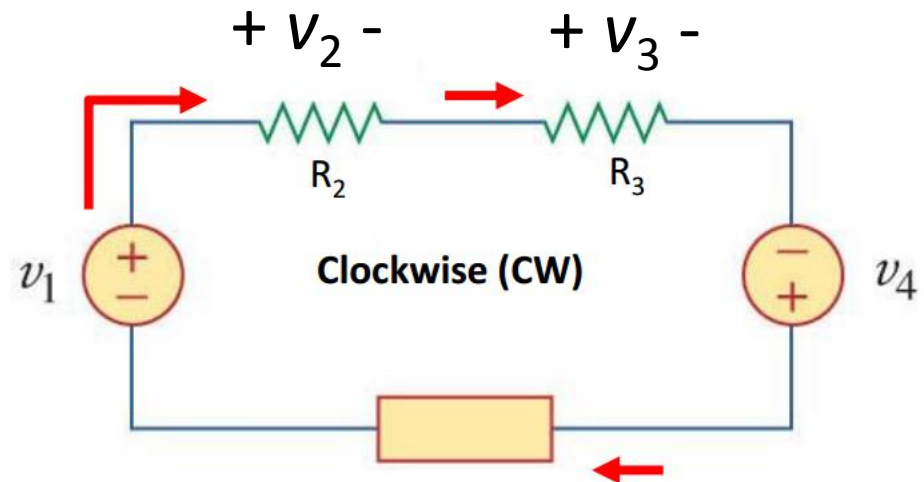

# KVL

- Find the  $V_{ab}$

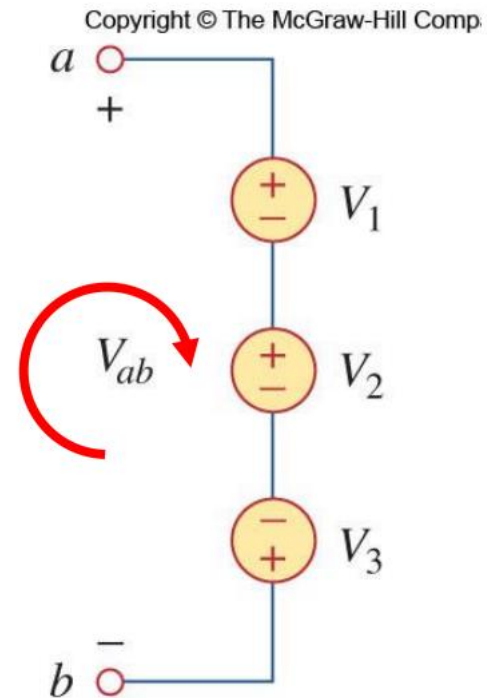


# Kirchhoff Current Law (KCL)

- Kirchhoff's current law is based on **conservation of charge**
- It states that the algebraic **sum of currents entering a node** (or a closed boundary) is **zero**.
- It can be expressed as:

$$\sum_{n=1}^N i_n = 0$$

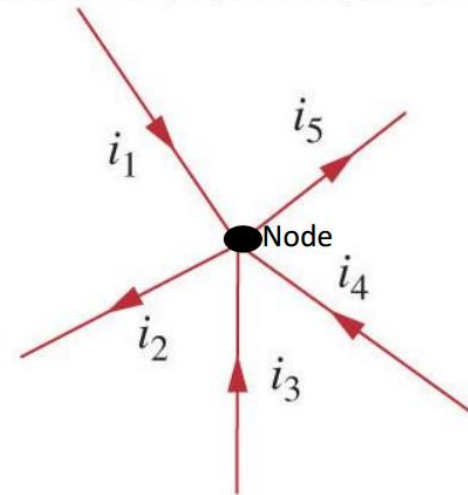Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






**ELECTRICAL AND ELECTRONICS  
FOR DESIGN  
(SRSD 3092)  
Semester II 2019/2020**

**DC SERIES CIRCUITS**

*Prepared by : DR NELIDYA MD  
YUSOFF*

# DC SERIES CIRCUITS

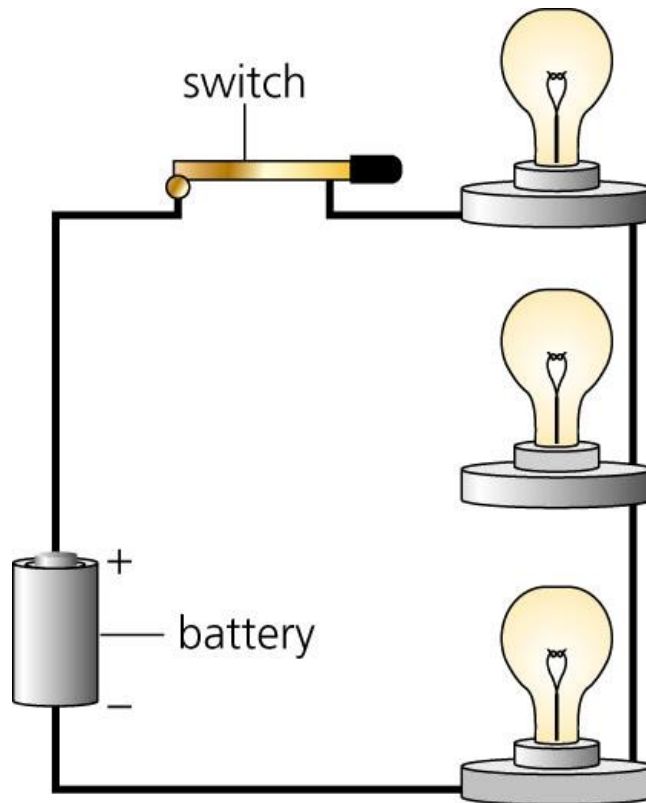

# Topics

- Series Circuits
  - Series Resistors
- Voltage Sources in Series
- Kirchhoff's Voltage Law
- Voltage Division in a Series Circuit
  - Voltage Divider Rule (VDR)
- Open circuit, closed circuit



# Series circuit

- A **series circuit** has more than one resistor (*anything that uses electricity to do work*) and
- Charges must move in "series" first going to one resistor then the next.
- If one of the items in the circuit is broken then no charge will move through the circuit because there is only one path.
- There is no alternative route


*Series connection*




only one path for electrons to flow!

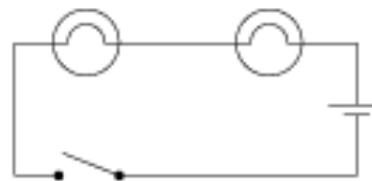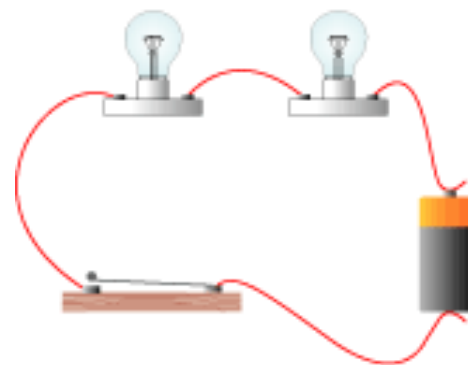


# Series circuit 1

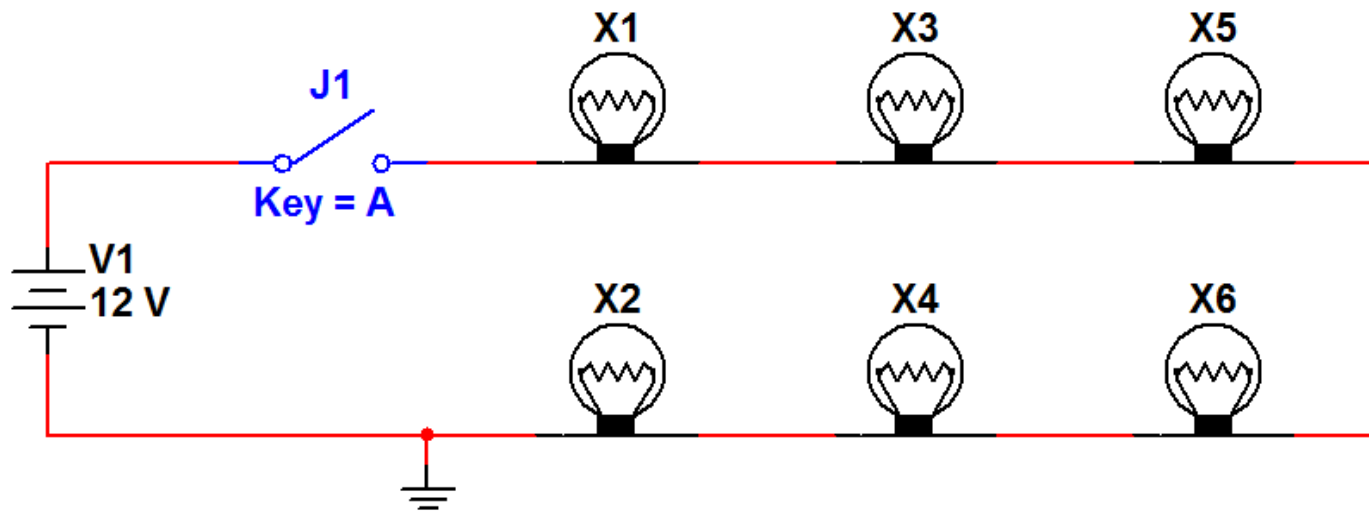



# Series circuit 2

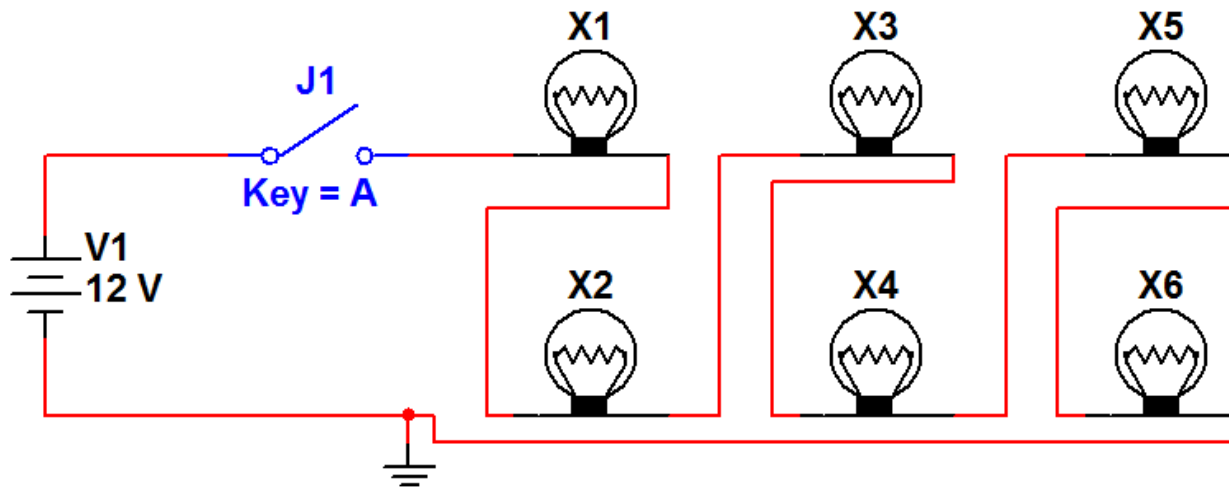

# Series circuit 3

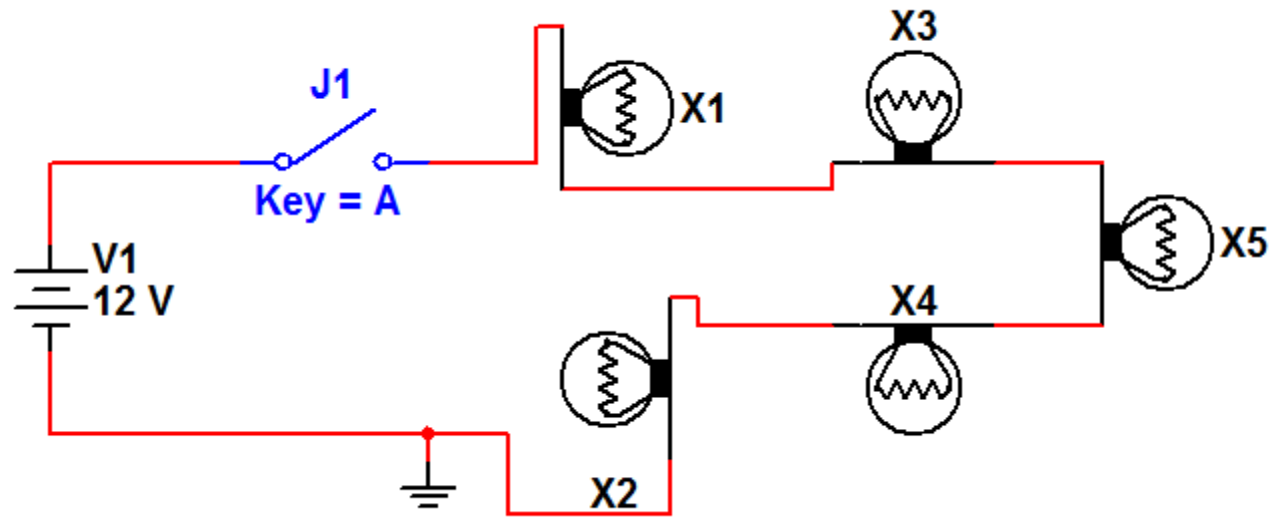
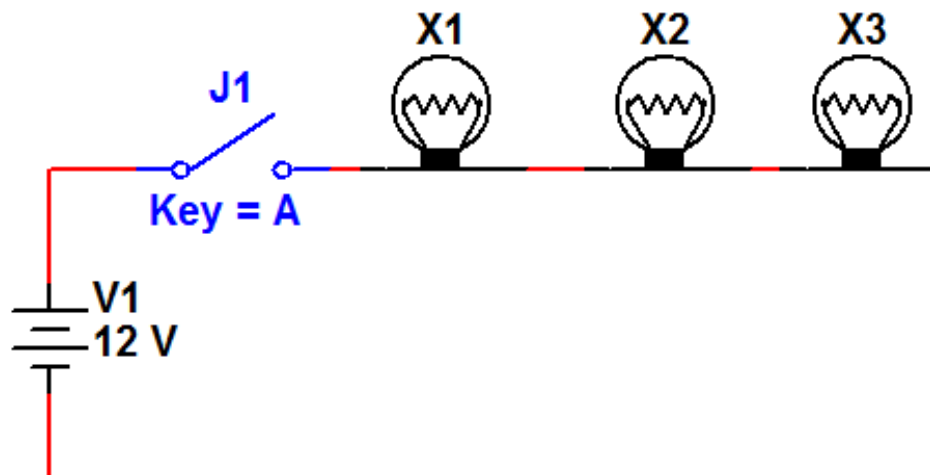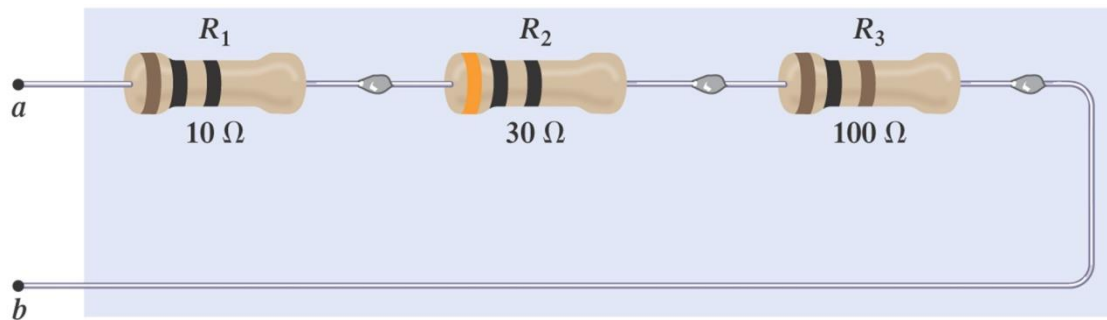
# Series connection of resistors and lamps.









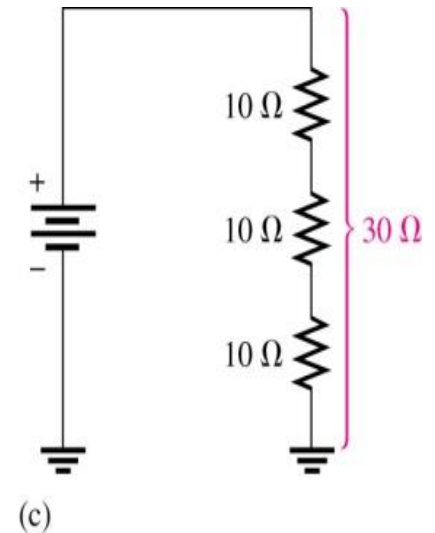
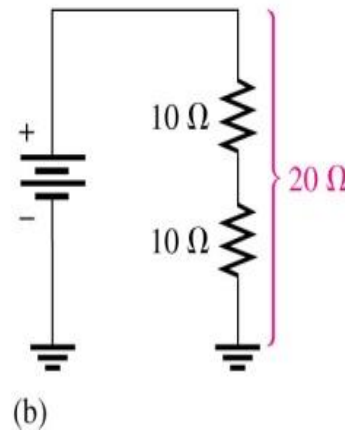
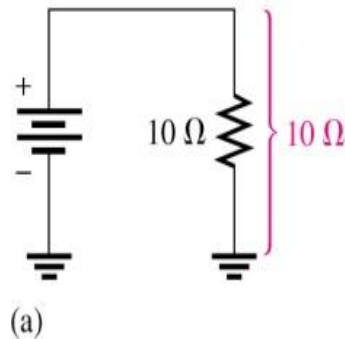
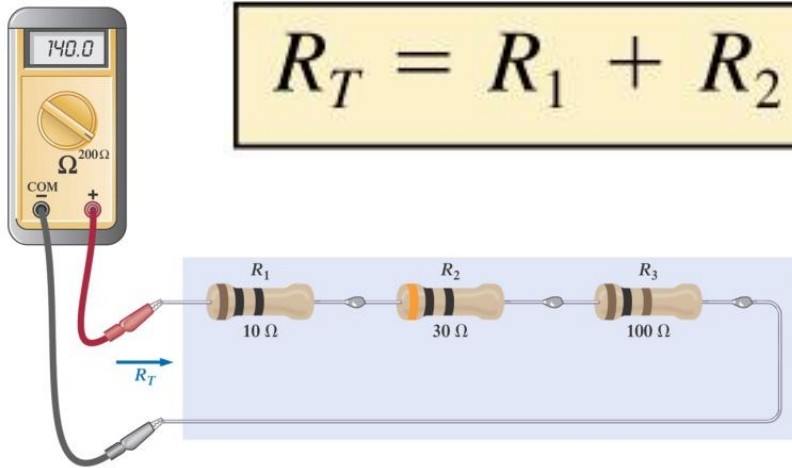
# Total Series Resistance

The **total resistance** of a series circuit is equal to the **sum** of the resistances of **each individual series resistor**.

$$R_T = R_1 + R_2 + R_3 + R_4 + \dots + R_N$$



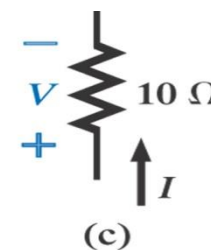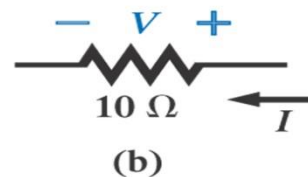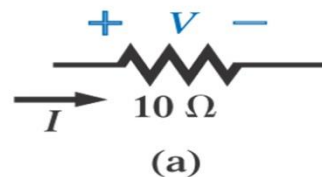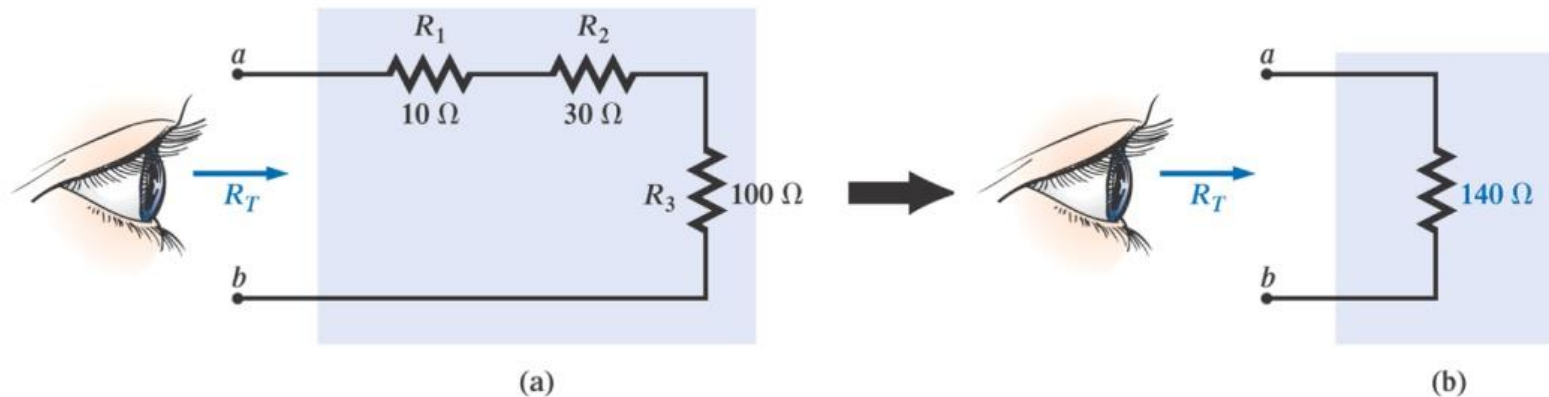
Resistance “seen” at the terminals of a series circuit,  $R_T$ .



The **polarities** across a resistor as determined by the **direction of the current**
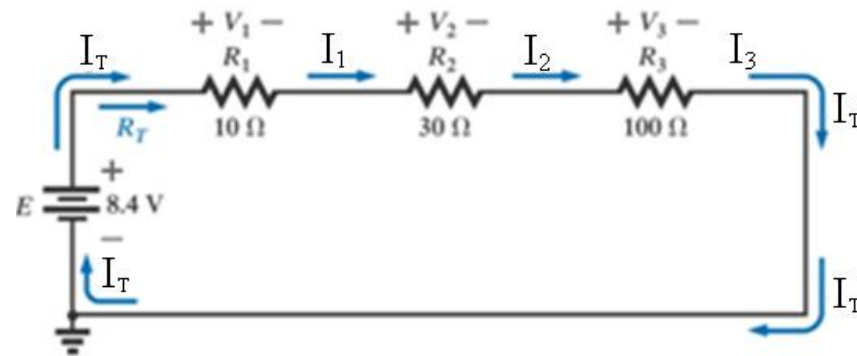
# Ohm's Law in Series Circuits

- Current through one of the series resistor is the same as the current through each of the other resistors and is the total current.



$$I_T = I_1 = I_2 = I_3$$

# Ohm's Law in Series Circuits

- If you know the total voltage and the total resistance, you can determine the total current by using:

$$I_T = \frac{V_T}{R_T}$$

$$V_T = V_1 + V_2 + V_3 = E$$

$$R_t = R_1 + R_2 + R_3$$


# Ohm's Law in Series Circuits

- If you know the voltage drop across one of the series resistors, you can determine the current by using:


$$I_T = I_1 = I_2 = I_3$$

$$I = \frac{V_1}{R_1} = \frac{V_2}{R_2} = \frac{V_3}{R_3} = \frac{V_T}{R_T}$$

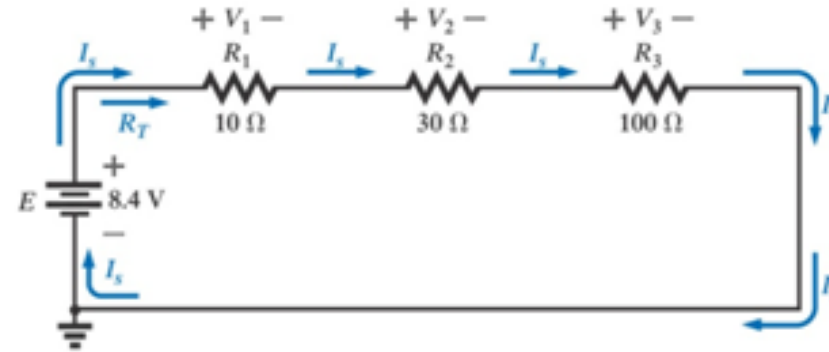
Applying a laboratory dc supply set at 8.4 V to the series circuit of (a) actual circuit; (b) schematic representation showing that the current is the same at every point.




(b)

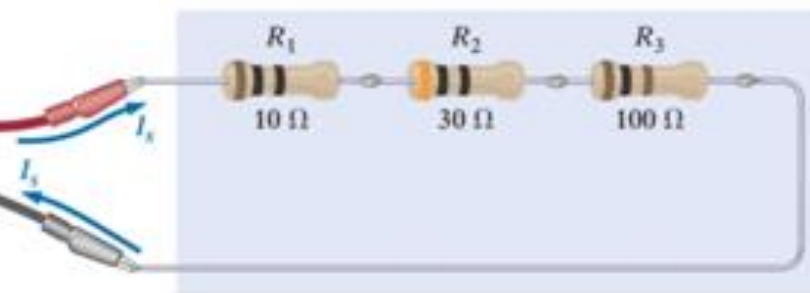

(a)

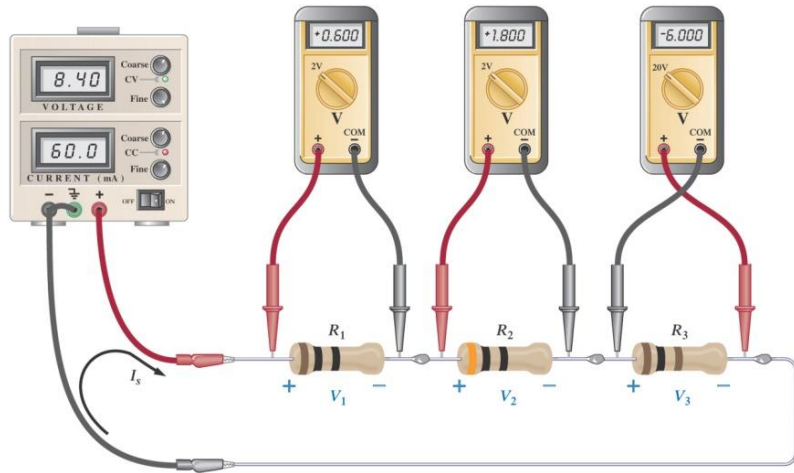


Measuring voltage

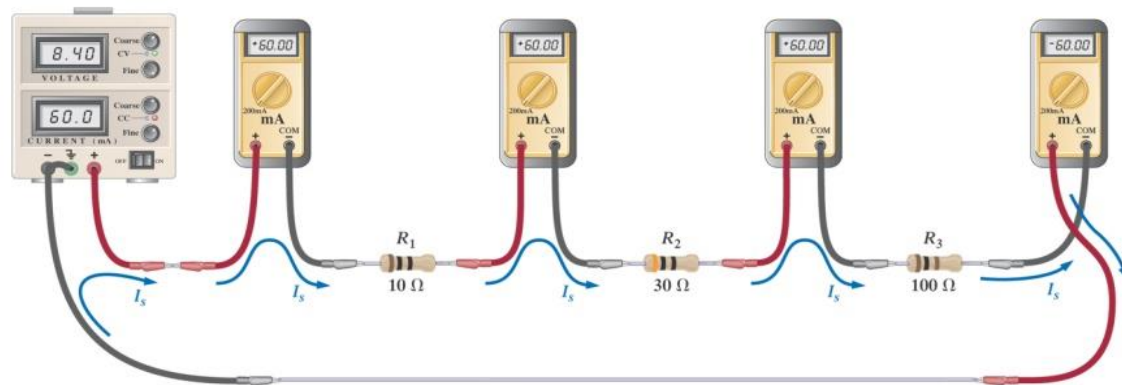


Measuring current

# Example: Find $R_T$

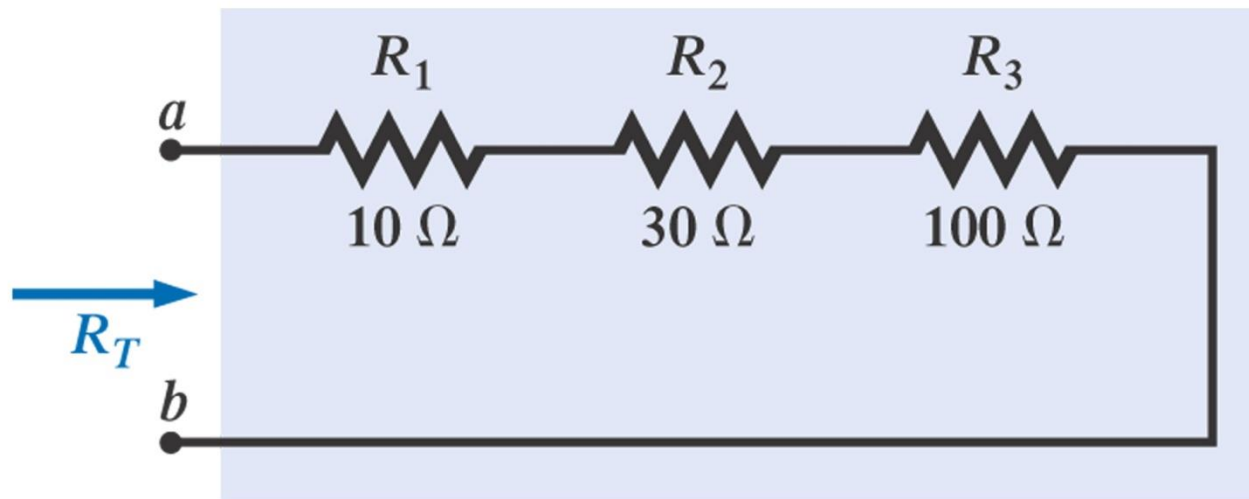





# Example: Find $R_T$

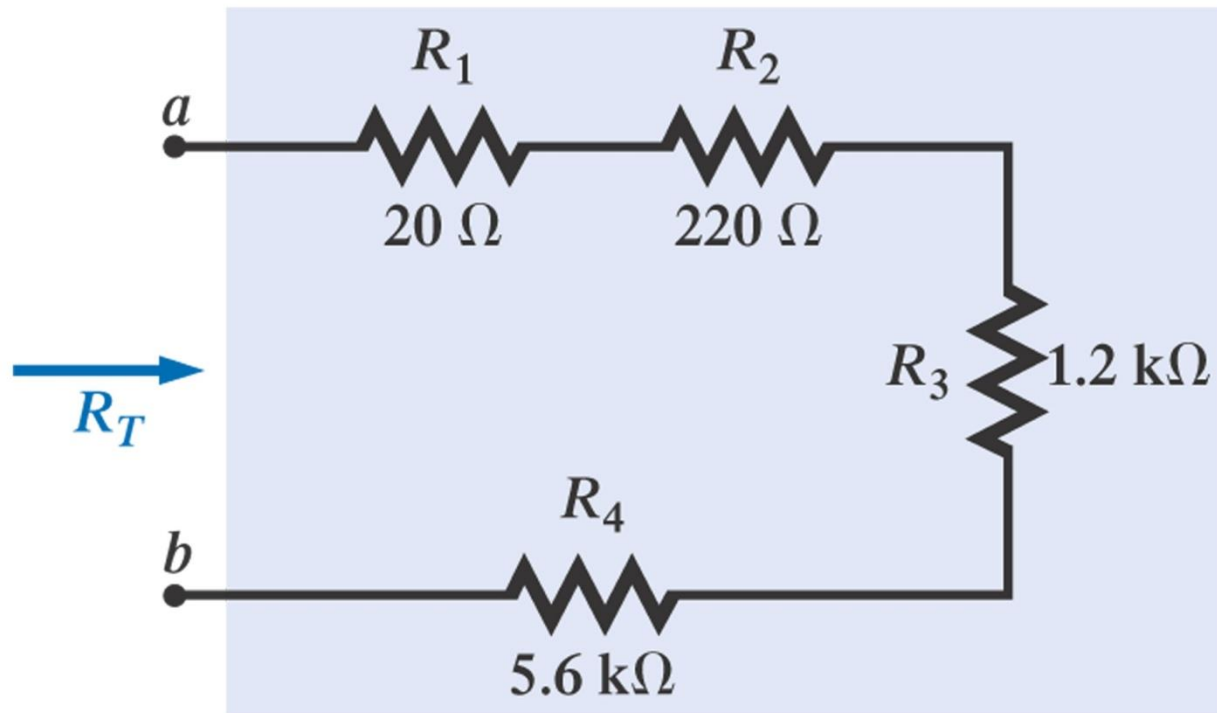


# Example: Find $R_T$

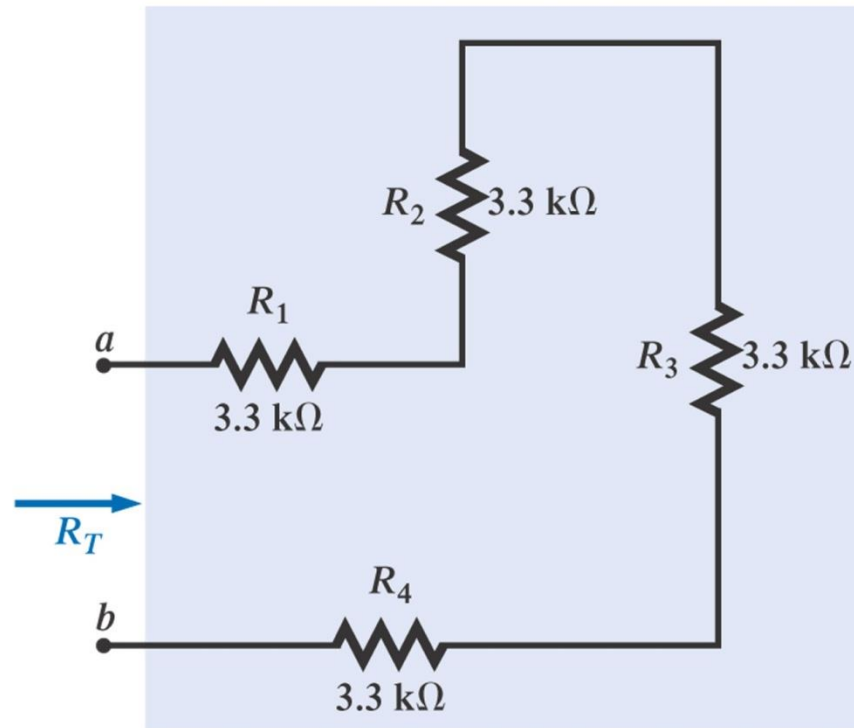

# Example: Find $R_T$

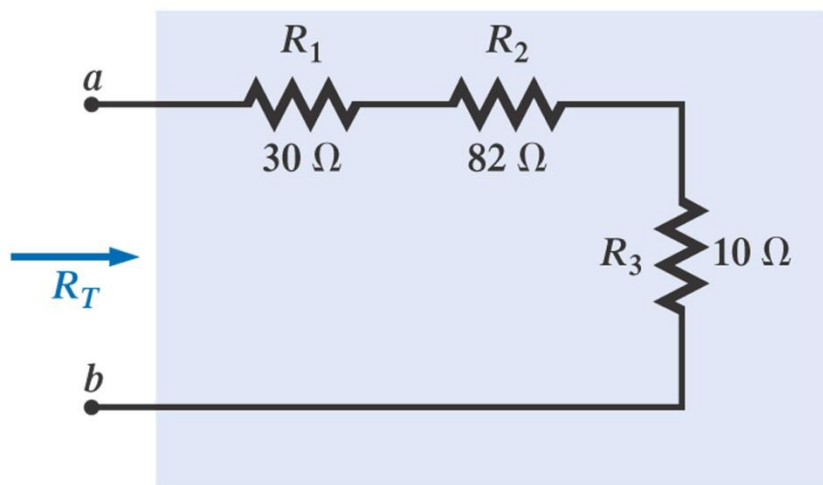


(a)

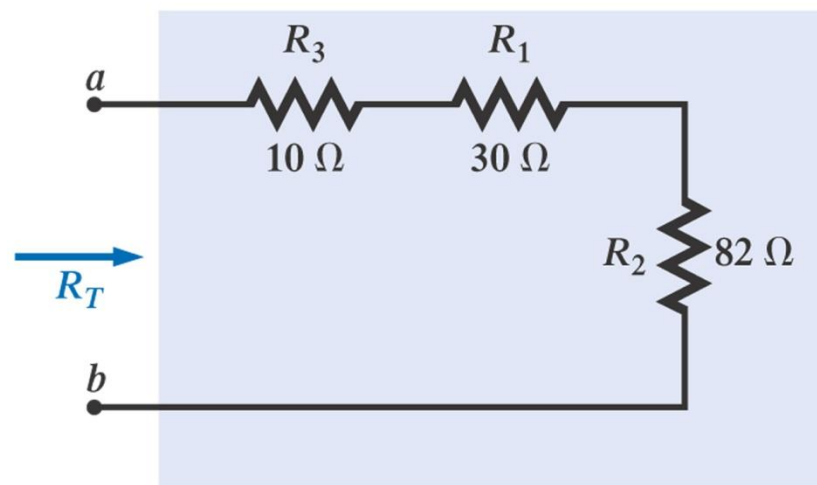



(b)

# Example: Find $R_T$

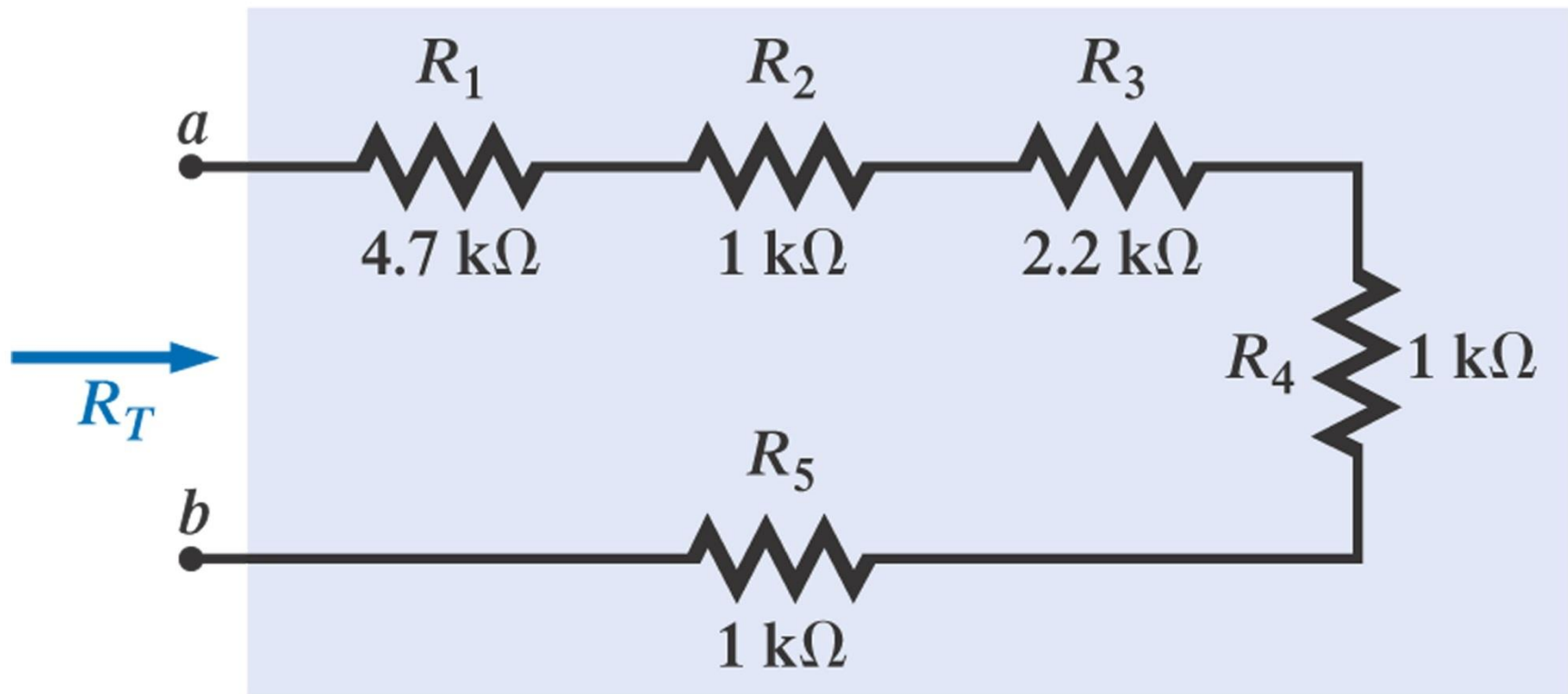


## Example: Find $R_T$

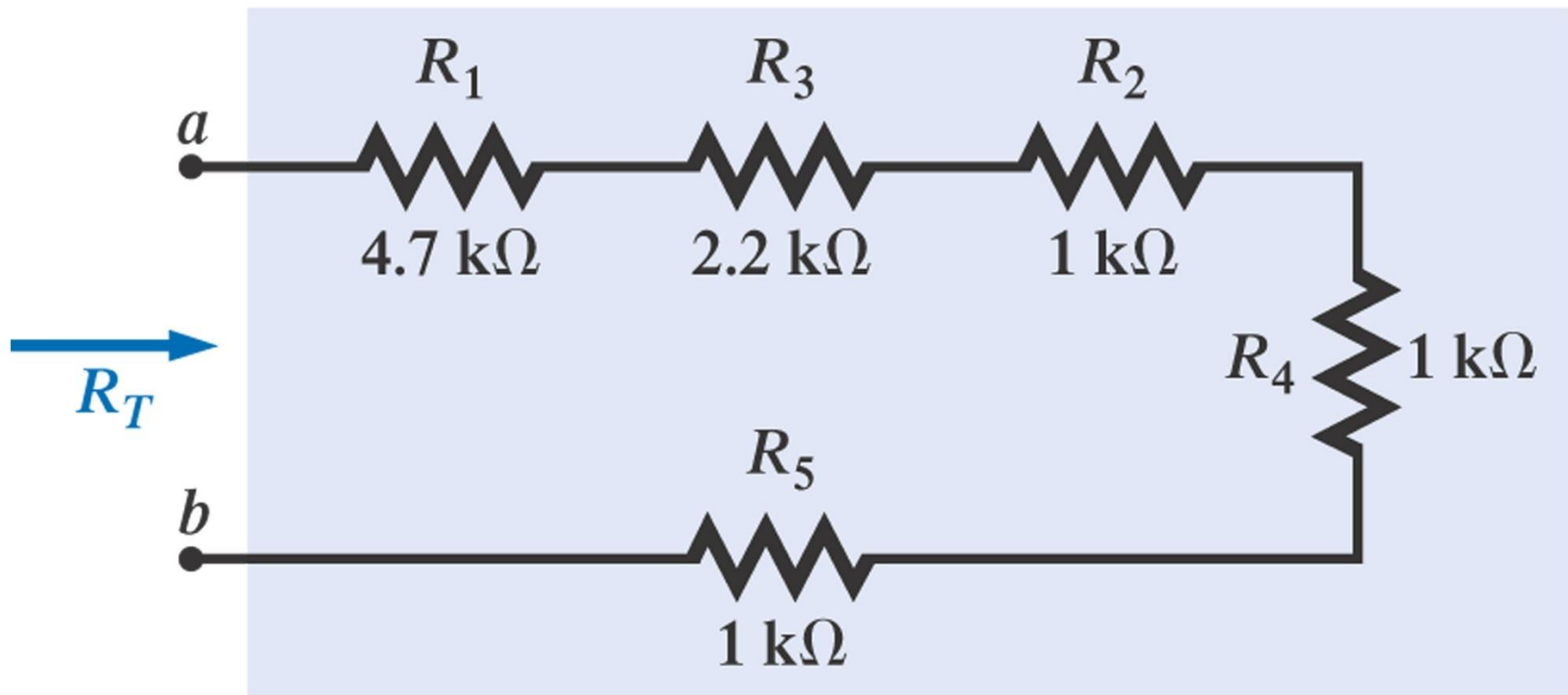


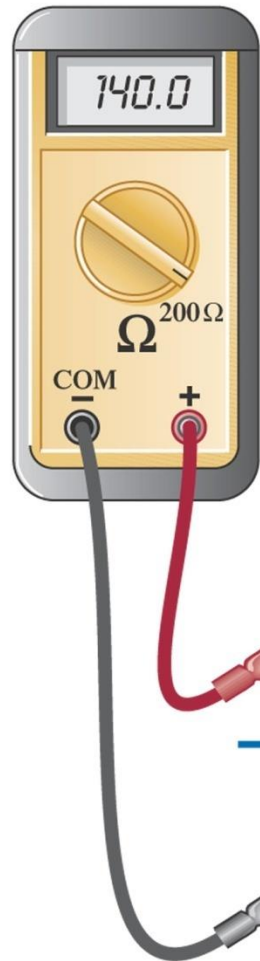


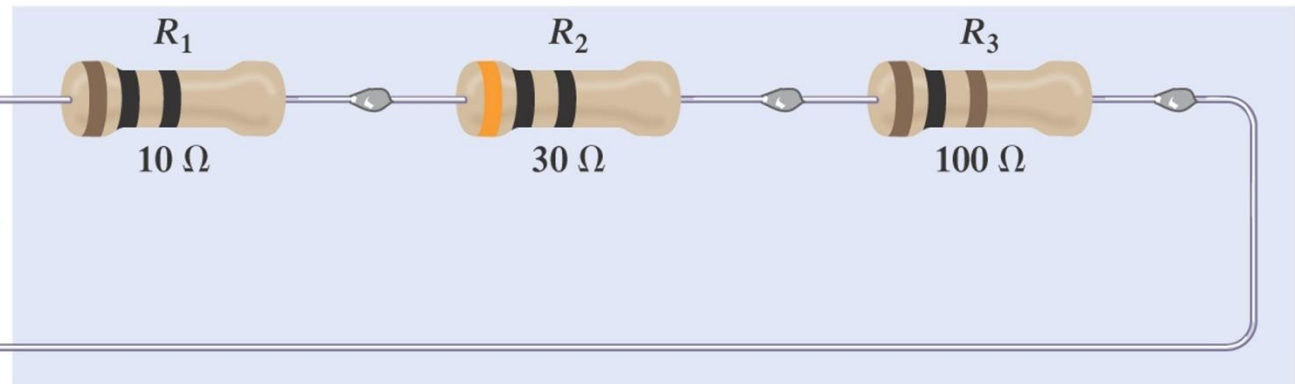
Using an ohmmeter to measure the total resistance of a series circuit.





# Voltage Sources in Series

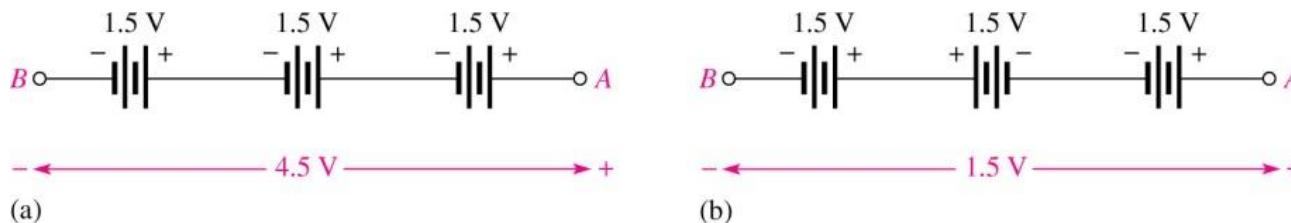

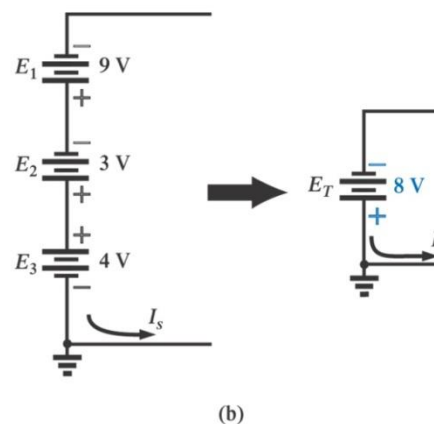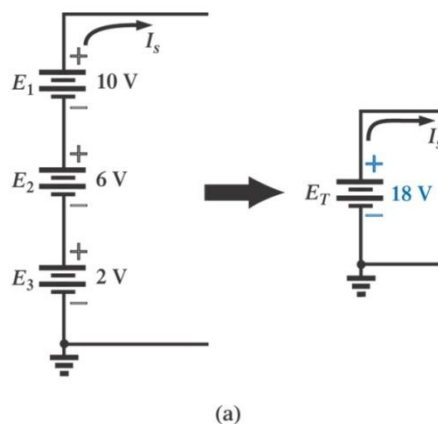
When two or more voltage sources are in series, the total voltage is equal to the algebraic sum (including polarities of the sources) of the individual source voltages.



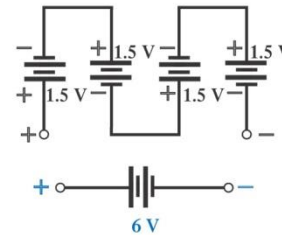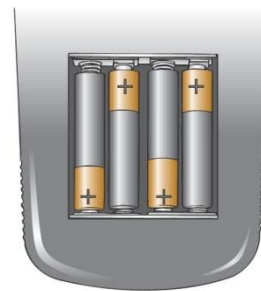
Series connection of dc supplies: (a) four 1.5 V batteries in series to establish a terminal voltage of 6V; (b) incorrect connections for two series dc supplies; (c) correct connection of two series supplies to establish 60 V at the output terminals.



(a)

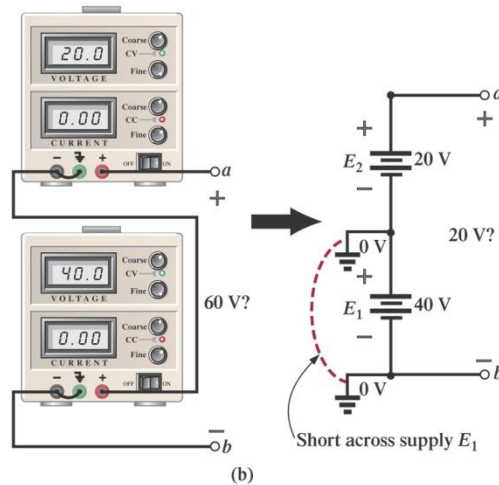

(b)

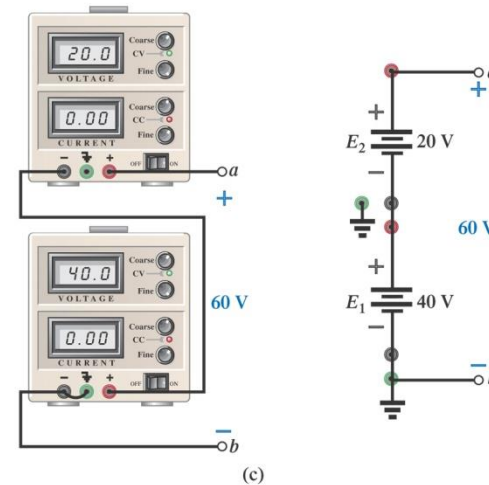

(c)




# Kirchhoff's Voltage Law

- The algebraic sum of the potential rises and drops around a closed path (or loop) is zero

$$\sum_{\text{C}} V = 0$$

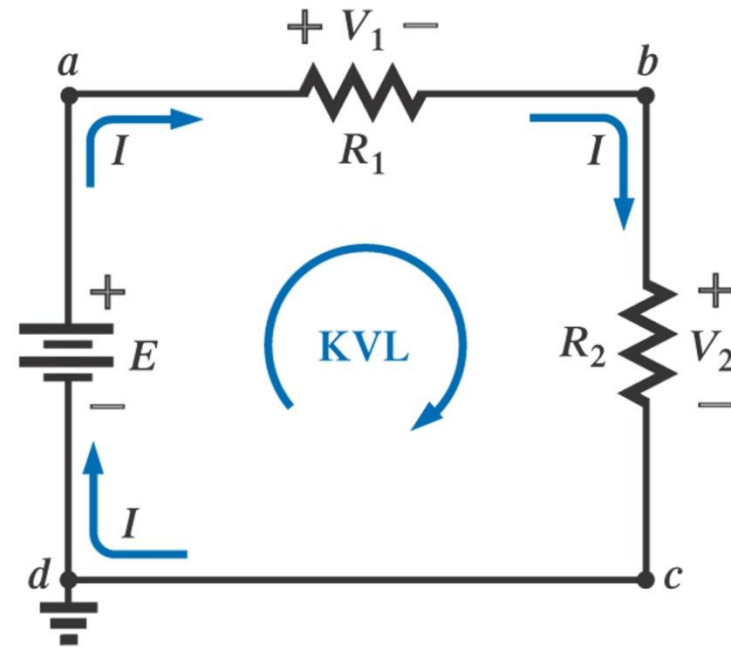
(Kirchhoff's voltage law in symbolic form)



$$0 = E - V_1 - V_2$$
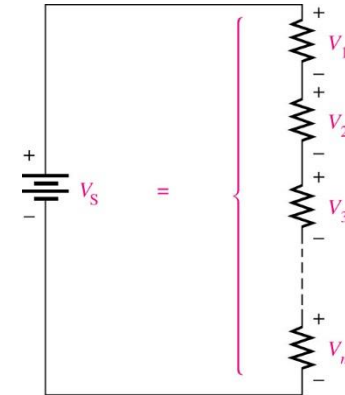
# Kirchhoff's Voltage Law


The sum of all the voltage drops around a single closed loop in a circuit is equal to the total source voltage in that loop.



$$\sum_{\text{C}} V = 0$$

$$V_S = V_1 + V_2 + V_3 + V_4 + \dots + V_N$$
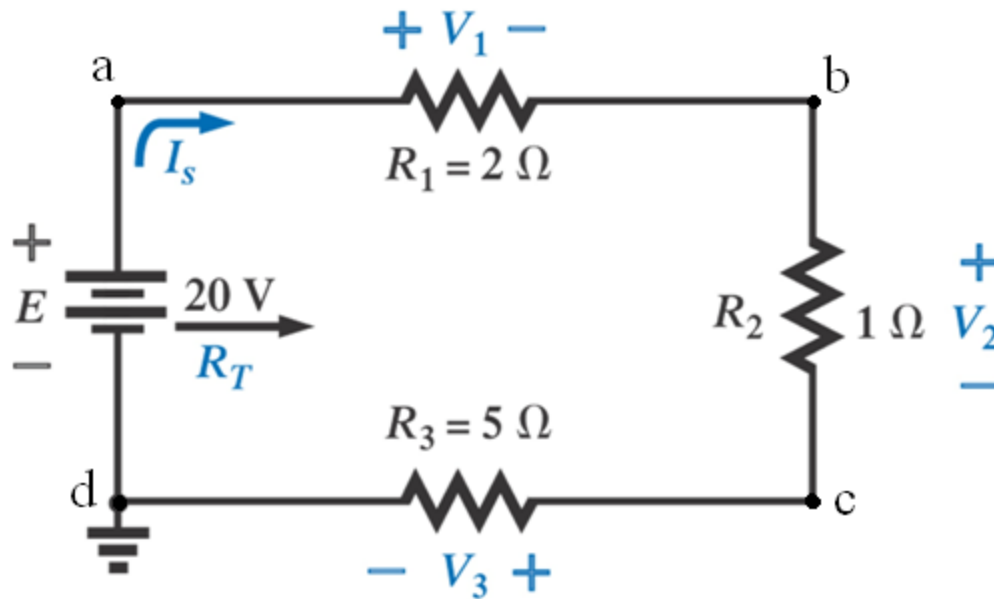
## Example: Series circuit to be analyzed



$$R_T = R_{ab} + R_{bc} + R_{cd}$$

$$R_T = R_1 + R_2 + R_3$$


$$R_T = R_{da} = R_{ad}$$

$$0 = V_{ab} + V_{bc} + V_{cd} + V_{da}$$


$$0 = V_1 + V_2 + V_3 - E$$

$$V_{ab} = V_a - V_b = V_1$$

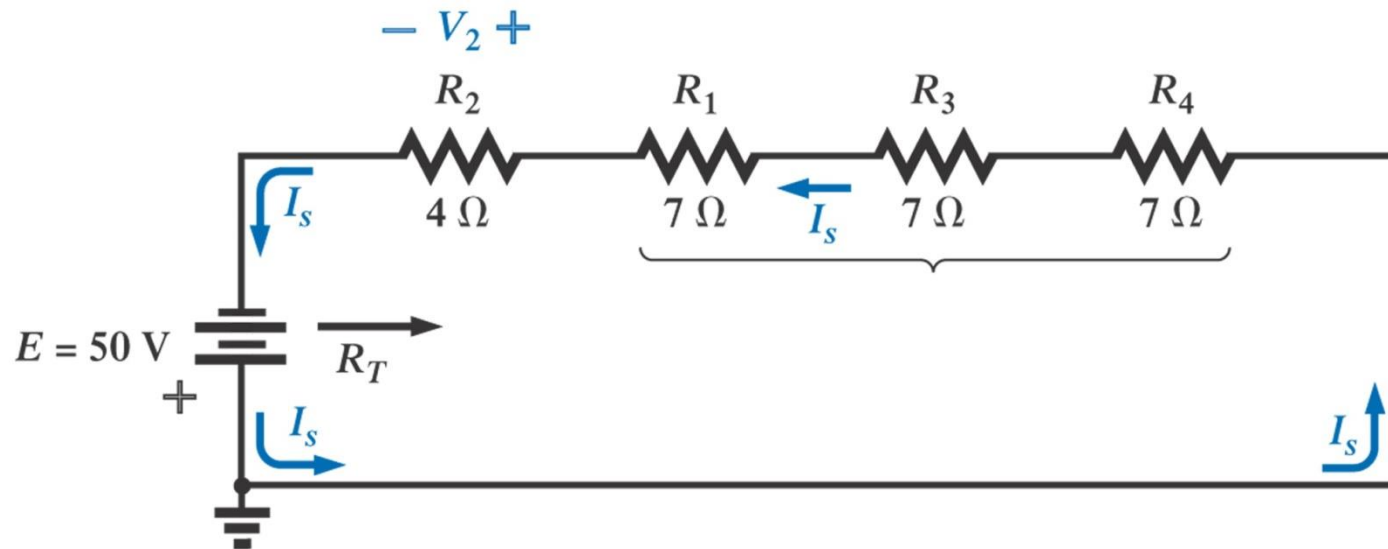
**Example:** Series circuit to be analyzed



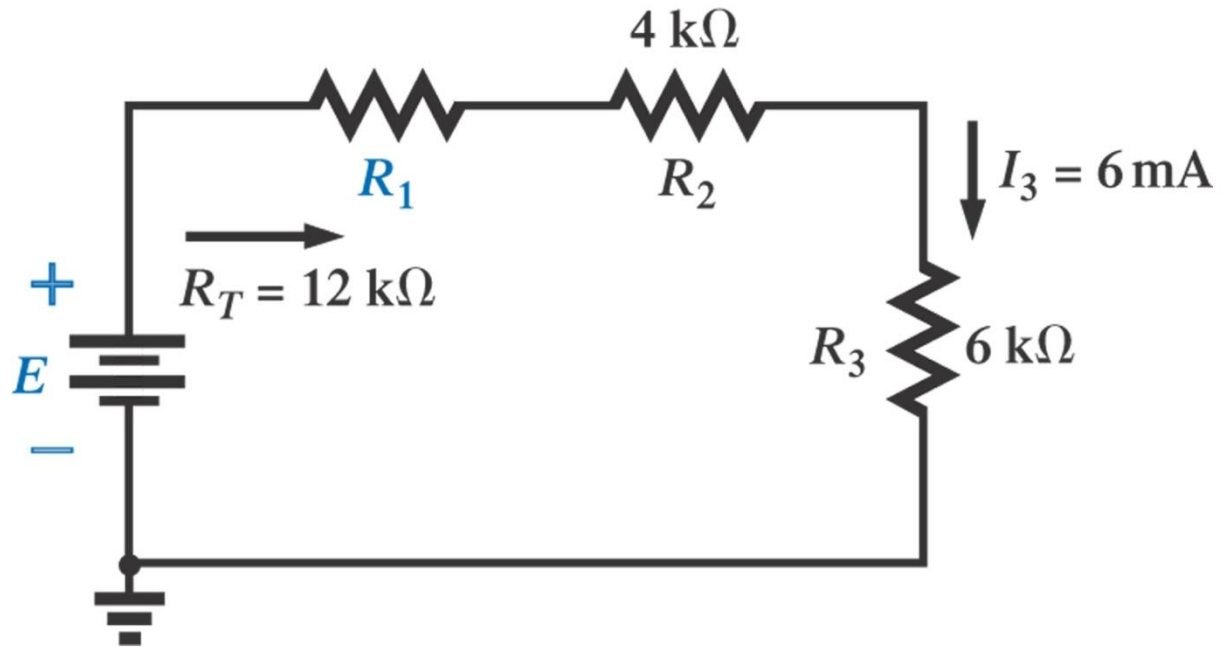
**Example:** Series circuit to be analyzed



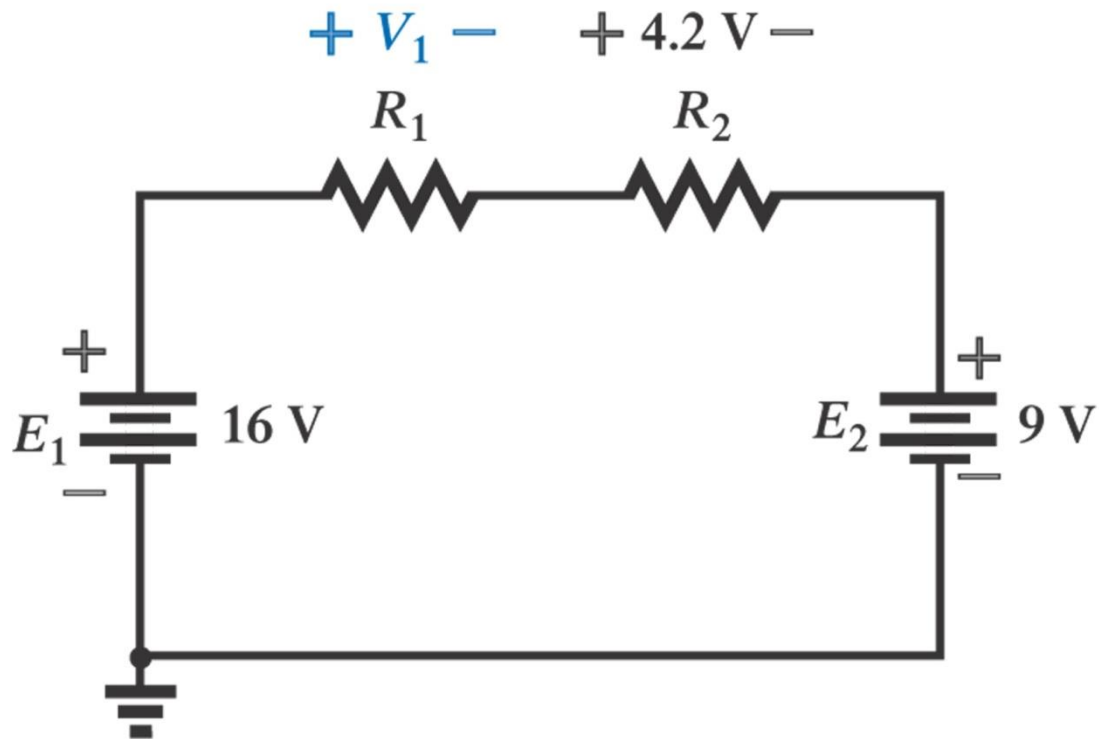
**Example:** Series circuit to be examined.



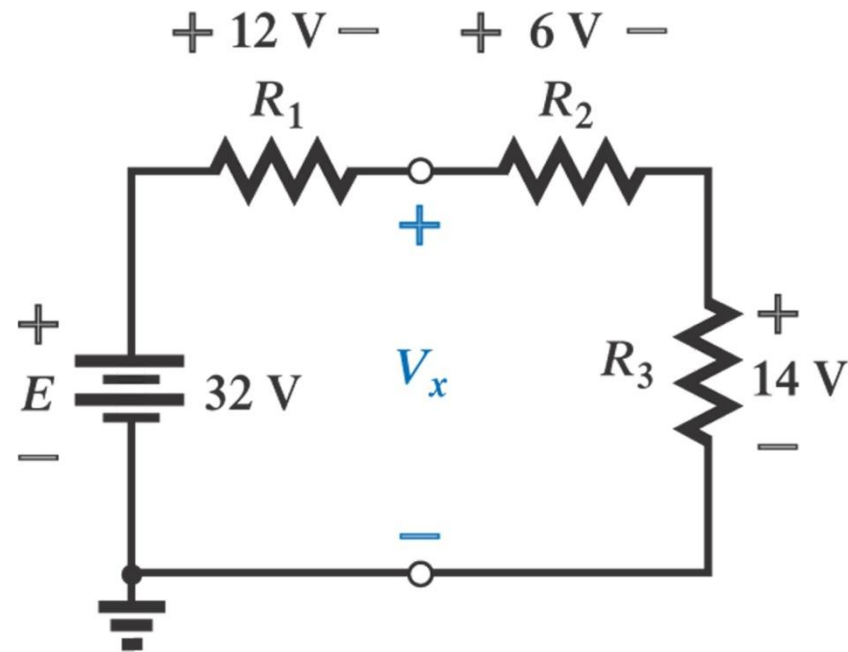**Example:** Series dc circuit to be analyzed.




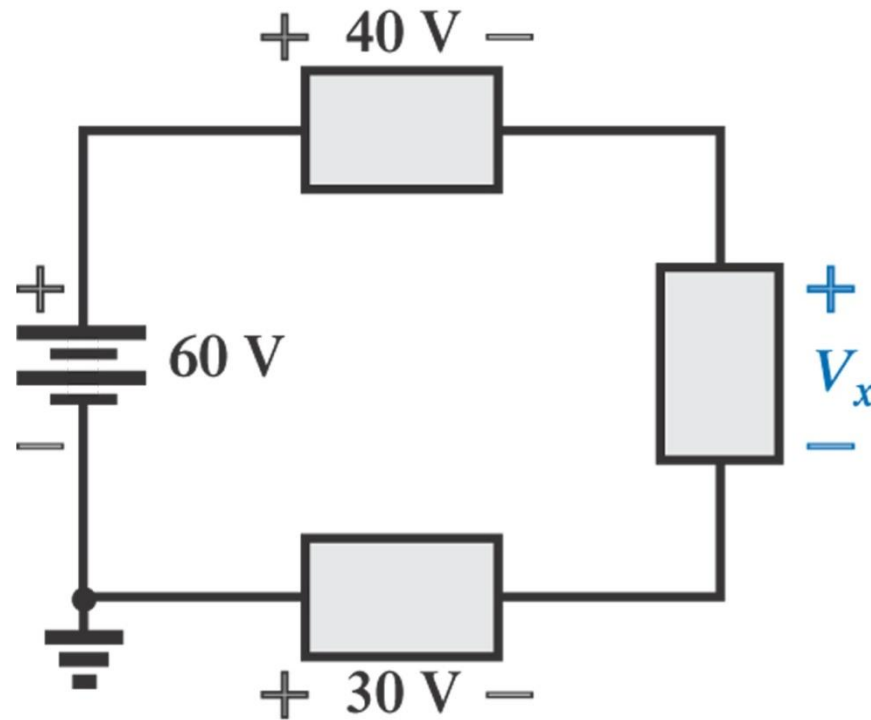**Example:** Series configuration to be examined.





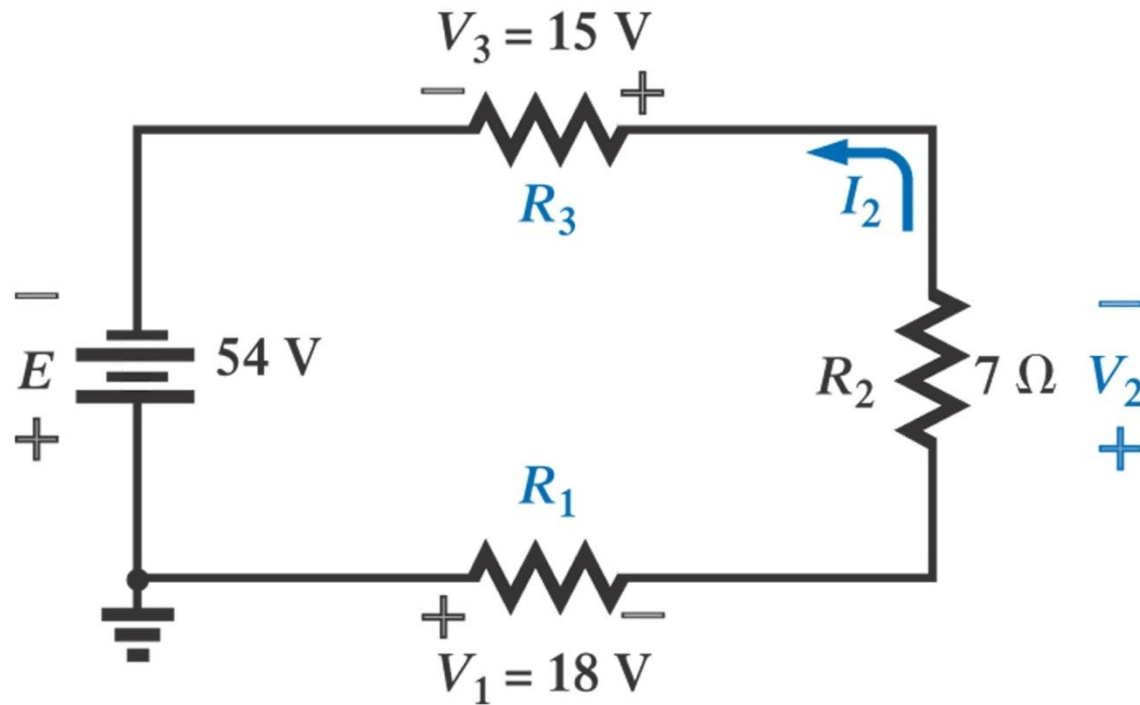**Example:** Series configuration to be examined.




## Voltage-Divider Rule

- The voltage across a resistor in a series circuit is equal to the value of that resistor times the total voltage applied, divided by the total resistance of the series configuration


$$I = \frac{V_1}{R_1} = \frac{V_2}{R_2} = \frac{V_T}{R_T} = \frac{E}{R_T}$$

$$V_2 = R_2 \frac{E}{R_T}$$

$$V_x = R_x \frac{E}{R_T}$$

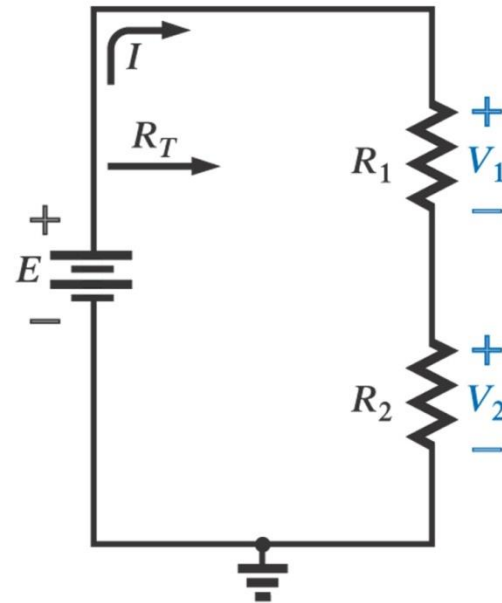

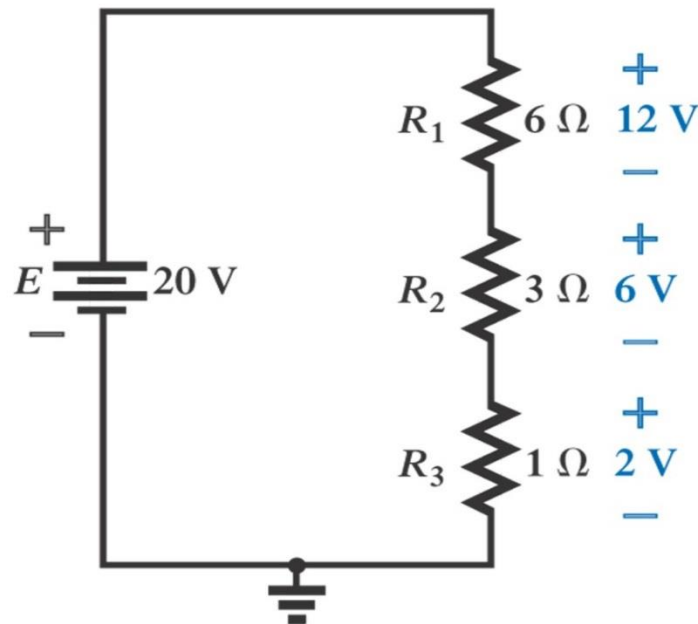- How the voltage will divide across series resistive elements.
- The ratio of the resistive values determines the voltage division of a series dc circuit.




$$I = \frac{E}{R_T}$$


$$I = \frac{V_1}{R_1} = \frac{V_2}{R_2}$$

$$V_x = R_x \frac{E}{R_T}$$

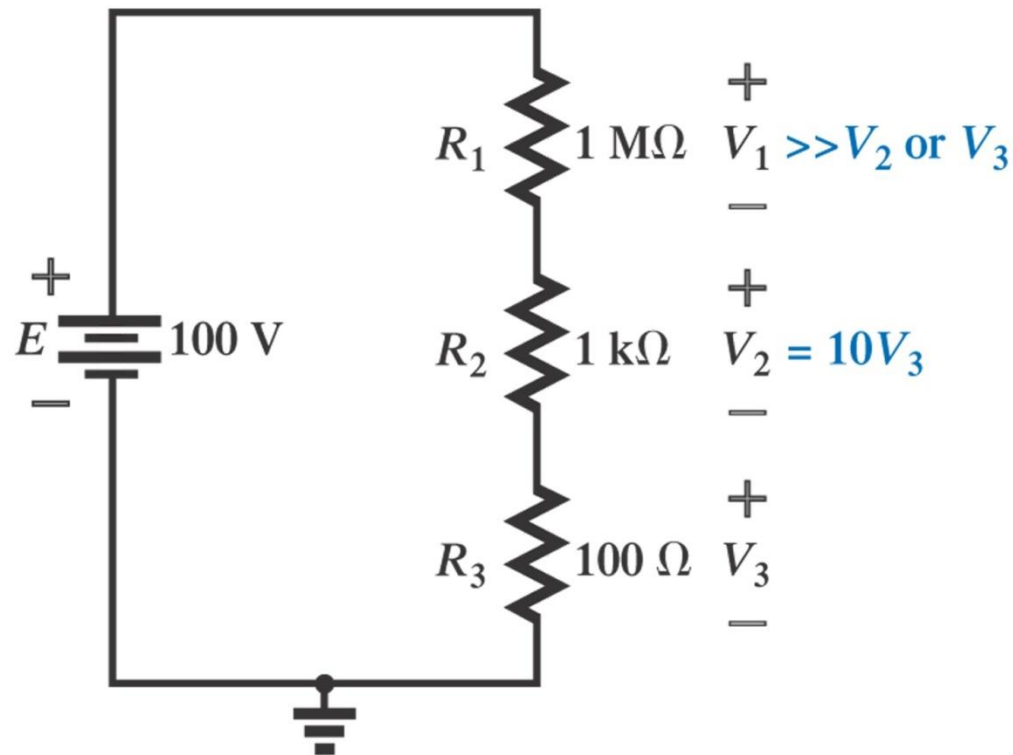The **largest** of the **series resistive** elements will capture the **major share** of the applied voltage.



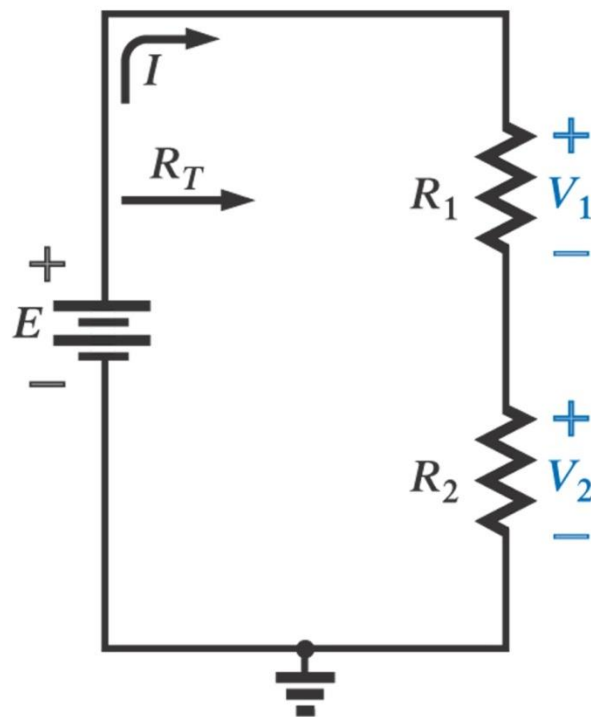**Example:** Developing the voltage divider rule.




$$I = \frac{E}{R_T}$$

$$I = \frac{V_1}{R_1} = \frac{V_2}{R_2}$$


$$V_x = R_x \frac{E}{R_T}$$

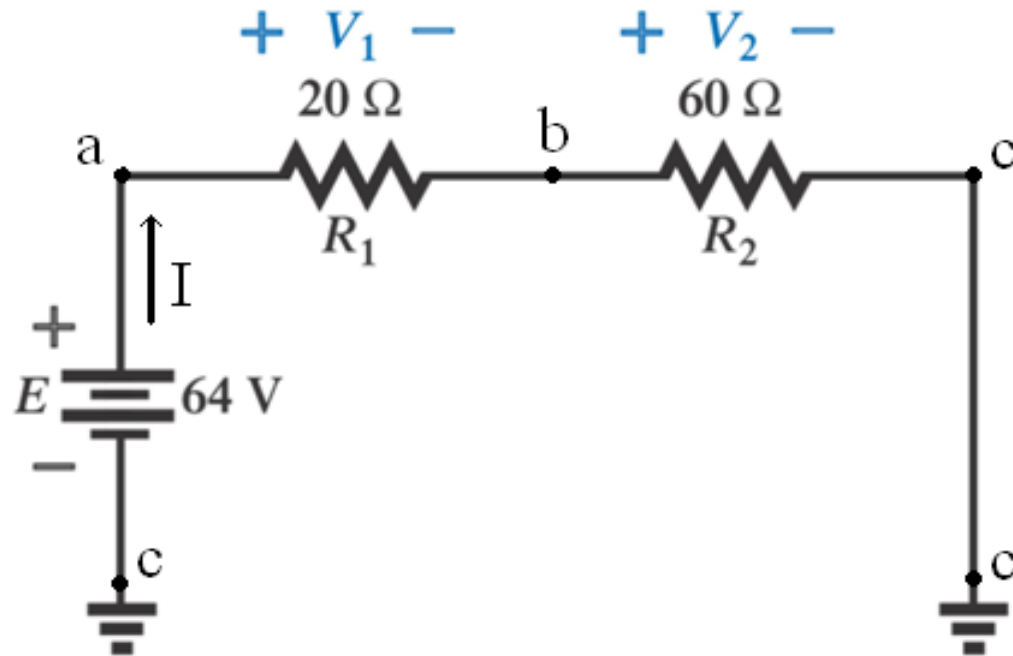Example:

In the series circuit, find  $V_1$  &  $V_2$  using the voltage divider rule.



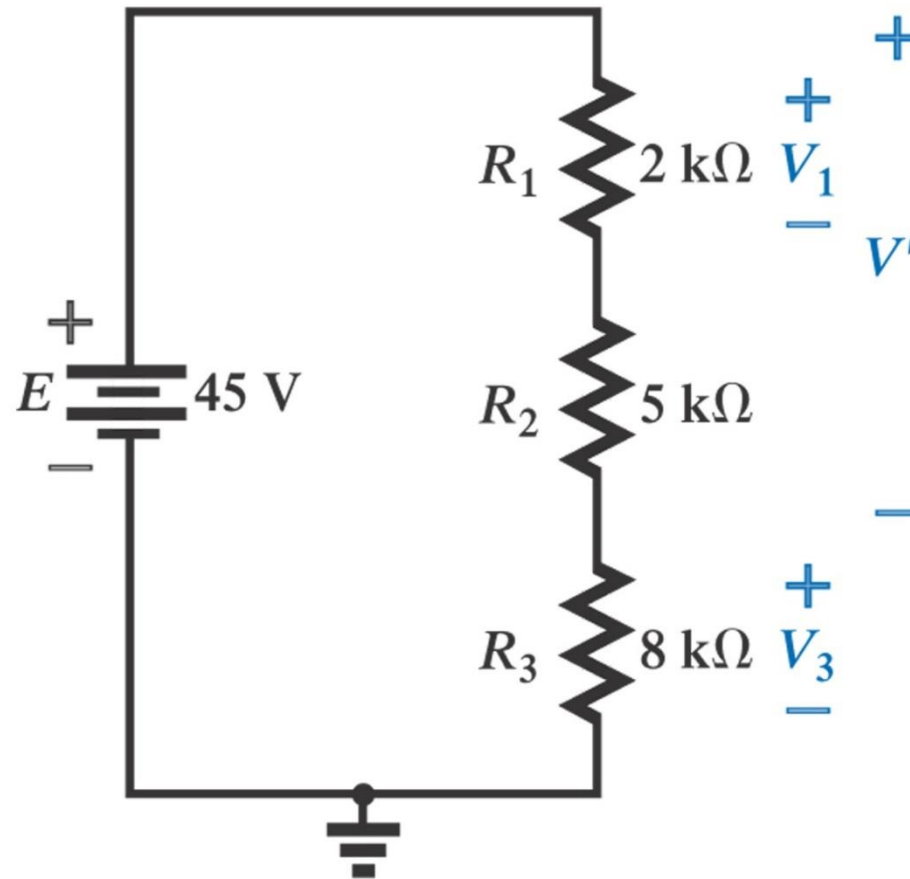**Example:** Series circuit to be investigated.




# Open Circuit

$$I_T = I_1 = I_2 = 0$$

$$E = V_{ab} + V_1 + V_2$$

$$E = V_{ab} + 0 + 0$$

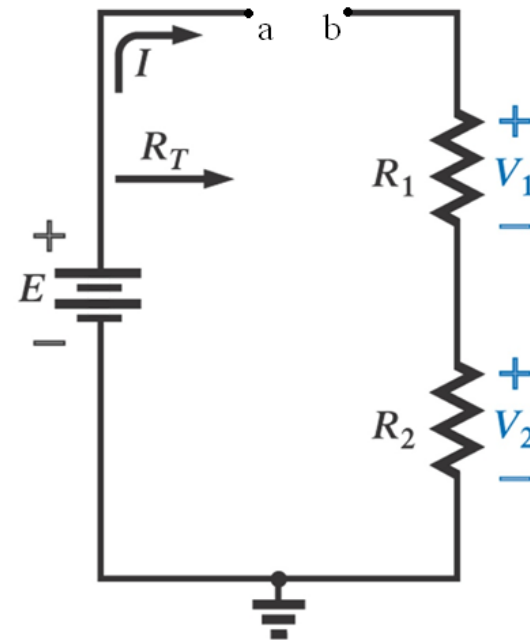


- The most common failure in a series circuit is an open.
- When an open occurs in a series circuit, all of the **source voltage appears across the open.**



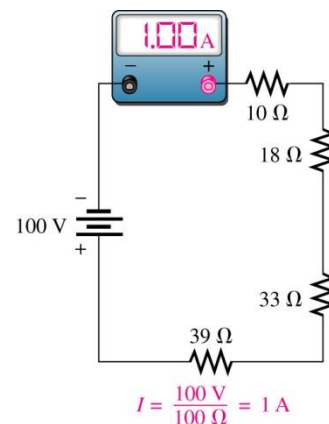
# Short Circuit

- When there is a short, a portion of the series resistance is bypassed, thus reducing the total resistance.
- A short in a series circuit results in more current than normal.



(a) Before short

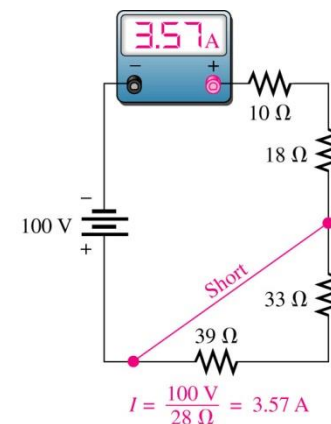

(b) After short

# Short Circuit

$$V_{ab} = V_a - V_b = V_{R1}$$

*short circuit* :  $V_a = V_b$

$$V_a - V_b = V_{ab} = 0$$

$$I_{R1} = 0$$


all the current flow along the short circuit path

$$0 = E - V_1 - V_2$$


$$0 = E - 0 - V_2$$

$$E = V_2 = IR_2$$


$$I = \frac{V_2}{R_2} = \frac{E}{R_2}$$

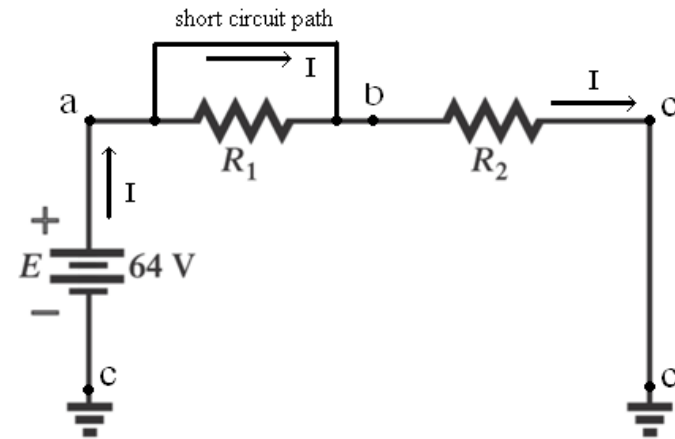

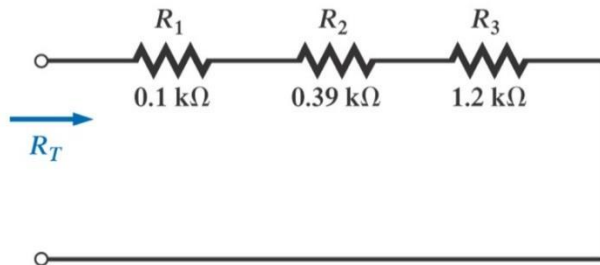
## Problem 2 : Determines the measured resistance, $R_T$




(a)

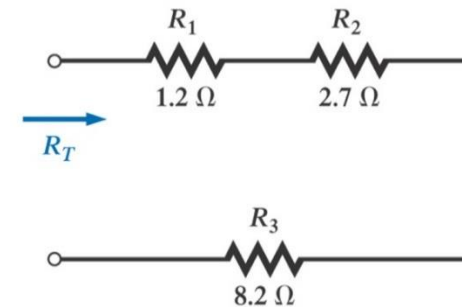

(b)

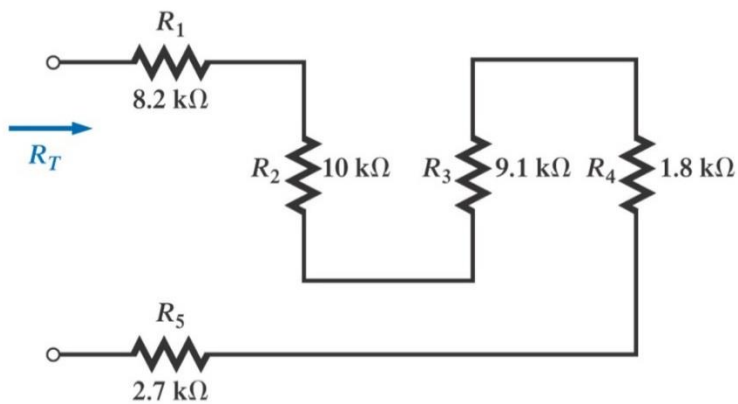


(c)

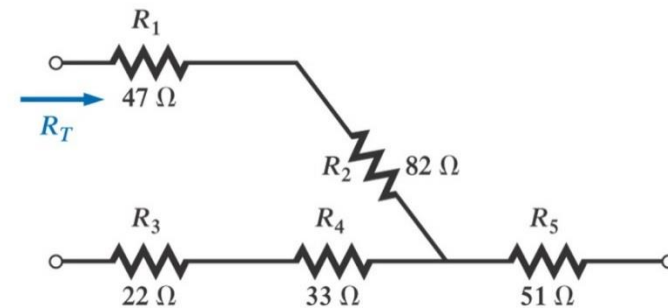


(d)

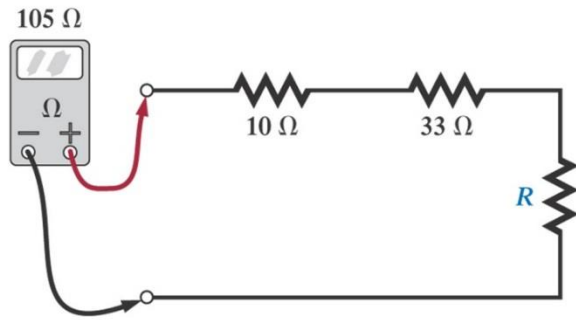
## Problem 5 : Determines the unknown resistance




(a)

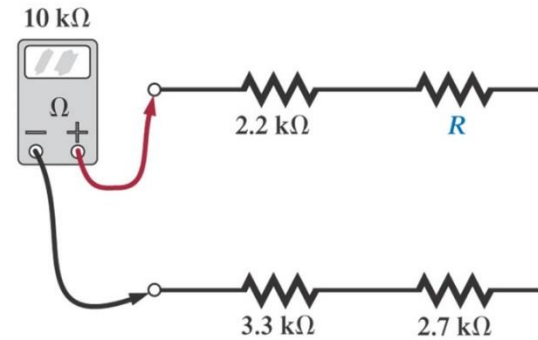

(b)




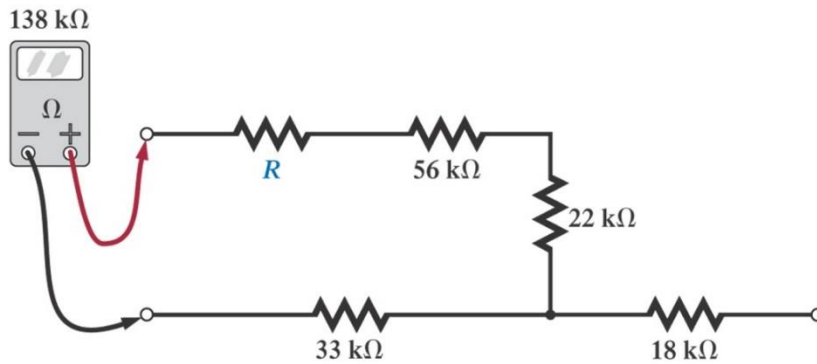






(c)

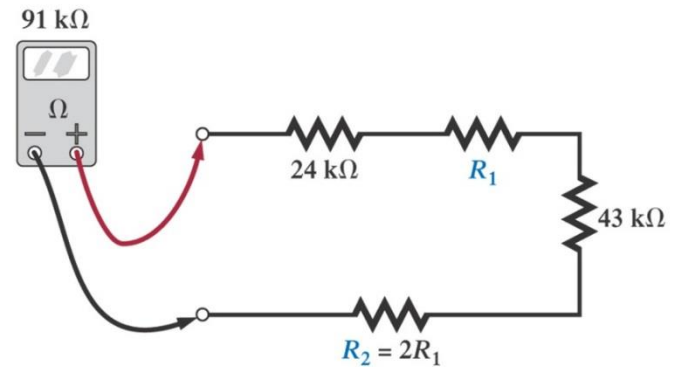


(d)

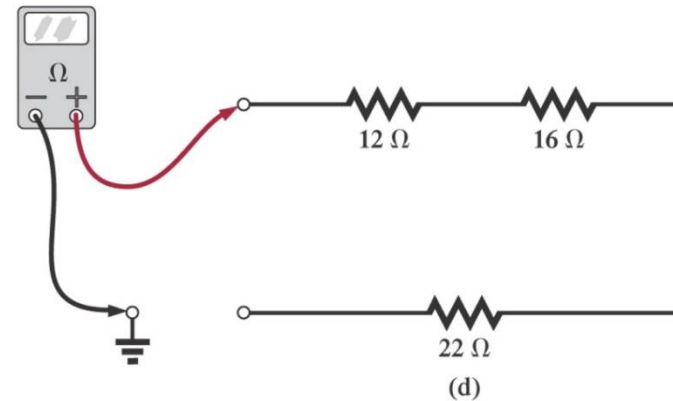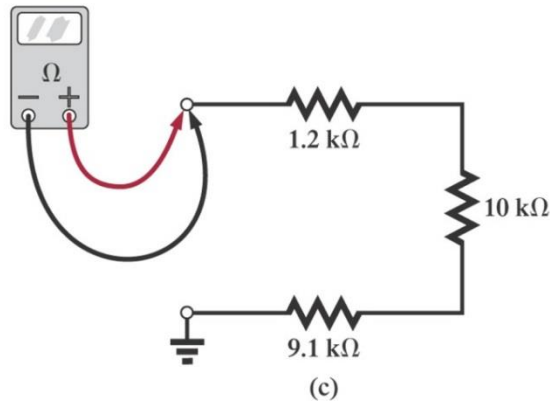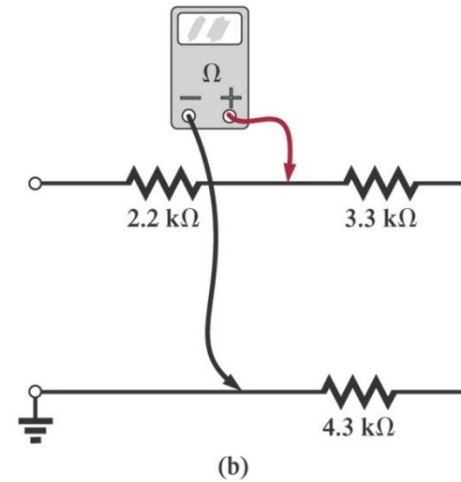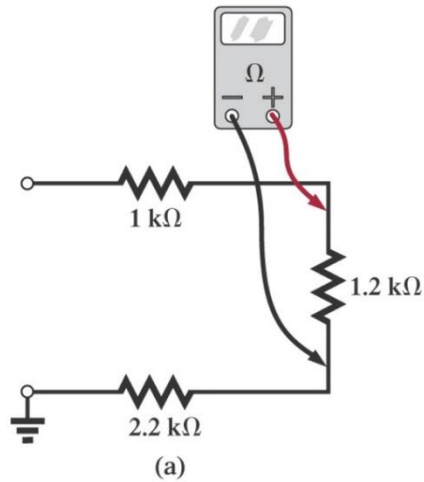
## Problem 6 : Determines the measured resistance.



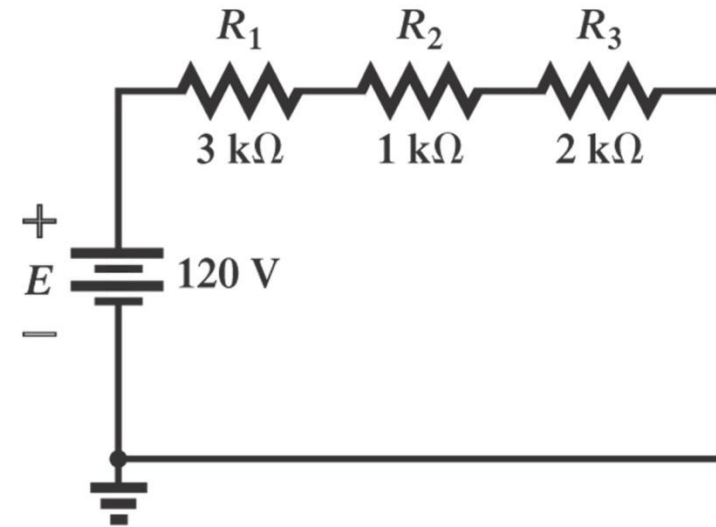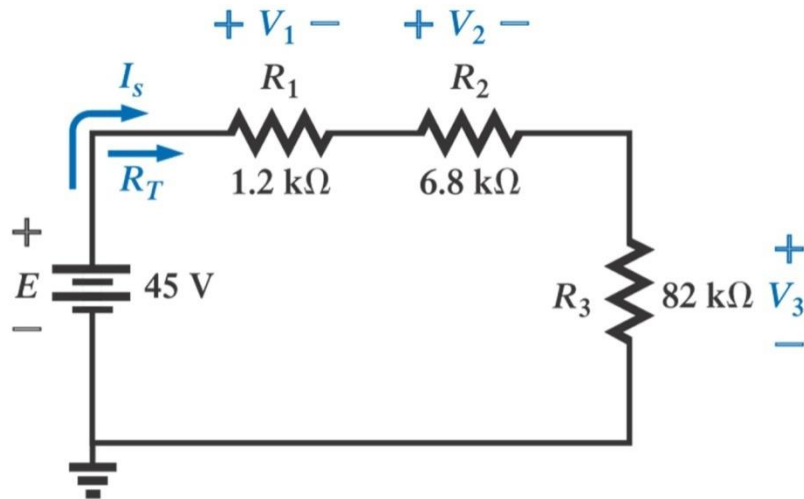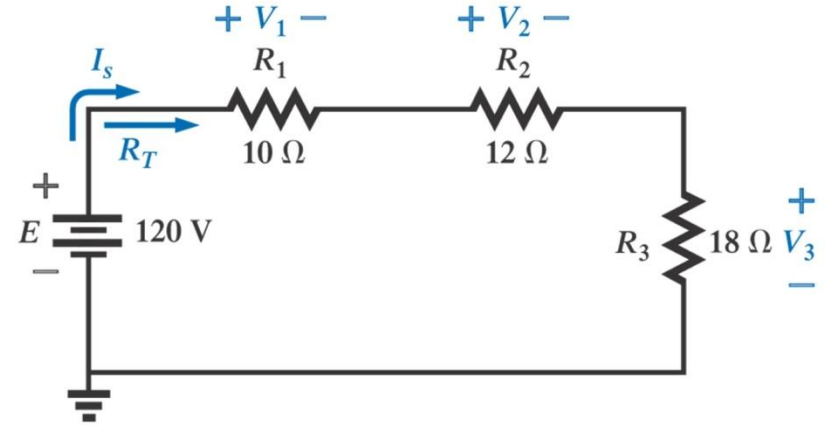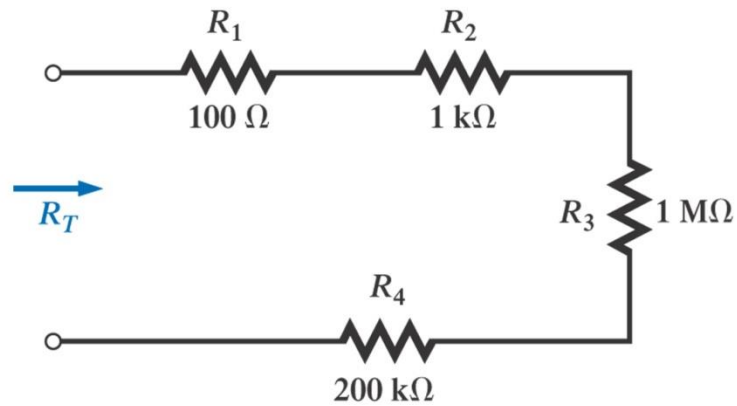


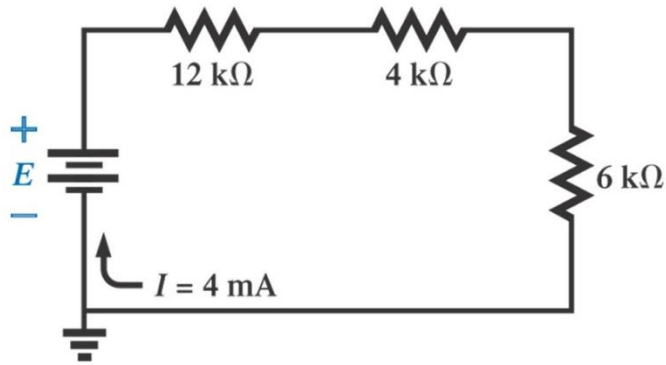


(a)

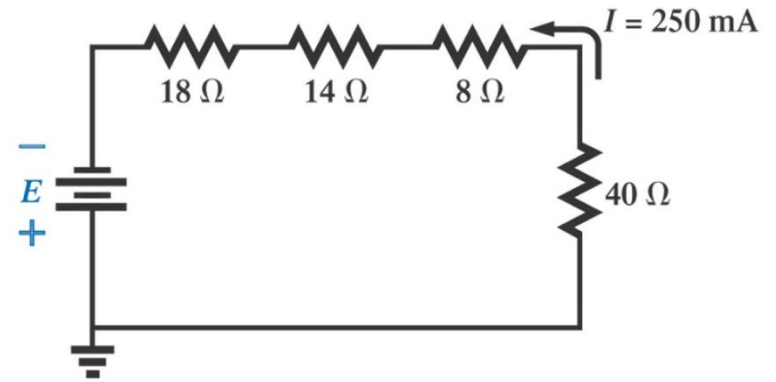


(b)

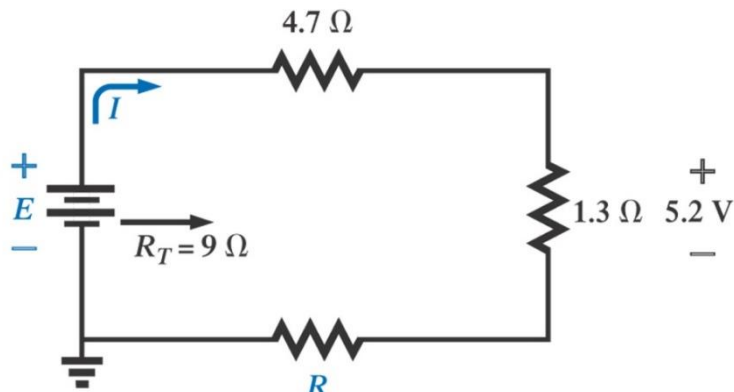


(a)

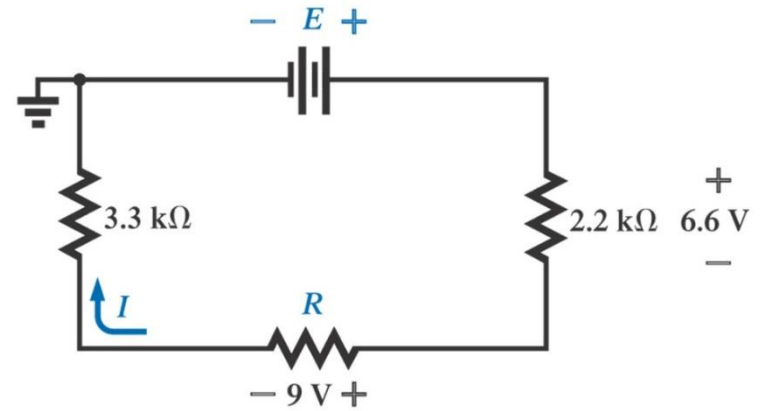


(b)

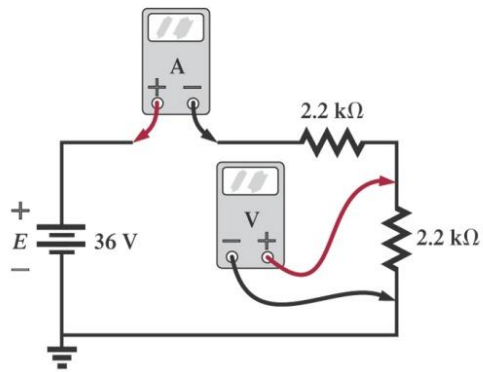

(a)

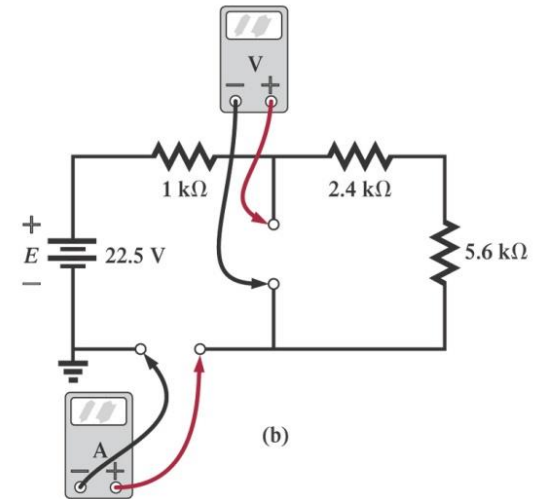


(b)

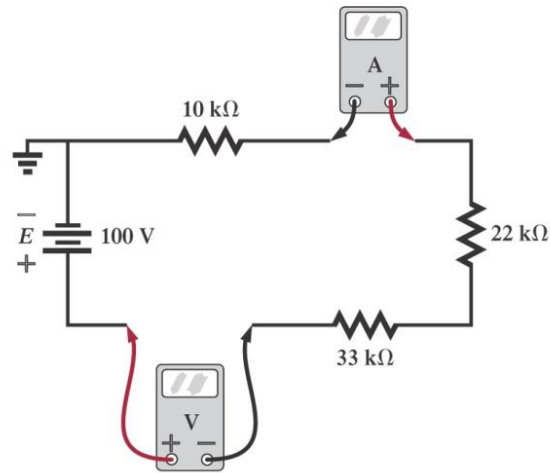


$R_{\text{int}}(\text{meter}) = 10 \text{ M}\Omega$

(c)









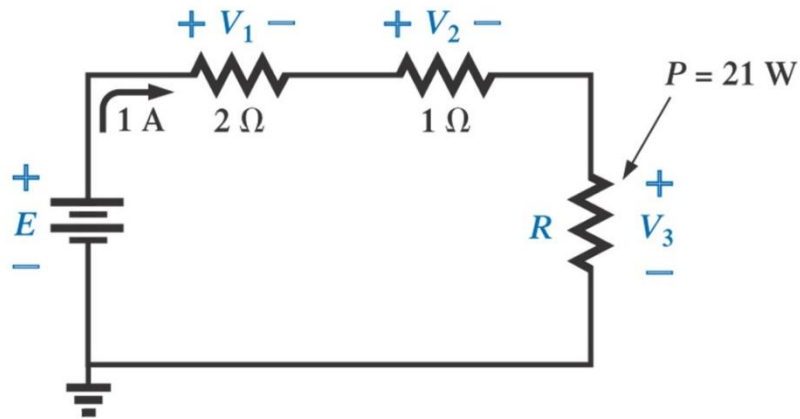





(a)

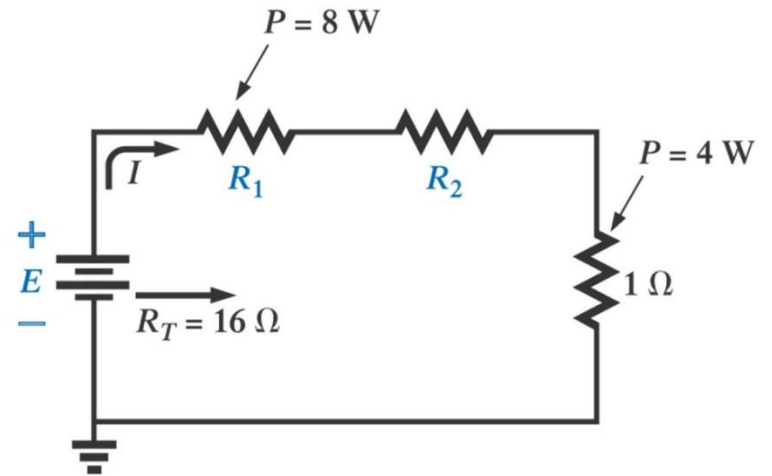


(b)

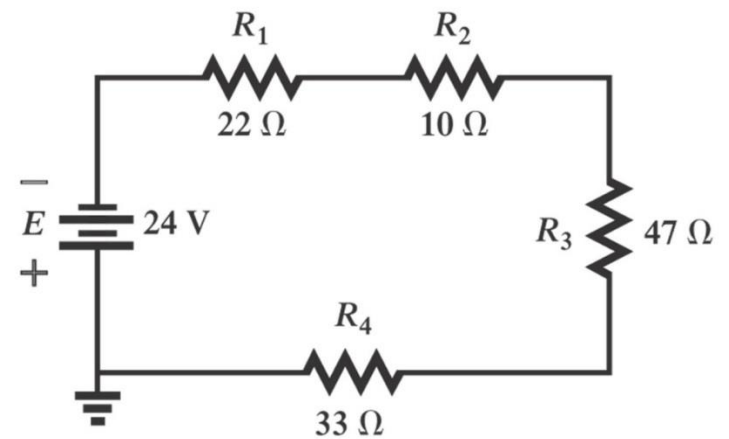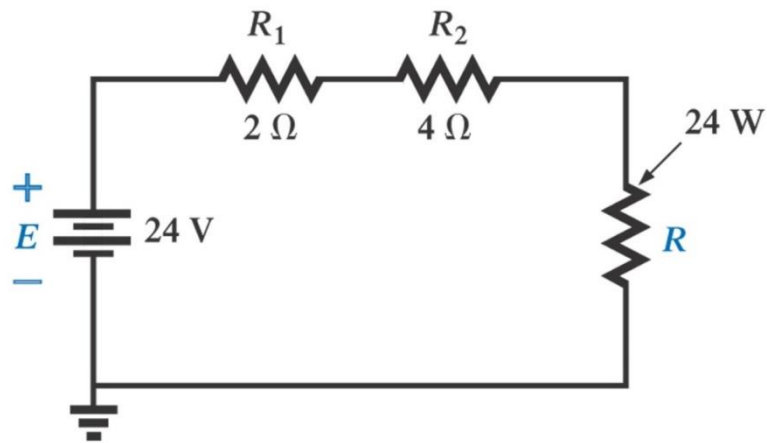


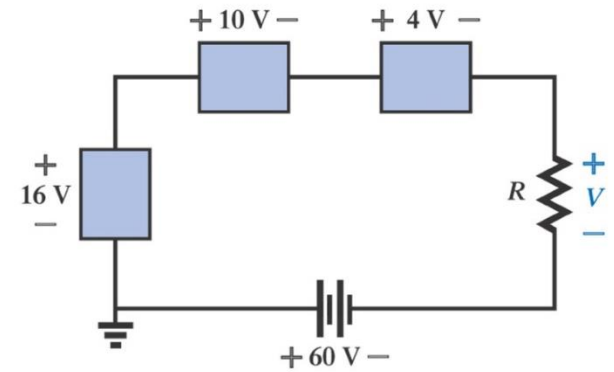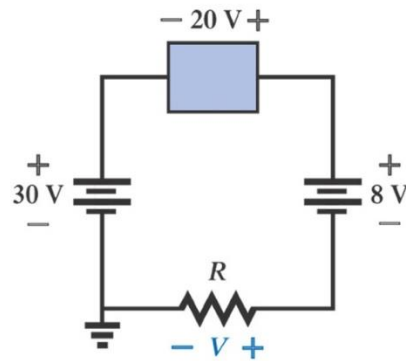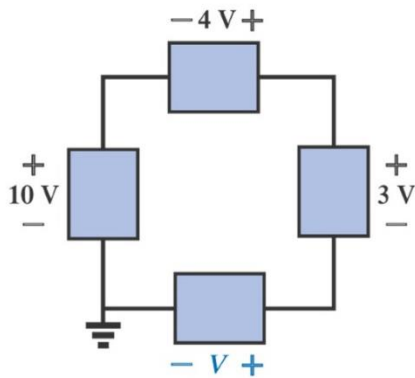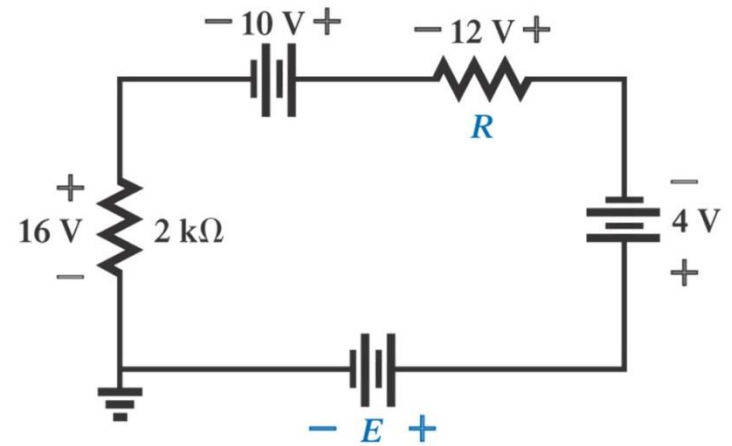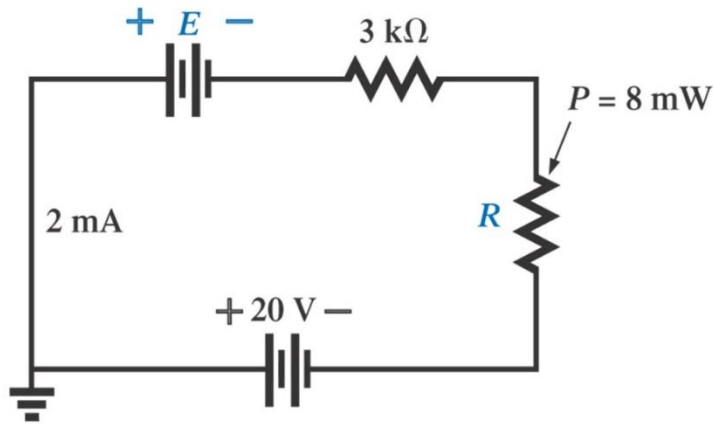

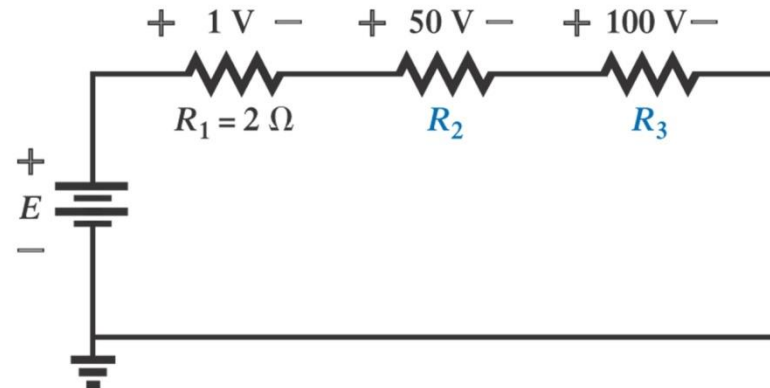
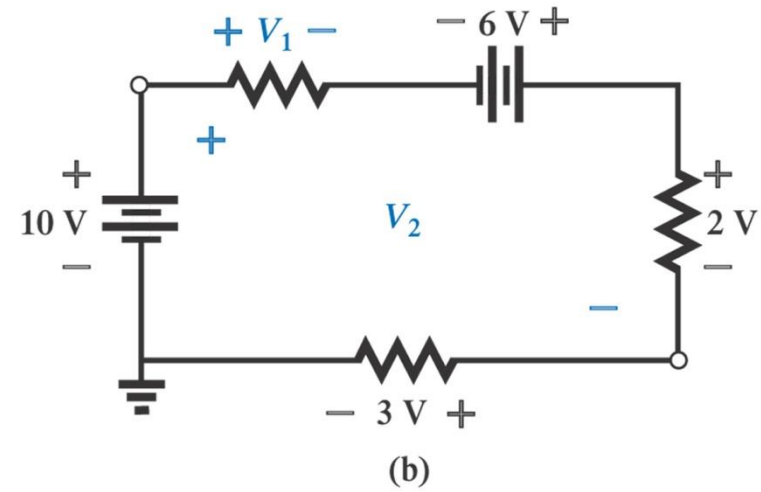
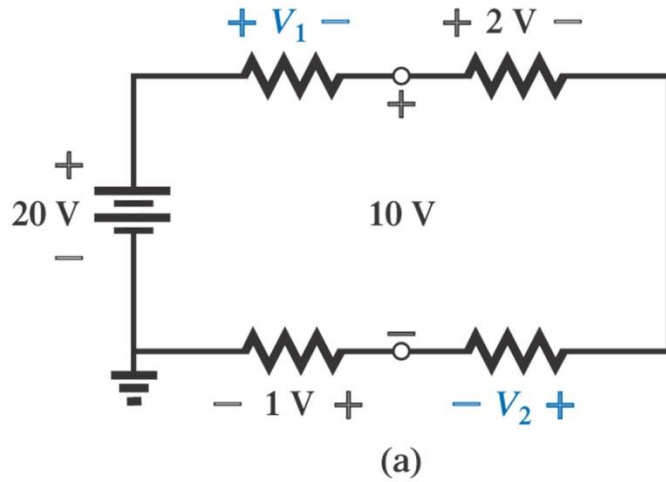


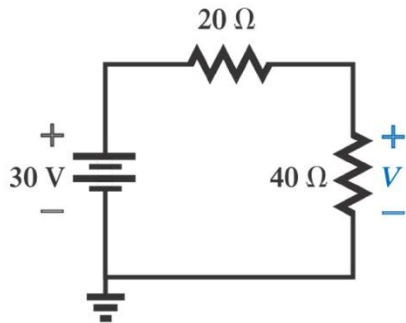


(a)

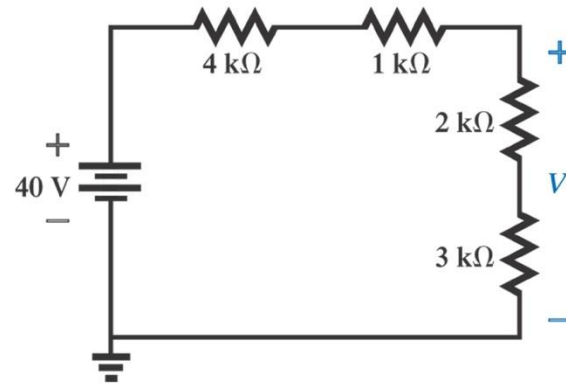


(b)

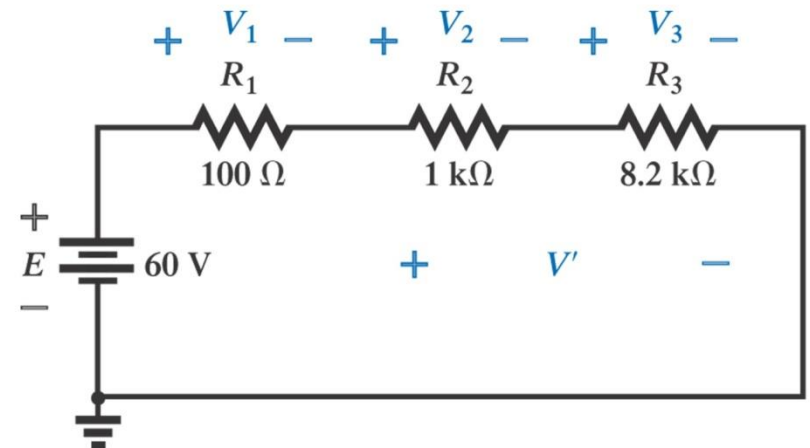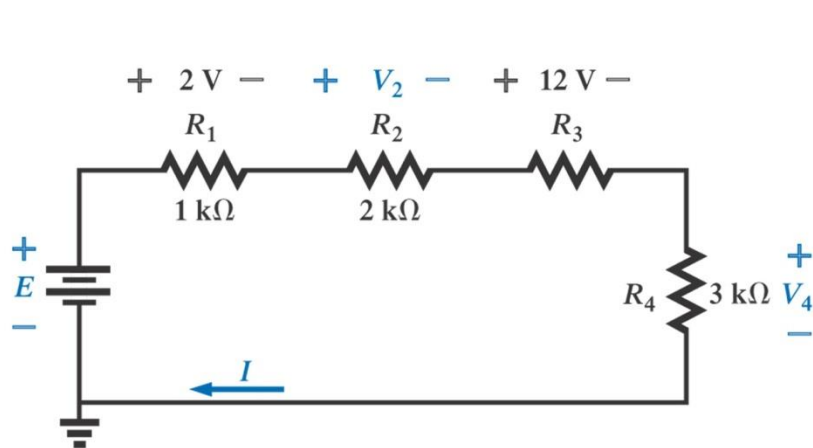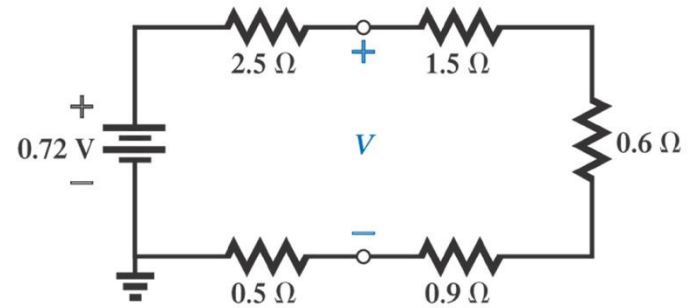


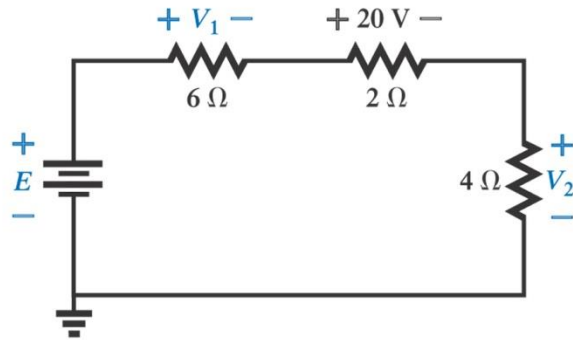


(a)

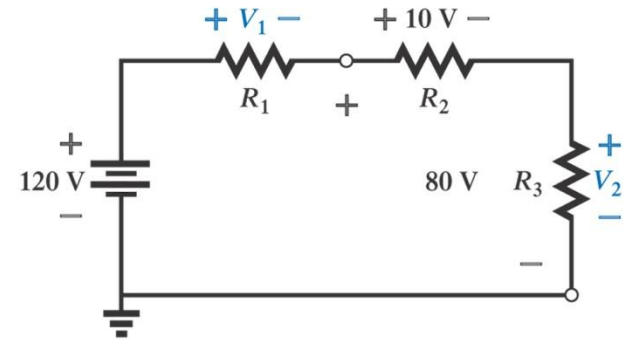





(b)

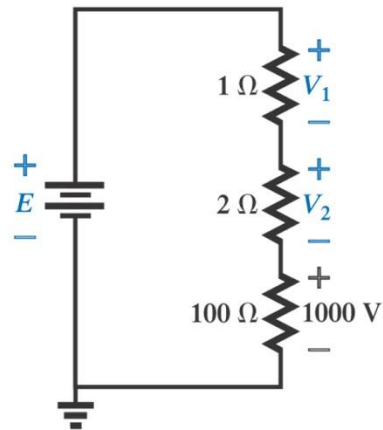

(c)

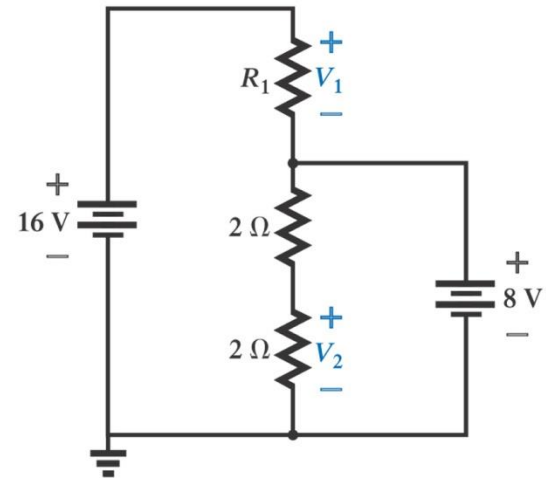

(d)

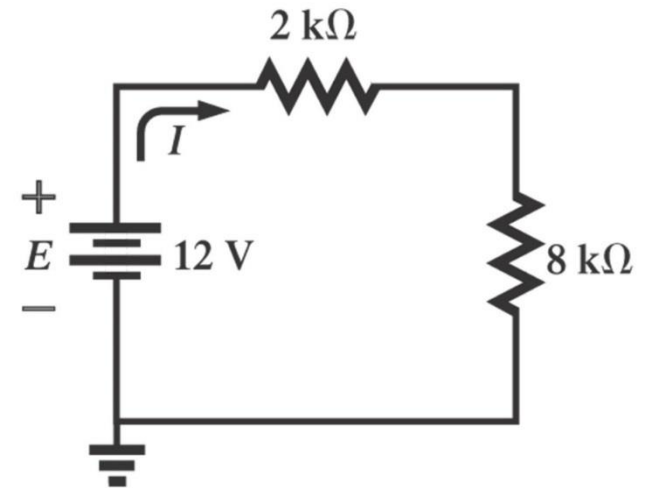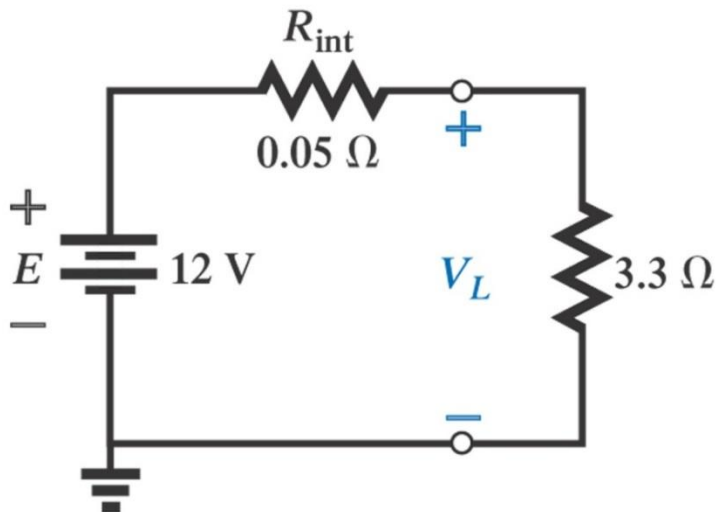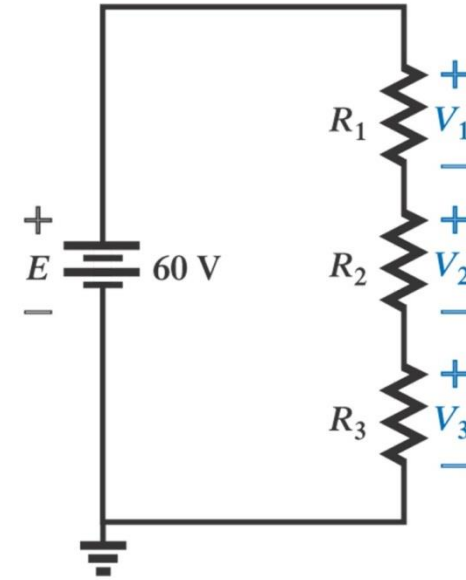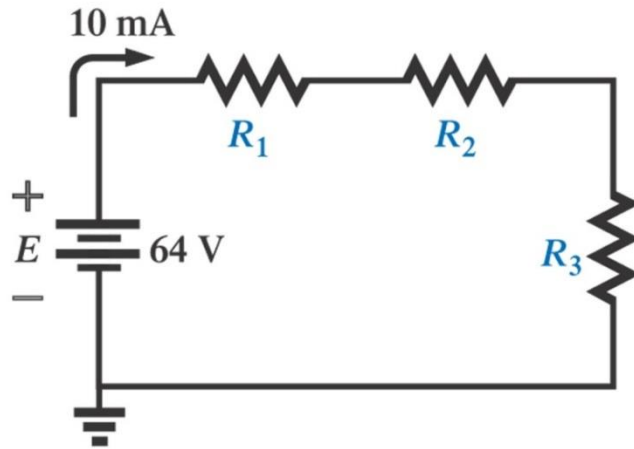

**ELECTRICAL AND ELECTRONICS  
FOR DESIGN  
(SRSD 3092)  
Semester II 2015/2016**

**(PARALLEL CIRCUIT)  
Week 3-1**

*Prepared by : DR NELIDYA MD YUSOFF*




# Topics

- 6.1 Parallel Resistors
- 6.2 Parallel Circuits
- 6.3 Power Distribution in a Parallel Circuit
- 6.4 Kirchhoff's Current Law
- 6.5 Current Divider Rule
- 6.6 Voltage Sources in Parallel



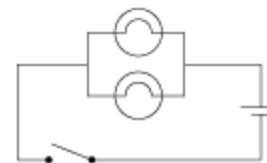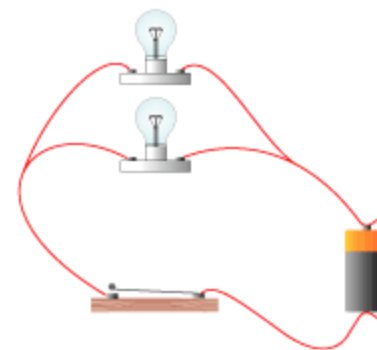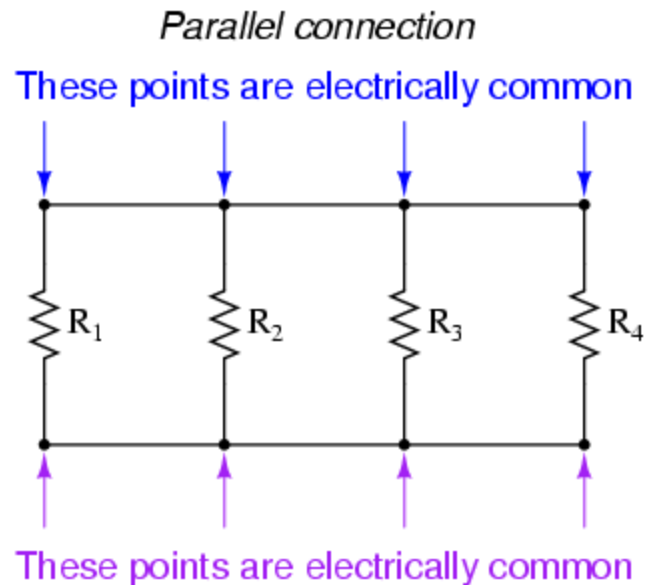
# Parallel circuit

- All components are connected across each other's leads.
- There are never more than two sets of electrically common points, no matter how many components are connected.






# Parallel circuit

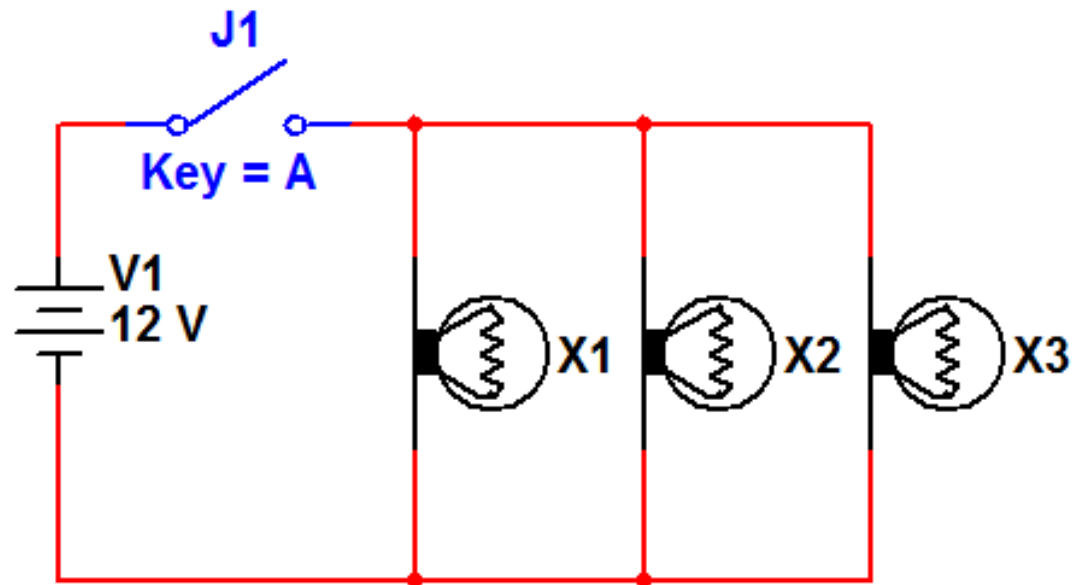
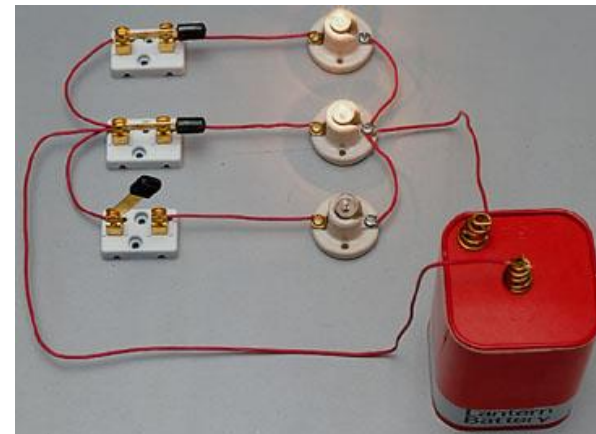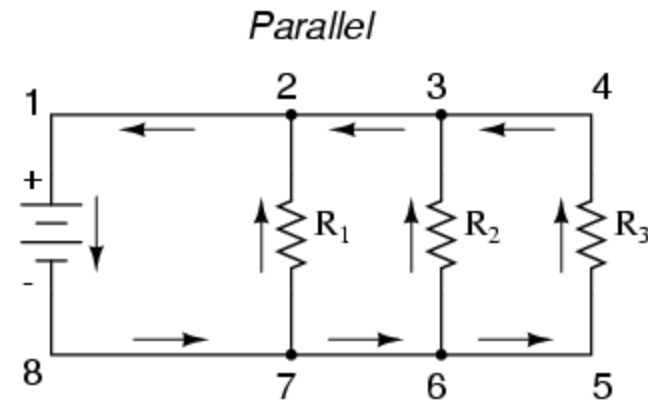
# Example of a parallel circuit


- 3 resistors form more than one continuous path for electrons to flow.
- Each individual path (through  $R_1$ ,  $R_2$ , and  $R_3$ ) is called a *branch*.
- All components are connected between the same set of electrically common points.
- Looking at the schematic diagram, we see that points 1, 2, 3, and 4 are all electrically common. So are points 8, 7, 6, and 5.



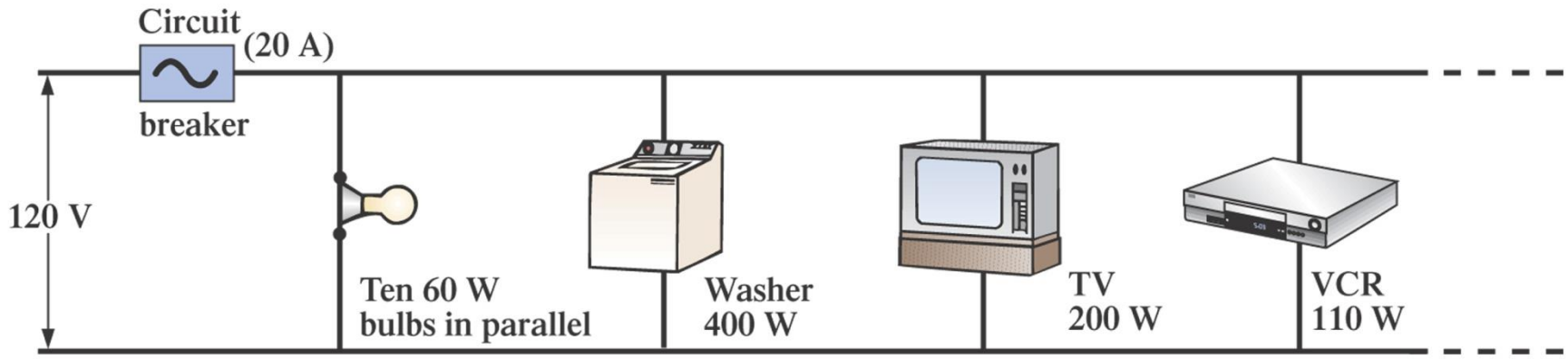

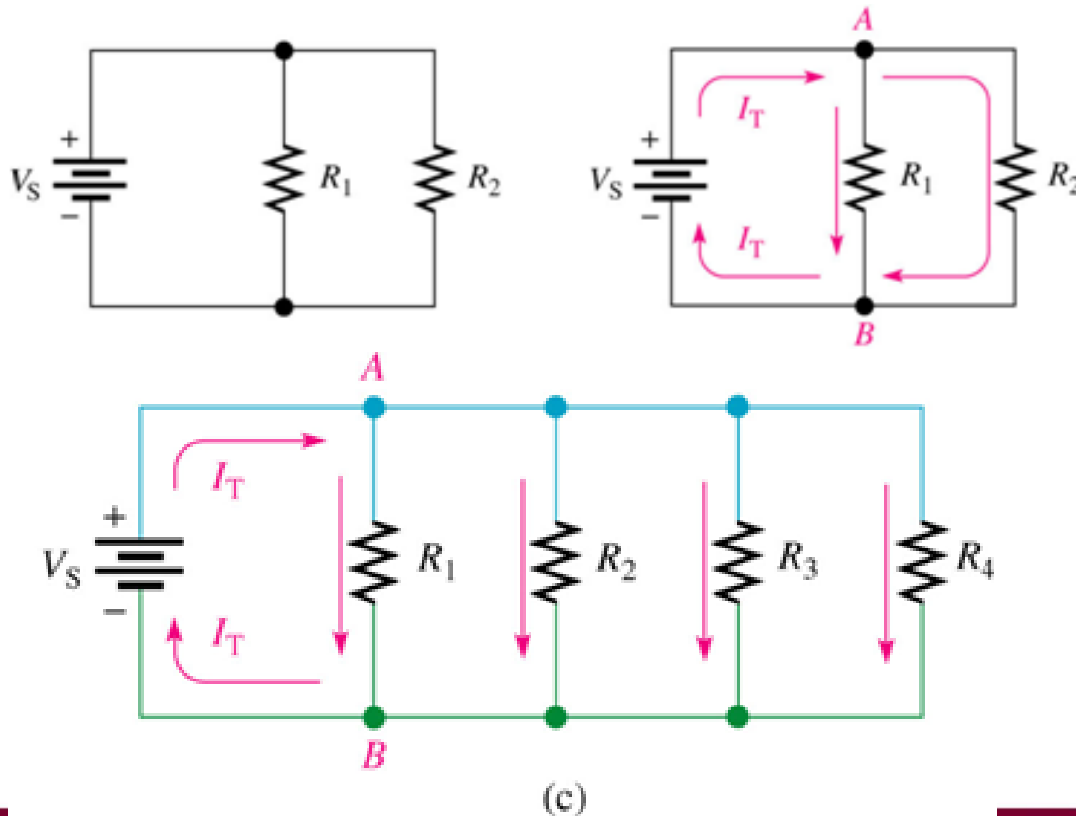
# Resistors in Parallel


- Two elements, branches or circuits are in parallel if they have two, and only **two points** in **common**
- Each current path is called a branch.
- A parallel circuit is one that has more than one branch.



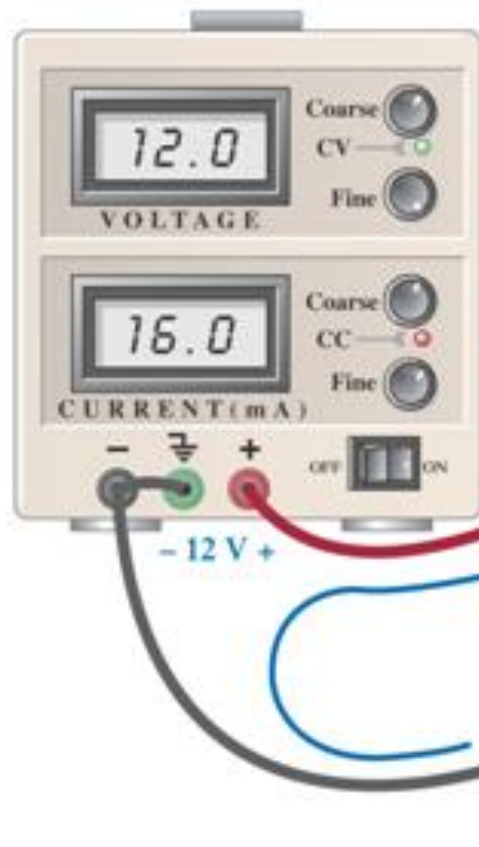
Parallel circuit: (a) actual; (b) schematic.




(a)

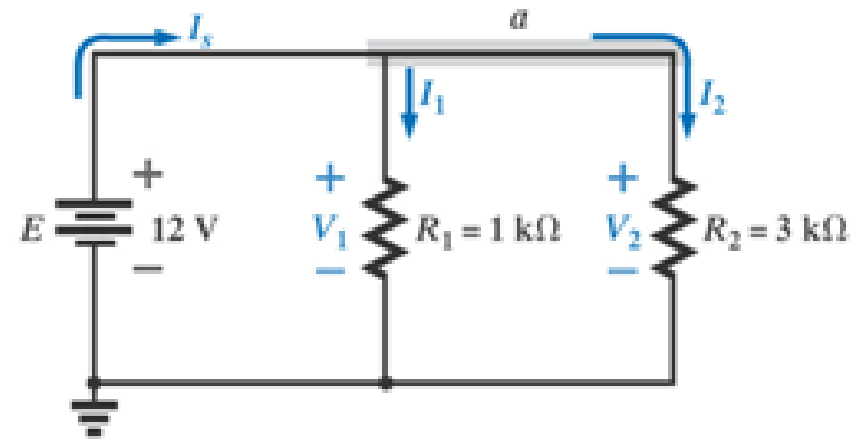


(b)

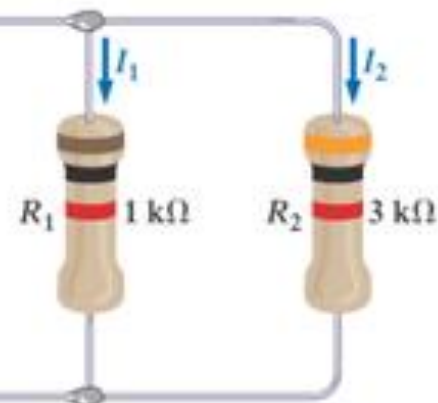


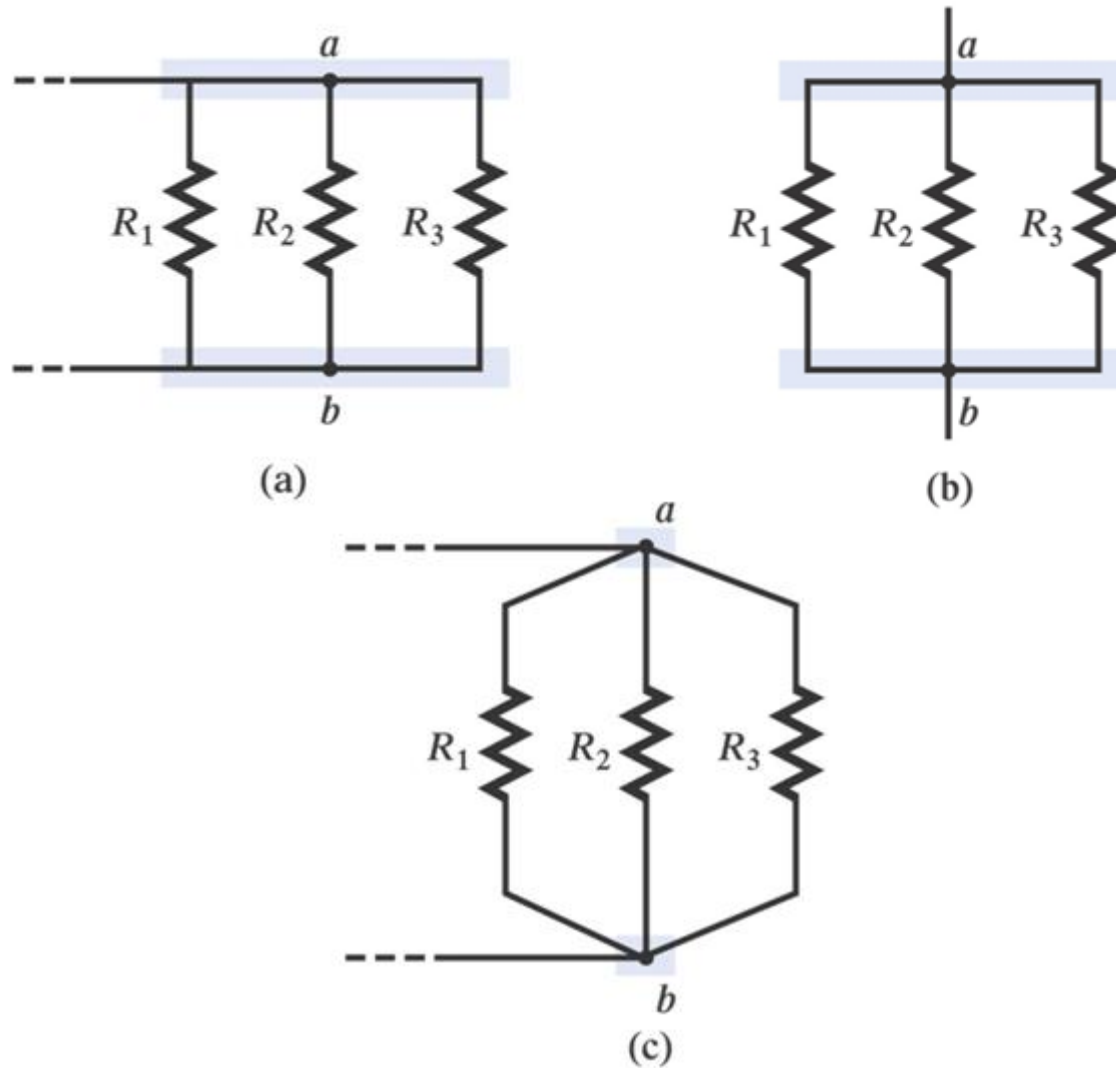
## Schematic representations of three parallel resistors.



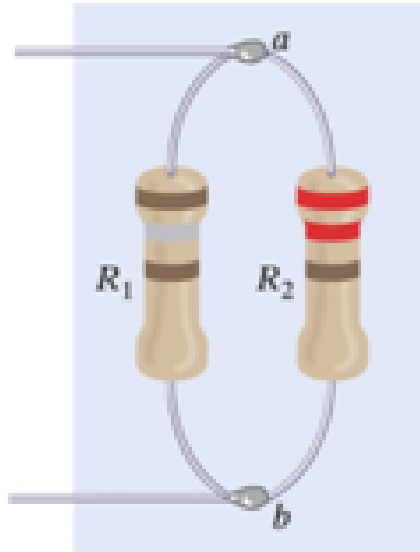
(a) Parallel resistors; (b)  $R_1$  and  $R_2$  are in parallel; (c)  $R_3$  is in parallel with the series combination of  $R_1$  and  $R_2$ .



(a)

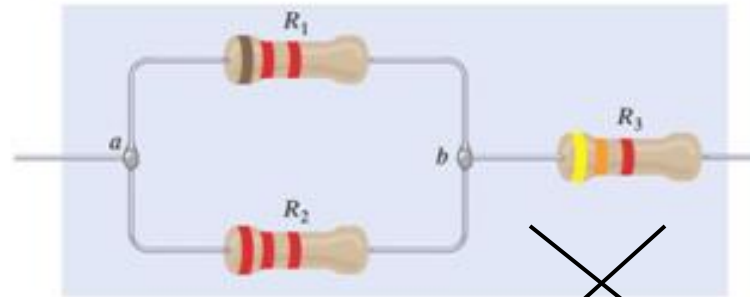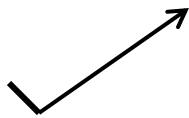

(b)

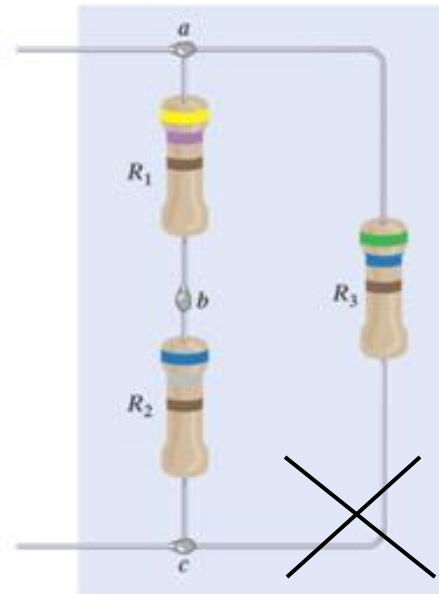

(c)



# Parallel Circuits

- Identifying Parallel Circuits


If there is **more than one current path (branch)** between two separate points (nodes), then there is a parallel circuit between those two points.

- Voltage in Parallel Circuits

The **voltage** across any given branch of a parallel circuit is **equal** to the voltage across each of the other branches in parallel
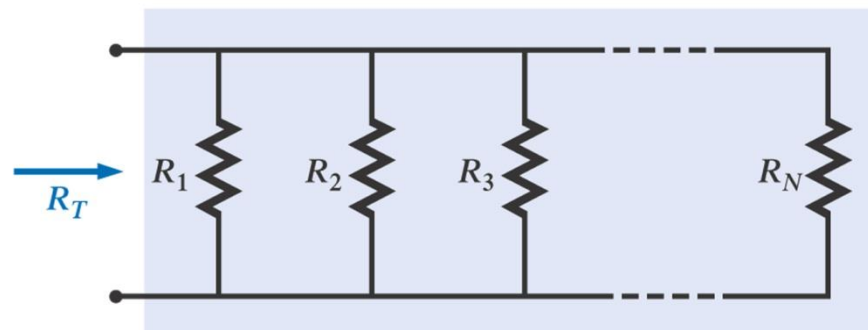
# Total Parallel Resistance

- When resistors are connected in parallel, the **total resistance** of the circuit **decreases**.
- The **total** resistance of a parallel circuit is always **less** than the value of the **smallest resistor**.



$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

# Parallel Resistors


- For resistors in parallel


The total resistance of **two parallel resistors** is the product of their values divided by their sum


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_2 + R_1}{R_1 R_2}$$


$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

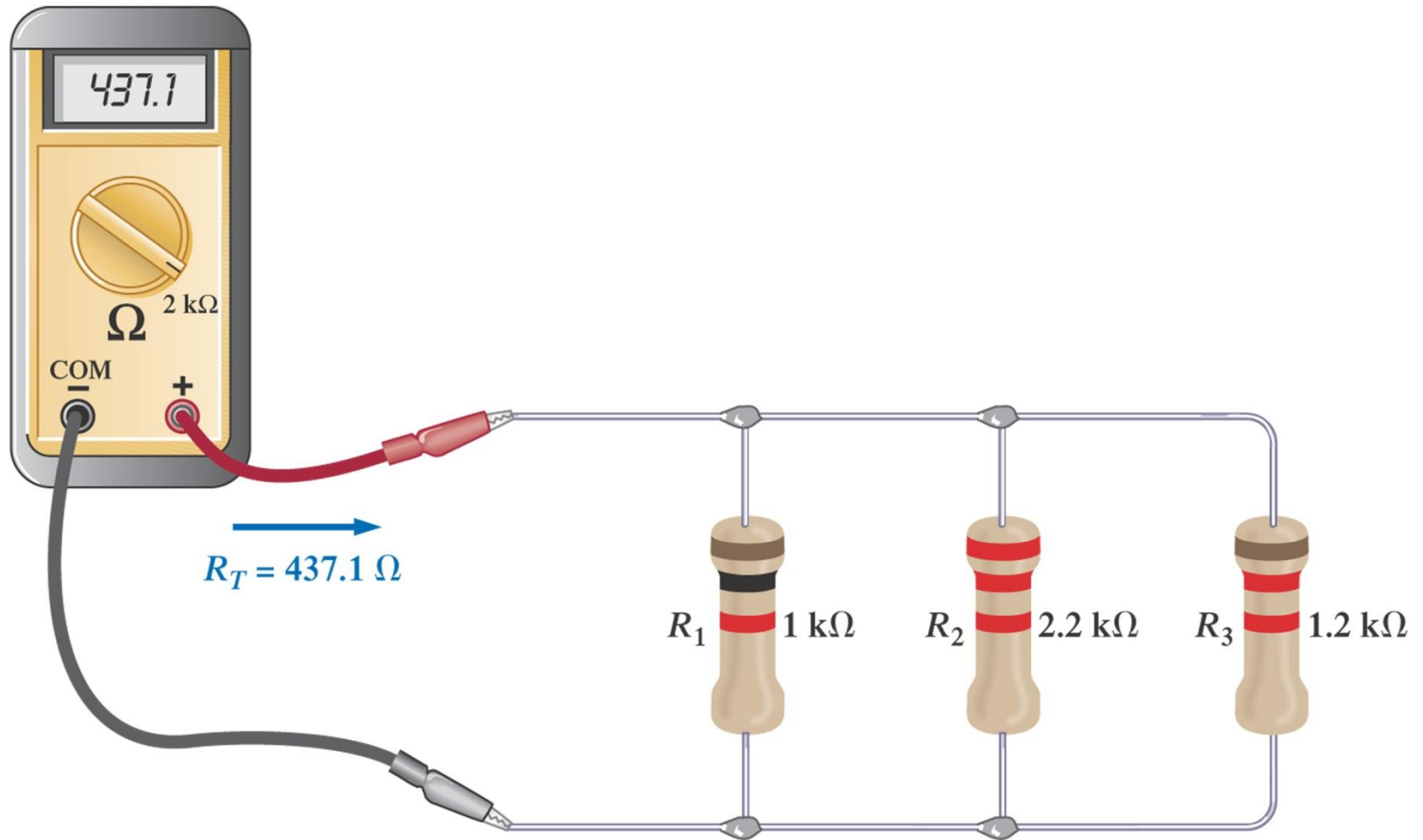Using an ohmmeter to measure the total resistance of a parallel network.




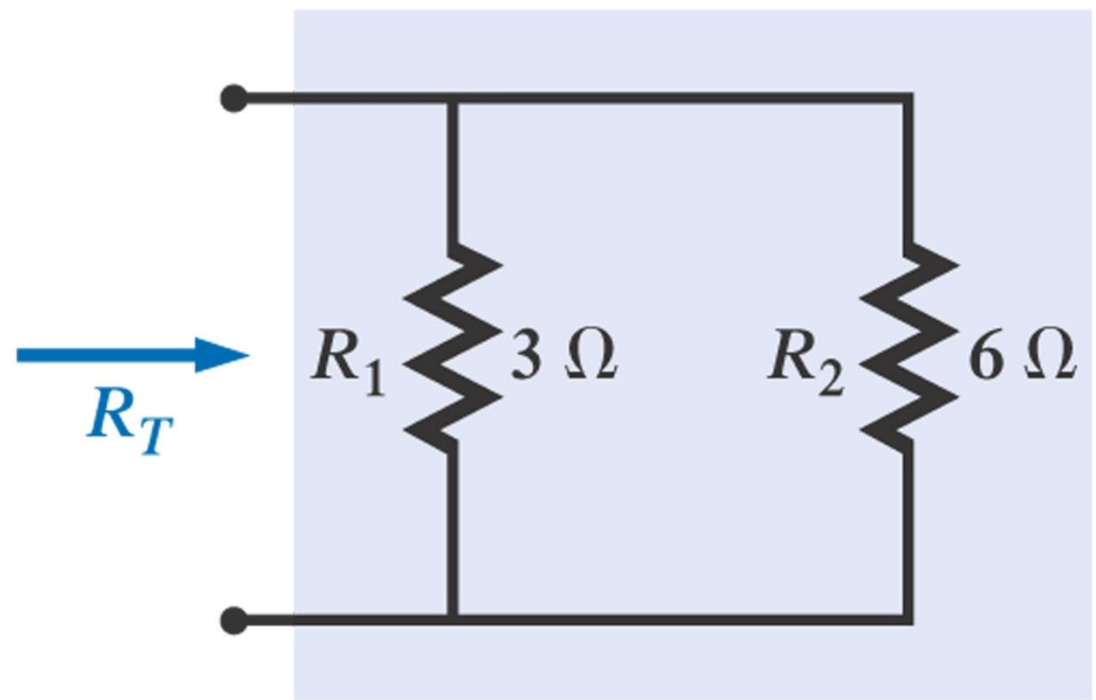

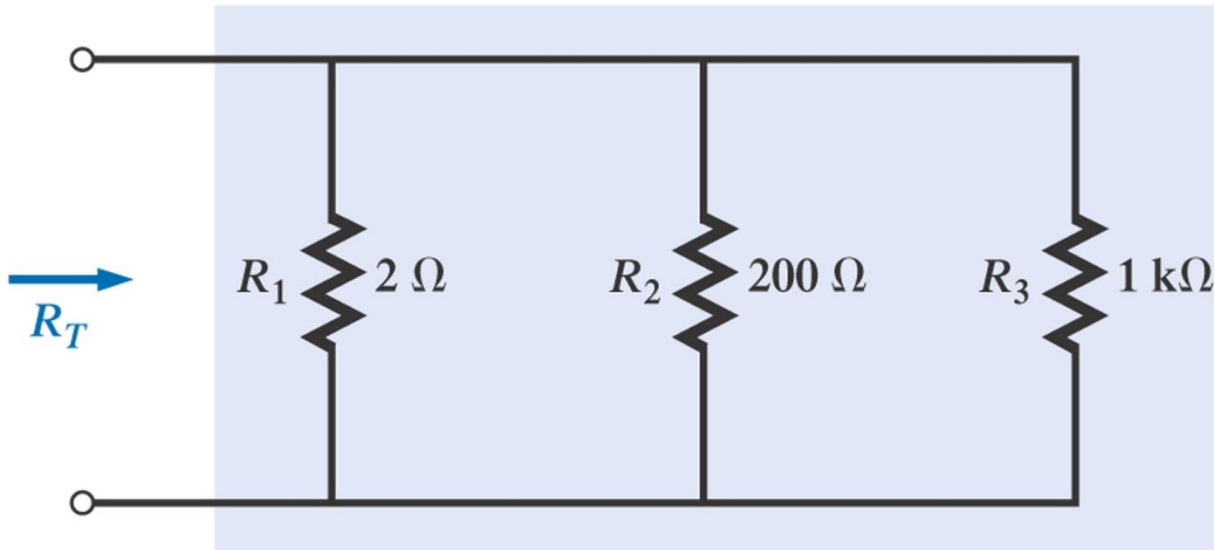


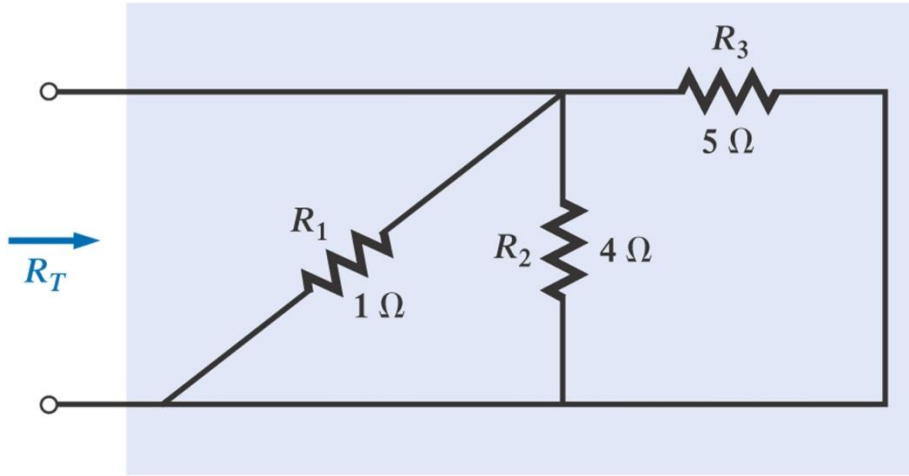

Redraw

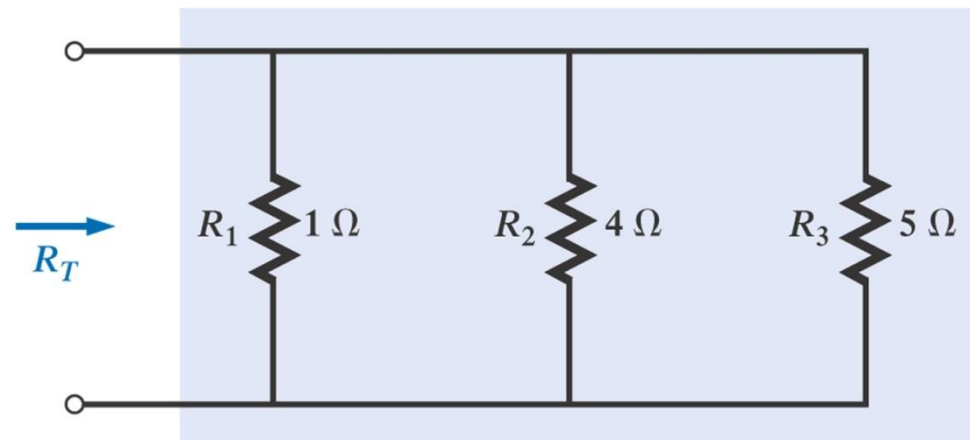


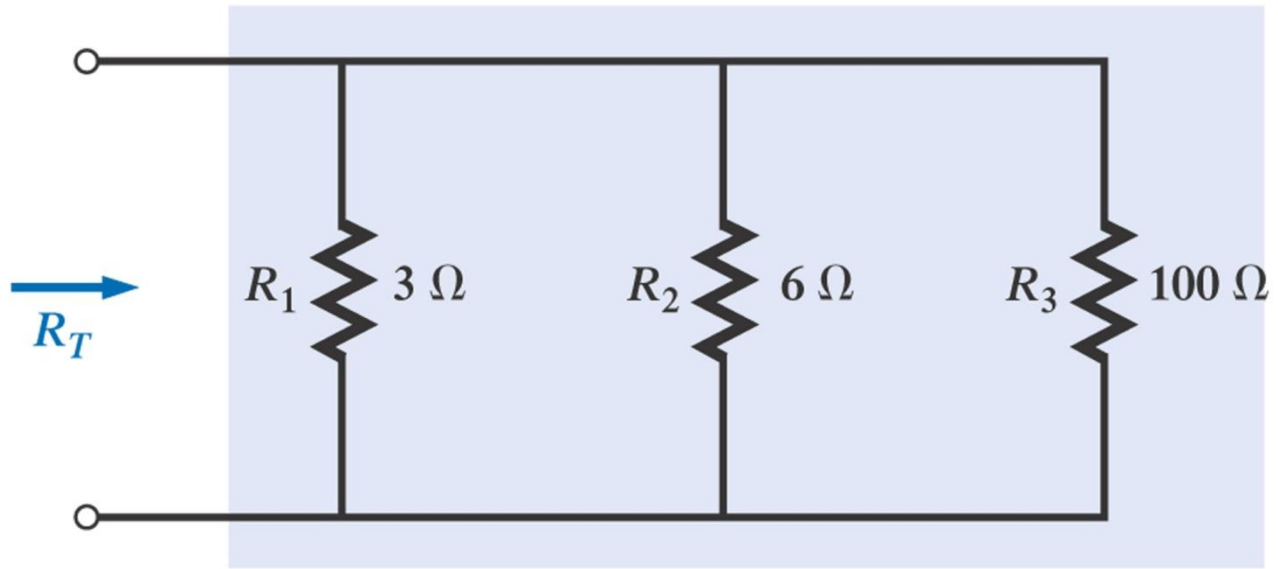Adding a parallel 100  $\Omega$  resistor to the network






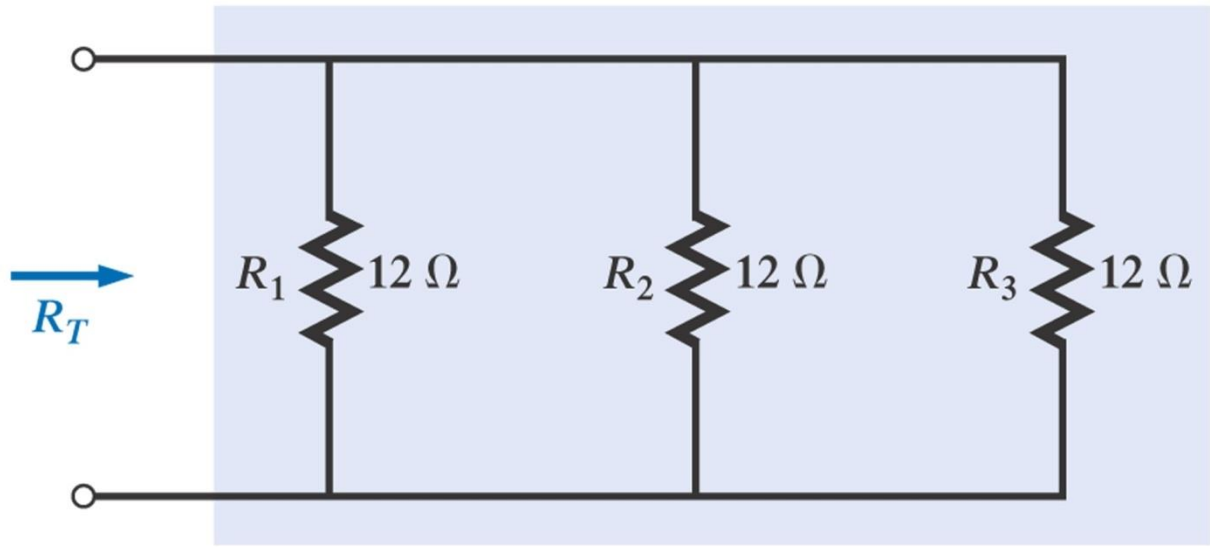
Three equal parallel resistors to be investigated






Parallel configuration

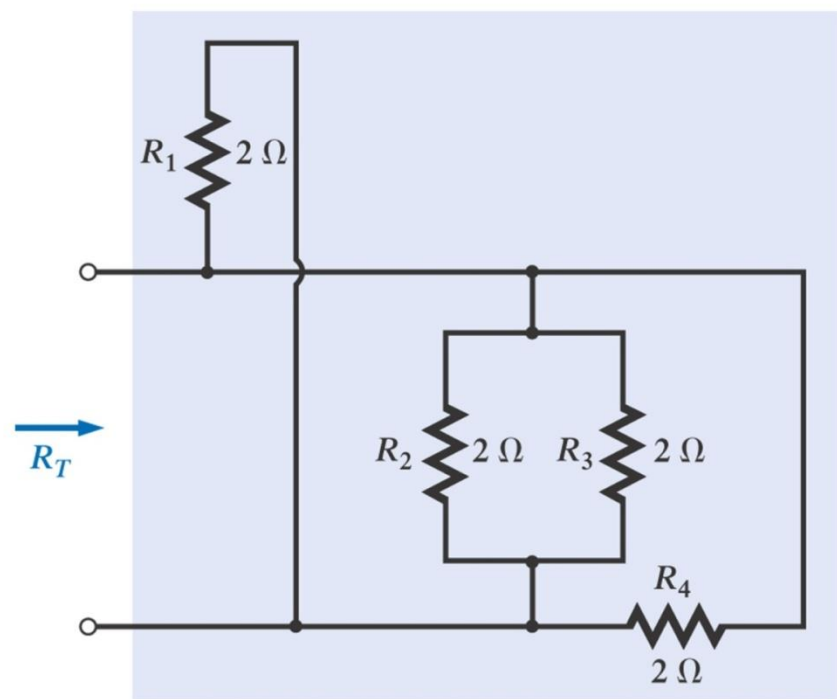

Redraw

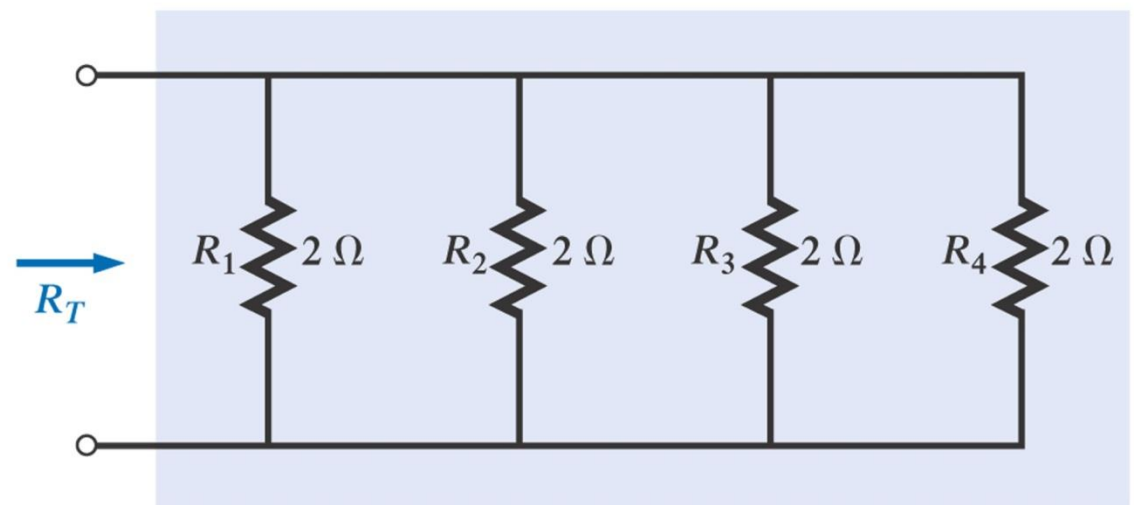


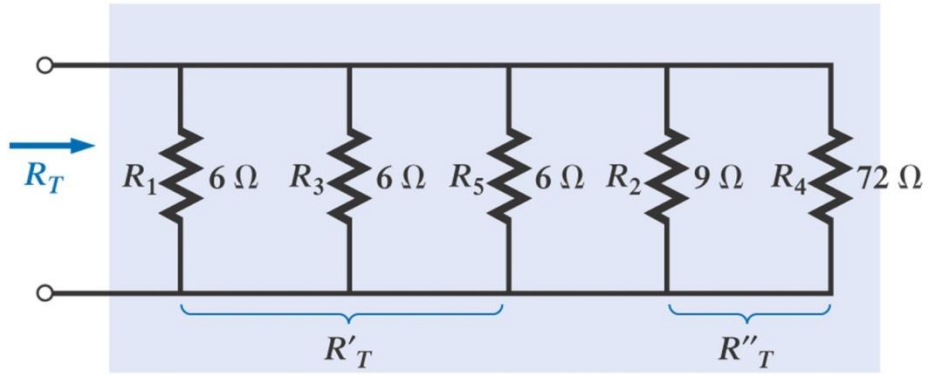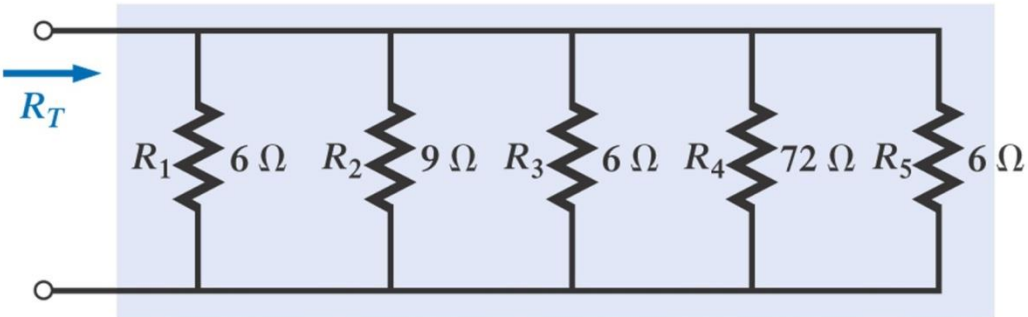

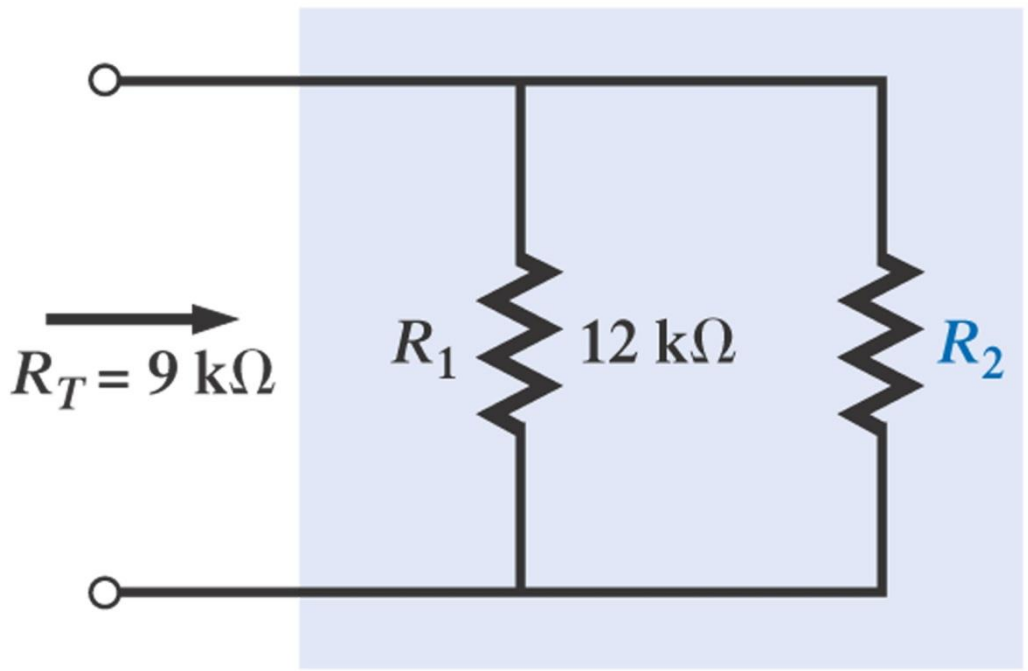
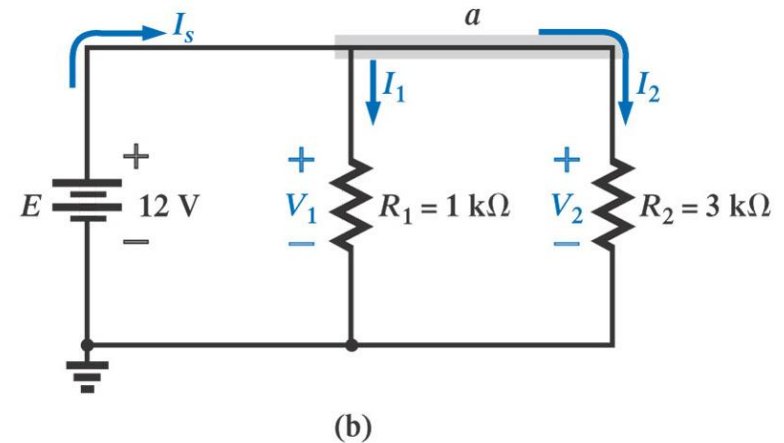
# Parallel Resistors


- The **voltage is the same** across parallel elements
- The source does not “see” the parallel combination, it only reacts to the total resistance
- The source current is:



$$V_{ab} = E = V_1 = V_2$$

$$I_s = \frac{E}{R_T}$$

# The voltages of a parallel dc network.

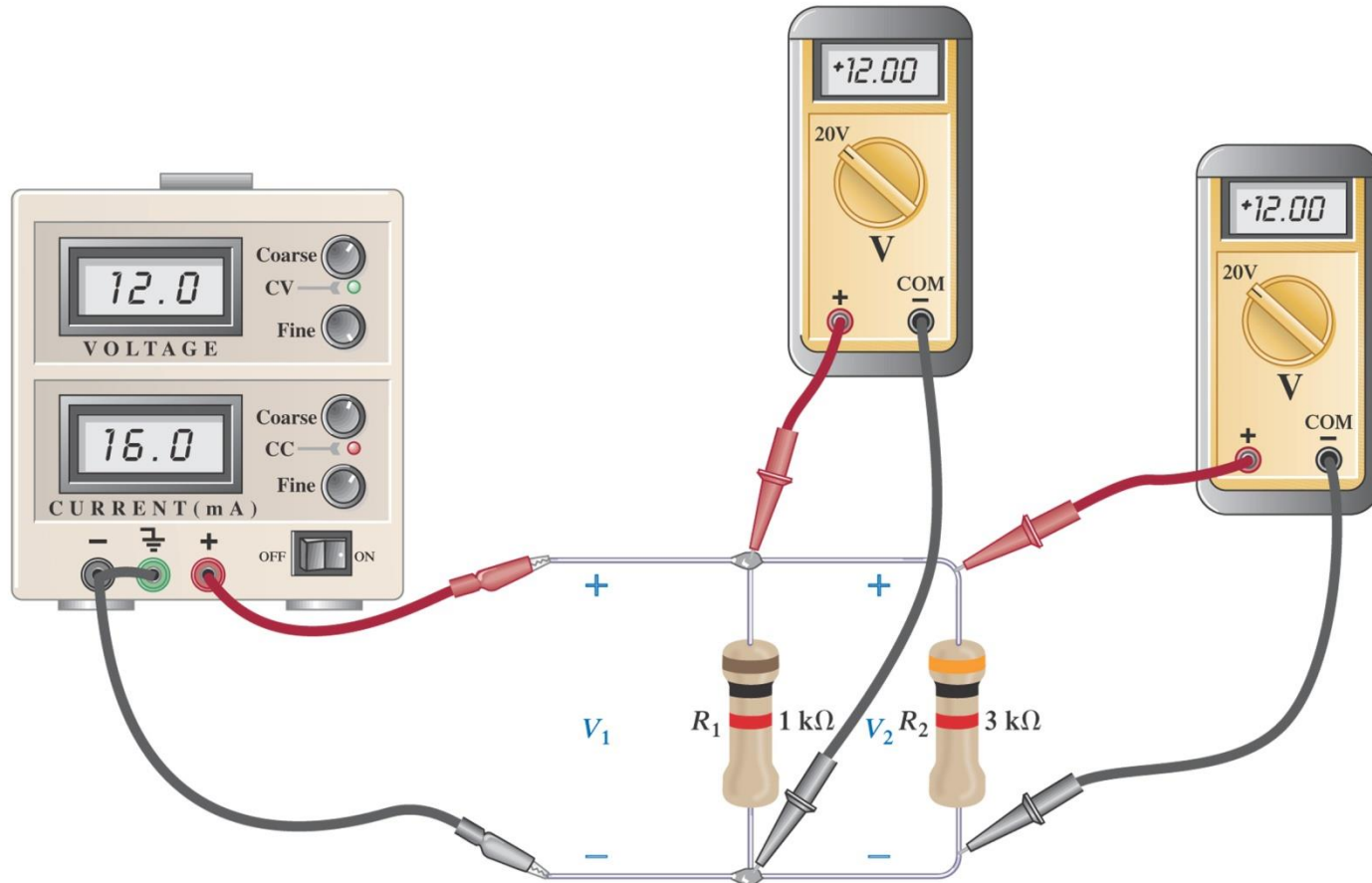

# Parallel Resistors

- Since the voltage is the same across parallel elements, the current through each resistor can be determined using Ohm's law


$$I_1 = \frac{V_1}{R_1} = \frac{E}{R_1} \quad \text{and} \quad I_2 = \frac{V_2}{R_2} = \frac{E}{R_2}$$
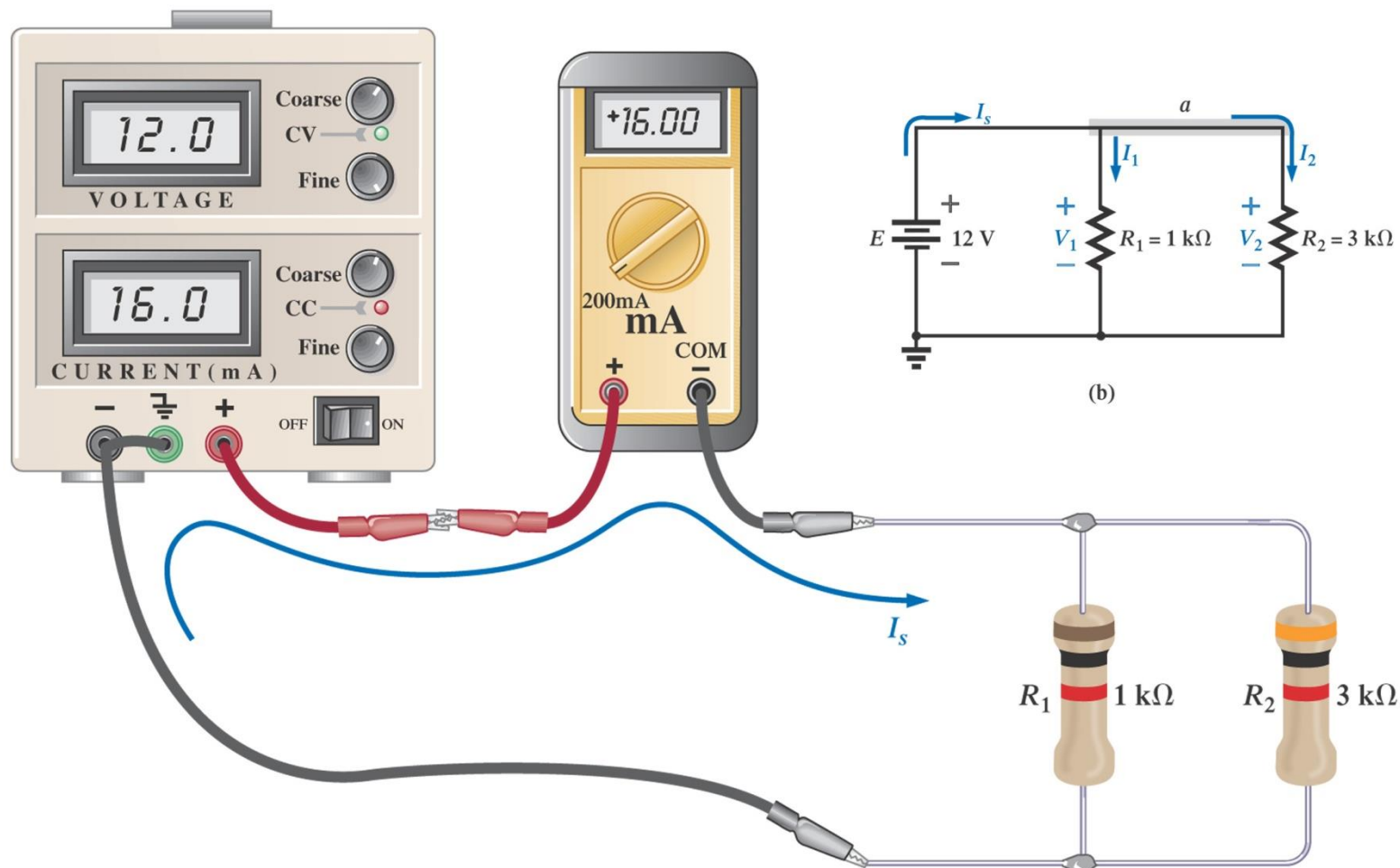
# Parallel Resistors


- For parallel resistors, the **greatest current** will exist in the branch with the **least resistance**
  - current always seeks the path of least resistance



To measure current through a resistor in a parallel circuit, break the **connection at the point of interest** and insert the ammeter with the current entering the positive (red) lead


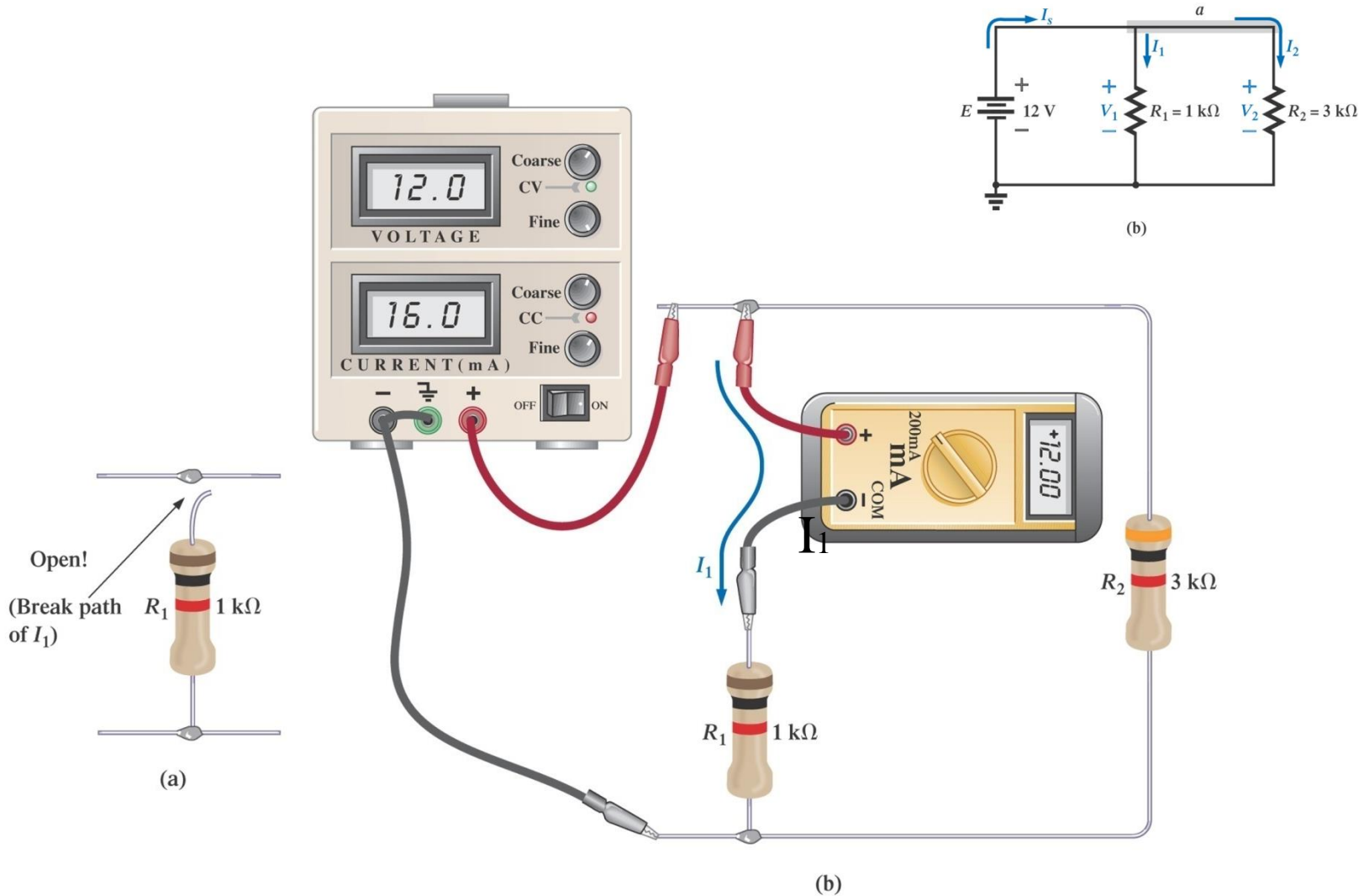
# Measuring the current through resistor $R_1$ .




# Kirchhoff's Current Law (KCL)

The sum of the currents into a junction (total current in) is equal to the sum of the currents out of that junction (total current out).

$$I_{IN(1)} + I_{IN(2)} + \dots + I_{IN(n)}$$
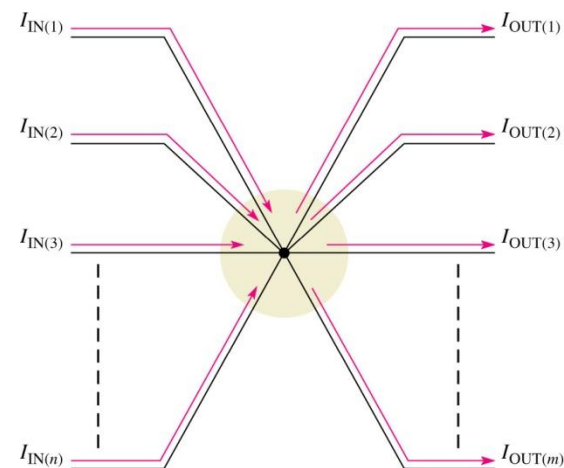
$$= I_{OUT(1)} + I_{OUT(2)} + \dots + I_{OUT(m)}$$




$$I_{IN(1)} + I_{IN(2)} + I_{IN(3)} + \dots + I_{IN(n)} = I_{OUT(1)} + I_{OUT(2)} + I_{OUT(3)} + \dots + I_{OUT(m)}$$

# Kirchhoff's Current Law


- Kirchhoff's current Law (KCL) can be stated another way:

**The algebraic sum of all the currents entering and leaving a junction is equal to zero.**


$$\Sigma I_i = \Sigma I_o$$

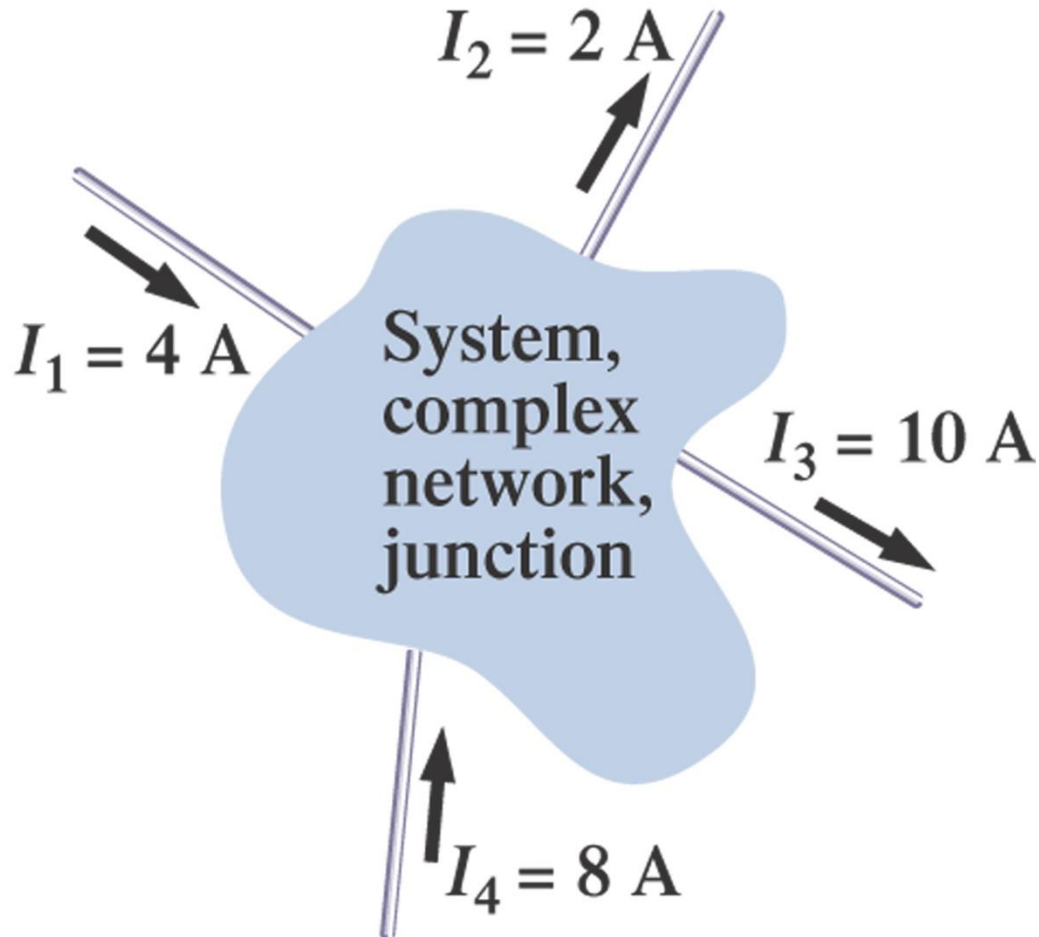

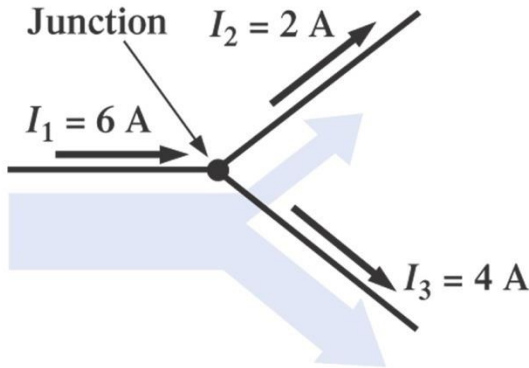(a) Demonstrating Kirchhoff's current law; (b) determining whether a current is entering or leaving a junction.




(a)

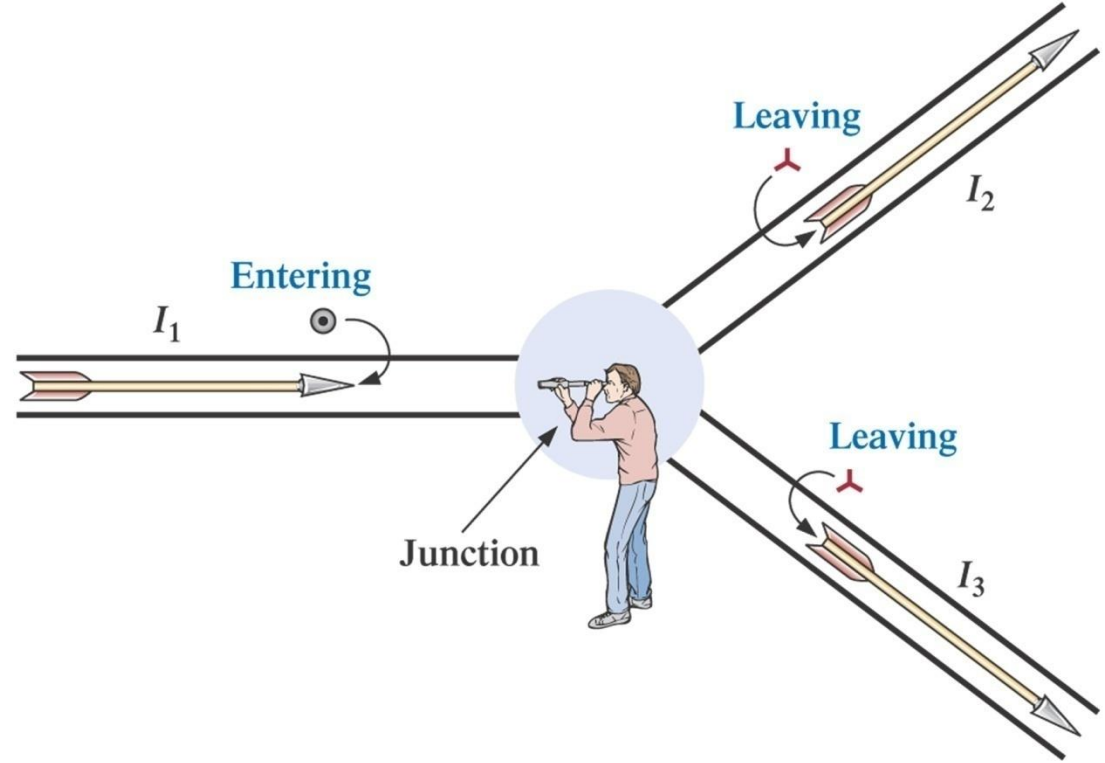


(b)





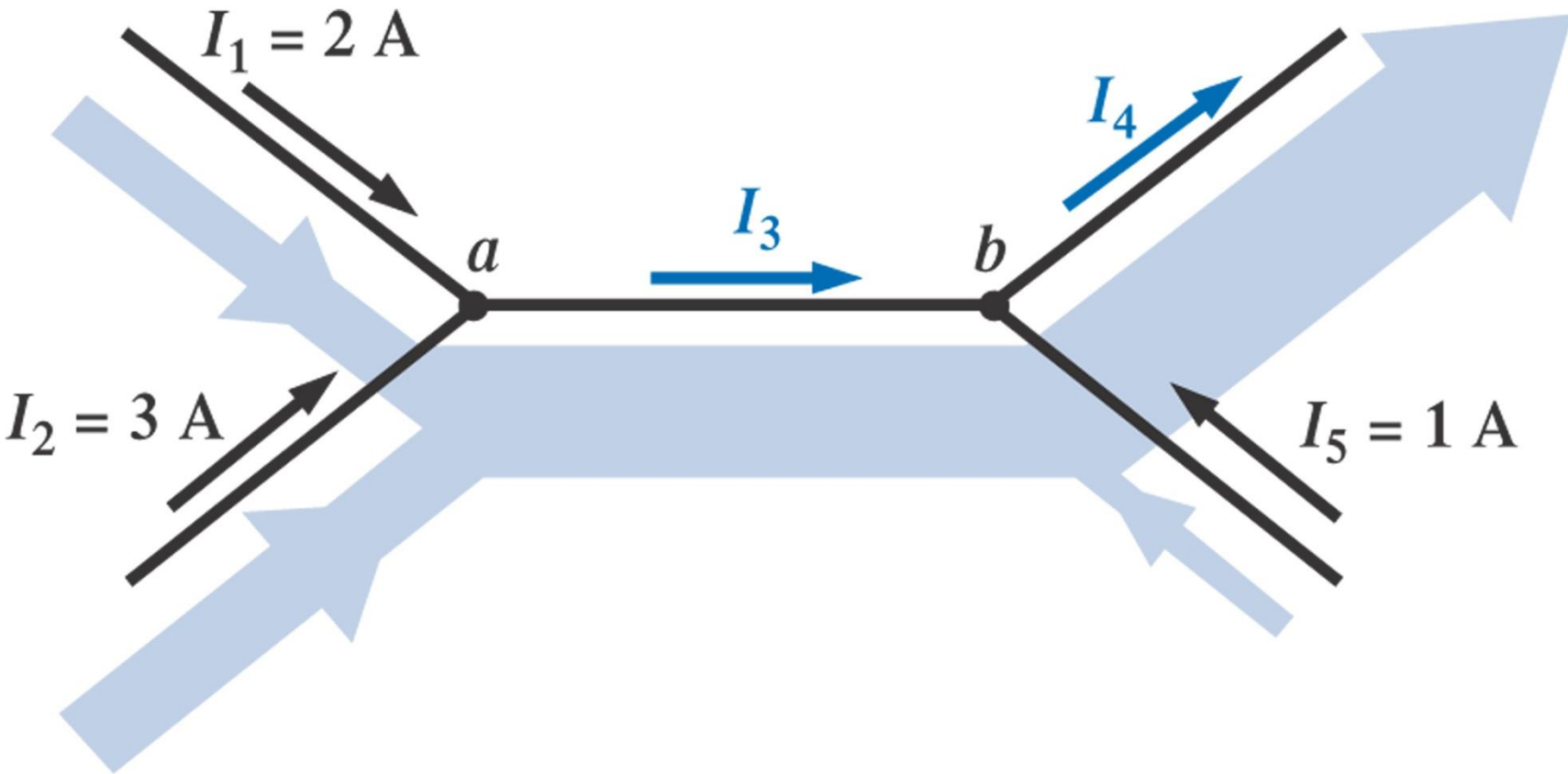



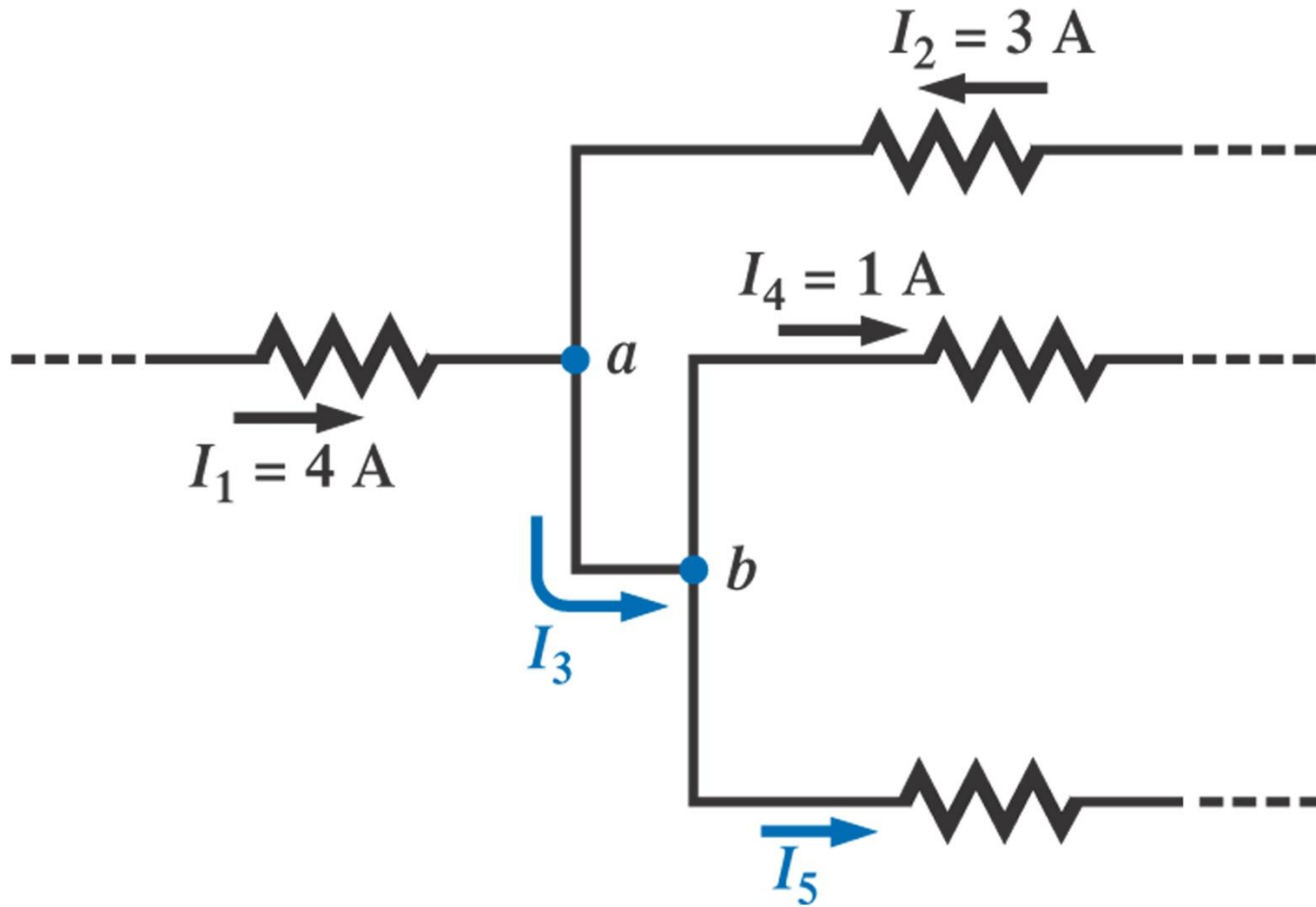

# Kirchhoff's Current Law

- If the direction of the current is not known:
  - make an **assumption** about the direction and then check out the result
  - if the result is negative, the wrong direction was assumed
  - if positive, the correct direction was assumed
  - in either case, the **magnitude** of the current will be **correct**

# Parallel Resistors

- For resistors in parallel


The total resistance of **two parallel resistors** is the product of their values divided by their sum

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_2 + R_1}{R_1 R_2}$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$
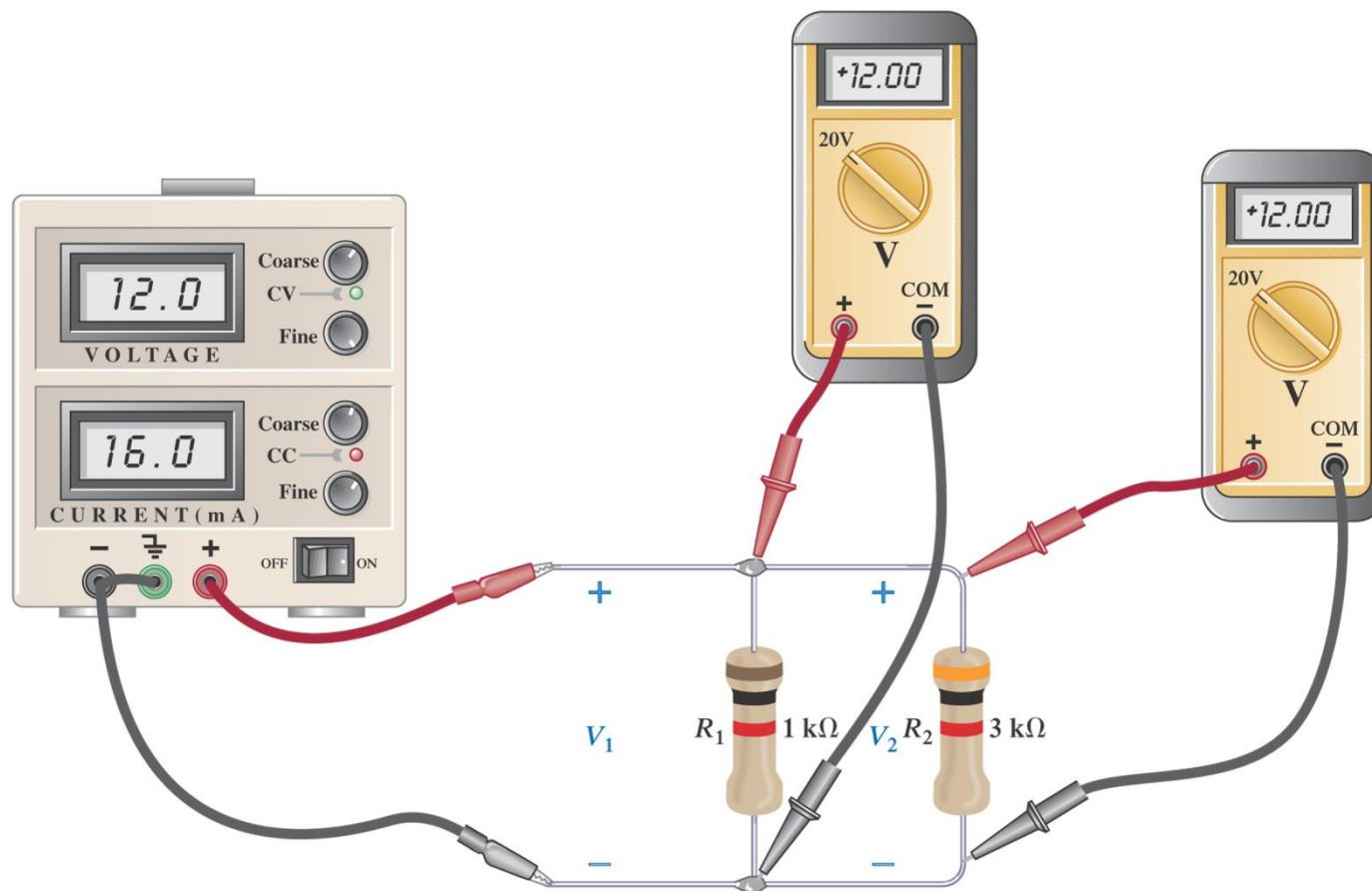
# Parallel Resistors

the voltage is the same across parallel elements



# Parallel Resistors


- Since the voltage is the same across parallel elements, the current through each resistor can be determined using Ohm's law

$$I_1 = \frac{V_1}{R_1} = \frac{E}{R_1} \quad \text{and} \quad I_2 = \frac{V_2}{R_2} = \frac{E}{R_2}$$
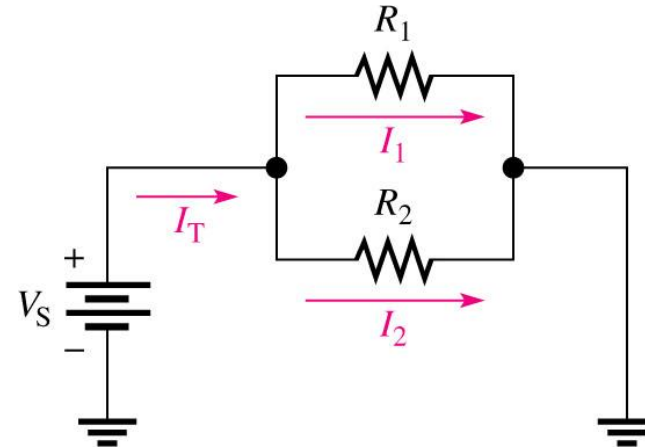
# Current Dividers

A parallel circuit acts as a current divider because the current entering the junction of parallel branches “divides” up into several individual branch currents.

The total current divides among parallel resistors into currents with values inversely proportional to the resistance values.



**Current Divider Rule:**

$$I_x = \frac{R_T}{R_x} I_T$$

# Current Divider Rule

- The current entering parallel resistive elements will **split as the inverse of their resistive values**
  - The voltage across parallel resistor is the same.
  - the current through equal parallel resistors will be the same.
- The **Current Divider Rule**:

$$I_x = \frac{R_T}{R_x} I_T$$

# Current Divider Rule

- For two parallel resistors, the current through one is equal to the *other* resistor times the total entering current divided by the *sum* of the two resistors



$$I_1 = \left( \frac{R_2}{R_1 + R_2} \right) I_T$$


$$I_2 = \left( \frac{R_1}{R_1 + R_2} \right) I_T$$



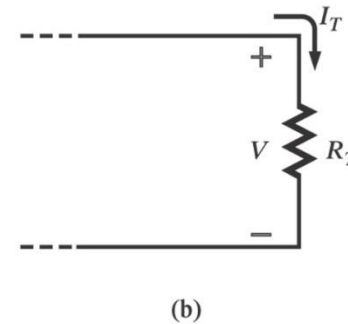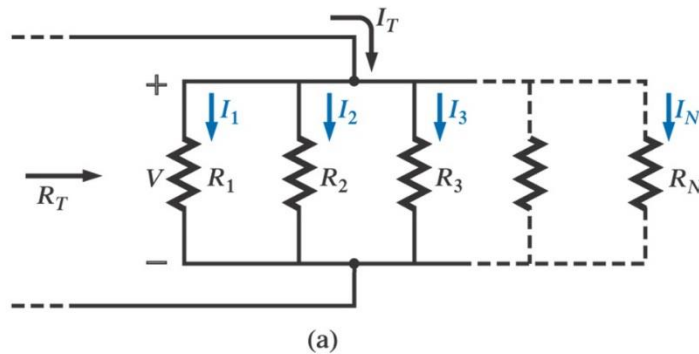
# Current Divider Rule


- In words:
  - The current through any branch of a parallel resistive network is equal to the total resistance of the parallel network divided by the resistor of interest and multiplied by the total current entering the parallel configuration




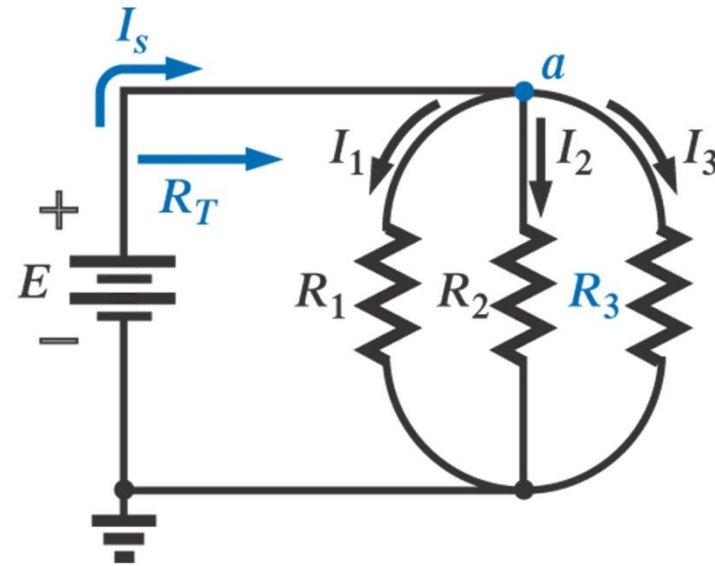



Redraw if required

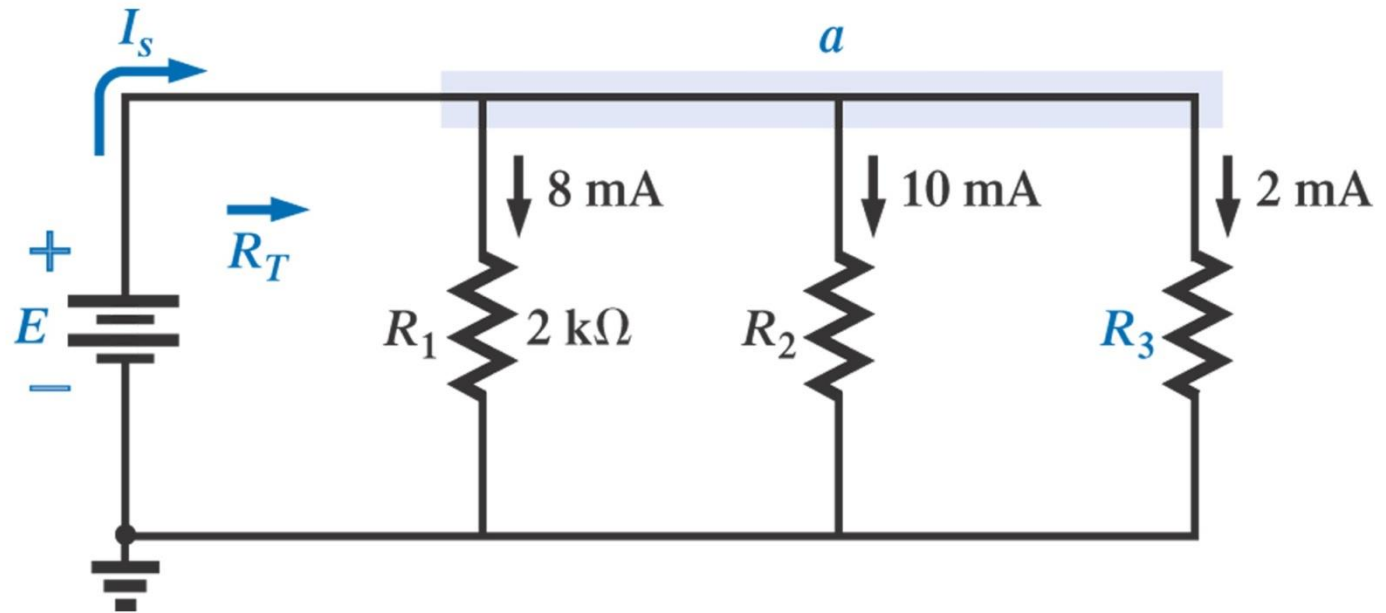

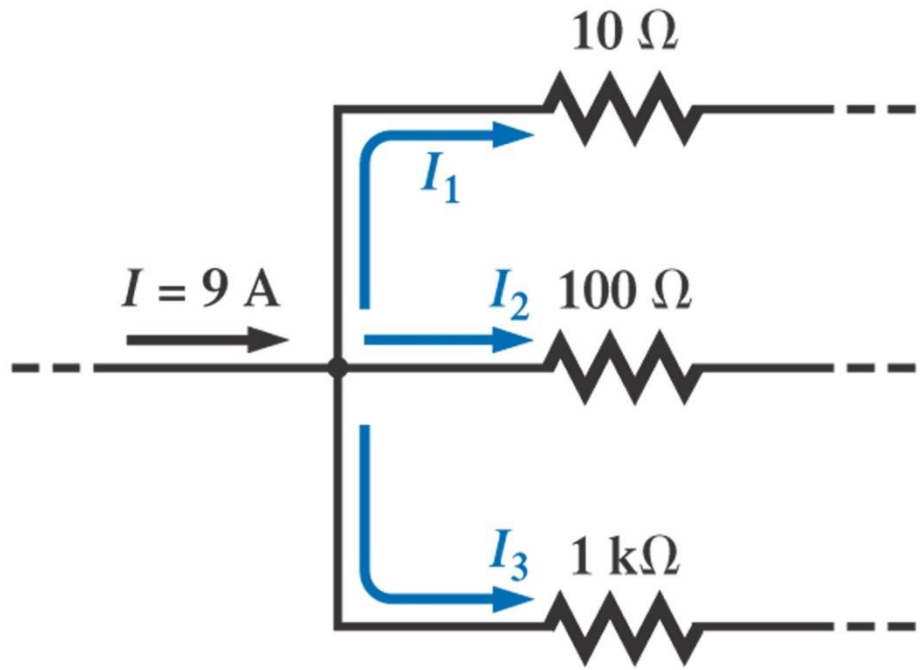


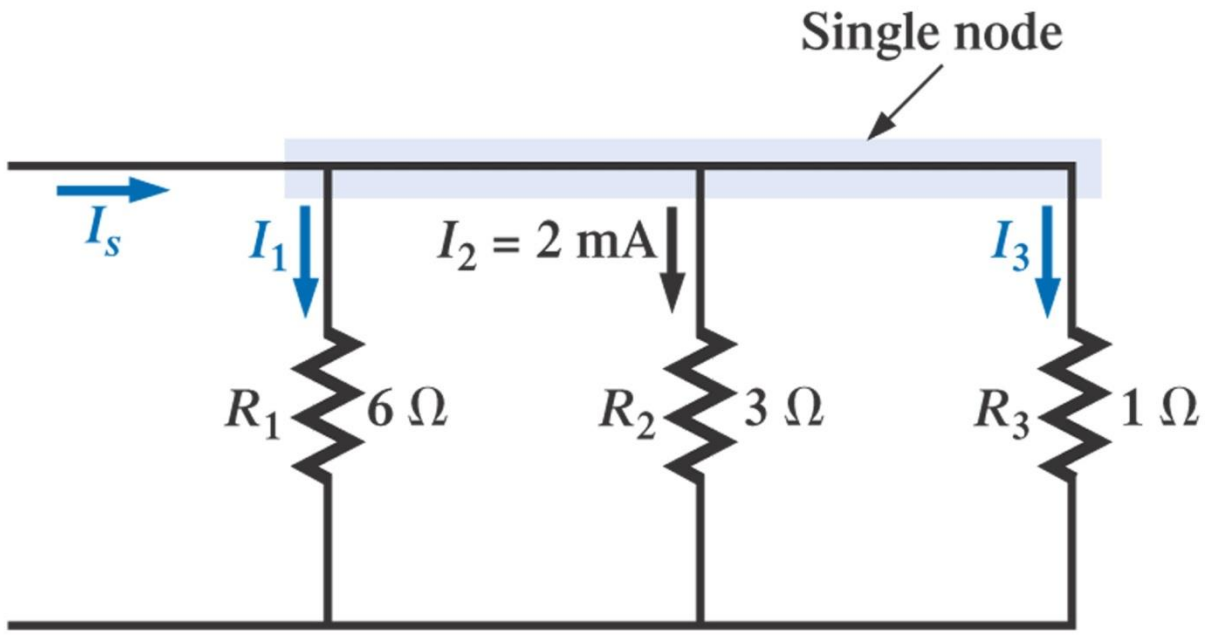

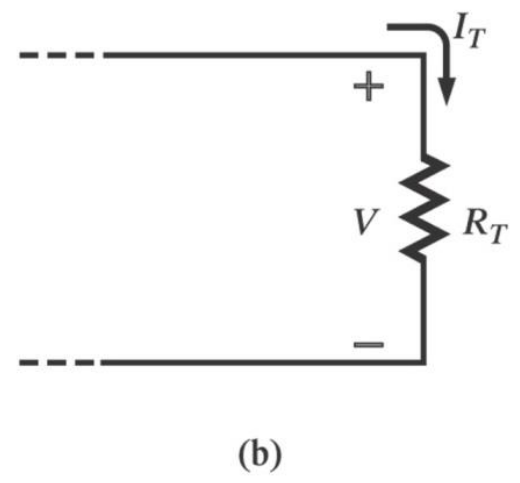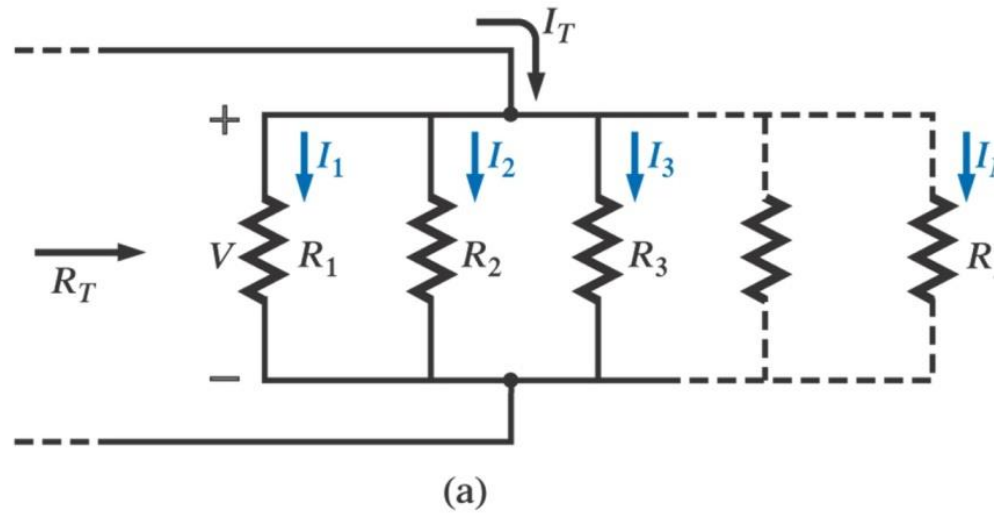
Deriving the current divider rule: (a) parallel network of  $N$  parallel resistors; (b) reduced equivalent of part (a).



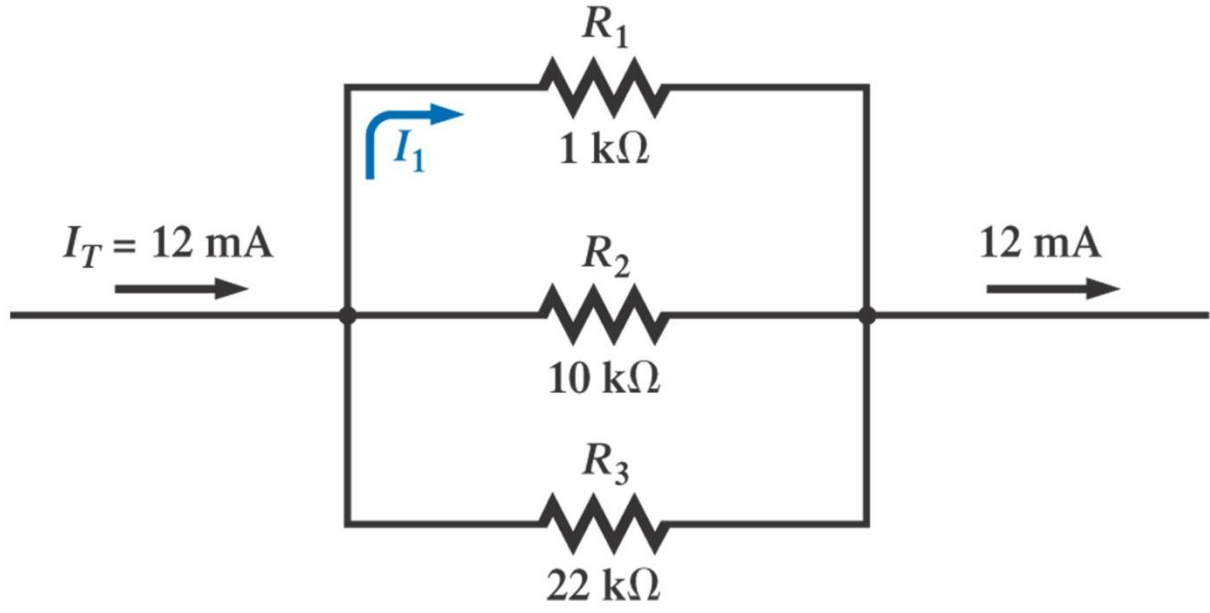
Using the current divider rule to calculate current  $I_1$



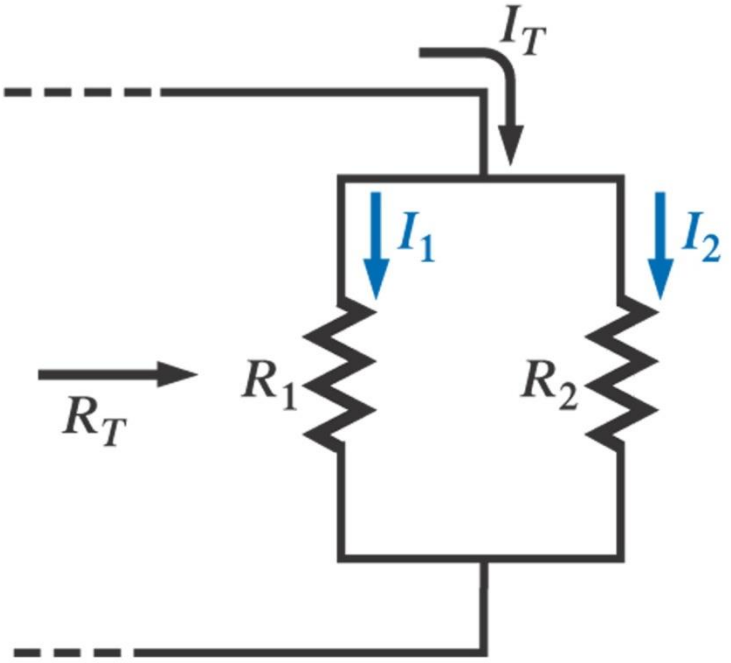
Deriving the current divider rule for the special case of only two parallel resistors.



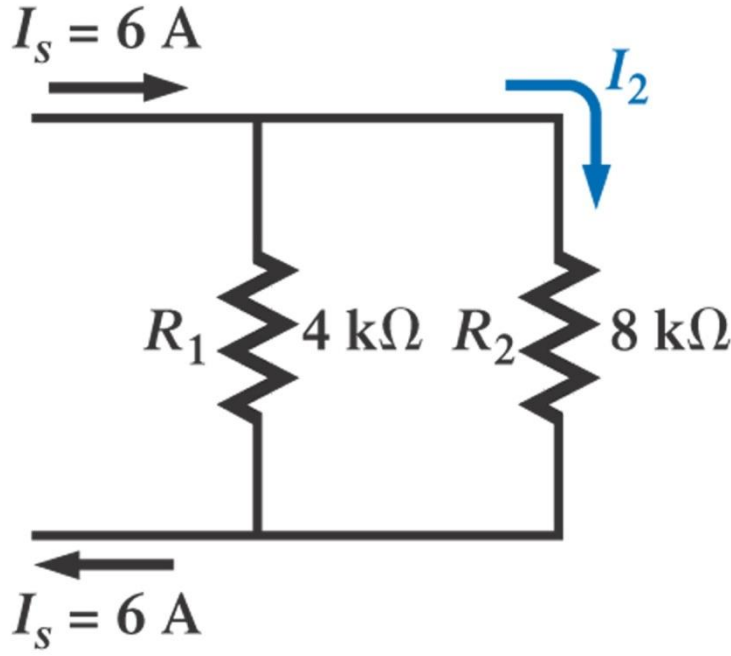
Using the current divider rule to determine current  $I_2$






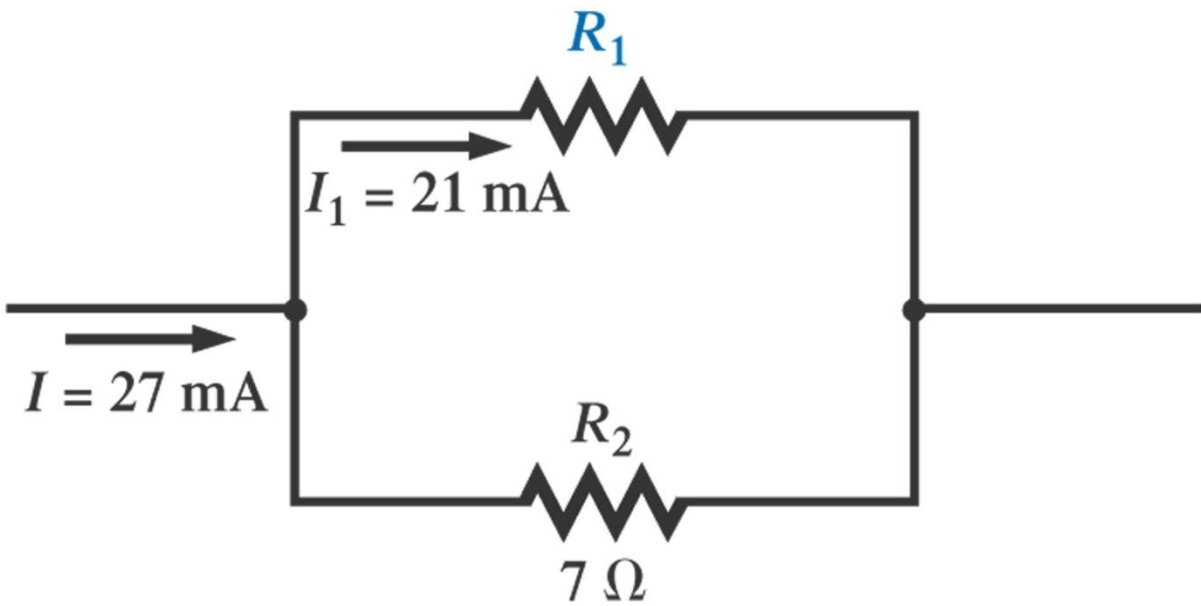

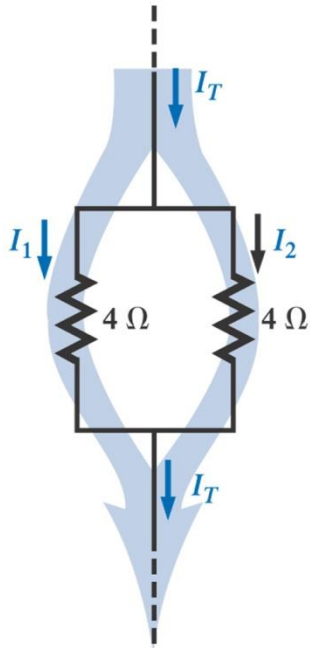
Demonstrating how current will divide through equal and unequal parallel resistors.




$$I_1 = I_2 = \frac{I_T}{2}$$

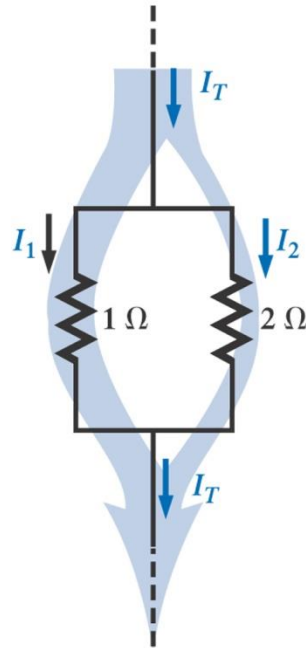

$$I_1 = 2I_2$$


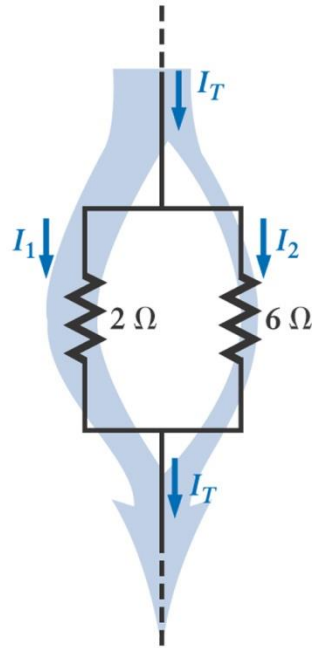

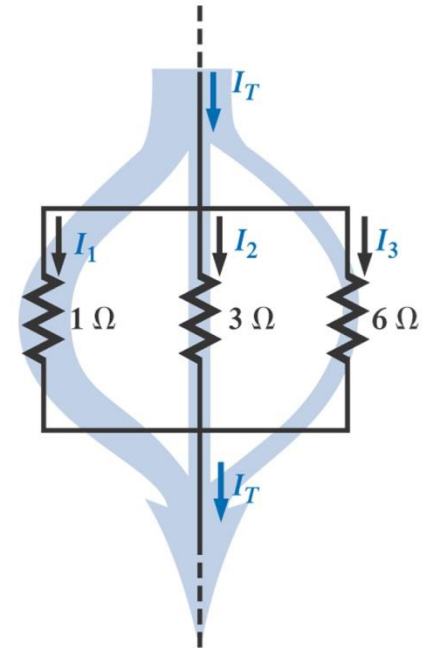
$$I_1 = \left(\frac{6}{2}\right) I_2 = 3I_2$$




$$\begin{aligned} I_1 &= 6I_3 \\ I_1 &= 3I_2 \\ I_2 &= \left(\frac{6}{3}\right) I_3 = 2I_3 \end{aligned}$$

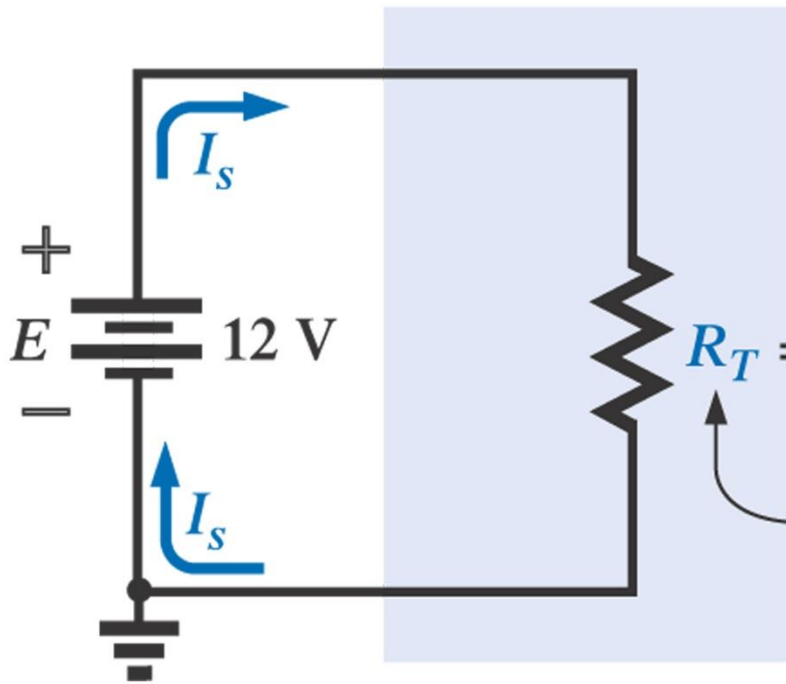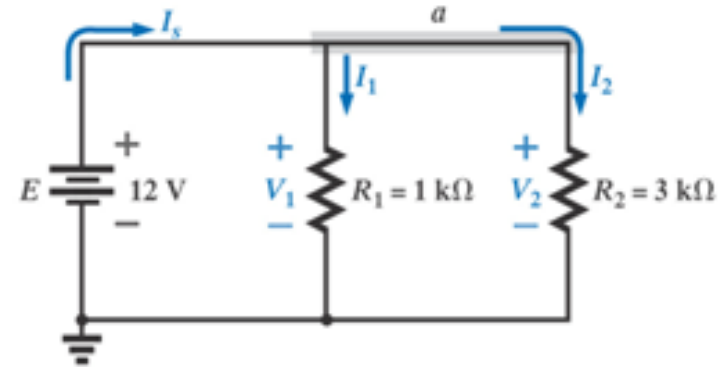
Replacing the parallel resistors of Fig. 6.20 with the equivalent total resistance.




$$R_T = \frac{(1 \text{ k}\Omega)(3 \text{ k}\Omega)}{1 \text{ k}\Omega + 3 \text{ k}\Omega} = 0.75 \text{ k}\Omega$$

Equivalent resistance

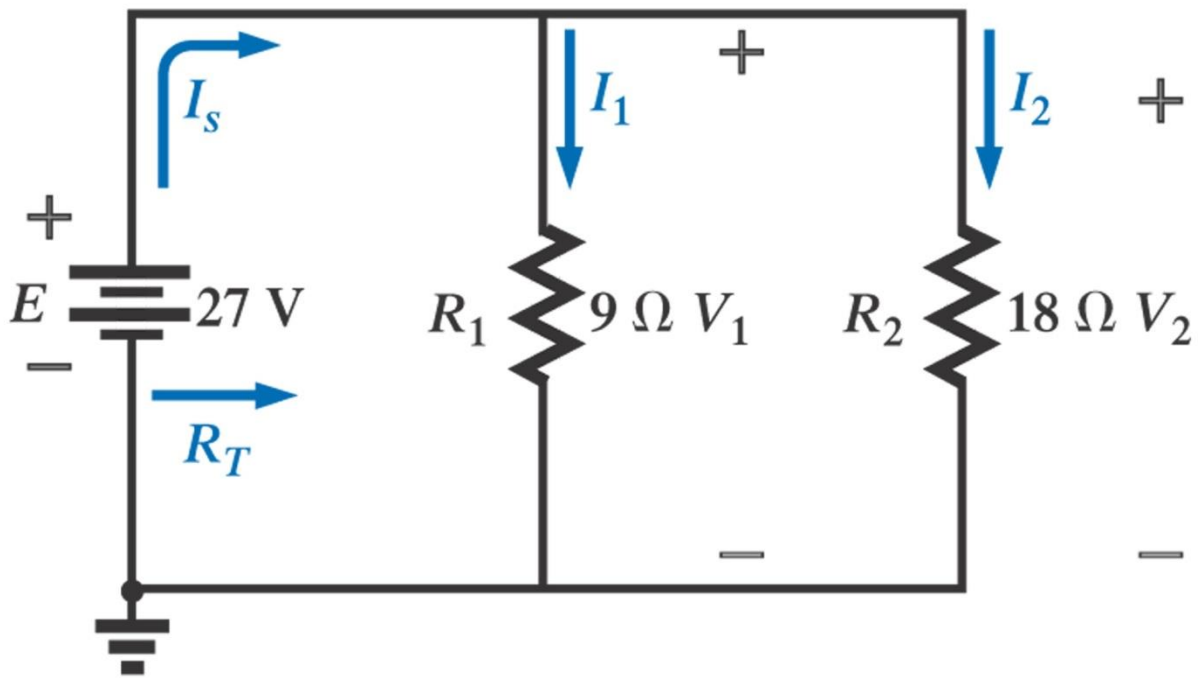

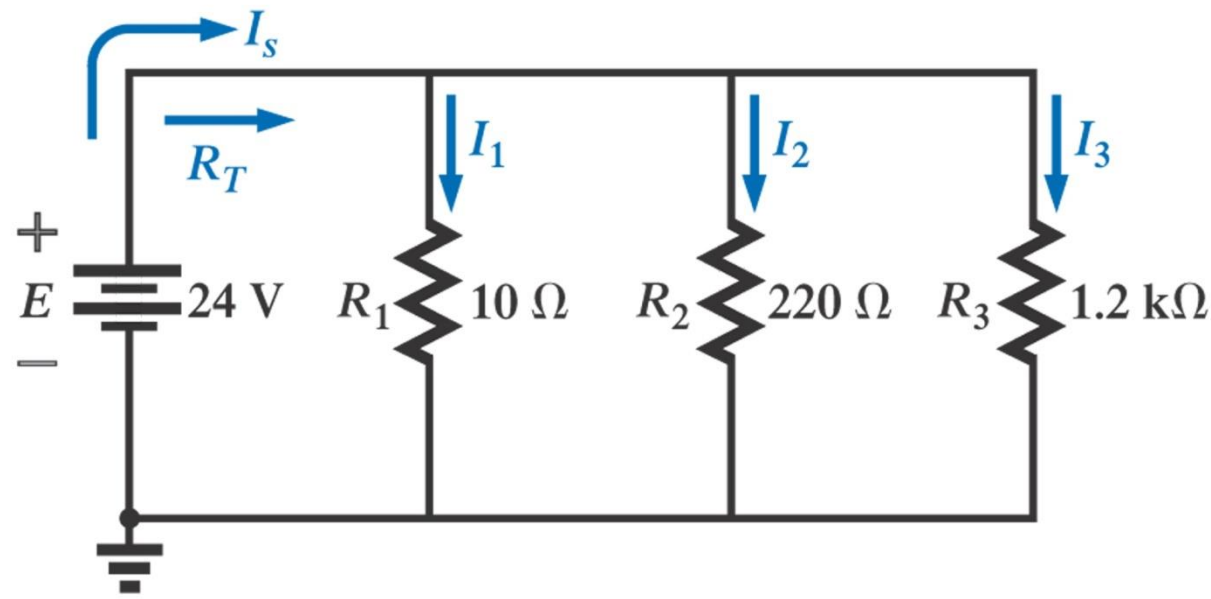


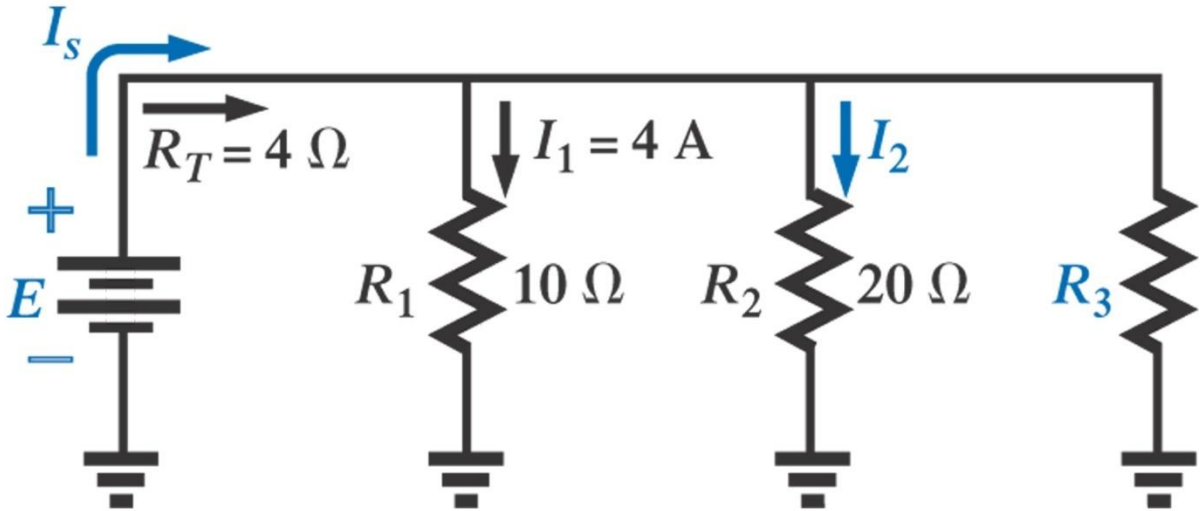

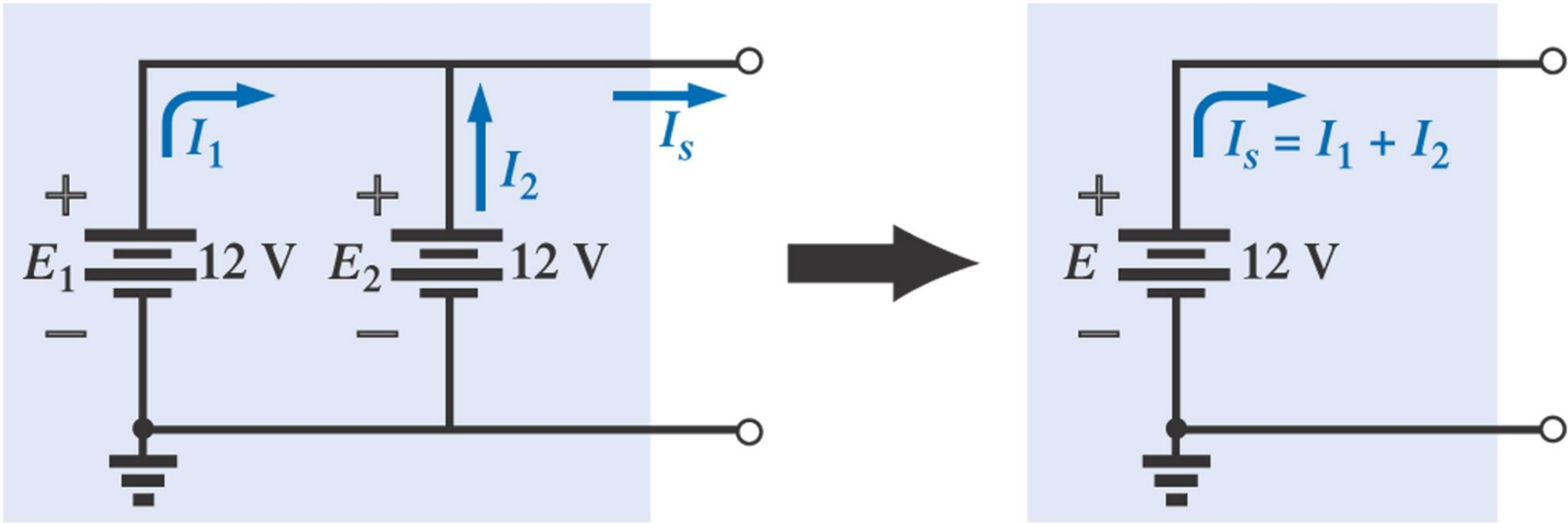
# Voltage Sources in Parallel

- Voltage sources can only be placed in parallel if they have the **same voltage**
  - the primary reason for placing two or more batteries or supplies in parallel would be to **increase the current rating** above that of a single supply
  - the total source current using Kirchhoff's current law is the sum of the rated currents of each supply

Demonstrating the effect of placing two ideal supplies of the same voltage in parallel.






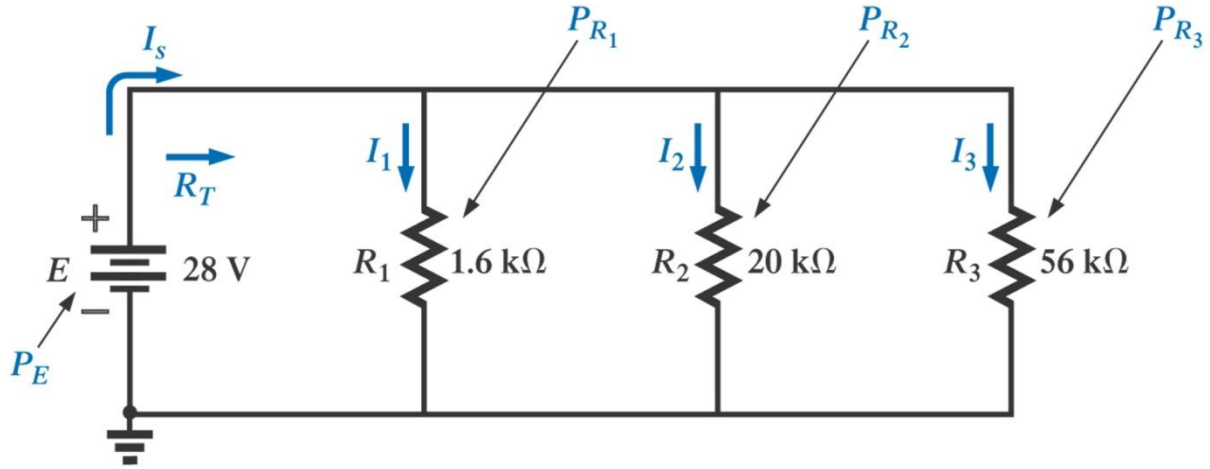

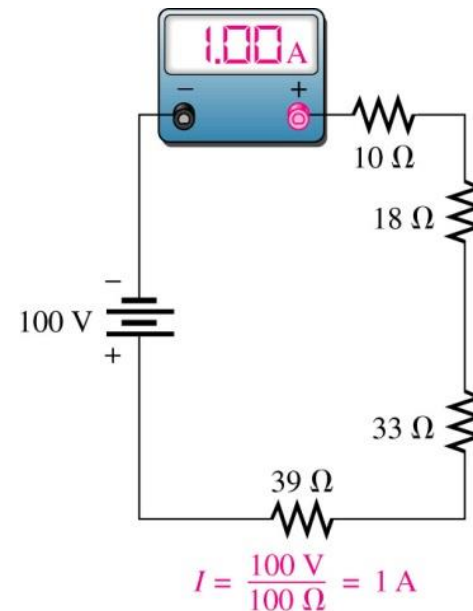
# Short Circuit

- When there is a short, a portion of the series resistance is bypassed, thus reducing the total resistance.
- A short in a series circuit results in more current than normal.
















(a) Before short

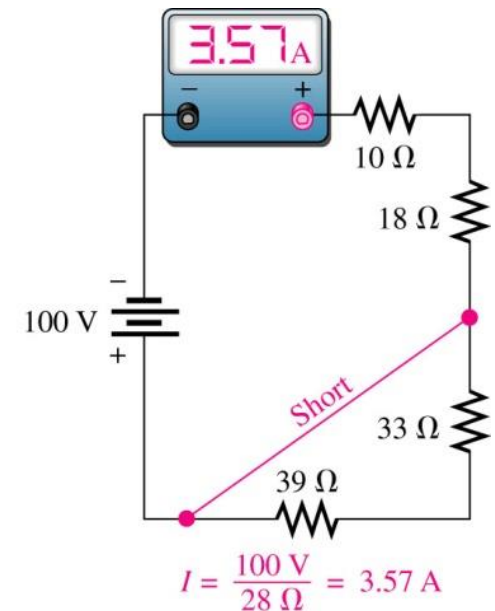


(b) After short


# Example:

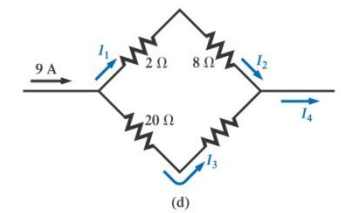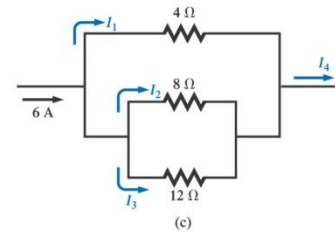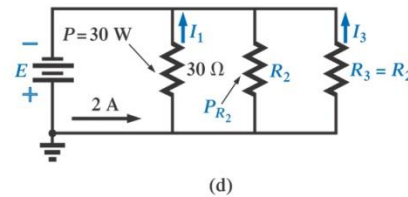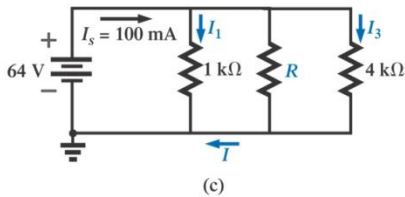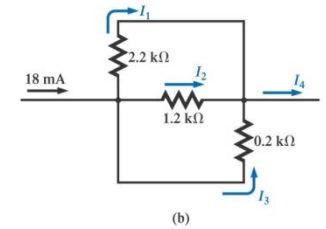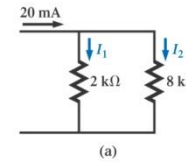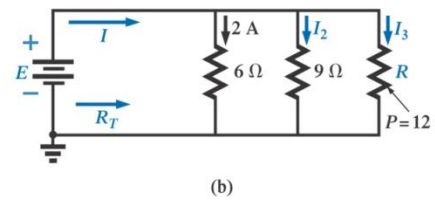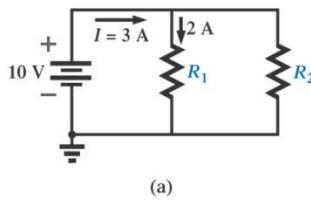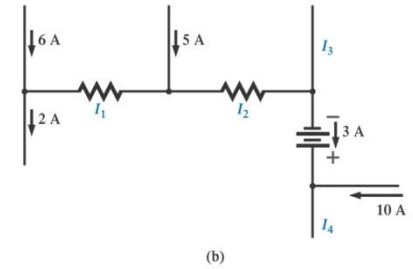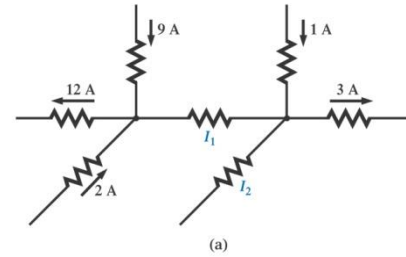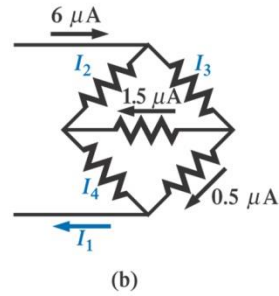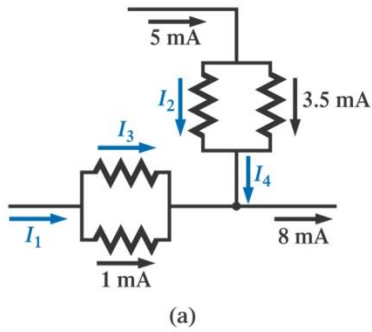

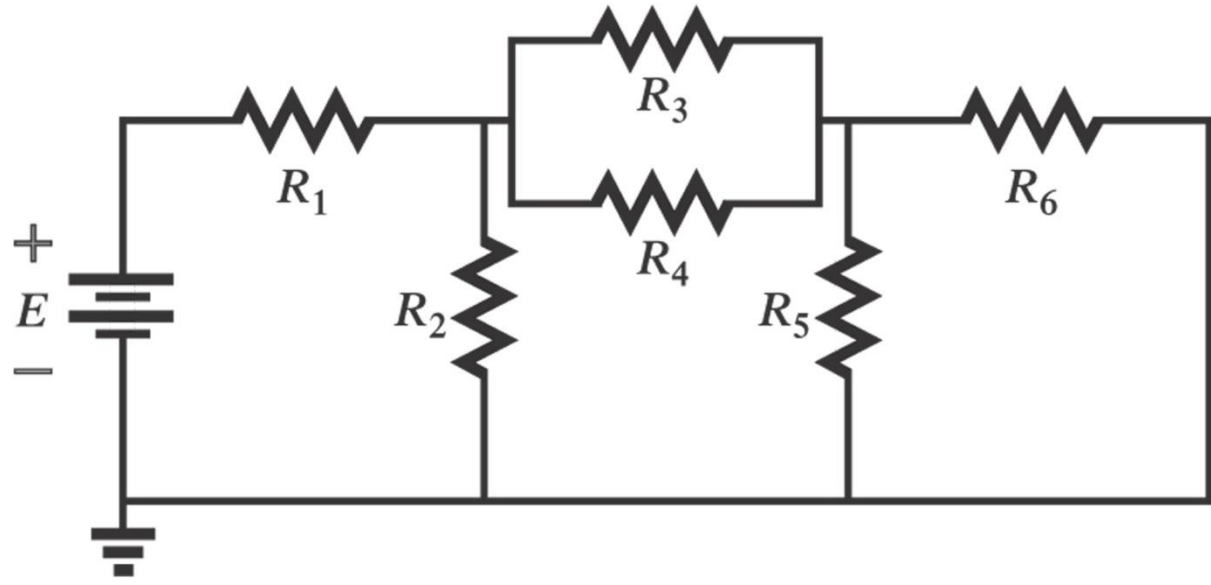


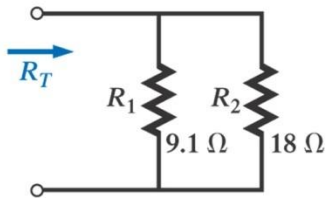


(a)

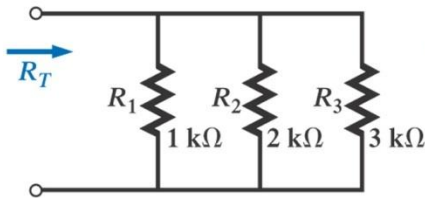


(b)

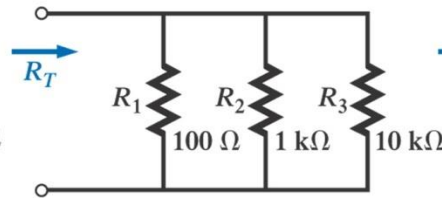


(c)

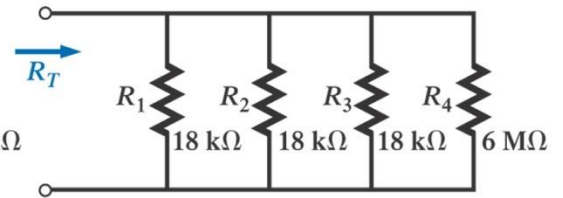






(d)

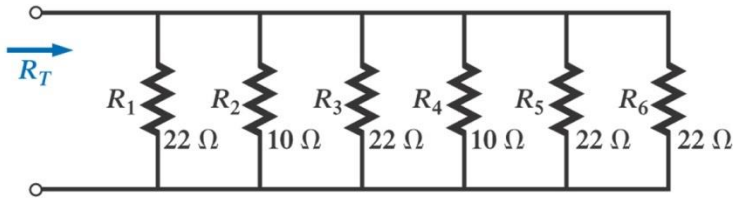


(e)

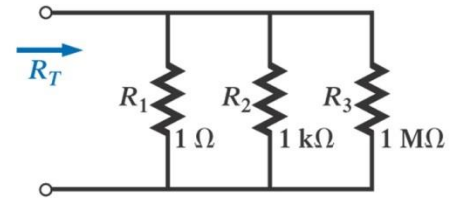

(f)

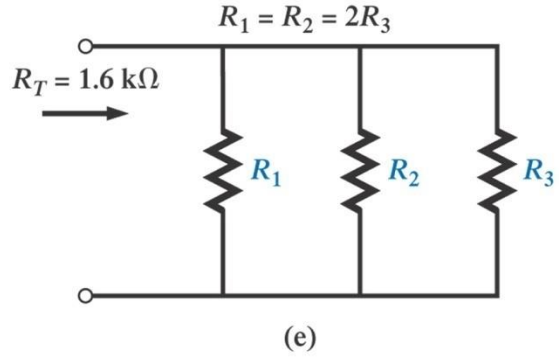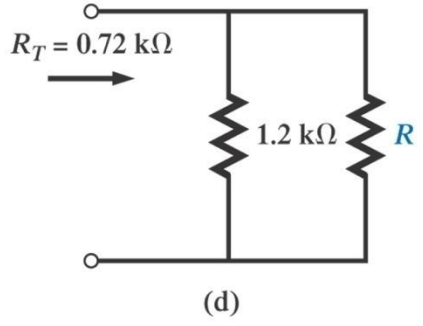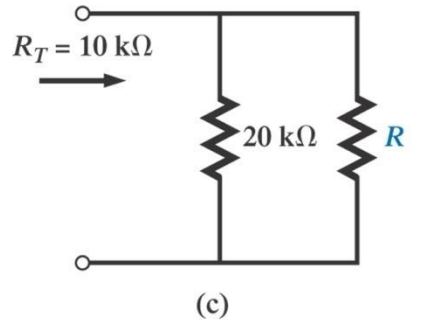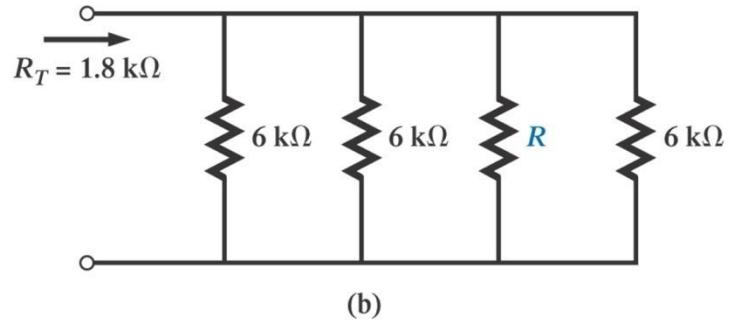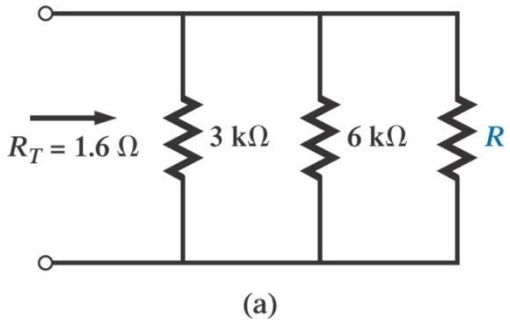

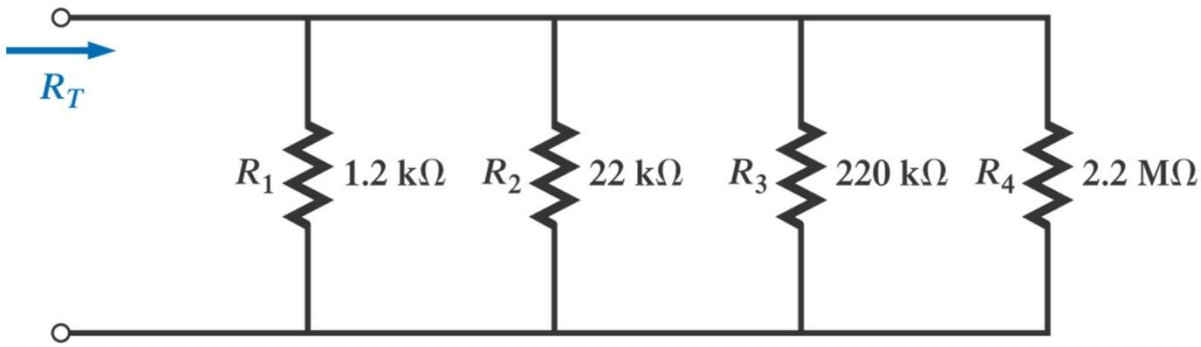

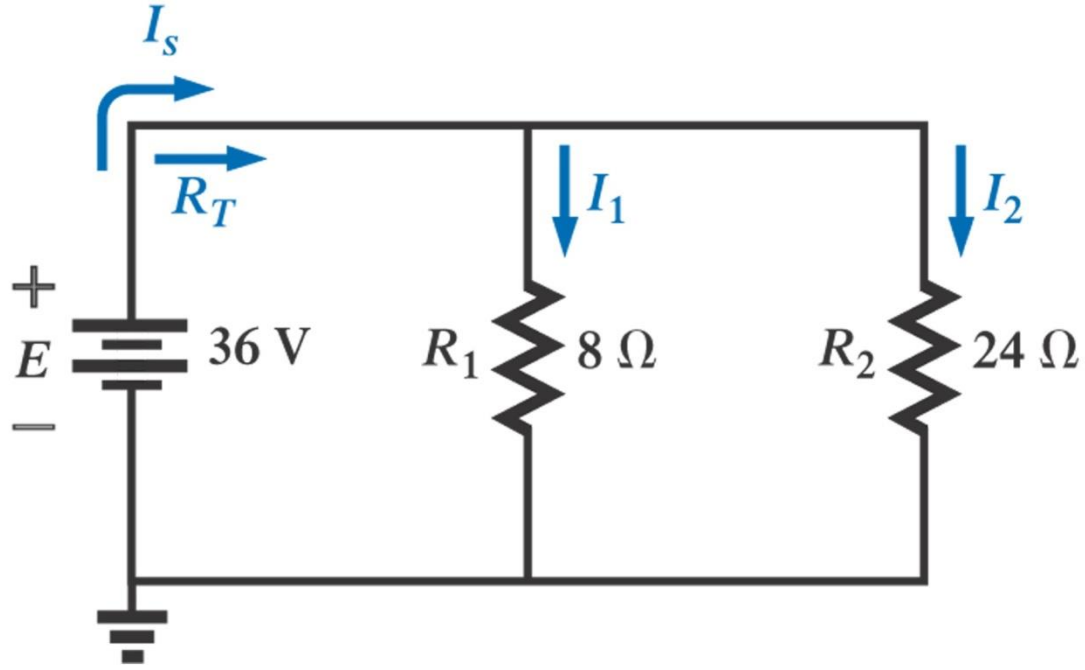
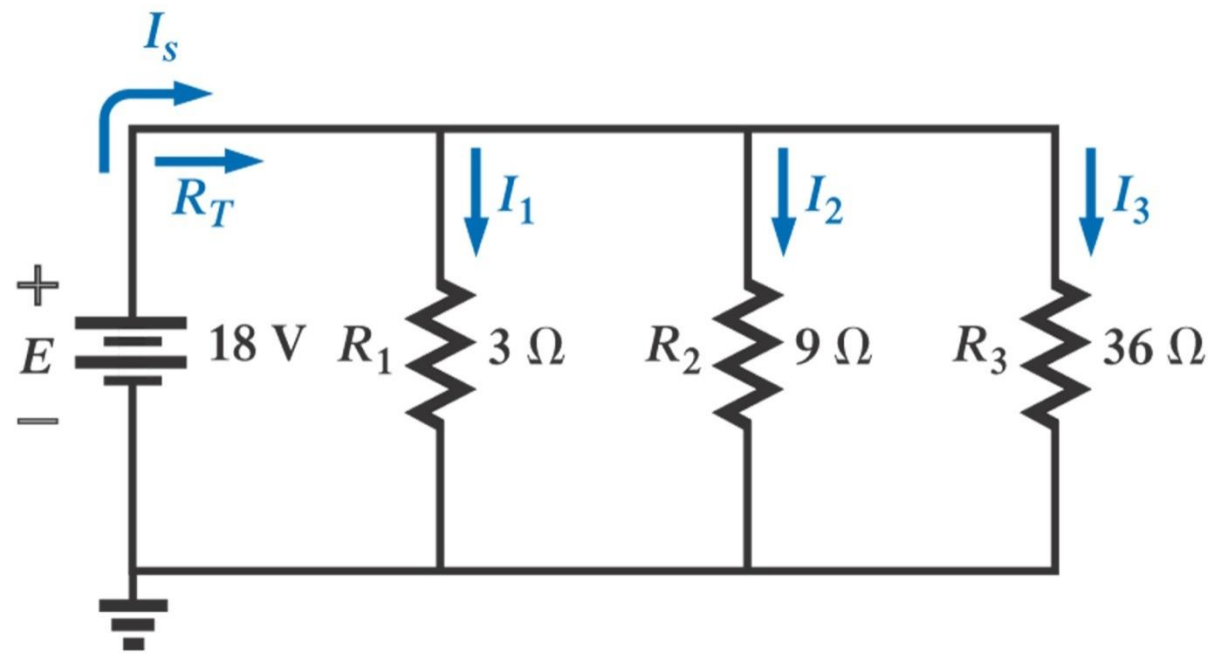
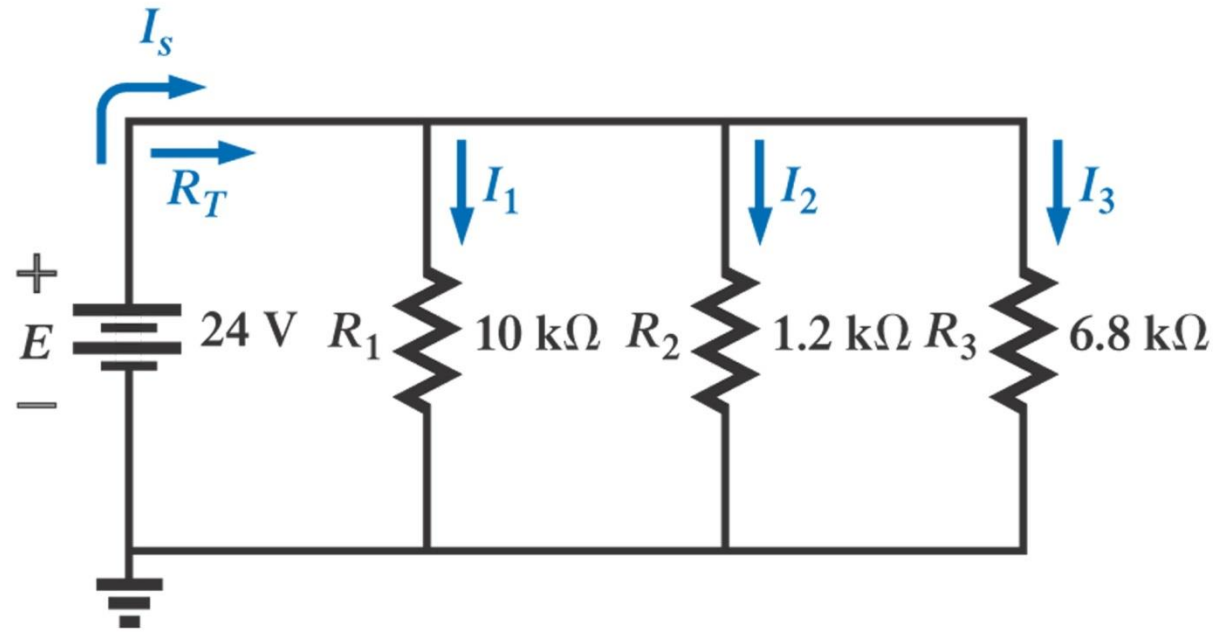
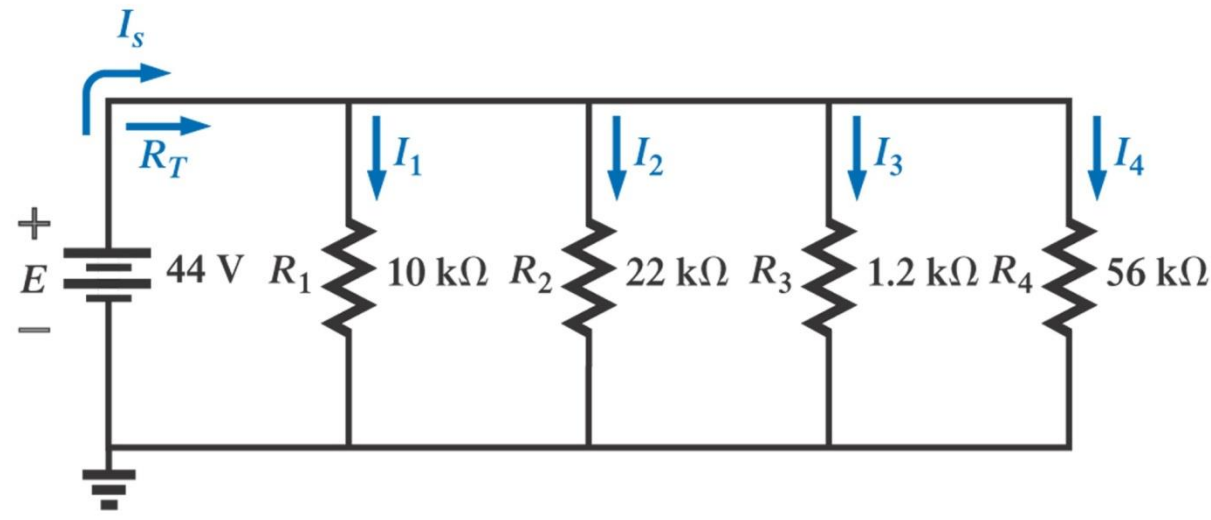


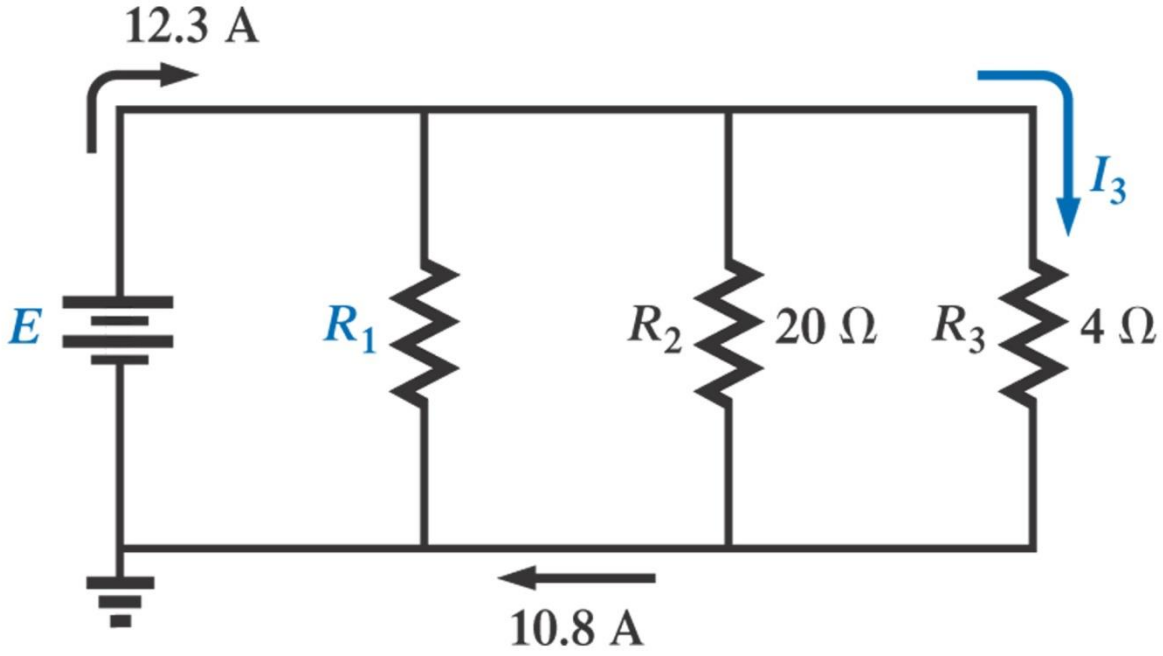



FIGURE 6-68 Problems 9 and 12.













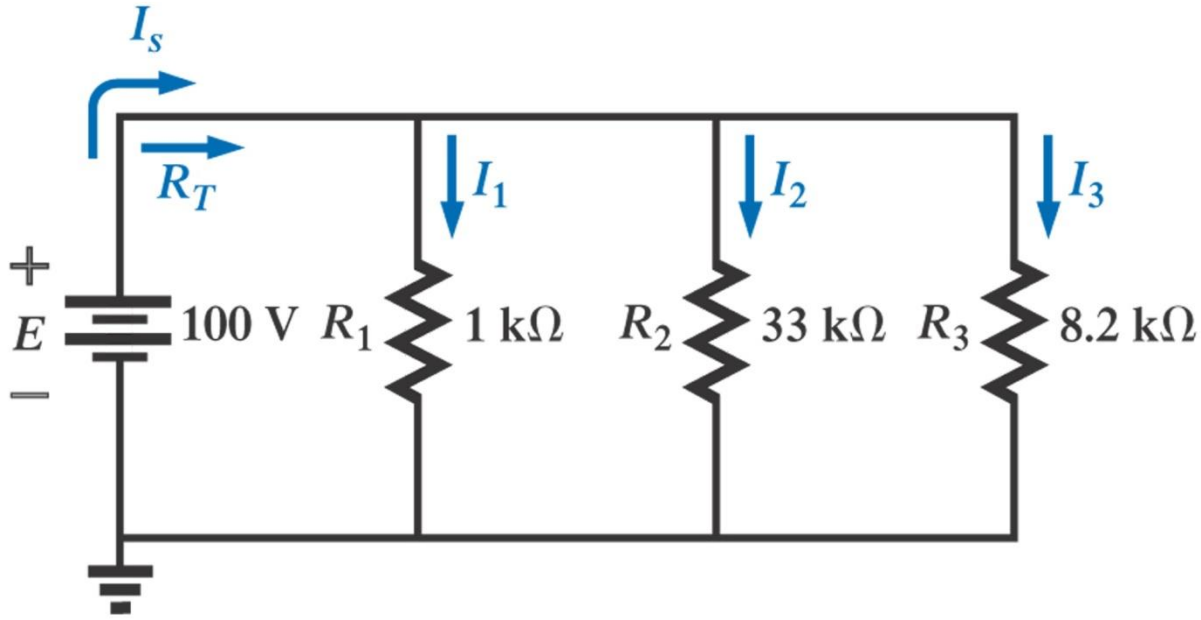


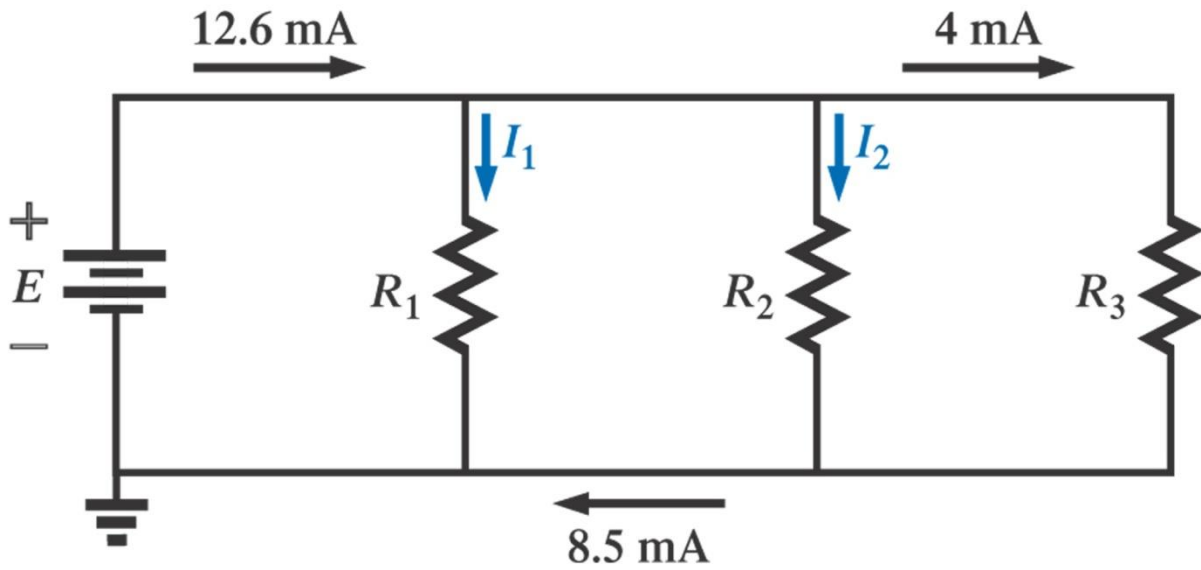

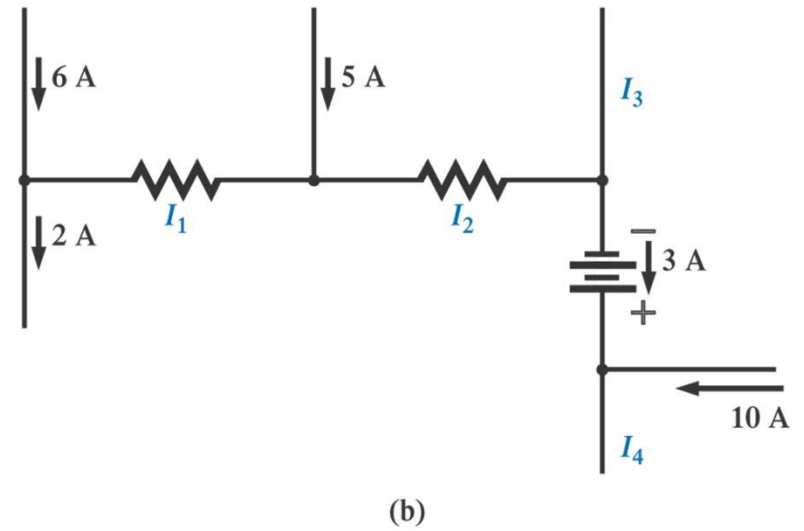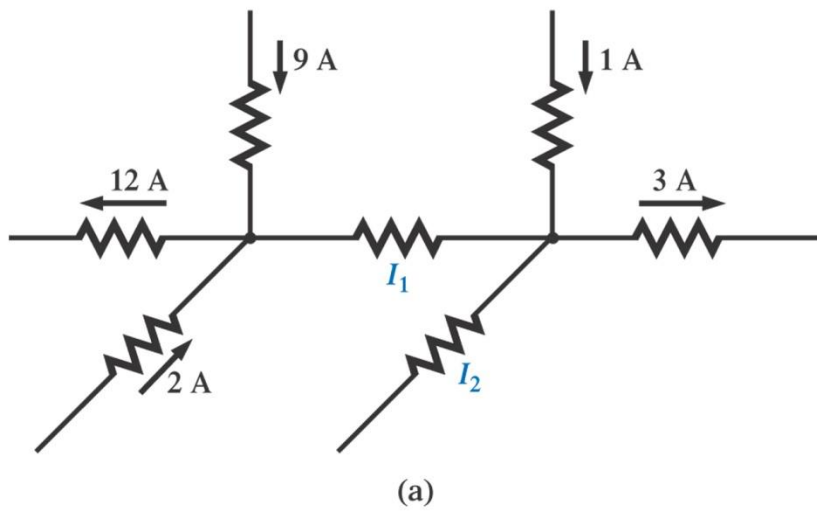

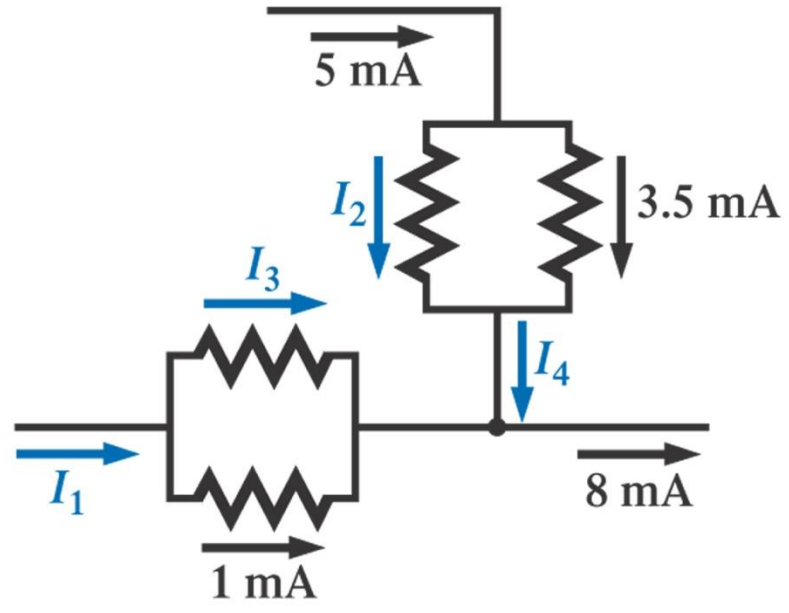



(a)

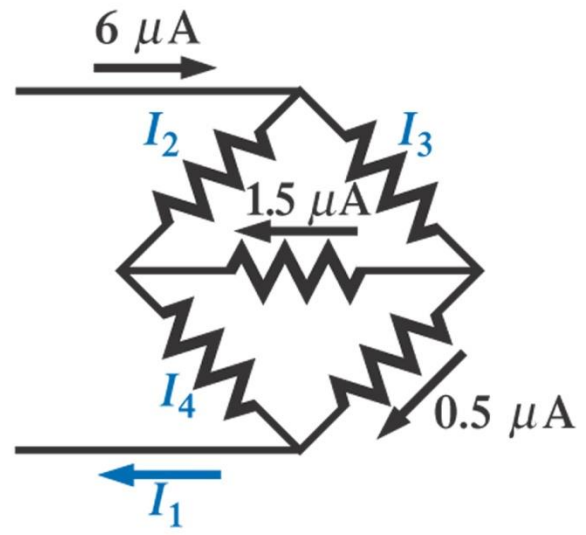


(b)



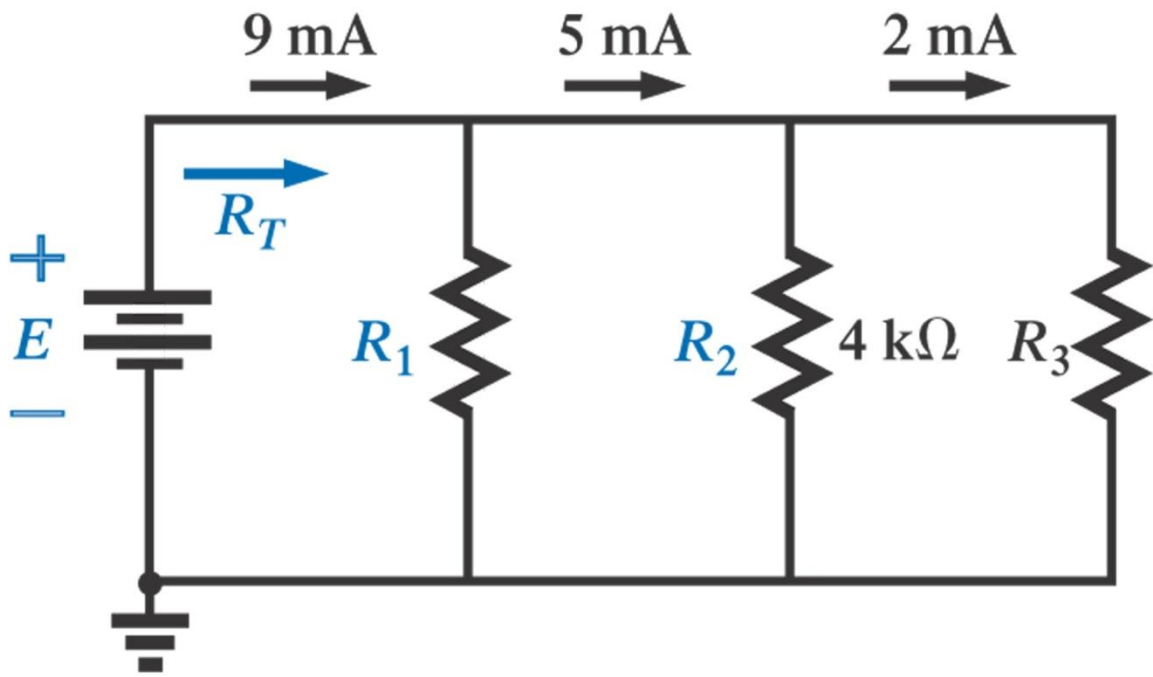


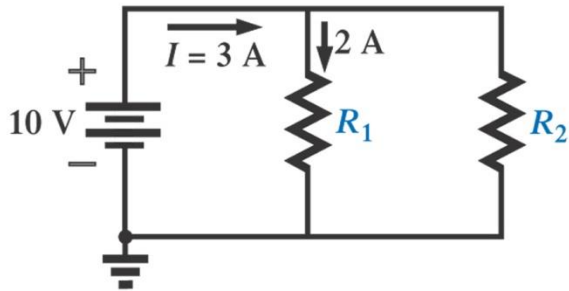


(a)

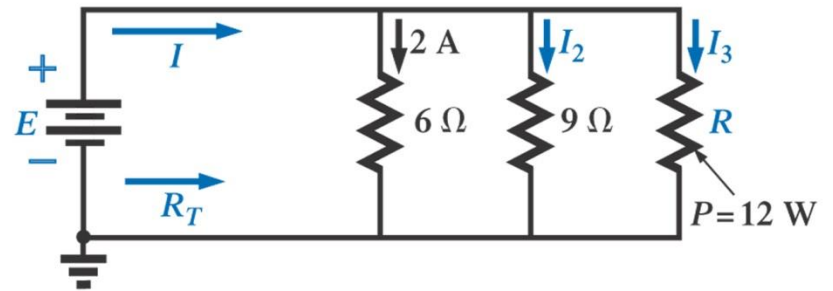


(b)




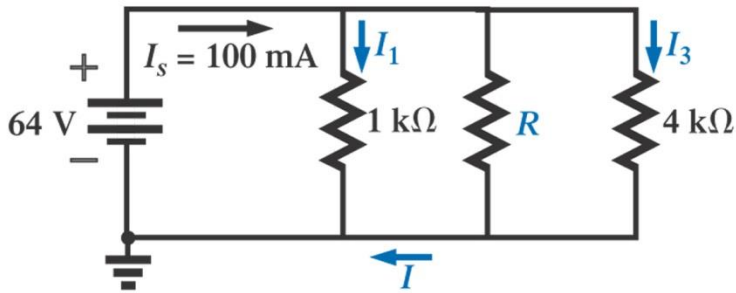



(c)

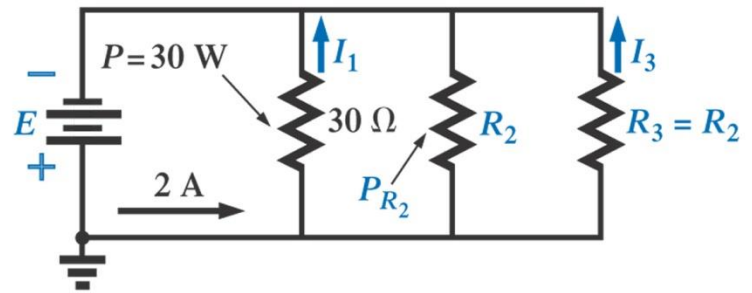


(d)

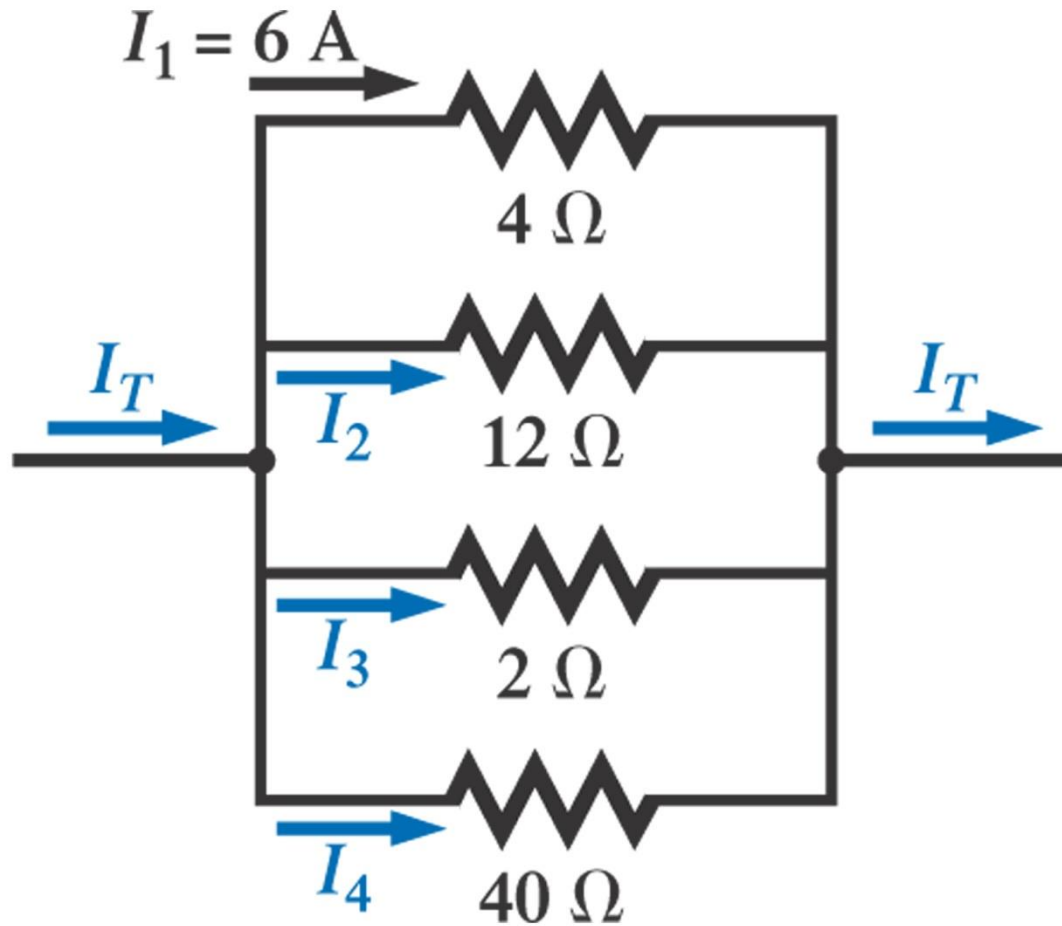


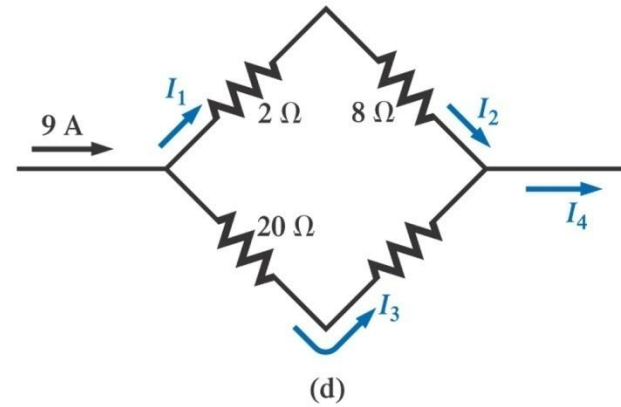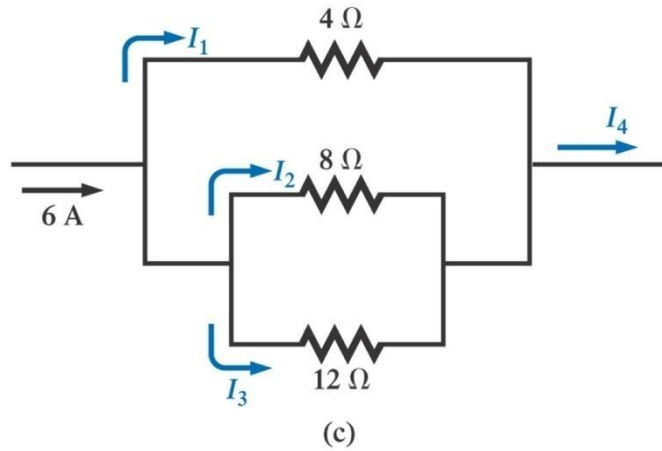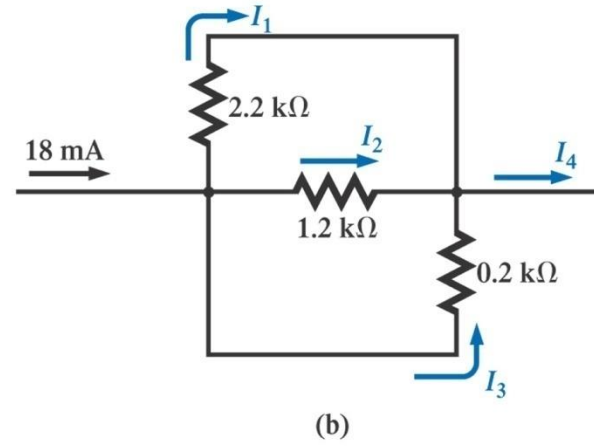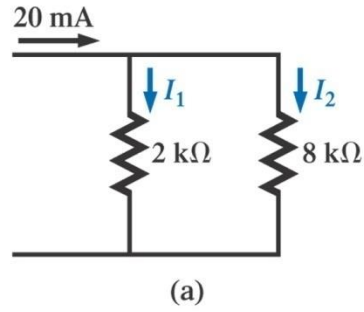

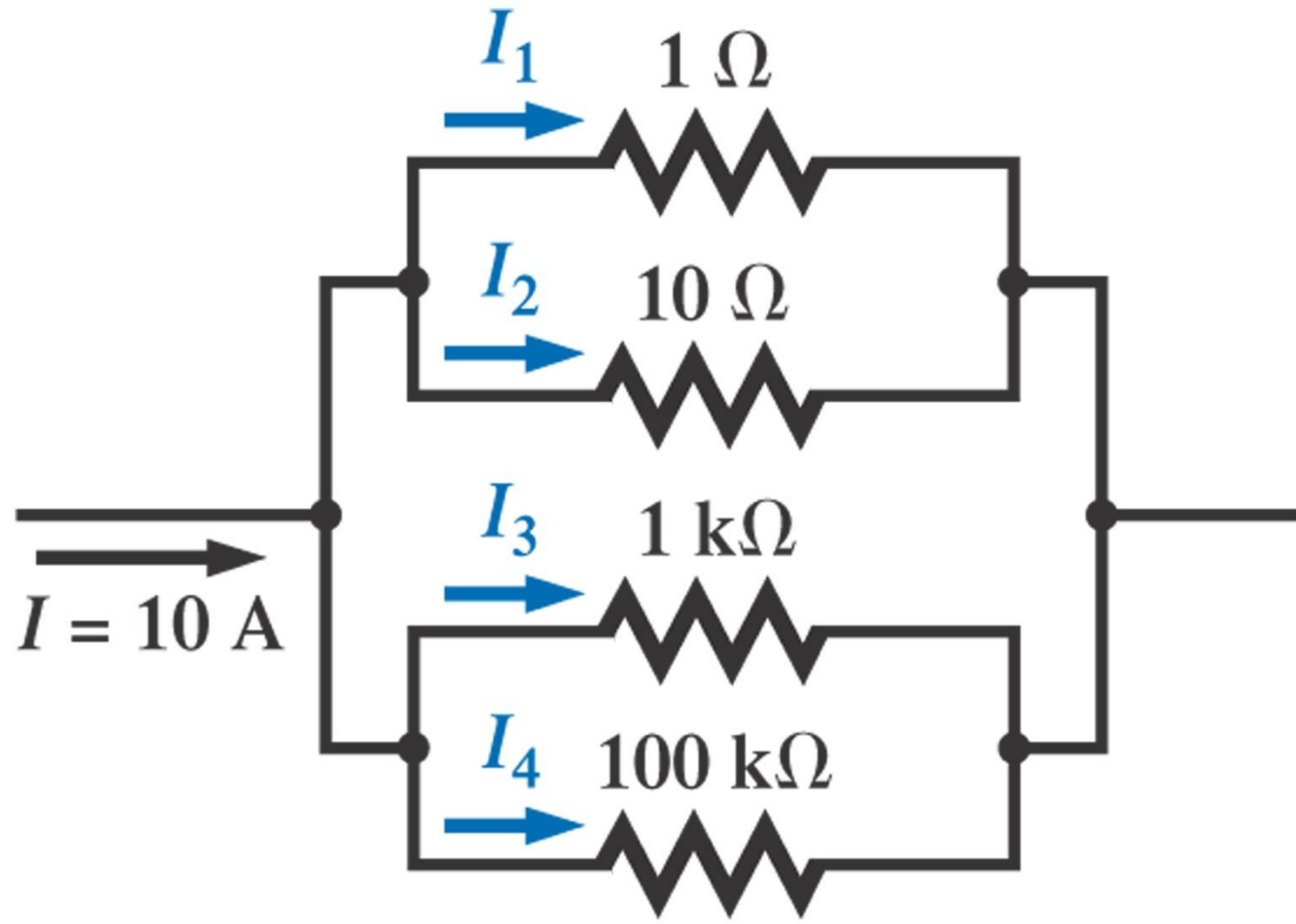

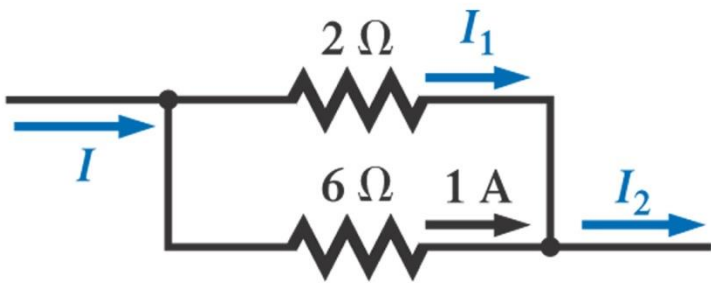

(a)

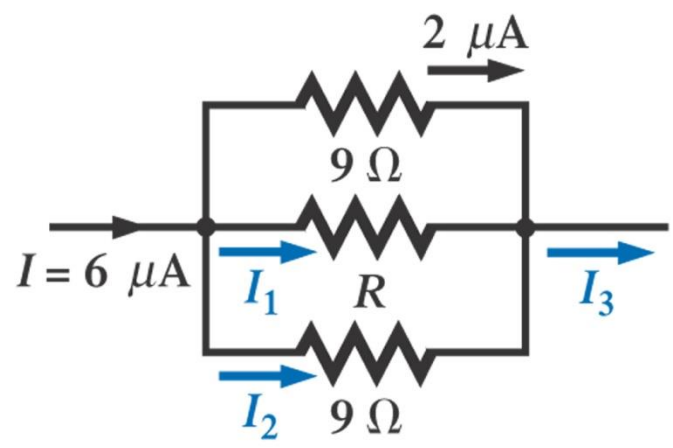

(b)

