

# **SKEE 1223**

# **DIGITAL ELECTRONICS**

## **CHAPTER 3: GATES AND BOOLEAN ALGEBRA**

**DR. MOHD SAIFUL AZIMI BIN MAHMUD**

**P19a-04-03-30**

**School of Electrical Engineering**

**Faculty of Engineering**

**Universiti Teknologi Malaysia**

**019-7112948**

**azimi@utm.my**




# LOGIC GATES

# LOGIC GATES
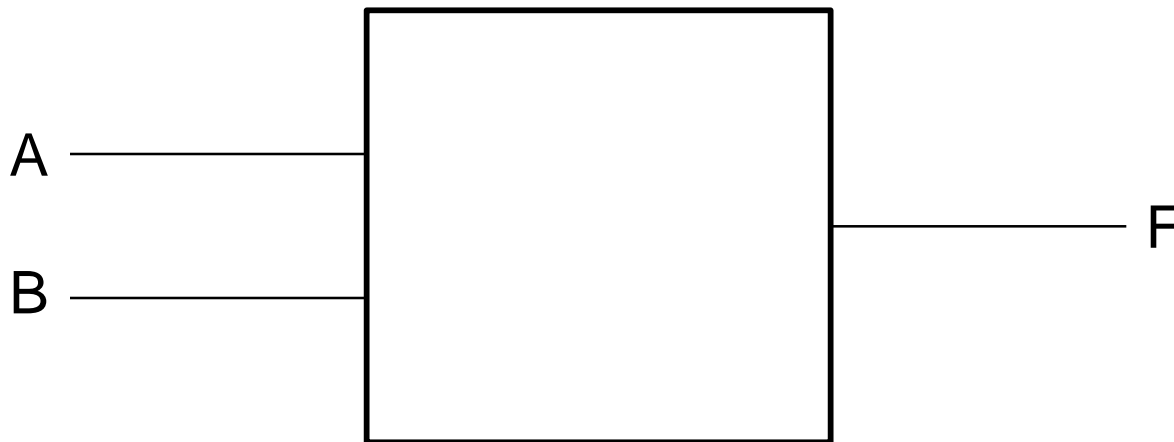
## INTRODUCTION

- **Logic gate** is fundamental building blocks for all digital circuits.
- Each gate **at least have one input** and **only one output**.
- The output depends on the function of the gate and combination of all its inputs.



A generic two-input logic gate

# LOGIC GATES

## AND GATE: INTRODUCTION

- It has two or more inputs and one output.
- Performs as **logic multiplication**.

### Logic expression

$$Z = XY \text{ or } Z = X \cdot Y$$

### Logic operation

- Output  $Z$  is **1** when **all input  $X$  and  $Y$**  are **1**.
- Output  $Z$  is **0** when **at least one of  $X$  and  $Y$**  is **0**.






AND symbol

AND Truth Table

Input		Output
X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

# LOGIC GATES

## AND GATE: TIMING DIAGRAM

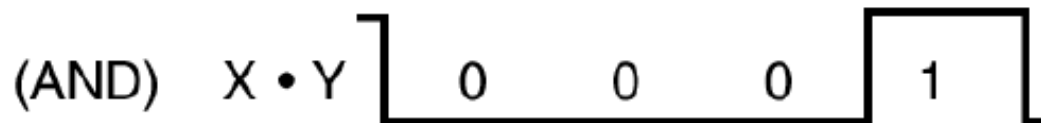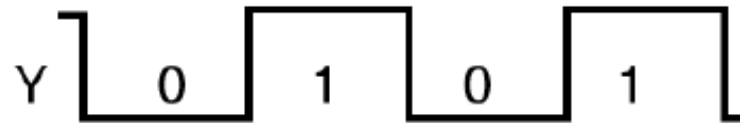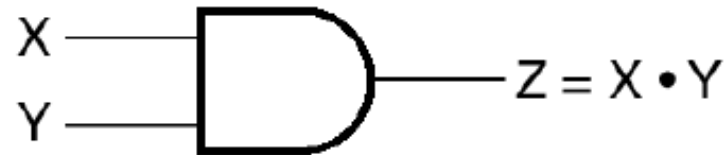

# LOGIC GATES

## OR GATE: INTRODUCTION

- It has two or more inputs and one output.
- Performs as **logic addition**.



OR symbol

### Logic expression

$$Z = X + Y$$

OR Truth Table





Input		Output
X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

### Logic operation

- Output  $Z$  is **1** when **at least one of  $X$  and  $Y$**  is **1**.
- Output  $Z$  is **0** when **all input  $X$  and  $Y$**  are **0**.

# LOGIC GATES

## OR GATE: TIMING DIAGRAM

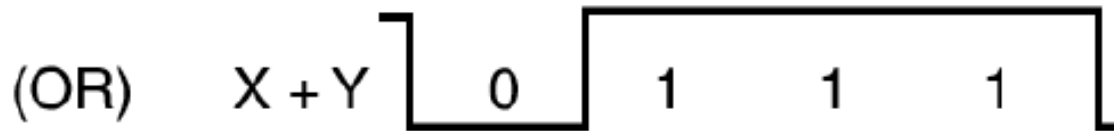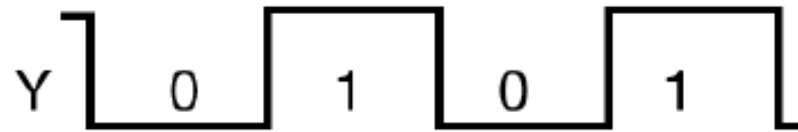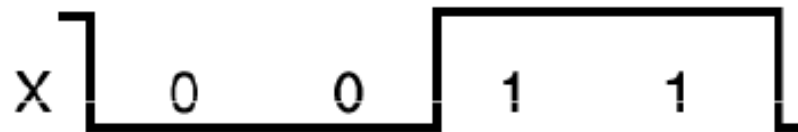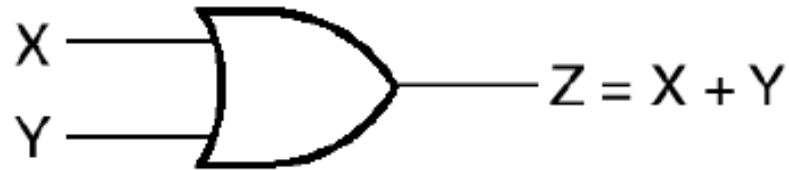

# LOGIC GATES

## NOT GATE: INTRODUCTION

- Also known as **inverter gate**.
- It only has one input and one output.
- Performs as **logic inversion**.


### Logic expression

$$Z = \bar{X} \text{ or } Z = X'$$

### Logic operation

- Output  $Z$  is opposite of input  $X$ .

This bubble indicates inversion

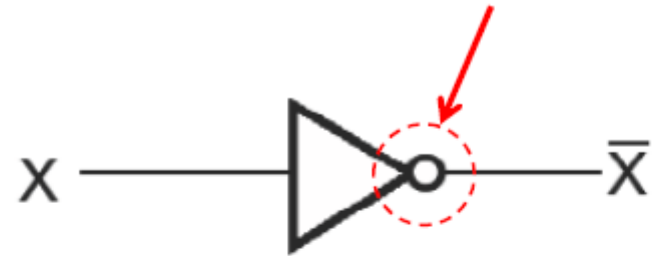

NOT symbol


NOT Truth Table

Input	Output
$X$	$Z$
0	1
1	0





# LOGIC GATES

## NOT GATE: TIMING DIAGRAM

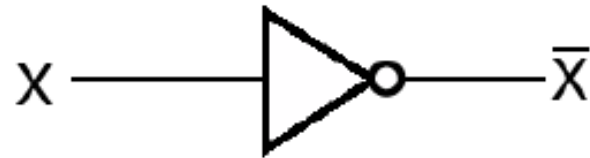

NOT gate or  
inverter

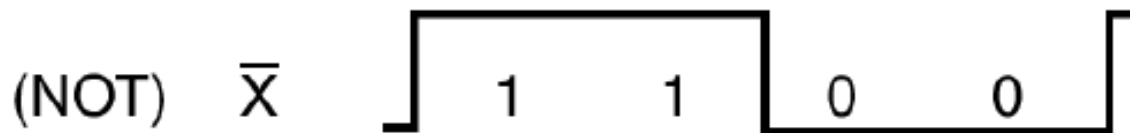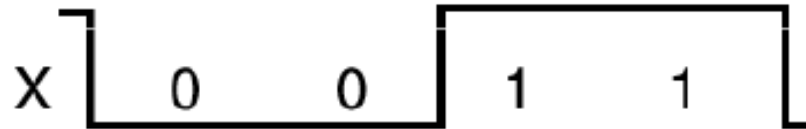


# LOGIC GATES

## MORE INPUTS GATE?

- Works the same way.


### Example

#### Three inputs AND gate

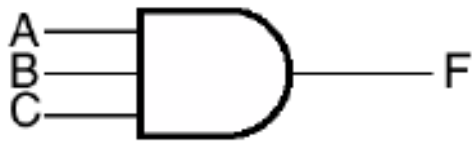

- Logic expression:  $F = ABC$
- Output:  $F$  is 1 when all inputs are 1.

#### Six inputs OR gate

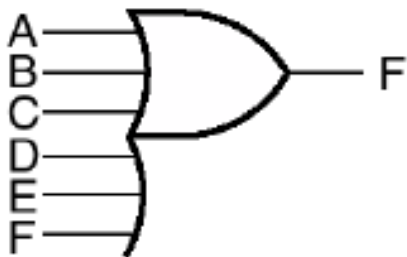


- Logic expression:  $F = A + B + C + D + E + F$
- Output:  $F$  is 1 when at least one input is 1.

# LOGIC GATES
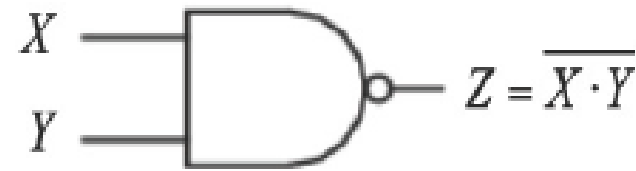
## NAND GATE: INTRODUCTION

- A **Universal gate**: used in combinations to perform AND, OR and NOT operations.
- NAND is a contraction of NOT-AND (implies AND function with an inverted output).



NAND symbol

### Logic expression

$$Z = \overline{XY}$$

### Logic operation






- Output Z is **1** when **at least one of X or Y** is **0**.
- Output Z is **0** when **all input X and Y** are **1**.

NAND Truth Table

Input		Output
X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

# LOGIC GATES


## NAND GATE IS UNIVERSAL GATE

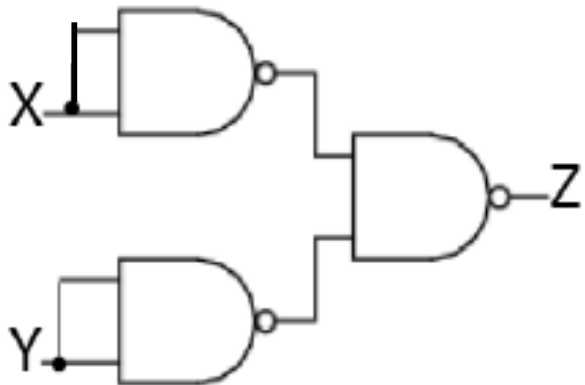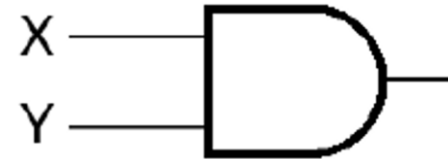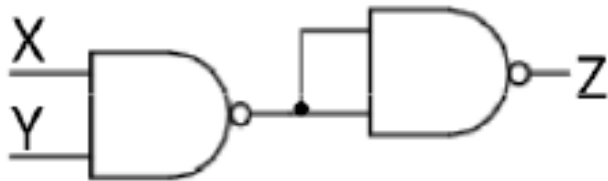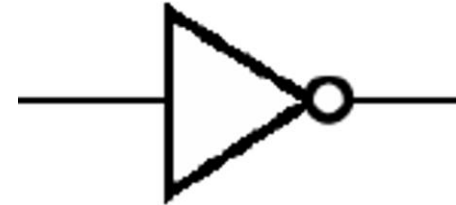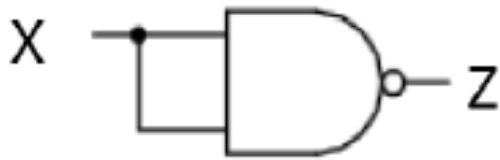

# LOGIC GATES
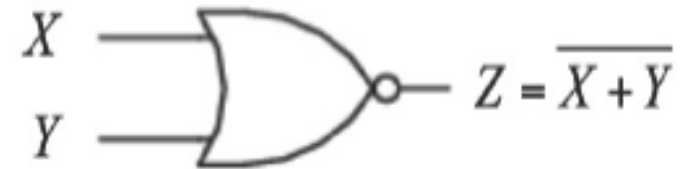
## NOR GATE: INTRODUCTION

- A **Universal gate**: used in combinations to perform AND, OR and NOT operations.
- NOR is a contraction of NOT-OR (implies OR function with an inverted output).



NOR symbol

### Logic expression

$$Z = \overline{X + Y}$$

### Logic operation





- Output Z is **1** when **all input X and Y** are **0**.
- Output Z is **0** when **at least one of X or Y** is **1**.

NOR Truth Table

Input		Output
X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

# LOGIC GATES

## NOR GATE IS UNIVERSAL GATE

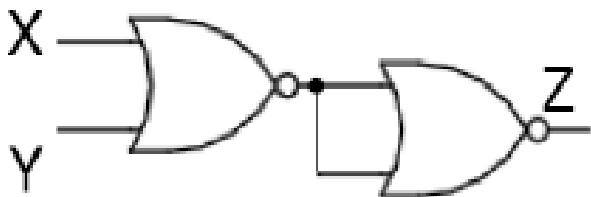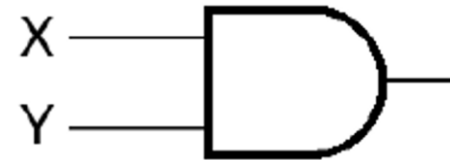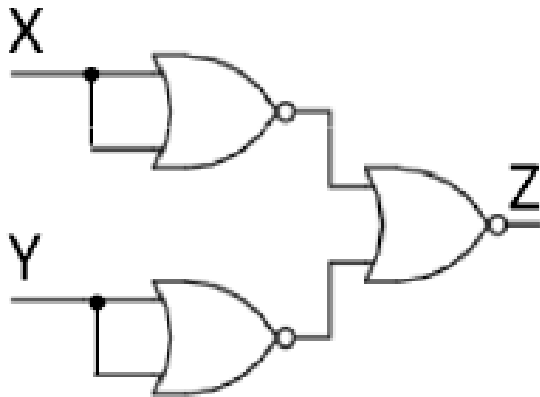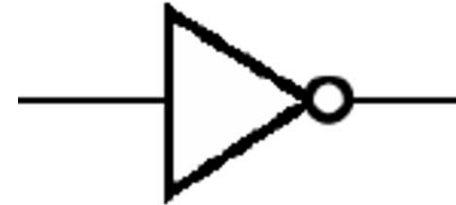

# LOGIC GATES

## EXCLUSIVE-OR GATE (XOR GATE): INTRODUCTION

- XOR gate only has two inputs.



XOR symbol

### Logic expression

$$Z = \bar{X}Y + X\bar{Y} \text{ or } Z = X \oplus Y$$

### Logic operation

- Output  $Z$  is **1** when **input  $X$  and  $Y$**  are **different**.
- Output  $Z$  is **0** when **input  $X$  and  $Y$**  are **same**.

XOR Truth Table


Input		Output
X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

# LOGIC GATES
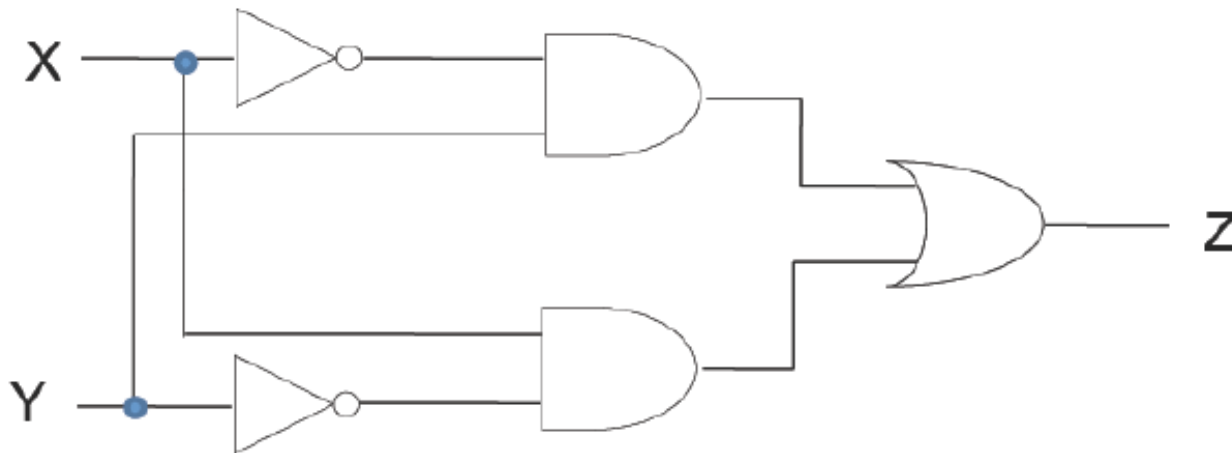
## EXCLUSIVE-OR GATE (XOR GATE): INTRODUCTION

- How to make XOR gate using basic gates (AND, OR and NOT)?

$$Z = X \oplus Y$$
$$Z = \bar{X} \cdot Y + X \cdot \bar{Y}$$





# LOGIC GATES

## EXCLUSIVE-NOR GATE (XNOR GATE): INTRODUCTION

- XNOR gate only has two inputs.
- The bubble on the output of XNOR symbol indicate that its outputs opposite that of XOR gate.



XNOR symbol

### Logic expression

$$Z = \overline{\overline{X}Y + X\overline{Y}} \text{ or } Z = \overline{X \oplus Y}$$

### Logic operation

- Output **Z** is **1** when **input X and Y** are **same**.
- Output **Z** is **0** when **input X and Y** are **different**.

XNOR Truth Table

Input		Output
X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1


# LOGIC GATES

## EXCLUSIVE-NOR GATE (XNOR GATE): INTRODUCTION

- How to make XNOR gate using basic gates (AND, OR and NOT)?

$$Z = \overline{X \oplus Y}$$



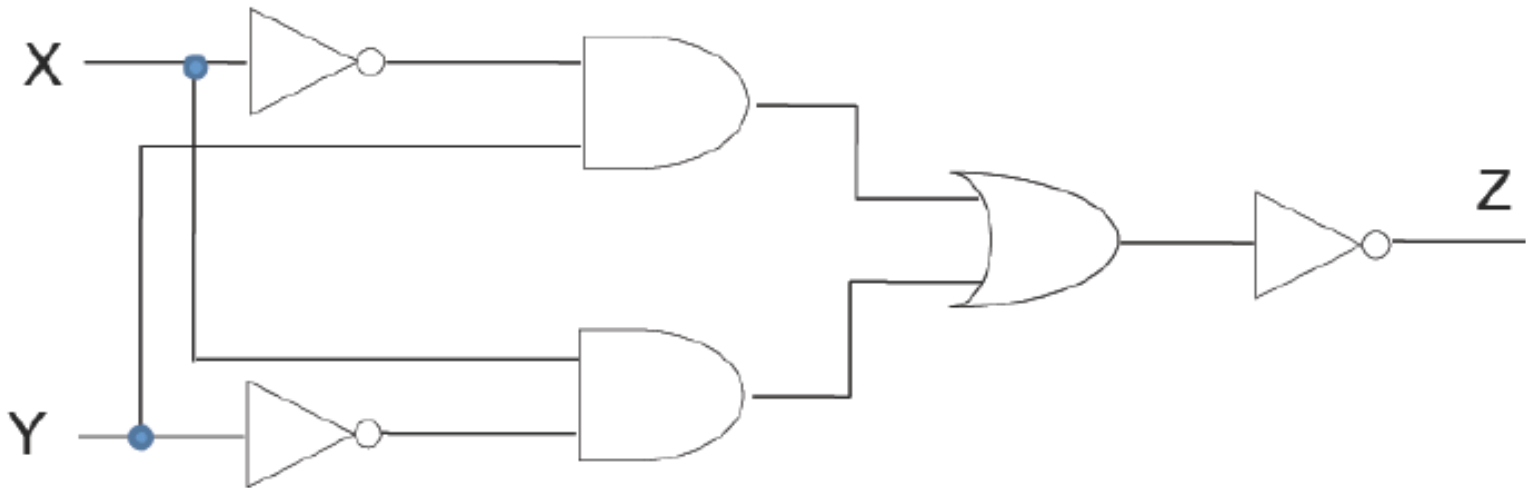
$$Z = \overline{\bar{X} \cdot Y + X \cdot \bar{Y}}$$



# LOGIC GATES
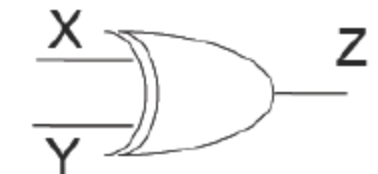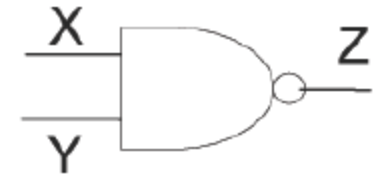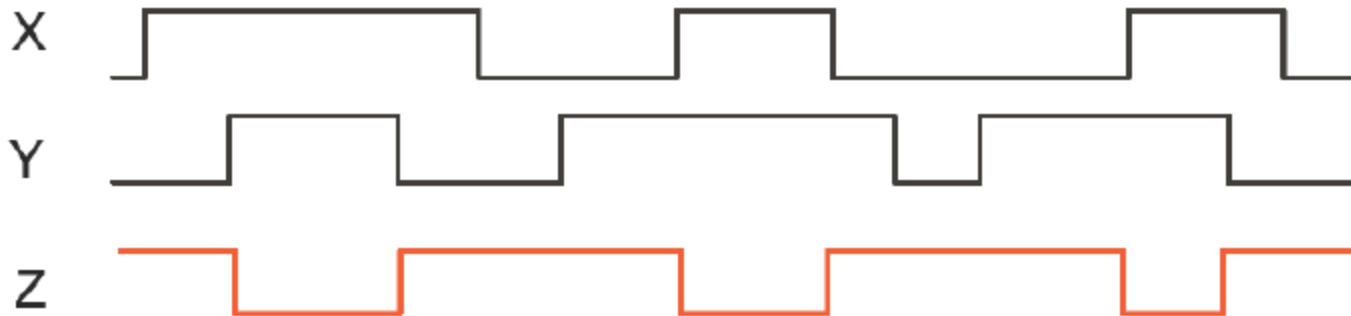
## ASSESSMENT 1


Draw the timing diagram for the following:



# LOGIC GATES
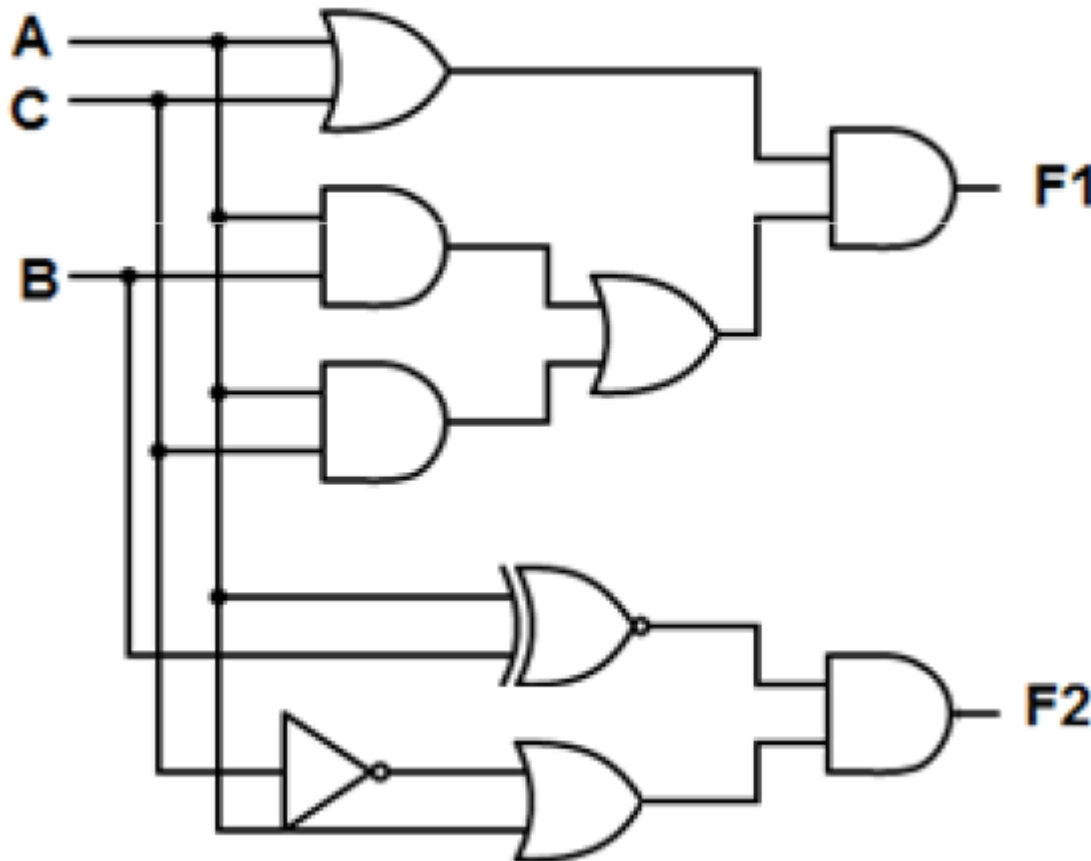
## ASSESSMENT 2


For the given circuit as shown below, obtain Boolean expression of F1 and F2?



# LOGIC GATES
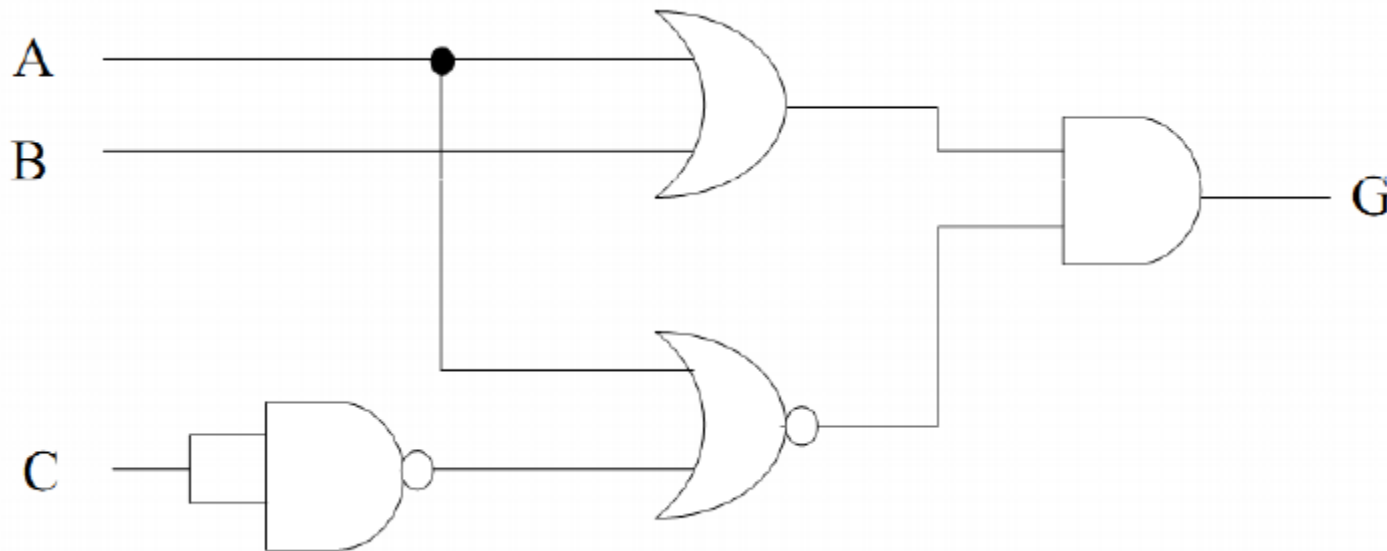
## HOMEWORK


Write the algebraic expression for the following circuit.



# LOGIC GATES
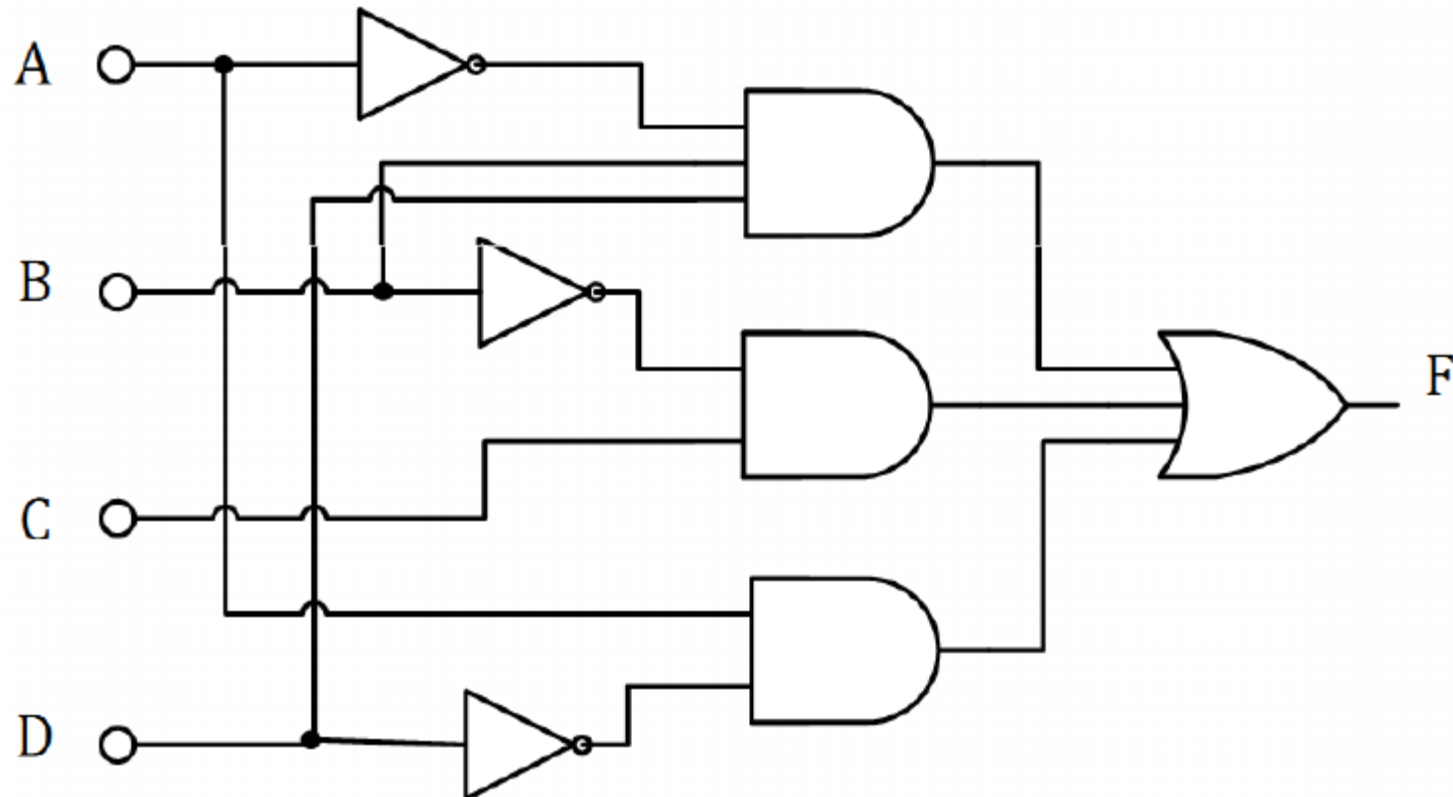
## HOMEWORK


Write the algebraic expression for the following circuit.



# LOGIC GATES
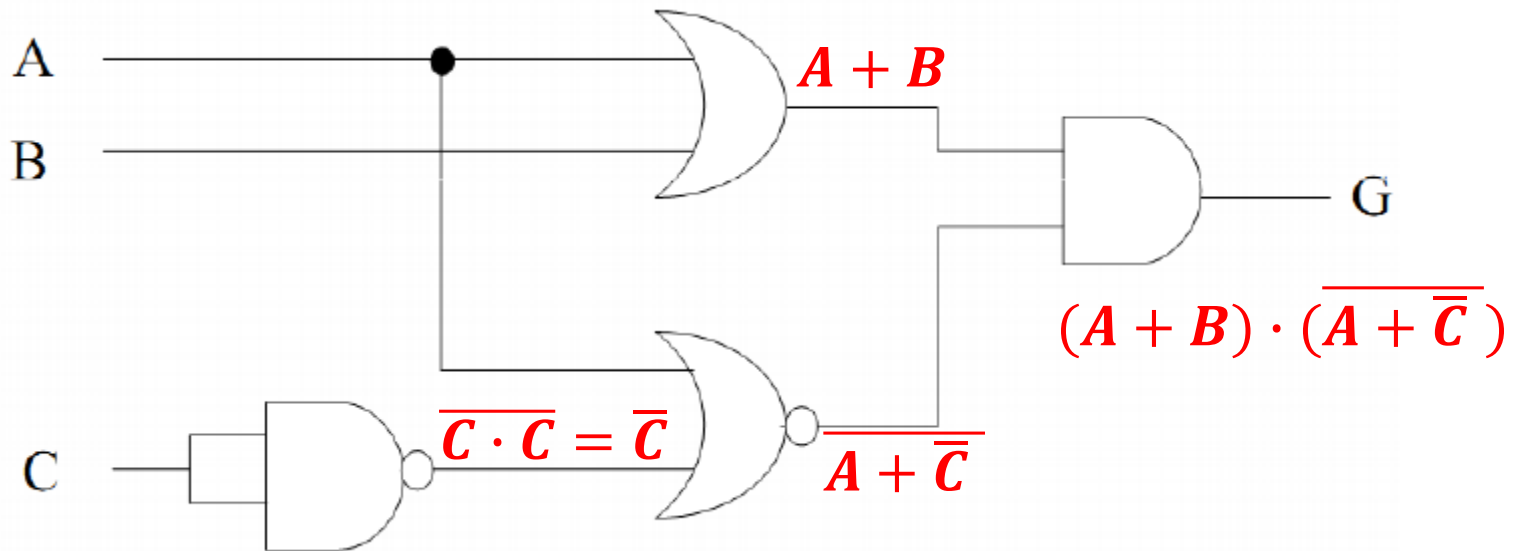
## HOMEWORK


Write the algebraic expression for the following circuit.



# LOGIC GATES
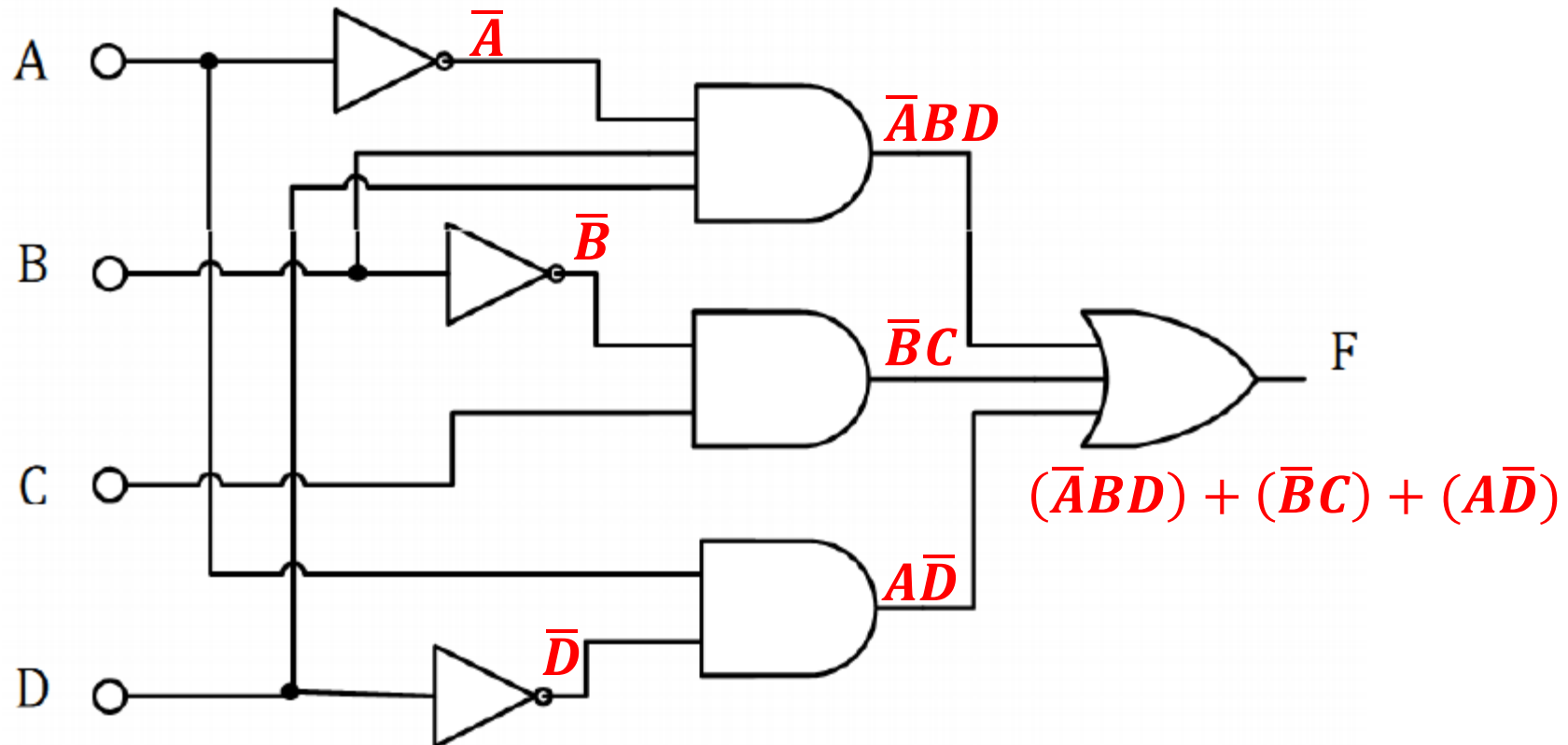
## HOMEWORK

Write the algebraic expression for the following circuit.





# BOOLEAN THEOREM

# BOOLEAN THEOREM

## BOOLEAN ALGEBRA

- Boolean algebra is the mathematics of digital systems.
- It is important in digital circuit analysis.
- Three terms that are used in Boolean algebra:

### Variable

A symbol (letter) used to represent logical quantity.

Example: F, X, Y, Z and etc. Any variable that can have **0** and **1** value.

### Complement

The **inverse** of variable.

Example:  
Complement of  
 $A = \bar{A} = A'$





### Literal

Variable or complement of variable.

# BOOLEAN THEOREM
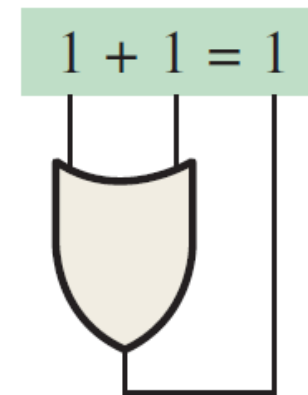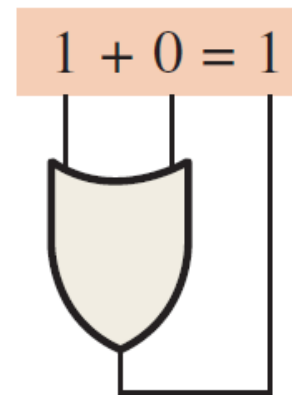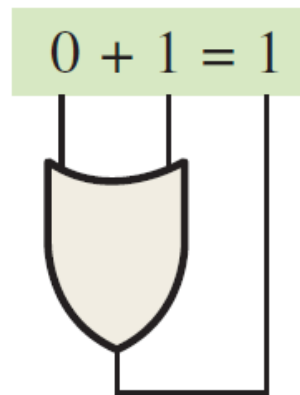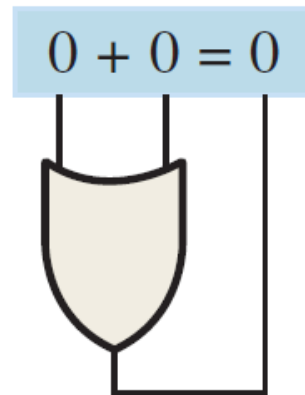
## BOOLEAN ALGEBRA (ADDITION)

- In Boolean algebra, a **sum term** is a sum of literals.
- In logic circuits, a **sum term** is produced by an **OR operation** with no AND operation involved.
- Example:  $A + B$ ,  $A + \bar{B}$ ,  $A + B + \bar{C}$




- A sum term equal to **1** when **one or more** of the literals are 1.
- A sum term equal to **0** only if **each** of the literals is 0.

# BOOLEAN THEOREM
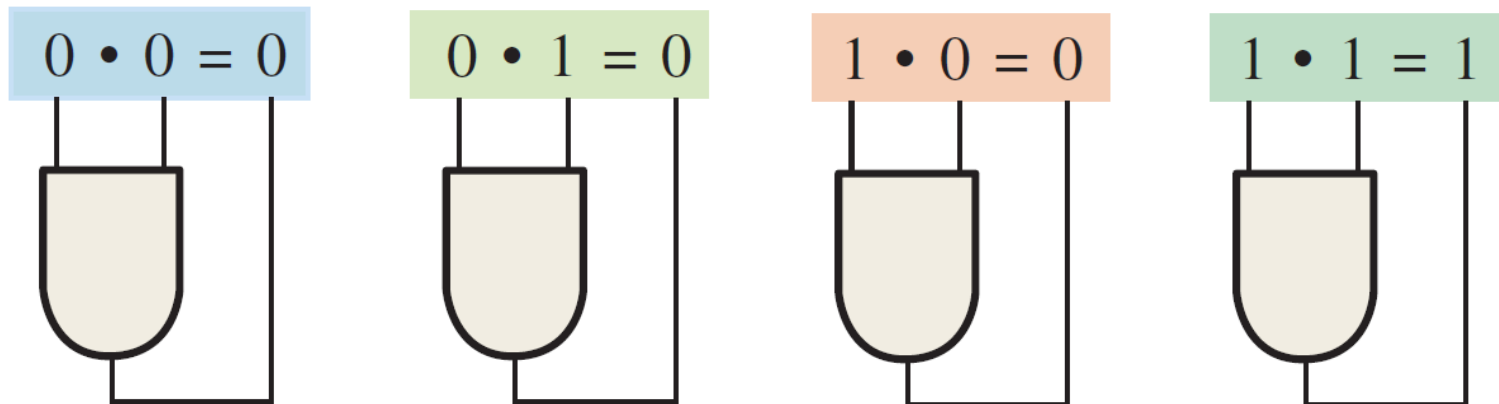
## BOOLEAN ALGEBRA (MULTIPLICATION)

- In Boolean algebra, a **product term** is a product of literals.
- In logic circuits, a **product term** is produced by an **AND operation** with no OR operation involved.
- Example:  $AB$ ,  $A\bar{B}$ ,  $AB + \bar{C}$



- A product term equal to **1** only if **each** of the literals is 1.
- A product term equal to **0** when **one or more** of the literals are 0.

# LAW AND RULES OF BOOLEAN ALGEBRA

# LAW AND RULES OF BOOLEAN ALGEBRA

## LAWS OF BOOLEAN ALGEBRA

There are **three** categories basic laws of Boolean algebra:

Commutative  
Laws

For addition  
and  
multiplication

Associative  
Laws

For addition  
and  
multiplication

Distributive  
Laws


Same as in  
ordinary  
algebra

# LAW AND RULES OF BOOLEAN ALGEBRA

## COMMUTATIVE LAWS


**The commutative law for addition:** The order variable are ORed make no different.

$$A + B = B + A$$

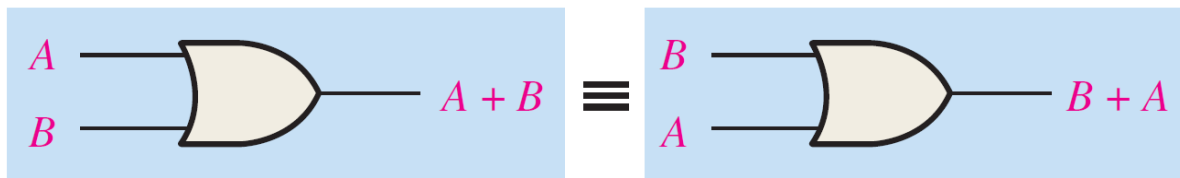

**The commutative law for multiplication:** The order variable are ANDed make no different.

$$A \cdot B = B \cdot A$$

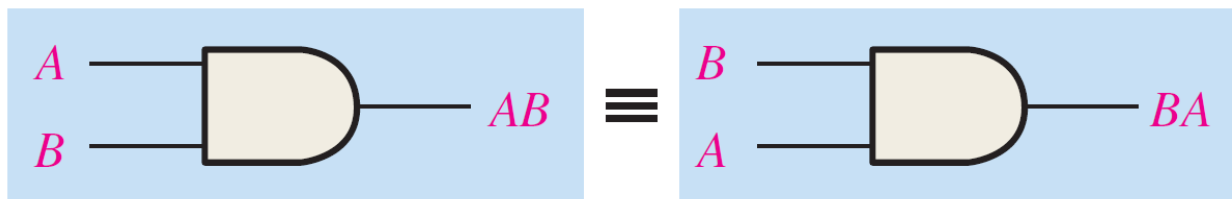


# LAW AND RULES OF BOOLEAN ALGEBRA

## ASSOCIATIVE LAWS


**The associative law for addition:** When ORing more than two variables, result are same regardless the grouping of variable.

$$A + (B + C) = (A + B) + C$$

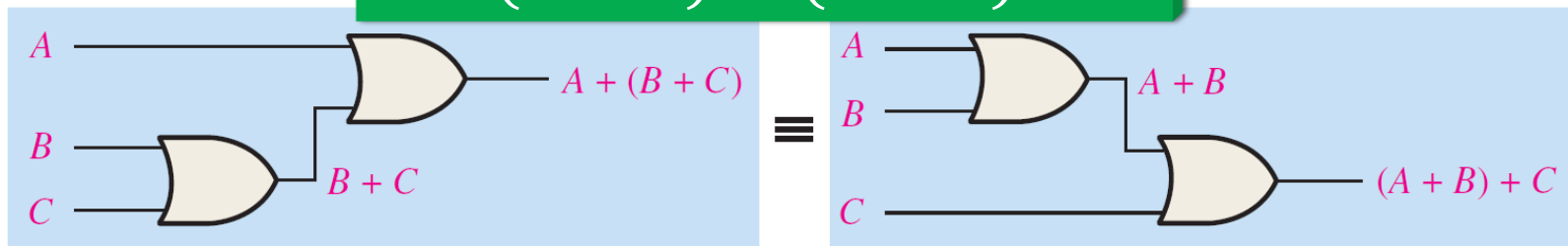

**The commutative law for multiplication:** When ANDing more than two variables, result are same regardless the grouping of variable.

$$A(BC) = (AB)C$$

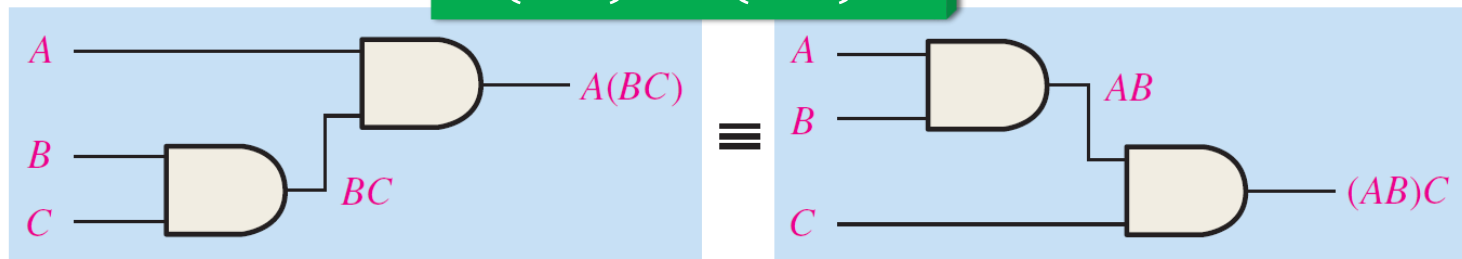




# LAW AND RULES OF BOOLEAN ALGEBRA

## DISTRIBUTIVE LAWS


Expanding an expression by multiplying term by term

$$A(B + C) = AB + AC$$

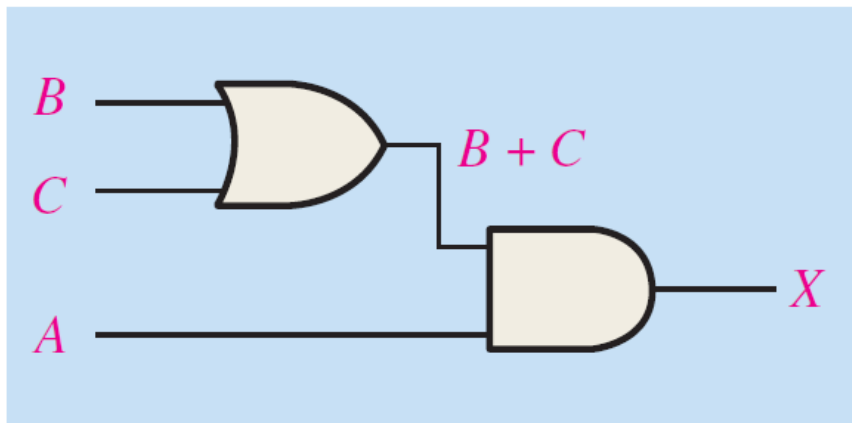

$$X = A(B + C)$$

≡

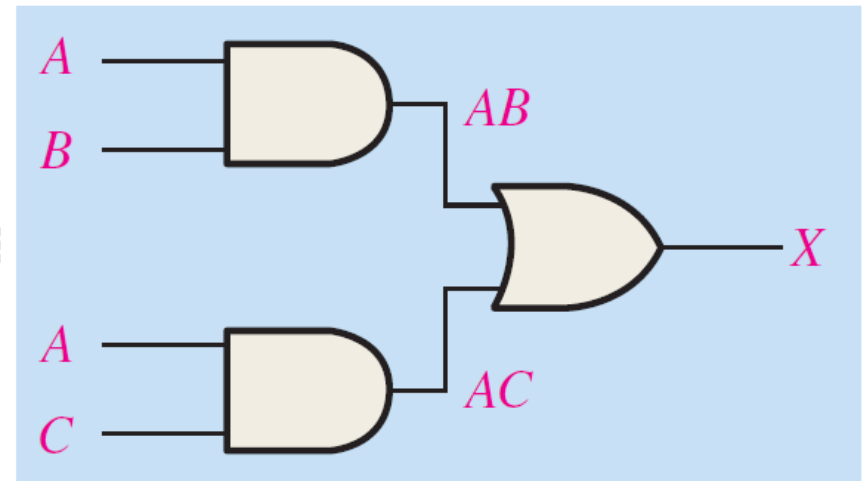

$$X = AB + AC$$

# LAW AND RULES OF BOOLEAN ALGEBRA

## BASIC 12 RULES

- List of Basic 12 rules that are useful in **manipulating and simplifying** Boolean expression.


1. $A + 0 = A$	7. $A \cdot A = A$
2. $A + 1 = 1$	8. $A \cdot \bar{A} = 0$
3. $A \cdot 0 = 0$	9. $\bar{\bar{A}} = A$
4. $A \cdot 1 = A$	10. $A + AB = A$
5. $A + A = A$	11. $A + \bar{A}B = A + B$
6. $A + \bar{A} = 1$	12. $(A + B)(A + C) = A + BC$

- Rule 1 to 9 can be viewed in terms of their application to logic gate.
- Rule 10 to 12 is derived in terms of simpler rules and laws previously discussed.

# LAW AND RULES OF BOOLEAN ALGEBRA



## BASIC 12 RULES

Rule 1:  $A + 0 = A$

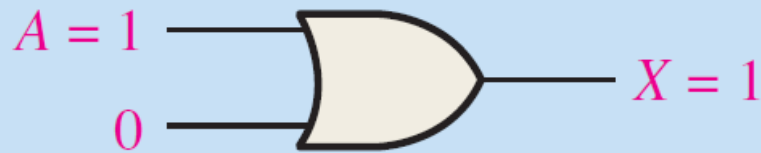

$$X = A + 0 = A$$

Rule 2:  $A + 1 = 1$

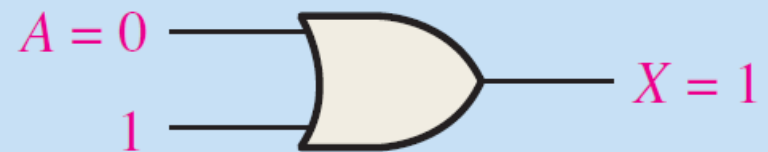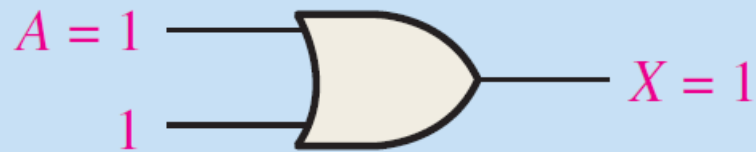


$$X = A + 1 = 1$$

# LAW AND RULES OF BOOLEAN ALGEBRA


## BASIC 12 RULES

Rule 3:  $A \cdot 0 = 0$

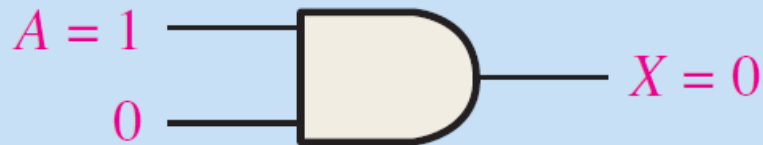

$$X = A \cdot 0 = 0$$

Rule 4:  $A \cdot 1 = A$


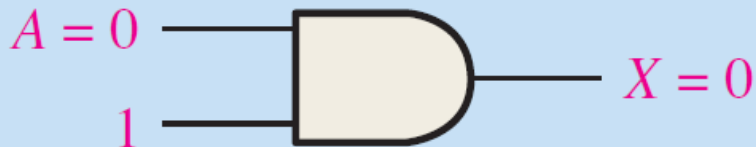


$$X = A \cdot 1 = A$$

# LAW AND RULES OF BOOLEAN ALGEBRA



## BASIC 12 RULES

Rule 5:  $A + A = A$

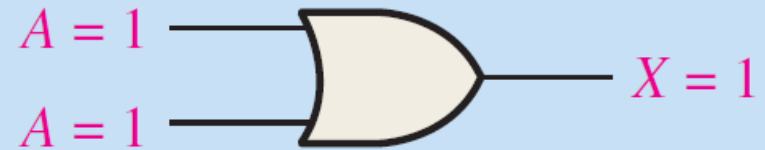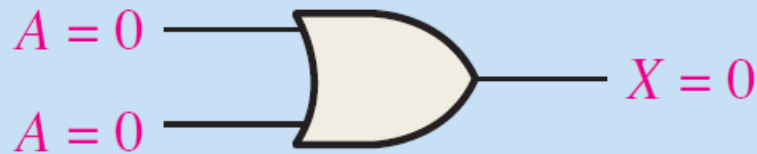

$$X = A + A = A$$

Rule 6:  $A + \bar{A} = 1$

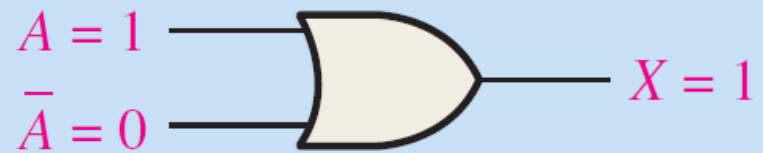
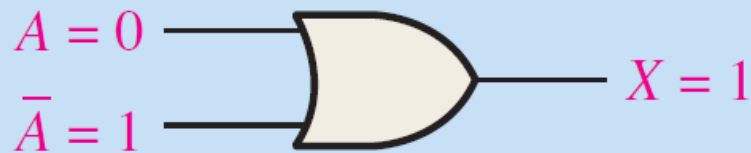


$$X = A + \bar{A} = 1$$

# LAW AND RULES OF BOOLEAN ALGEBRA



## BASIC 12 RULES

Rule 7:  $A \cdot A = A$

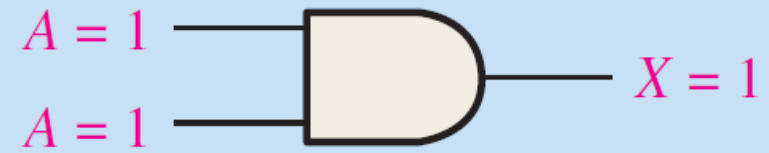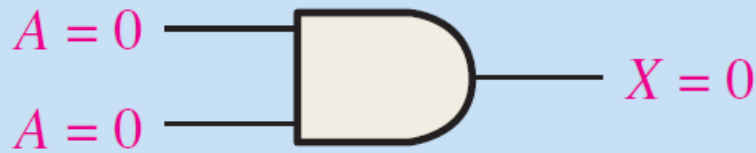

$$X = A \cdot A = A$$

Rule 8:  $A \cdot \bar{A} = 0$

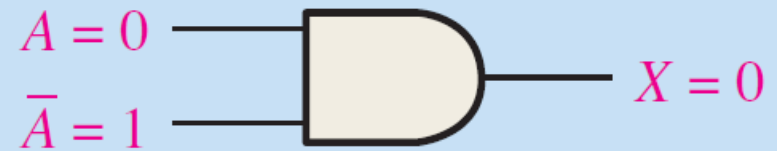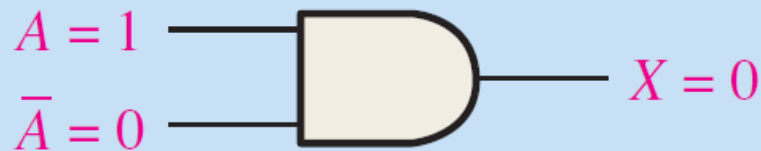


$$X = A \cdot \bar{A} = 0$$

# LAW AND RULES OF BOOLEAN ALGEBRA

## BASIC 12 RULES

Rule 9:  $\overline{\overline{A}} = A$

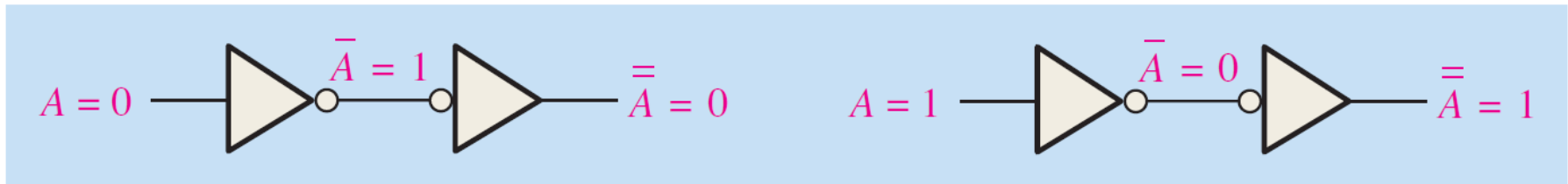

$$\overline{\overline{A}} = A$$

# LAW AND RULES OF BOOLEAN ALGEBRA

## BASIC 12 RULES

Rule 10:  $A + AB = A$

$$\begin{aligned} A + AB &= A(1 + B) \\ &= A(1) \\ &= A \end{aligned}$$


Factoring (Distributive law)

Rule 2:  $1 + B = 1$

Rule 4:  $A \cdot 1 = A$

$A$	$B$	$AB$	$A + AB$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

↑ equal ↑

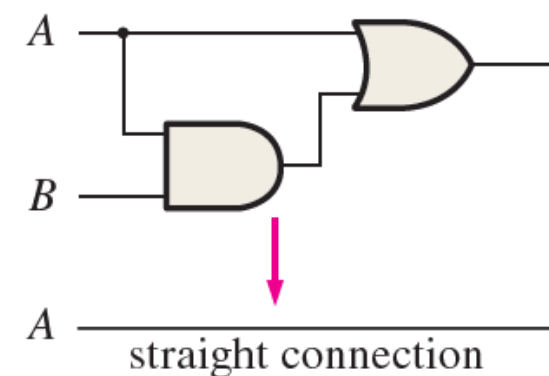

A logic diagram illustrating the implementation of Rule 10. It shows an OR gate with two inputs:  $A$  and  $AB$ . The output of the OR gate is  $A + AB$ . A straight connection from input  $A$  is shown below the OR gate, with a pink arrow pointing to it, indicating that the output is equal to  $A$ .



# LAW AND RULES OF BOOLEAN ALGEBRA

## BASIC 12 RULES

Rule 11:  $A + \bar{A}B = A + B$

$$\begin{aligned} A + \bar{A}B &= A + AB + \bar{A}B \\ &= A + B(A + \bar{A}) \\ &= A + B(1) \\ &= A + B \end{aligned}$$

Rule 10:  $A + AB$


Factoring (Distributive law)

Rule 6:  $A + \bar{A} = 1$

Rule 4:  $B \cdot 1 = B$

$A$	$B$	$\bar{A}B$	$A + \bar{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

↑ equal ↑

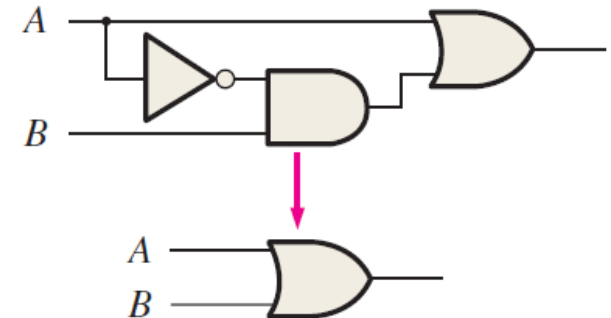

# LAW AND RULES OF BOOLEAN ALGEBRA

## BASIC 12 RULES

Rule 12:  $(A + B)(A + C) = A + BC$

$$\begin{aligned}(A + B)(A + C) &= AA + AC + AB + BC && \text{Distributive law} \\ &= A + AC + AB + BC && \text{Rule 7: } A \cdot A = A \\ &= A(1 + C) + AB + BC && \text{Factoring (Distributive law)} \\ &= A(1) + AB + BC && \text{Rule 2: } C + 1 = 1 \\ &= A + AB + BC && \text{Rule 4: } A \cdot 1 = A \\ &= A(1 + B) + BC && \text{Factoring (Distributive law)} \\ &= A(1) + BC && \text{Rule 2: } B + 1 = 1 \\ &= A + BC && \text{Rule 4: } A \cdot 1 = A\end{aligned}$$


# LAW AND RULES OF BOOLEAN ALGEBRA

## BASIC 12 RULES

Rule 12:  $(A + B)(A + C) = A + BC$

$A$	$B$	$C$	$A + B$	$A + C$	$(A + B)(A + C)$	$BC$	$A + BC$
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

↑ equal ↑

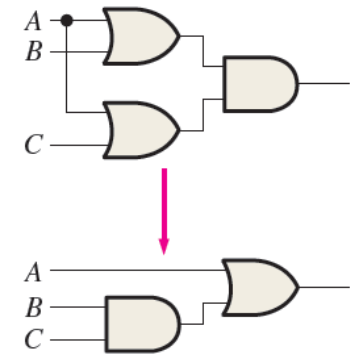

# LAW AND RULES OF BOOLEAN ALGEBRA

## DEMORGAN'S THEOREM


DeMorgan proposed two theorems that are important part of Boolean algebra.

Truth Table

Input		Output	
X	Y	$X + Y$	$X \cdot Y$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

1<sup>st</sup> Theorem
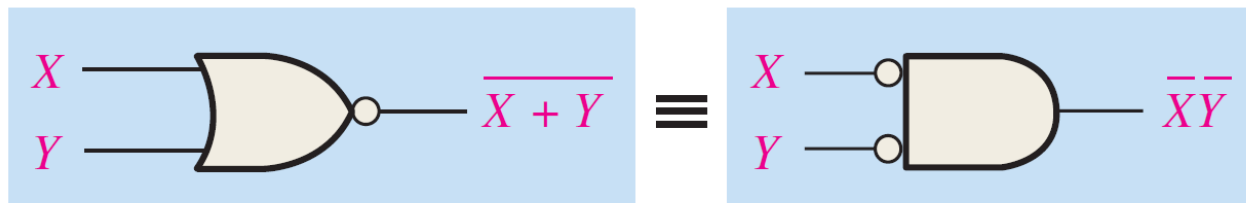
$$\overline{X + Y} = \bar{X} \cdot \bar{Y}$$



NOR

Negative-AND

# LAW AND RULES OF BOOLEAN ALGEBRA

## DEMORGAN'S THEOREM


DeMorgan proposed two theorems that are important part of Boolean algebra.

Truth Table

Input		Output	
X	Y	$X \cdot Y$	$X + Y$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

2<sup>nd</sup> Theorem
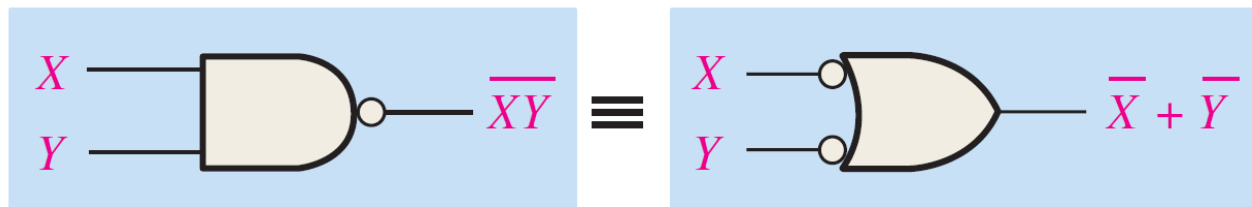
$$\overline{X \cdot Y} = \overline{X} + \overline{Y}$$



NAND

Negative-OR

# LAW AND RULES OF BOOLEAN ALGEBRA

## HOMEWORK

Apply DeMorgan's Theorem to each of following expressions:

$$1. F = \overline{(A + B + C)D}$$

$$2. F = \overline{ABC + DEF}$$

$$3. F = \overline{A\bar{B} + \bar{C}D + EF}$$

# **BOOLEAN EXPRESSION SIMPLIFICATION**

# BOOLEAN EXPRESSION SIMPLIFICATION

## BOOLEAN SIMPLIFICATION

Simplify Boolean expression below:

$$AB + A(B + C) + B(B + C)$$

$$= AB + AB + AC + BB + BC \quad \text{Distributive Law}$$

$$= AB + AC + B + BC \quad \text{Rule 5: } AB + AB = AB,$$

$$\text{Rule 7: } BB = B$$

$$= AB + AC + B(1 + C) \quad \text{Distributive Law}$$

$$\text{Rule 2: } C + 1 = 1$$

$$= AB + AC + B \quad \text{Distributive Law}$$

$$= B(A + 1) + AC \quad \text{Rule 2: } A + 1 = 1$$


$$= B + AC$$




# BOOLEAN EXPRESSION SIMPLIFICATION
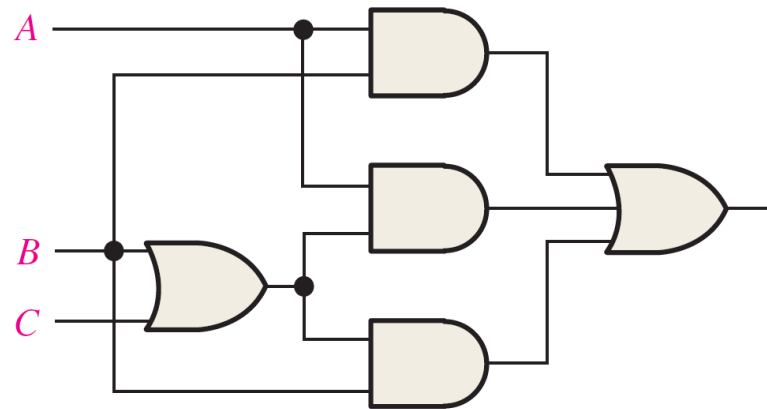
## BOOLEAN SIMPLIFICATION

Original Expression:  $AB + A(B + C) + B(B + C)$




Simplified Expression:  $B + AC$

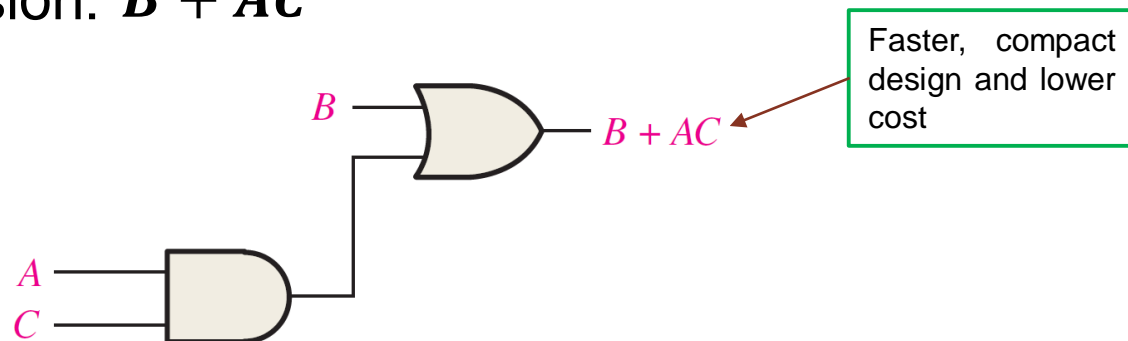

# BOOLEAN EXPRESSION SIMPLIFICATION
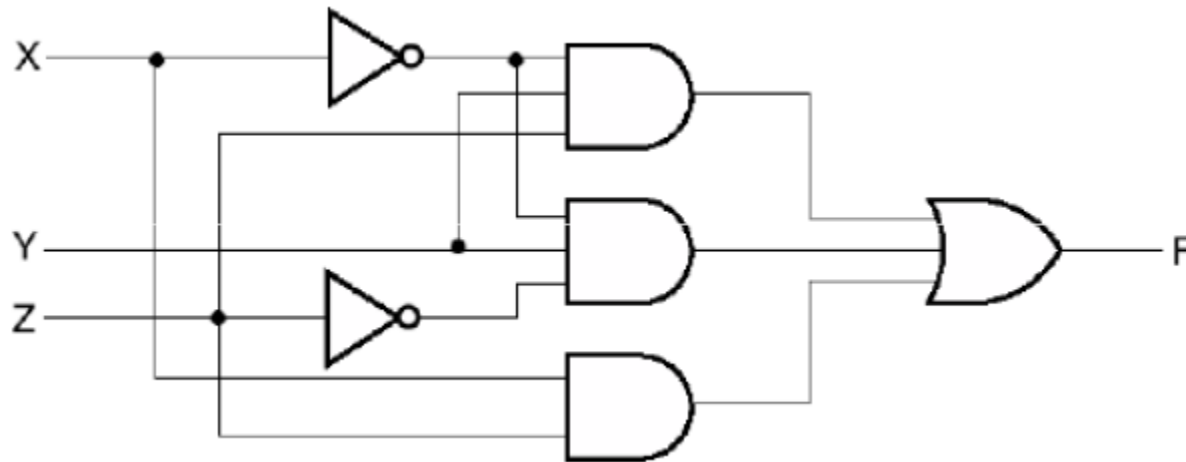
## ASSESEMENT 3

Find the Boolean expression for given logic circuit. Then simplify the Boolean expression.



$$F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$$

# BOOLEAN EXPRESSION SIMPLIFICATION

## ASSESSMENT 3 (SOLUTION)

Do the simplification of Boolean expression as follows:

$$F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$$

$$F = \bar{X}Y(Z + \bar{Z}) + XZ$$

*Distributive Law*


$$F = \bar{X}Y(1) + XZ$$

*Rule 6:  $Z + \bar{Z} = 1$*

$$F = \bar{X}Y + XZ$$

*Rule 4:  $\bar{X}Y \cdot 1 = \bar{X}Y$*

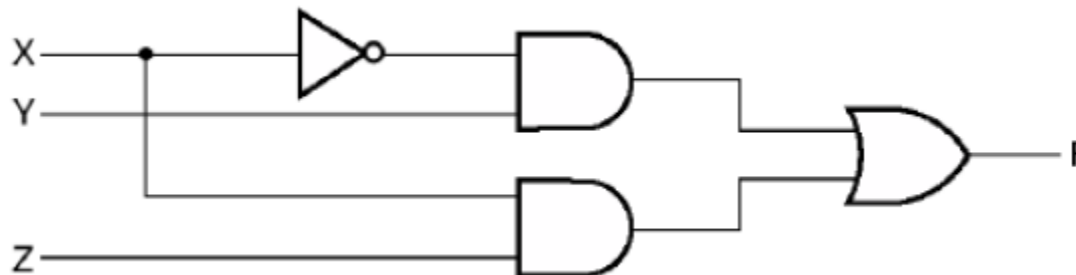Simplified Boolean expression,  $F = \bar{X}Y + XZ$



# BOOLEAN EXPRESSION SIMPLIFICATION

## HOMework


Simplify the following using Boolean algebra techniques and draw the simplified logic circuit:

1.  $A\bar{B} + AB$
2.  $AB + A(B + C) + B(B + C)$
3.  $[A\bar{B}(C + BD) + \bar{A}\bar{B}]C$
4.  $\overline{AB + AC} + \bar{A}\bar{B}C$

# BOOLEAN EXPRESSION SIMPLIFICATION

## HOMEWORK

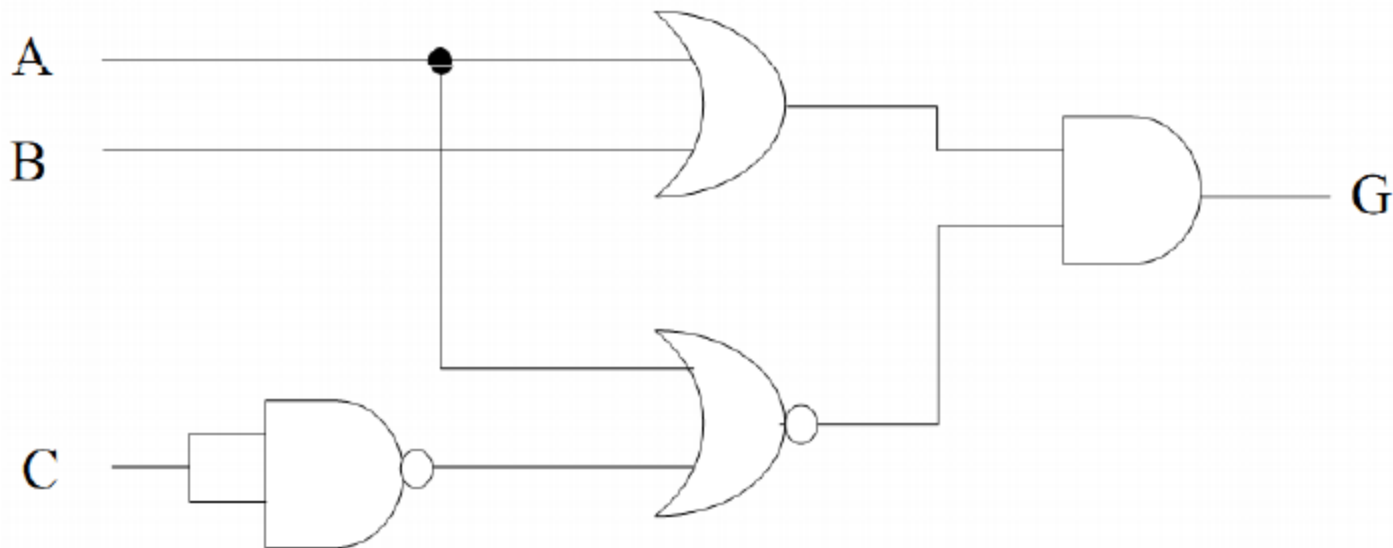1. Write the algebraic expression for the following circuit.
2. Produce a truth table for the circuit.
3. Design a simpler circuit having the same output.



# BOOLEAN EXPRESSION SIMPLIFICATION

## HOMEWORK

1. Derive a Boolean expression from the truth table.
2. Simplify the Boolean expression using Boolean algebra.
3. Draw a logic circuit for the simplified Boolean expression using only OR and AND gates.
4. Draw the logic circuit using only 2-input NAND gates.

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1