

TUTORIAL CHAPTER 4 (SEEU2012)

1. Explain briefly why the operating point (Q-point) of a BJT small-signal amplifier circuit is chosen to be located at the centre of the load line.
2. Referring to the values of voltage V_{BE} and voltage V_{BC} of the silicon npn BJT for each biasing condition in Table QA.2, state whether the BJT is operated in active, saturation or cut-off region.

Table QA.2

V_{BE} (V)	V_{BC} (V)	Operation region
0.3	0.7	
0.7	-1	
0.7	0.65	

3. Referring to Figure QA.3, assume the BJT is operated in active region.


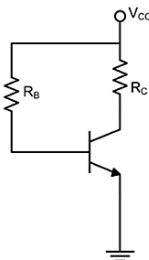


Figure QA.3


- a. When the value of base resistor R_B is increased, current I_C _____.
 - b. When the value of collector resistor R_C is decreased, current I_C _____ and voltage V_{CE} _____.
4. Referring to the amplifier circuit shown in Figure QB.1, given the BJT parameters: $V_{BE} = 0.7$ V, $\beta = h_{FE} = h_{fe} = 140$, $V_T = 26$ mV and $r_o = \infty$.
 - a. By doing DC analysis, prove the collector current $I_C = 0.76$ mA.
 - b. Draw and label the small-signal hybrid- π ac equivalent circuit at mid-frequency range.
 - c. Calculate the values of parameters g_m and r_π .
Answer: $g_m = 29.23$ mS and $r_\pi = 4.79$ k Ω .
 - d. Calculate the input impedance, Z_i .
Answer: 3.86 k Ω
 - e. Calculate the output impedance, Z_o .
Answer: 10 k Ω
 - f. Calculate the voltage gain, $A_V = V_o / V_i$ at mid-frequency range.
Answer: -26.57

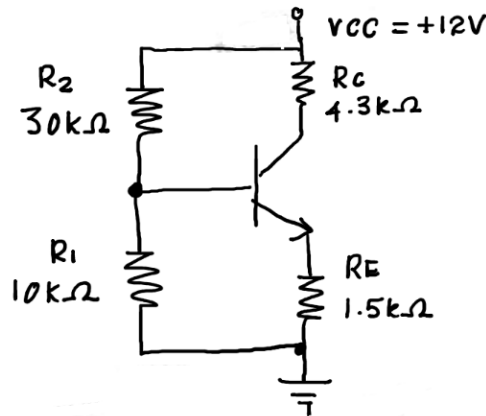5. One of the important aspects in designing biasing circuit is the stability of the Q –point. If you want to design a small-signal amplifier using BJT, would you choose a circuit with an emitter resistor, R_E ? State a reason for your choices.
6. The Q – point is best located in the active region. Explain the behaviour of the collector current, I_C and V_{CE} when the BJT is operating in the active, saturation and cut – off region.
7. Referring to the BJT DC circuit in Figure Q.1B. Given $V_{BE} (ON) = 0.65 \text{ V}$ and $\beta = 100$.



- a. Find the Q – point, V_{CEQ} and I_{CQ} .
Answer: $I_{BQ} = 15\mu\text{A}$, $I_{CQ} = 1.5\text{mA}$ and $V_{CE} = 3.3\text{V}$.
- b. Determine the value for $I_{C(SAT)}$ and $V_{CE(CUT-OFF)}$. Then draw the DC load line and show the position of the Q – point. State if the biasing circuit is suitable to use in small signal amplification.
Answer: $I_{C(sat)} = 2.07\text{mA}$ and $V_{CE} = 12\text{V}$.

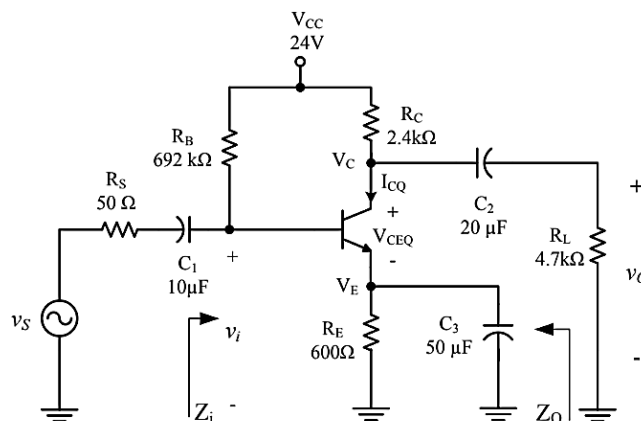
8. A bipolar junction transistor (BJT) amplifier circuit as in Figure below has the following specifications: $\beta = 140$, $V_{BE} = 0.7 \text{ V}$, $V_T = 26 \text{ mV}$ and $r_o = \infty$.



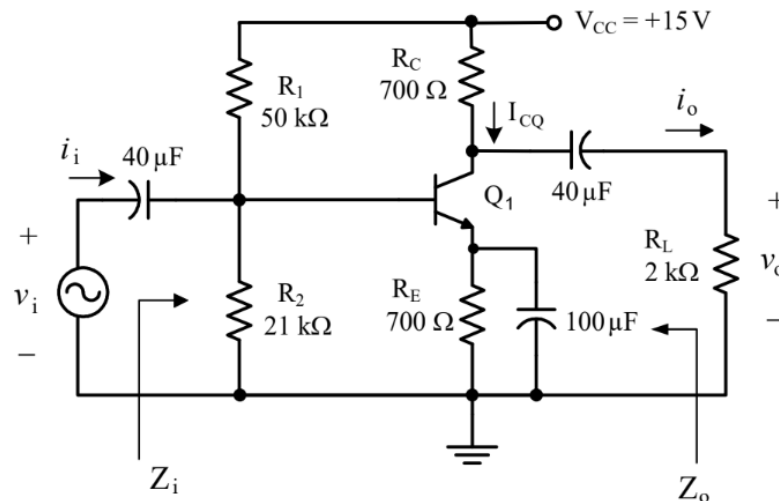
- a. Show that $I_{CQ} = 4.2 \text{ mA}$.
- b. Calculate V_{CEQ} and V_C .
Answer: $V_{CEQ} = 11.4\text{V}$ and $V_C = 13.92\text{V}$.

- Draw the hybrid- π ac equivalent circuit at mid-frequency.
- Calculate g_m , r_π , input impedance (Z_i) and output impedance (Z_o).
Answer: $g_m = 161.5 \text{ mS}$, $r_\pi = 866.7 \Omega$, $Z_i = 0.87 \text{ k}\Omega$ and $Z_o = 2.4 \text{ k}\Omega$
- Determine $A_{v_s} = v_o/v_s$.
Answer: -241.7

- State the suitable application for BJT that works in (i) active and (ii) saturation regions.
- A BJT amplifier circuit in figure below has the following specifications: $h_{FE} = h_{fe} = \beta = 350$, $V_T = 26 \text{ mV}$, and $r_o = \infty$.



- By doing DC analysis, prove that current $I_{CQ} = 5 \text{ mA}$.
 - Draw and label the small-signal hybrid- π AC equivalent circuit at mid-frequency range.
 - Calculate the value of parameter g_m and r_π .
Answer: $g_m = 192.31 \text{ mS}$ and $r_\pi = 1.82 \text{ k}\Omega$.
 - Calculate the input impedance, Z_i .
Answer: $1.62 \text{ k}\Omega$.
 - Calculate the output impedance, Z_o .
Answer: 700Ω .
 - Calculate the voltage gain, $A_v = V_o / V_i$.
Answer: -99.72
 - If the input voltage $V_i = 0.01 \sin(100\pi t) \text{ (V)}$, draw and label the output voltage, V_o .
- Figure below represents a common emitter amplifier circuit. Assume the BJT is in the active region. The parameters of the BJT amplifier circuit are: $\beta = 100$, $V_{BE} = 0.7 \text{ V}$, $V_T = 26 \text{ mV}$ and $I_{EQ} = 2.31 \text{ mA}$.

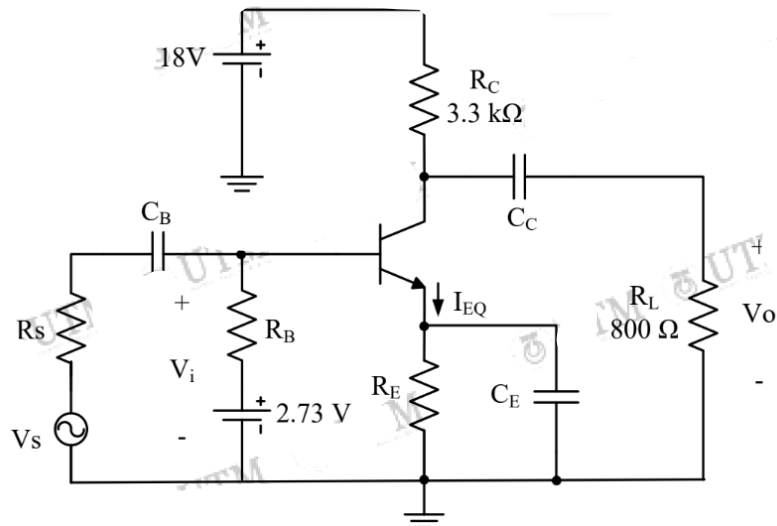

- Draw the AC equivalent circuit at mid – frequency using Hybrid-pi model at mid- frequency band.
- Calculate the value of r_{π} and g_m .
Answer: $g_m = 88.8 \text{ mS}$ and $r_{\pi} = 1.126 \text{ k}\Omega$.
- The input impedance, Z_i is $1.07 \text{ k}\Omega$, determine the value of resistor R_B and the output impedance, Z_o .
Answer: $3.3\text{k}\Omega$.
- From the AC equivalent circuit, derive an expression for the open circuit voltage gain, $A_v = V_o/V_i$, then calculate the value.
Answer: -57
- The source resistance, R_s is very small compared to input impedance, Z_i resulting source voltage, $V_s = V_i$. If $V_s = 0.15 \sin(\omega t) \text{ V}$ with frequency 50Hz , determine the output voltage V_o . Then draw and the output waveform.
Answer: $-8.6 \sin(\omega t) \text{ V}$
- Determine the minimum peak amplitude of the source voltage, $V_s(p)$ to avoid the output signal, V_o from clipping.
Answer: 0.32V