

**SEEU2012  
Electronics  
20212022/2**

# **Chapter 4 Bipolar Junction Transistor (BJT) DC Analysis**

**Dr. Nur Najahatul Huda Saris**  
School of Electrical Engineering,  
Faculty of Engineering  
UNIVERSITI TEKNOLOGI MALAYSIA  
[nurnajahatulhuda@utm.my](mailto:nurnajahatulhuda@utm.my)

# Course Learning Outcomes

1

Apply the basic law and theorems of electronic devices to describe their basic operation.

2

Apply the basic law, theorems and methods of analysis to solve complex problem related to circuitry.

3

Work in a team and communicate effectively.

# Learning Outcomes


- i. Describe the basic structure of a BJT.
- ii. Explain and analyze basic BJT bias and operation.
- iii. Discuss on the function of a BJT as an amplifier.
- iv. Discuss the parameters and characteristic of a BJT and its application in electrical circuit.

- 
- PN2222A
- TO-92
- EBC

-
 
# What is Transistor?

- ❑ Two basic types of transistor is **bipolar junction transistor (BJT)** and **Field Effect Transistor (FET)**.
- ❑ Transistor is like **2 diodes** connected.





- ❑ Each region have **different doping** concentration.
- ❑ Transistor is widely been used as **switch and amplifier**.

# Introduction to BJT

- ❑ BJT is bipolar because both majority and minority carriers take part in the current flow. (a) N-type - electrons as majority carrier  
(b) P-type – holes as majority carrier.
- ❑ 2 types of BJT: (a) NPN and (b) PNP
- ❑ BJT regions are:
  - Emitter (E) – send the carries into the base region and then into the collector.
  - Base (B) act as control region. Carriers flow depending on the biased voltage.
  - Collector (C) – collects the carries.



# Structure & Symbol of BJT

## PNP TYPE

  


$$I_E = I_C + I_B$$

## NPN TYPE

  

$$I_E = I_C + I_B$$

# NPN Transistor Structure

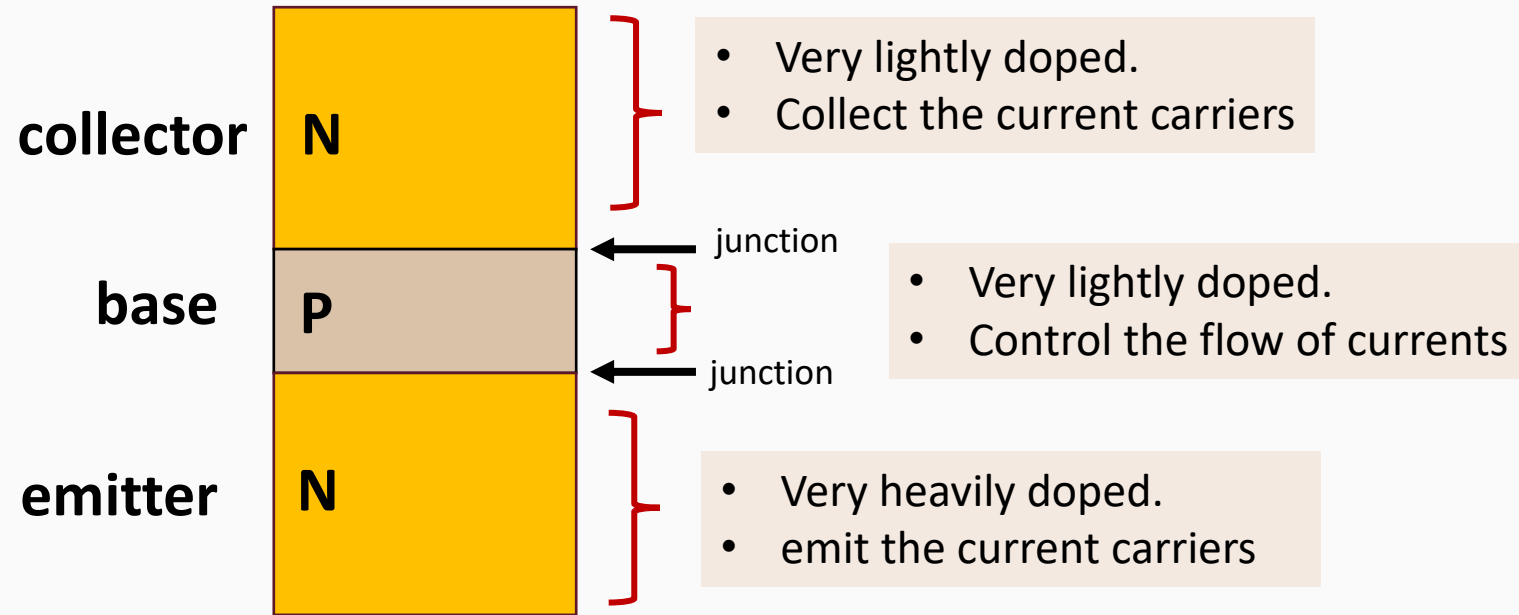

- ☐ The emitter is rich in current carriers. It send the carriers into the base region and on to the collector.
- ☐ The collector collect the carriers.
- ☐ The emitter emits the carriers.
- ☐ The base act as a control region. It can allow none, some or many carriers to flow from emitter to collector.



# BJT Characteristic & Parameters

- ❑  $\beta_{DC}$  – is the ratio of the DC collector current,  $I_C$  to the DC base current, ( $I_B$ )
- ❑ Typical value range from less than 20 to 200 or higher.

$$\beta_{DC} = \frac{I_C}{I_B}$$

- ❑  $\alpha_{DC}$  – is the ratio of the DC emitter current,  $I_E$  to the DC collector current, ( $I_C$ ).
- ❑ The value range from 0.95 to 0.99 but always less than 1.

$$\alpha_{DC} = \frac{I_C}{I_E}$$

$$\beta = \left( \frac{\alpha}{1 - \alpha} \right)$$



# BJT Behavior: Current-Voltage Characteristics



- ❑ The behaviour of the transistor can be represented by current-voltage (I-V) curves (called the characteristic curves of the device).
- ❑ **Input Characteristics**
  - The relation between **input current** and **input voltage** for different values of **output voltage**
- ❑ **Output Characteristics**
  - The relation between **output current** and **output voltage** for different values of **input current**



# BJT Basic Operation Region

- ❑ To produce a desired mode of operation, the two P-N junctions must be correctly biased
- ❑ NPN transistor will be used for illustrationThe operation of the PNP is the same as for the NPN except that
  - the roles of the electrons and holes
  - the bias voltage polarities
  - the current directions - are all reversed
- ❑ A single PN junction has two different types of bias: forward and reverse.
- ❑ Thus, a 2 PN junction device has four types of bias.

# BJT Mode of Operation for NPN and PNP

 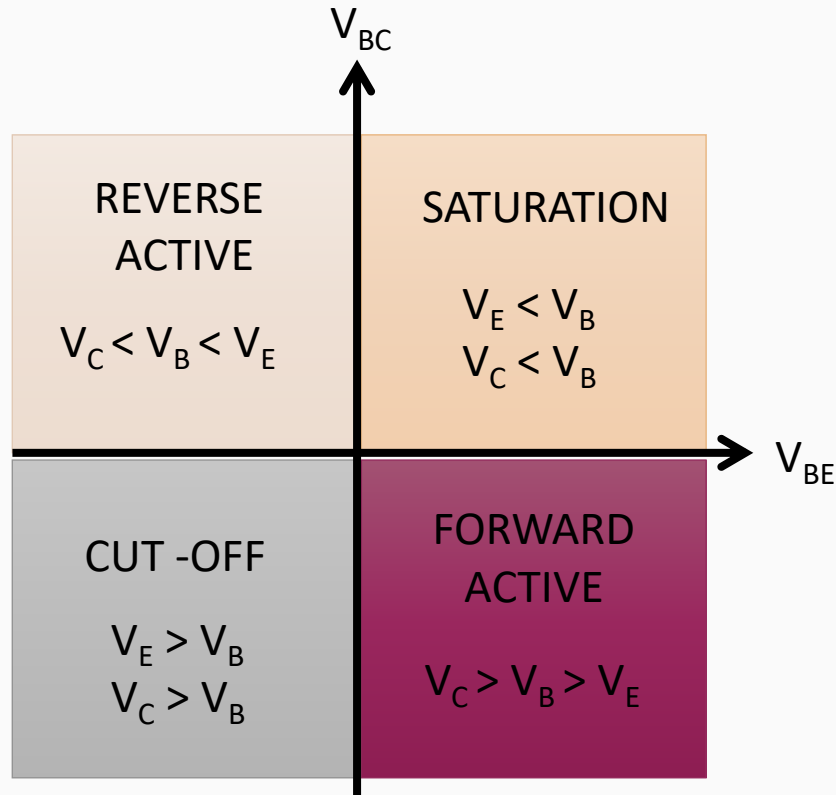

- ❑ Saturation and cut-off operations are important for digital circuits like switching.
- ❑ Active region are important for amplifier application.



## Operating regions of BJT

Cut-off region

Saturation region

Active region



OFF

CUT OFF  
NO-FLOW



ON

INTERMEDIATE  
CONTROLLED  
CURRENT FLOW



FULL  
ON

SATURATION  
FULL CURRENT  
FLOW

## Example – NPN Transistor

Base -Emitter Junction	Base - Collector Junction	Operating Region
Reverse biased	Reverse biased	
Forward biased	Reverse biased	
Forward biased	Forward biased	


❑ What are the two (2) main applications of BJT?

## Exercise -

<https://padlet.com/nurnajahatulhuda/hba67po8p9ok8oun>


Figure below illustrate a structure of NPN transistor contain collector (C), base (B) and emitter (E). Fill in the blank.

 - ☐ The base (B) to emitter (E) junction is normally \_\_\_\_\_ biased and the resistance at the junction is \_\_\_\_\_.
- ☐ The collector (C) to base (B) junction is normally \_\_\_\_\_ biased and the resistance at the junction is \_\_\_\_\_.
- ☐ The smallest current in NPN bipolar junction transistor is the \_\_\_\_\_ current.



 
# Collector - Base Characteristic Curve Input Characteristic

- ❑ The characteristic resembles a family of **forward biased diode** curves
- ❑  $I_B$  increases as  $V_{CE}$  decreases for a fixed value of  $V_{BE}$




 
# Collector Characteristic Curve Output Characteristic



# BJT Region Comparison


Active Region	Saturation Region	Cut – Off Region
<input type="checkbox"/> B-E junction forward biased	<input type="checkbox"/> B-E and C-E junction are forward biased.	<input type="checkbox"/> B-E and C-E junction are reverse biased.
<input type="checkbox"/> C- B junction reverse biased	<input type="checkbox"/> $I_B$ and $I_C$ are too big but $V_{CE}$ is very small.	<input type="checkbox"/> $I_B < \mu A$ but $I_C$ is not zero. Avoid this region for undistorted signal.
<input type="checkbox"/> Can be employed to used as voltage and current amplification	<input type="checkbox"/> Suitable region to used as logic switch.	<input type="checkbox"/> Suitable region to used as logic switch.

# What is Q – Point? (DC Operating Point)


- ☐ When the BJT only have DC input (no ac input) it will have specific value of  $I_C$  and  $V_{CE}$ .
- ☐ It correspond on the specific point on the DC load line. This point is called Q – point.
- ☐ It's a point on the collector characteristic curve ( $I_C - V_{CE}$ ) with constant  $I_B$ .
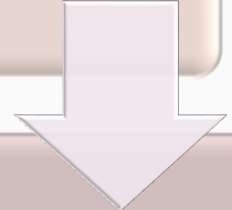
# Purpose of BJT Biasing

BJT should be biased to determine its operating point or Q point.




To ensure whether it is in active region to be used as amplifier or in saturation or cut-off region to be used as switch.




A good biasing circuit must have Q – point at the center of the DC load line to obtain maximum symmetrical output swing.
 
# Q – Point at the center of DC Load line


 
# Q – Point NOT at the center of DC Load line




# BJT DC Load Line

- ❑ A straight line intersecting the vertical axis at approximately  $I_{C(sat)}$  and the horizontal axis at  $V_{CE(off)}$ .
- ❑  $I_{C(sat)}$  occurs when transistor operating in *saturation region*


$$I_{C_{sat}} = \left. \frac{V_{CC}}{R_C} \right|_{V_{CE}=0}$$

- ❑  $V_{CE(off)}$  occurs when transistor operating in *cut-off region*

$$V_{CE(off)} = V_{CC} - I_C R_C \Big|_{I_C=0}$$

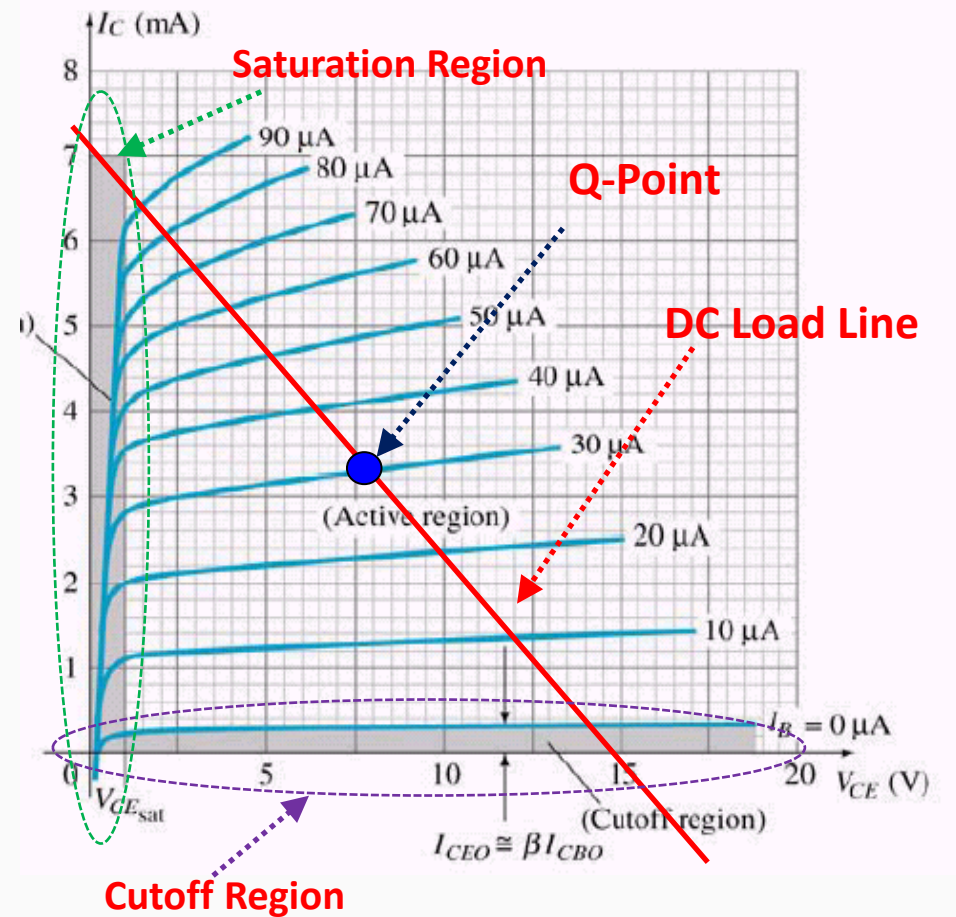

# BJT DC Load Line

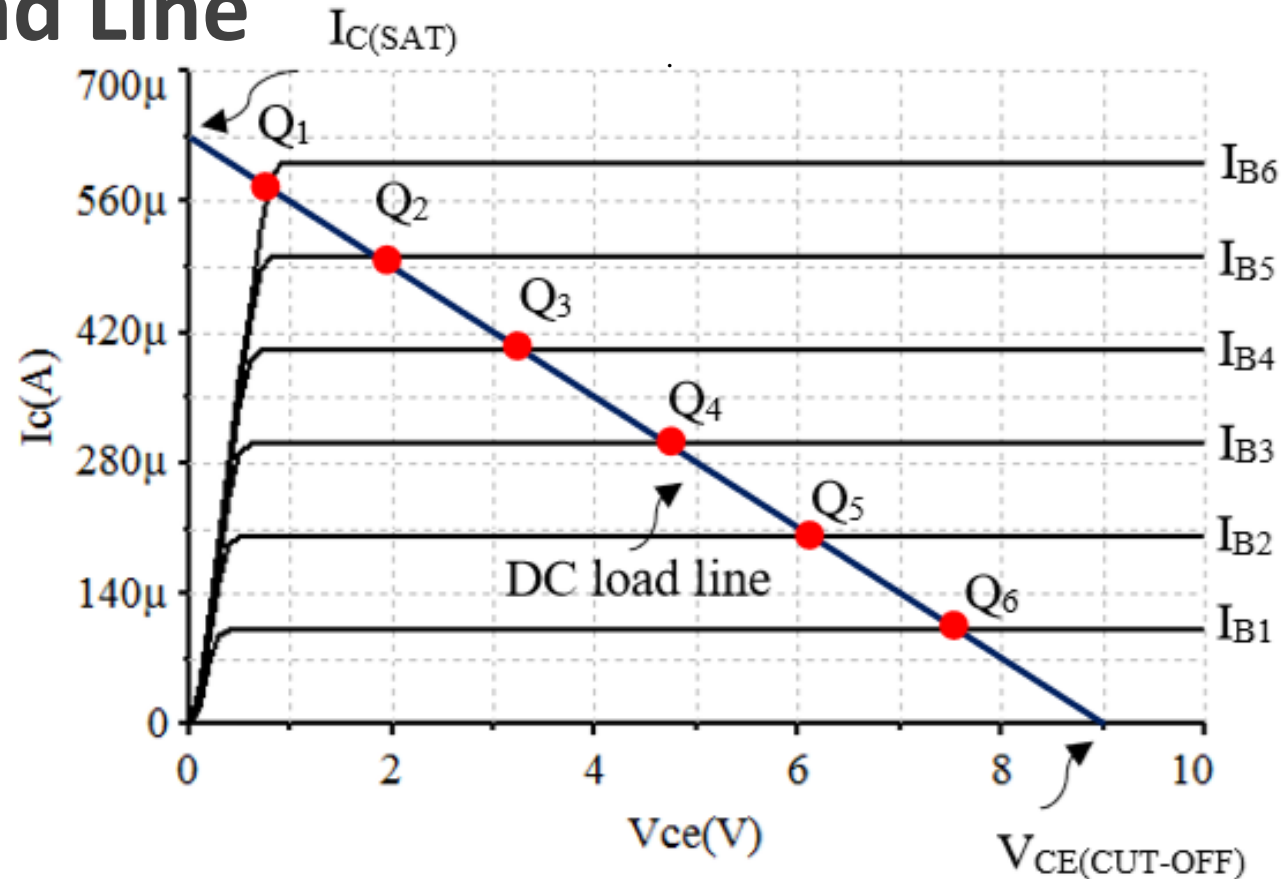

To make sure that the chosen Q –point is useful for amplifier application, the Q-point, it is best located at the canter of the DC load line where:


$$I_{CQ} = \frac{1}{2} I_{C(SAT)} \text{ and } V_{CEQ} = \frac{1}{2} V_{CC}$$



# Exercise

Referring to the output characteristic shown, identify the operation region if :

- |                                   |                        |                          |                               |
|-----------------------------------|------------------------|--------------------------|-------------------------------|
| (a) $I_C = 3\text{mA}$            | $V_{CE} = 15\text{V}$  | (b) $I_C = 2.5\text{mA}$ | $I_B = 35\text{ }\mu\text{A}$ |
| (c) $I_B = 10\text{ }\mu\text{A}$ | $V_{CE} = 8\text{V}$   | (d) $I_B = 0$            | $V_{CE} = 8\text{V}$          |
| (d) $I_B = 20\text{ }\mu\text{A}$ | $V_{CE} = 0.2\text{V}$ |                          |                               |

 




# Main Types of BJT Biasing Circuit

Fixed Base Bias Circuit

Fixed Base Bias with emitter resistor  
(Emitter stabilized bias circuit)




Voltage-Divider Bias Circuit
 
# BJT Circuit Analysis: Fixed Bias Circuit





- ❑ This is common emitter (CE) configuration
- ❑ Solve the circuit using HVK
- ❑ 1<sup>st</sup> step: Locate capacitors and replace them with an open circuit
- ❑ 2<sup>nd</sup> step: Locate 2 main loops which;
  - BE loop
  - CE loop
  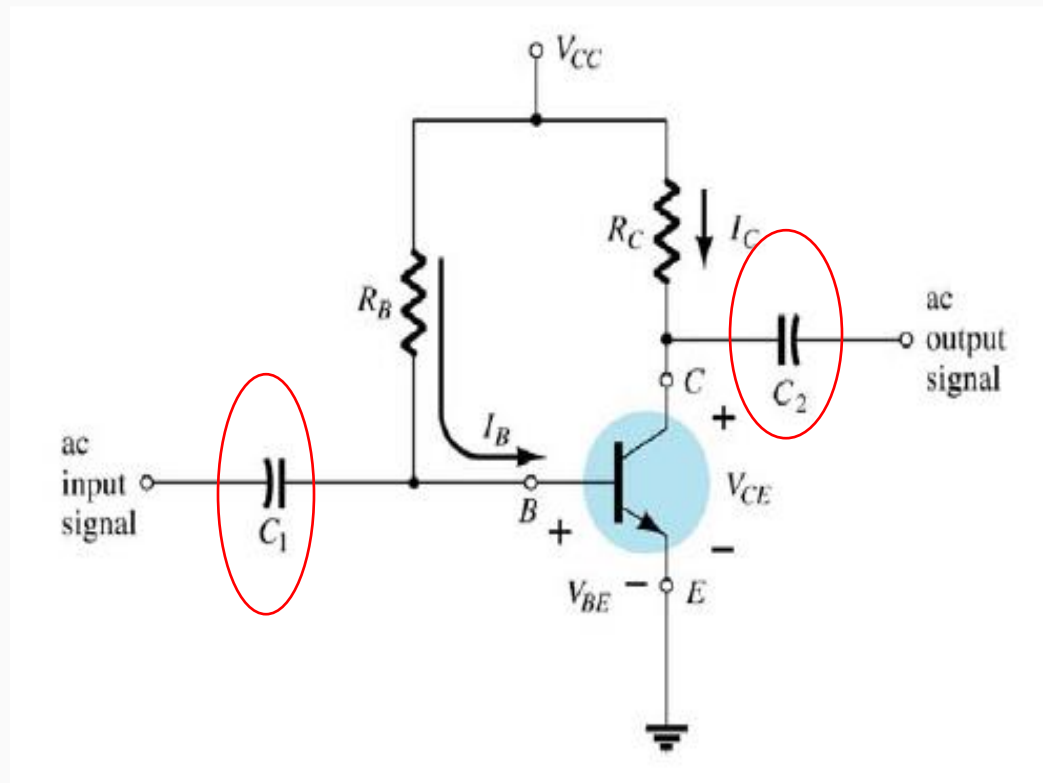
# 1<sup>st</sup> step: Locate capacitors and replace them with an open circuit




# 2<sup>nd</sup> step: Locate 2 main loops


## Fixed Base Bias Circuit

  

**BE Loop**

 


**CE Loop**

 

# BE Loop Analysis

## Fixed Base Bias Circuit

 


□ From HVK;

$$V_{CC} - I_B R_B - V_{BE} = 0 \quad \text{(A)}$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

# CE Loop Analysis

 

- From HVK;  $V_{CC} - I_C R_C - V_{CE} = 0$   
 $\therefore V_{CE} = V_{CC} - I_C R_C$


- As we known;

- Substituting (A) with (B)

$$I_C = \beta I_B \quad \text{(B)}$$

$$I_C = \beta_{DC} \left( \frac{V_{CC} - V_{BE}}{R_B} \right)$$
 
# BJT Circuit Analysis: Fixed Bias Circuit



- Taking the Kirchhoff voltage law (KVL) around the B – E loop yield the following equation:

$$V_{CC} - I_B R_B - V_{BE} = 0$$

- Solving for  $I_B$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

- The collector current  $I_C$  is then given by

$$I_C = \beta I_B = \beta \left( \frac{V_{CC} - V_{BE}}{R_B} \right)$$

- The voltage at the base, collector and emitter can be calculated using

$$V_C = V_{CC} - I_C R_C$$

$$V_B = V_{CC} - I_B R_B$$

- $I_C$  is directly dependent on  $\beta$ . This is unfavourable since  $\beta$  varies with temperature and  $I_C$ .


When  $I_C$  is changing, it cause  $V_{CE}$  to change. This will change the Q – point of the transistor

and make the fixed base biasing circuit very unstable.


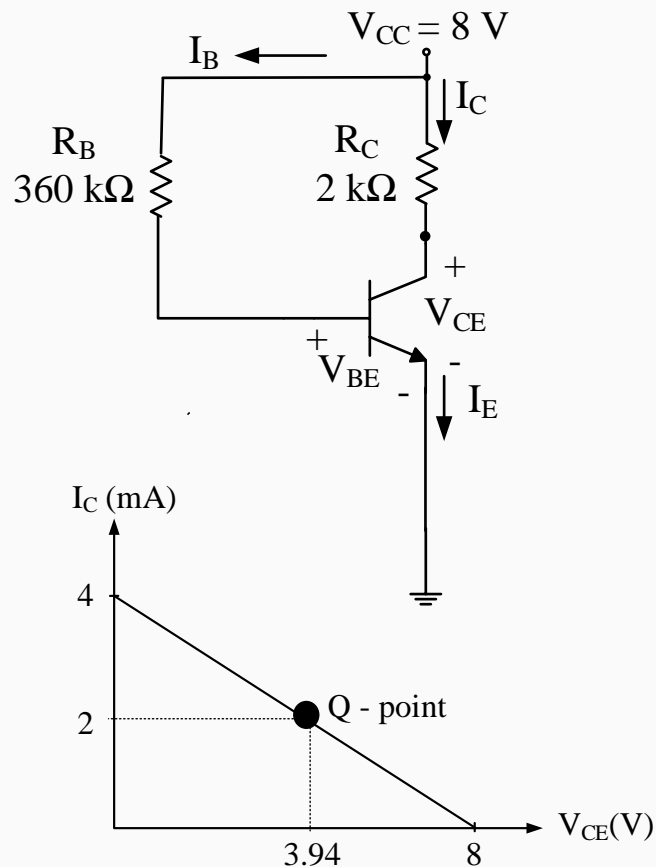
# Example : Fixed Biasing Circuit

Draw the DC load line and find  $I_{BQ}$ ,  $I_{CQ}$ ,  $V_{CEQ}$ ,  $V_{CQ}$ ,  $V_{EQ}$  and  $V_{BQ}$ .  
 Comment on the location of the Q – point.



Using C - E Loop:

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{8 - 0.7}{360\text{k}} = \underline{20.28\text{ }\mu\text{A}}$$

$$I_C = I_{CQ} = \beta I_B = (100) 20.28\mu = \underline{2.03\text{ mA}}$$

Using C - E Loop:

$$V_{CC} - I_C R_C - V_{CE} = 0 \dots\dots\dots (A)$$

$$V_{CE} = V_{CEQ} = V_{CC} - I_{CQ} R_C = 8 - (2.03\text{ mA} \times 2\text{ k}) = 3.94\text{ V}$$


$$\text{when } I_C = 0, V_{CE} = V_{CE(\text{CUT-OFF})} = V_{CC} = 8\text{ V}$$

$$\text{when } V_{CE} = 0, I_C = I_{C(\text{SAT})} = \frac{V_{CC}}{R_C + R_E} = \frac{8}{2\text{k}} = 4\text{ mA}$$

**\*\* The Q – point is in the active region. Therefore this biasing circuit is suitable to be used in amplifier.**
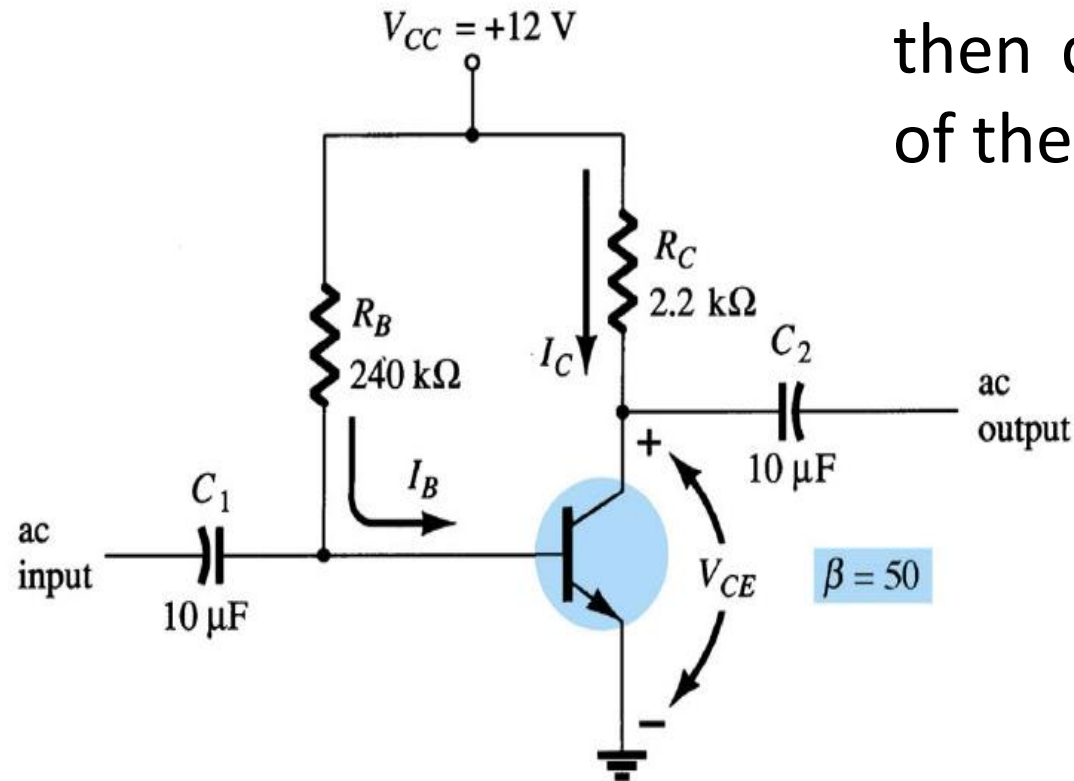
# Example : Fixed Bias Circuit

Find  $I_C$ ,  $I_B$ ,  $V_{CE}$ ,  $V_B$ ,  $V_C$ ,  $V_{BC}$ ? (Silicon transistor) Construct the DC load line then determine the operation region of the Q – point.



Answers;

$$I_C = 2.35\text{ mA}$$

$$I_B = 47.08\text{ }\mu\text{A}$$

$$V_{CE} = 6.83\text{ V}$$

$$V_B = 0.7\text{ V}$$

$$V_C = 6.83\text{ V}$$

$$V_{BC} = -6.13\text{ V}$$

step 1 : open all capacitors and redraw the circuit.

step 2 :

B - E Loop KVL

$$12 - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{12 - V_{BE}}{R_B} = \frac{12 - 0.7}{240k} = \underline{47.1 \mu A} \quad \checkmark$$

using relation  $I_E = (1 + \beta) I_B$  and  $I_E \approx I_C$


$$I_E \approx I_C = (1 + 50) \times 47.1 \mu = \underline{2.40 \text{ mA}} \quad \checkmark$$


step 3

C - E Loop KVL

$$12 - I_C R_C - V_{CE} = 0$$
 
$$V_{CE} = 12 - I_C R_C = 12 - (2.40 \text{ mA} \times 2.2k) = \underline{6.72V} \quad \checkmark$$



 

From the circuit,  $V_E = 0V$ . ✓

it is known that  $V_{BE} = 0.7V$

$$V_{BE} = V_B - V_E$$

$$\therefore V_B = V_{BE} = \underline{0.7V}$$
 ✓

at the collector (C) terminal :

$$V_{CE} = V_C - V_E \quad \text{and} \quad V_E = 0V$$

$$\therefore V_C = V_{CE} = \underline{6.72V}$$

at the base (B) terminal :


$$V_{BC} = V_B - V_C$$

$$V_{BC} = V_B - V_C = 0.7 - 6.72 = \underline{-6.02V}$$
 ✓



 
## Exercise : Fixed Bias Circuit

For the biasing circuit shown, determine the Q – point ( $I_{CQ}$ ,  $V_{CEQ}$ ) and confirm its operation region. Construct the DC load line and evaluate the location of the Q – point. Given  $\beta = 100$ . Redo if  $\beta$  is changed to 129.


 
# Load Line Analysis – Fixed Bias Circuit

- We investigate how the actual Q-point is determined.
- Referring to the figure below (output loop), a straight line can be drawn at the output characteristics curve. This line is called the load line.
- This line connects each separate Q-point.
- At any point along the load line, values of  $I_B$ ,  $I_C$  and  $V_{CE}$  can be picked from the graph.
- The process to plot the load line are as follows:



# Load Line Analysis – Fixed Bias Circuit

- Step 1:

Apply KVL at output loop,  $V_{CE} = V_{CC} - I_C R_C$  (1)

Choose  $I_C = 0$  mA. Substitute into (1), we get

$$V_{CE} = V_{CC} \text{ (2)} \rightarrow \text{intersects the x-axis}$$


- Step 2:

Choose  $V_{CE} = 0$  V and substitute into (1), we get


$$I_C = V_{CC} / R_C \text{ (3)} \rightarrow \text{intersects the y-axis}$$

- Step 3:

 Joining these two points defined by step (2) & (3), we get a straight line that can be drawn as in the next figure.



 
# Load Line Analysis – Fixed Bias Circuit




 
# Example

Given the load line in the figure below, define the Q-point & determine the required values of  $V_{CC}$ ,  $R_C$  and  $R_B$  for a fixed bias configuration. (Given  $I_{BQ}$  at  $17 \mu A$ )



$$V_{CC} = 40 \text{ V}$$

$$I_C = \frac{V_{CC}}{R_C}$$

$$R_C = \underline{\underline{2.67 \text{ k}\Omega}}$$

$$\text{at Q - point; } I_B = 17 \mu A$$


$$R_B = \underline{\underline{2311 \text{ k}\Omega}}$$

# Disadvantages of Fixed Biasing

## Fixed Base Bias Circuit


- ❑ Unstable – because it is too dependent on  $\beta$  and produce change of Q-point
- ❑ For improved bias stability , add emitter resistor to dc bias.
 
# Fixed Bias with emitter resistor (Emitter Stabilized Bias)




- An emitter resistor,  $R_E$  is added to improve stability
- Solve the circuit using HVK
- 1<sup>st</sup> step: Locate capacitors and replace them with an open circuit
- 2<sup>nd</sup> step: Locate 2 main loops which;
  - BE loop
  - CE loop
 
# 1<sup>st</sup> step: Locate capacitors and replace them with an open circuit




## 2<sup>nd</sup> step: Locate 2 main loops

Fixed Base Bias with Emitter Resistor

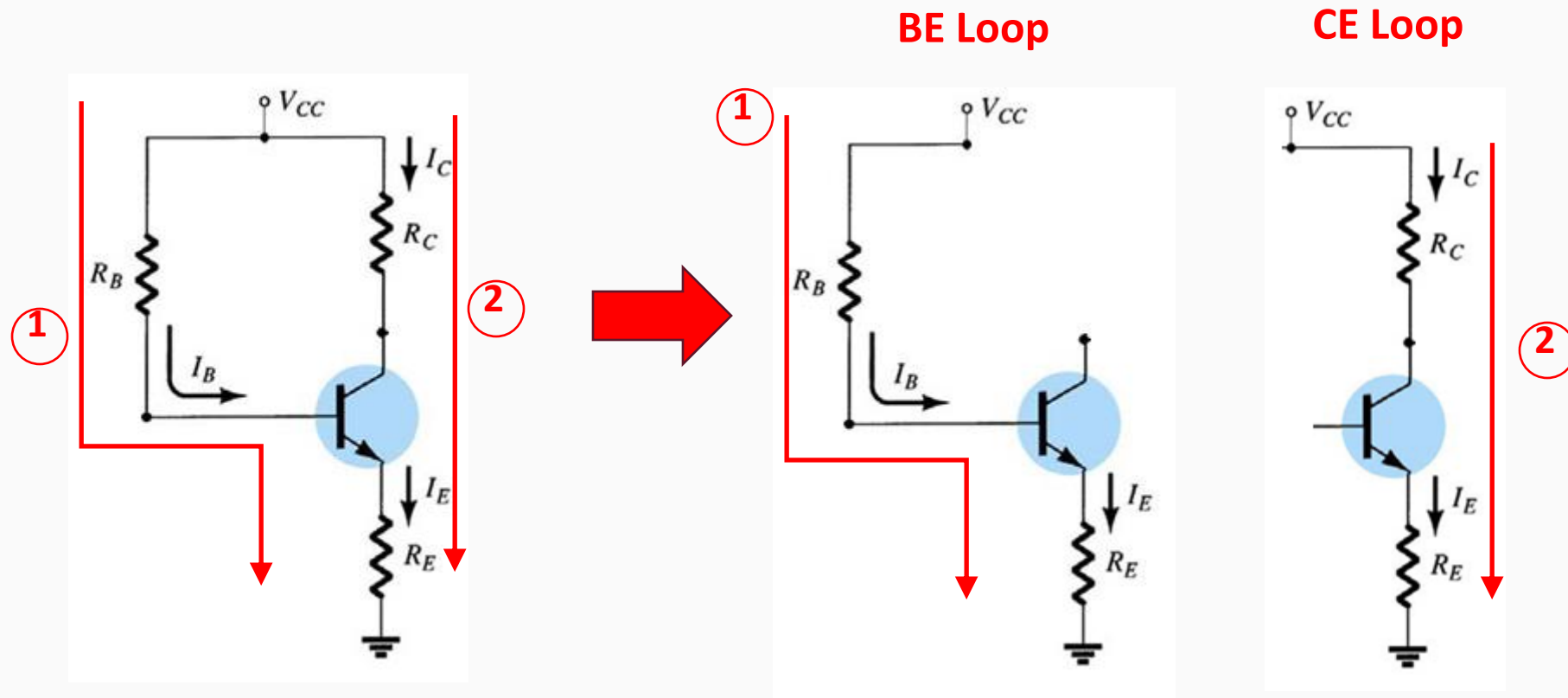

# BE Loop Analysis

Fixed Base Bias with Emitter Resistor

 

■ From HVK;

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

Recall;  $I_E = (\beta + 1)I_B$


Substitute for  $I_E$

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1)I_B R_E = 0$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$

# CE Loop Analysis

Fixed Base Bias with Emitter Resistor

 

■ From HVK;

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

■ Assume;


$$I_E \approx I_C$$

■ Therefore;

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$



# Example Emitter Stabilized Bias

 

■ Find  $I_{CQ}$ ,  $I_{BQ}$ ,  $V_{CEQ}$ ,  $V_{BQ}$ ,  $V_{CQ}$ ,  $V_{EQ}$  &  $V_{BCQ}$ ? (Silicon transistor);

■ Answers;

$$I_{CQ} = 2.01 \text{ mA}$$

$$I_{BQ} = 40.1 \text{ } \mu\text{A}$$

$$V_{CEQ} = 13.97\text{V}$$

$$V_{BQ} = 2.71\text{V}$$

$$V_{EQ} = 2.01\text{V}$$

$$V_{CQ} = 15.98\text{V}$$

$$V_{BCQ} = -13.27\text{V}$$



step 1 : open all capacitors and redraw the circuit.

step 2 :

B - E Loop KVL

$$20 - I_B R_B - V_{BE} - I_E R_E = 0$$

using relation  $I_E = (1 + \beta) I_B$

$$20 - I_B R_B - V_{BE} - R_E (1 + \beta) I_B = 0$$

$$I_B = \frac{20 - V_{BE}}{R_B + R_E (1 + \beta)} = \frac{20 - 0.7}{430k + 1k(1 + 50)} = \underline{40.1 \mu A}$$

using relation  $I_E = (1 + \beta) I_B$  and  $I_E \approx I_C$


$$I_E \approx I_C = (1 + 50) \times 40.1 \mu = \underline{2.05 \text{ mA}}$$

step 3

C - E Loop KVL

$$20 - I_C R_C - I_E R_E - V_{CE} = 0$$
 
$$\begin{aligned} V_{CE} &= 20 - I_C R_C - I_E R_E \\ &= 20 - (2.05 \text{ mA} \times 2k) - (2.05 \text{ mA} \times 1k) = \underline{13.85V} \end{aligned}$$





it is known that  $V_{BE} = 0.7V$

and  $V_{BE} = V_B - V_E$  and  $V_E = I_E R_E$

$$\therefore V_E = I_E R_E = 2.05\text{m} \times 1\text{k} = \underline{2.05\text{ V}}$$

$$\therefore V_B = V_{BE} + V_E = 0.7 + 2.05 = \underline{2.75\text{ V}}$$

from  $V_{CE} = V_C - V_E$

$$\therefore V_C = V_{CE} + V_E = 13.85 + 2.05 = \underline{15.9\text{ V}}$$

$$V_{BC} = V_B - V_C = 2.75 - 15.9 = \underline{-13.15V}$$

this BJT is biased in FORWARD ACTIVE


# Load Line Analysis – Emitter (Stabilized Bias) Circuit

- For  $V_{CE} = 0$ , the transistor will be in saturation region
- Taking the transistor's saturation equation:  $I_{C_{sat}} = \frac{V_{CC}}{R_C + R_E}$

- For  $I_C = 0$ :  $I_C \approx I_E$   
$$I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E} = 0$$
  
$$\therefore V_{CE} = V_{CC}$$


# Load Line Analysis – Emitter (Stabilized Bias) Circuit

So, the load-line becomes:

 
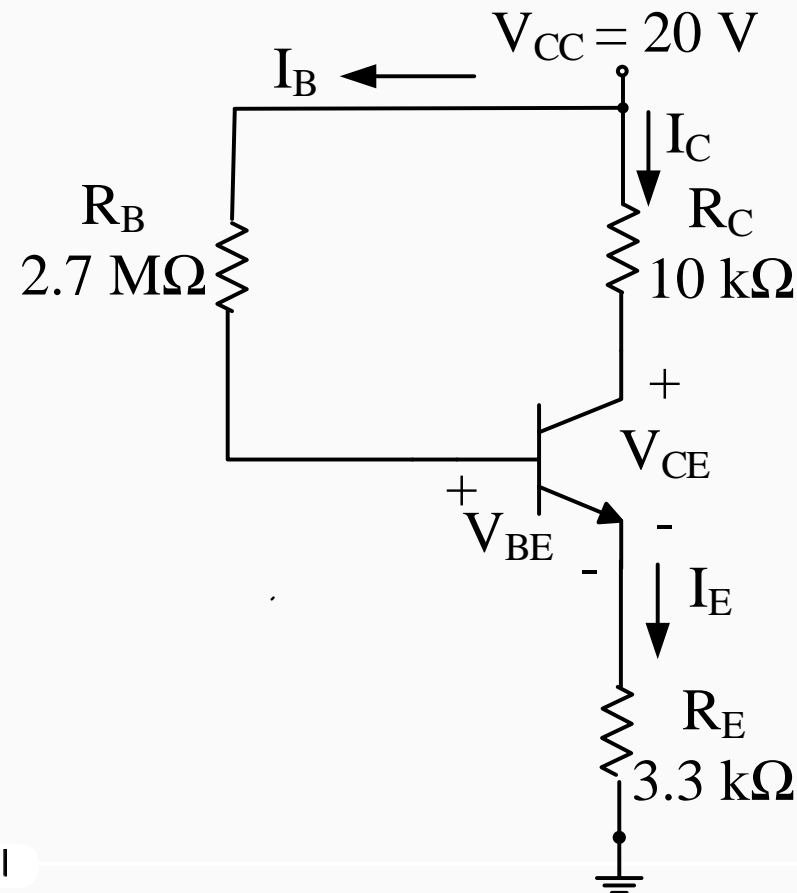
## **Exercise : Emitter Stabilized Bias**

Find  $I_{CQ}$ ,  $I_{BQ}$ ,  $V_{CEQ}$ ,  $V_{BQ}$ ,  $V_{CQ}$ ,  $V_{EQ}$  &  $V_{BCQ}$ ? (Silicon transistor). Construct the DC load line and determine the transistor operation region



# Exercise Test 2 2013/2014/2

A BJT amplifier circuit in Figure Q2(a) has the following specifications:  $I_{BQ} = 30\mu\text{A}$  and  $V_{BE} = 0.7\text{V}$ .

(i) Determine Q-point ( $I_{CQ}$ ,  $V_{CEQ}$ ) of the circuit using the output characteristic graph in Figure Q2(b)



**[Ans:  $I_{CQ} = 4.2\text{mA}$  :  $V_{CEQ} = 11.5\text{V}$ ]**

(ii) Calculate  $\beta$  at the Q-point **[Ans:  $\beta=140$ ]**


(iii) Calculate  $R_B$  **[Ans:  $692\text{k}\Omega$ ]**

(iv) What is the effect on the Q-point of the circuit, when  $R_B$  is decreased?

 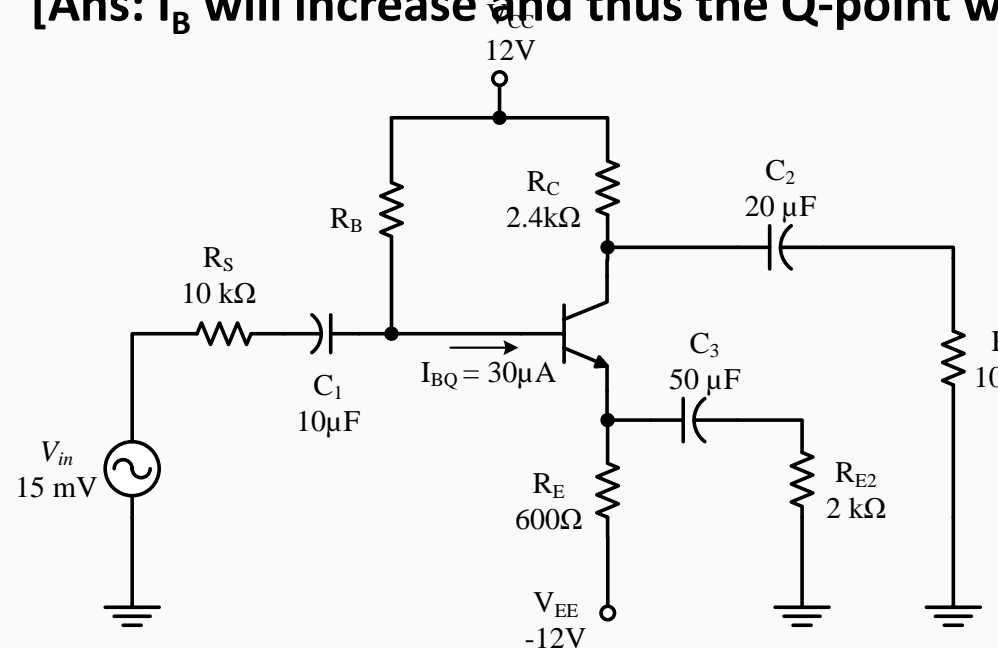**[Ans:  $I_B$  will increase and thus the Q-point will move upwards]**






 

# Exercise


Determine  $I_{BQ}$ ,  $I_{CQ}$ ,  $V_{CEQ}$ ,  $V_B$ ,  $V_C$ ,  $V_E$ . Given  $\beta = hFE = 100$  and  $V_{BE} = 0.7V$ . Sketch the DC load line of the circuit.

 **[Ans:  $I_{BQ} = 29.18\mu A$ ,  $I_{CQ} = 2.92\text{ mA}$ ,  $V_{CEQ} = 8.61V$ ,  $V_B = 5.12V$ ,  $V_C = 12.99V$ ,  $V_E = 4.38V$ ]**





# Voltage Divider Bias Circuit

 

- ☐ Provides good Q-point stability with a single polarity supply voltage
- ☐ Solve the circuit using HVK
- ☐ 1<sup>st</sup> step: Locate capacitors and replace them with an open circuit
- ☐ 2<sup>nd</sup> step: Simplified circuit using Thevenin Theorem
- ☐ 3<sup>rd</sup> step: Locate 2 main loops which;
  - BE loop
  - CE loop

# Voltage Divider Bias Approximation Analysis




For approximation analysis we can assume

$$V_{TH} = V_B$$

but the following condition must satisfy:


$$\beta R_E \geq 10R_2$$
   
# 1<sup>st</sup> step: Locate capacitors and replace them with an open circuit





# 2<sup>nd</sup> step: : Simplified circuit using **Thevenin Theorem**

## Voltage Divider Bias Circuit

 

Thevenin Theorem;

  



Simplified Circuit

From Thevenin Theorem;


$$R_{TH} = R_1 // R_2 = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$

  
# 3<sup>rd</sup> step: Locate 2 main loops




**BE Loop**

 

**CE Loop**

 

# BE Loop Analysis

 

■ From HVK;

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

Recall;  $I_E = (\beta + 1)I_B$


Substitute for  $I_E$

$$V_{TH} - I_B R_{TH} - V_{BE} - (\beta + 1)I_B R_E = 0$$

$$\therefore I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1)R_E}$$

# CE Loop Analysis

## Voltage Divider Bias Circuit

 

■ From HVK;

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

■ Assume;


$$I_E \approx I_C$$

■ Therefore;

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$
 
# Example Voltage Divider Bias Circuit: Single Supply

- Find  $R_{TH}$ ,  $V_{TH}$ ,  $I_{CQ}$ ,  $I_{BQ}$ ,  $V_{CEQ}$ ,  $V_{BQ}$ ,  $V_{CQ}$ ,  $V_{EQ}$  &  $V_{BCQ}$ ? (Silicon transistor).  
Construct the DC load line



## ■ Answers;

$$R_{TH} = 3.55 \text{ k}\Omega$$

$$V_{TH} = 2\text{V}$$

$$I_{CQ} = 0.85 \text{ mA}$$

$$I_{BQ} = 6.05 \text{ }\mu\text{A}$$

$$V_{CEQ} = 12.9\text{V}$$

$$V_{BQ} = 1.978\text{V}$$

$$V_{EQ} = 1.275\text{V}$$

$$V_{CQ} = 13.5\text{V}$$

$$V_{BC} = -12.81\text{V}$$



step 1 : open all capacitors and redraw the circuit.

step 2 : calculate  $V_{th}$  and  $R_{th}$

$$V_{th} = \frac{3.9k}{3.9k + 39k} \times 22 = 2V$$

$$R_{th} = \frac{3.9k \times 39k}{3.9k + 39k} = 3.55 k\Omega$$

then redraw the circuit.

step 3:

B - E Loop KVL

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

$$2 - I_B (3.55 k) - 0.7 - I_E (1.5k) = 0$$



using relation  $I_E = (1 + \beta) I_B$

$$2 - I_B (3.55 k) - 0.7 - I_B (1 + \beta) (1.5k) = 0$$

$$I_B = \frac{2 - 0.7}{3.55k + 1.5k(1 + 140)} = \underline{6.05 \mu A}$$

using relation  $I_E = (1 + \beta) I_B$  and  $I_E \approx I_C$
  
$$I_E \approx I_C = (1 + 140) \times 6.05 \mu = \underline{0.85 mA}$$



## C - E Loop KVL

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\text{assume } I_C \approx I_E$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 22 - 10k(0.85m) - 1.5k(0.85m)$$

$$V_{CE} = \underline{12.19V}$$

it is known that  $V_{BE} = 0.7V$

and  $V_{BE} = V_B - V_E$  and  $V_E = I_E R_E$

$$\therefore V_E = I_E R_E = 0.85m \times 1.5k = \underline{1.28 V}$$

$$\therefore V_B = V_{BE} + V_E = 0.7 + 1.28 = \underline{1.98 V} \approx V_{TH}$$

from  $V_{CE} = V_C - V_E$

$$\therefore V_C = V_{CE} + V_E = 12.19 + 1.28 = \underline{13.51 V}$$


$$V_{BC} = V_B - V_C = 0.7 - 13.51 = \underline{-12.81V}$$

this BJT is biased in FORWARD ACTIVE

# Example Voltage Divider Bias with 2 supply

Determine  $I_{BQ}$ ,  $I_{CQ}$ ,  $V_{CEQ}$ ,  $V_{BQ}$ ,  $V_{CQ}$ ,  $V_{EQ}$ . Given  $\beta = h_{FE} = 120$  and  $V_{BE} = 0.7V$ .

 **[Ans:  $I_{BQ} = 35.35\mu A$ ,  $I_{CQ} = 4.24\text{ mA}$ ,  $V_{CEQ} = 20.92\text{ V}$ ,  $V_{BQ} = -11.6\text{ V}$ ,  $V_{CQ} = 8.55V$ ,  $V_{EQ} = -12.37V$ ]**



step 1: open all capacitors and draw the DC equivalent circuit

step 2: calculate  $V_{th}$  and  $R_{th}$

$$V_{th} = \frac{R_2}{R_1 + R_2} \times (+V_{CC}) + \frac{R_1}{R_1 + R_2} \times (-V_{CC})$$

$$V_{th} = \frac{2.2k}{2.2k + 8.2k} \times (+20) + \frac{8.2k}{2.2k + 8.2k} \times (-20) = \underline{-11.54V}$$

$$R_{th} = \frac{2.2k \times 8.2k}{2.2k + 8.2k} = 1.73k\Omega$$

step 3:

B - E Loop KVL

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E + V_{EE} = 0$$

using relation  $I_E = (1 + \beta) I_B$

$$V_{TH} - I_B R_{TH} - V_{BE} - (1 + \beta) I_B R_E + V_{EE} = 0$$

$$-11.54 - I_B (1.73k) - 0.7 - (1 + 120) I_B (1.8k) + 20 = 0$$

$$I_B = I_{BQ} = \frac{20 - 11.54 - 0.7}{1.73k + 1.8k(1 + 120)} = \underline{35.35 \mu A}$$

using relation  $I_E = (1 + \beta) I_B$  and  $I_E \approx I_C$

$$I_E \approx I_C \approx I_{CQ} = (1 + 120) \times 35.35 \mu = \underline{4.28 mA}$$



### C - E Loop KVL

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E + V_{EE} = 0$$

$$\text{assume } I_C \approx I_E$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E + V_{EE} = 20 - 2.7k(4.28m) - 1.8k(4.28m) + 20$$

$$V_{CE} = \underline{V_{CEQ} = 20.74V}$$

It is known that  $V_{BE} = 0.7V$

and

$$V_{BE} = V_B - V_E \quad \text{and} \quad V_E = I_E R_E - V_{EE}$$

$$\therefore V_E = I_E R_E - V_{EE} = 1.8k(4.28m) - 20 = \underline{-12.3 V}$$

$$\therefore V_B = V_{BE} + V_E = 0.7 - 12.3 = \underline{-11.6V} \approx V_{TH}$$

from

$$V_{CE} = V_C - V_E$$


$$\therefore V_C = V_{CE} + V_E = 20.74 - 12.3 = \underline{8.44 V}$$

# Exercise FINAL SEU 2012 2010/2011/2

Refer to a small signal amplifier circuit in Figure Q3. The transistor's parameter are:

$$\beta_{DC} = \beta_{AC} = 100, V_{BE} = 0.7V, V_T = 26mV$$

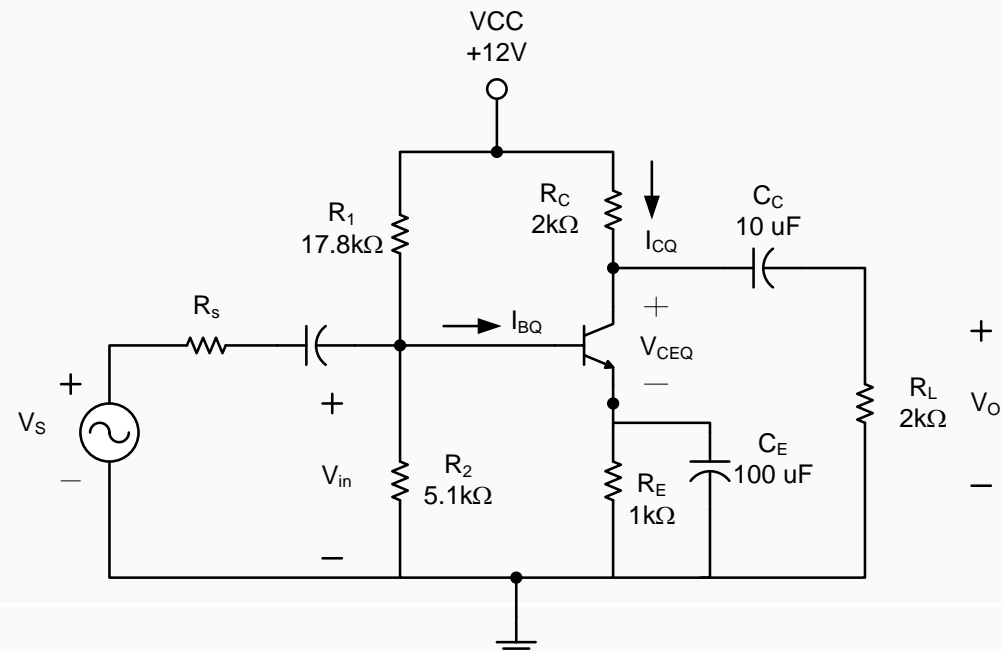- I. Draw the DC equivalent circuit.
- II. Calculate the base and collector current,  $I_{BQ}$  and  $I_{CQ}$ . [Ans:  $I_{BQ}=18.7\mu A$ ,  $I_{CQ}=1.87mA$ ]
- III. Calculate the collector to emitter voltage,  $V_{CEQ}$ . [Ans:  $V_{CE}=6.3V$ ]
- IV. Calculate new Q-point ( $I_{BQ}$  and  $I_{CQ}$ ) if  $R_2$  is halved [Ans:  $I_B=7.7\mu A$ ,  $I_C=0.77mA$ ]



# Load Line Analysis - Voltage Divider Bias

- ❑ For the load-line analysis, the cutoff region still results the same as the fixed bias and emitter bias configuration:

$$V_{CE} = V_{CC} \Big|_{I_C=0}$$



- ❑ And for the saturation region:

$$I_{C_{sat}} = \frac{V_{CC}}{R_C + R_E} \Big|_{V_{CE} = 0}$$

# Exercise Final Exam 2013/2014/2

The dc load line of the circuit and the characteristic is as shown. Based on the figures,

  
- (i) Determine the common emitter current gain,  $\beta$ , and the emitter current,  $I_E$ .  
**[Ans:  $\beta = 75$ ,  $I_E = 5.71\text{mA}$ ]**
- (ii) Determine  $R_B$  and  $R_C$  such that the circuit yields the given Q-point. Given  $V_{BE} = 0.7\text{ V}$ ,  $V_{BB} = 6\text{ V}$ , and  $R_E = 600\ \Omega$ . **[Ans:  $R_B = 25\text{k}\Omega$ ,  $R_C = 400\ \Omega$ ]**




 
# DC Biasing Circuit for PNP BJT


- ❑ All the previous analysis and technique used in NPN BJT can be applied to PNP BJT.
- ❑ This is because the amount of current is the same;  $I_E = I_B + I_C$
- ❑ The major different is the direction of current flowing.
- ❑ PNP BJT current flow from emitter to collector.


 
## Example Voltage Divider PNP

Determine  $I_{BQ}$ ,  $I_{CQ}$ ,  $V_{CEQ}$ ,  $V_B$ ,  $V_C$  and  $V_E$ . Given  $\beta = 120$  and  $V_{EB} = 0.7$ .

[Ans:  $I_{BQ} = 17.4 \mu A$ ,  $I_{CQ} = 2.09 \text{ mA}$ ,  $V_{CEQ} = -10.68$ ,  $V_B = -3V$ ,  $V_C = -12.98V$  and  $V_E = -2.32V$ ]



# Solution

step 1: open all capacitors and draw the DC equivalent circuit.

step 2: calculate  $V_{th}$  and  $R_{th}$

$$V_{th} = \frac{10k}{10k + 47k} \times -18 = -3.16V$$

$$R_{th} = \frac{10k \times 47k}{10k + 47k} = 8.25 k\Omega$$

then redraw the circuit.

step 3:

E - B Loop KVL

$$I_E R_E - V_{EB} - I_B R_{TH} + V_{TH} = 0$$

using relation  $I_E = (1 + \beta) I_B$


$$I_B (1 + \beta) R_E - V_{EB} - I_B R_{TH} + V_{TH} = 0$$

$$I_B (1 + 120)(1.1k) - 0.7 - I_B (8.25 k) + 3.16 = 0$$

$$I_B = I_{BQ} = \frac{3.16 - 0.7}{8.25 k + 1.1k(1 + 120)} = 17.4 \mu A$$

using relation  $I_E = (1 + \beta) I_B$  and  $I_E \approx I_C$
 
$$I_E \approx I_C \approx I_{CQ} = (1 + 120) \times 17.4 \mu = 2.09 mA$$



## E - C Loop KVL

$$-I_E R_E - V_{EC} - I_C R_C + V_{CC} = 0$$

$$\text{assume } I_C \approx I_E$$

$$V_{EC} = I_E R_E - I_C R_C + V_{CC} = -1.1k(2.09m) - 2.4k(2.09m) + 18$$

$$V_{EC} = V_{ECQ} = \underline{10.69V} \quad \therefore V_{CE} = V_{CEQ} = \underline{-10.69V}$$

it is known that  $V_{EB} = 0.7V$

$$\text{and} \quad V_{EB} = V_E - V_B \quad \text{and} \quad V_E = -I_E R_E$$

$$\therefore V_E = -I_E R_E = -2.09m \times 1.1k = \underline{-2.3 V}$$

$$\therefore V_B = V_E - V_{EB} = -2.3 - 0.7 = \underline{-3 V}$$


$$\text{from} \quad V_{EC} = V_E - V_C$$

$$\therefore V_C = V_E - V_{EC} = -2.3 - 10.69 = \underline{-12.99 V}$$
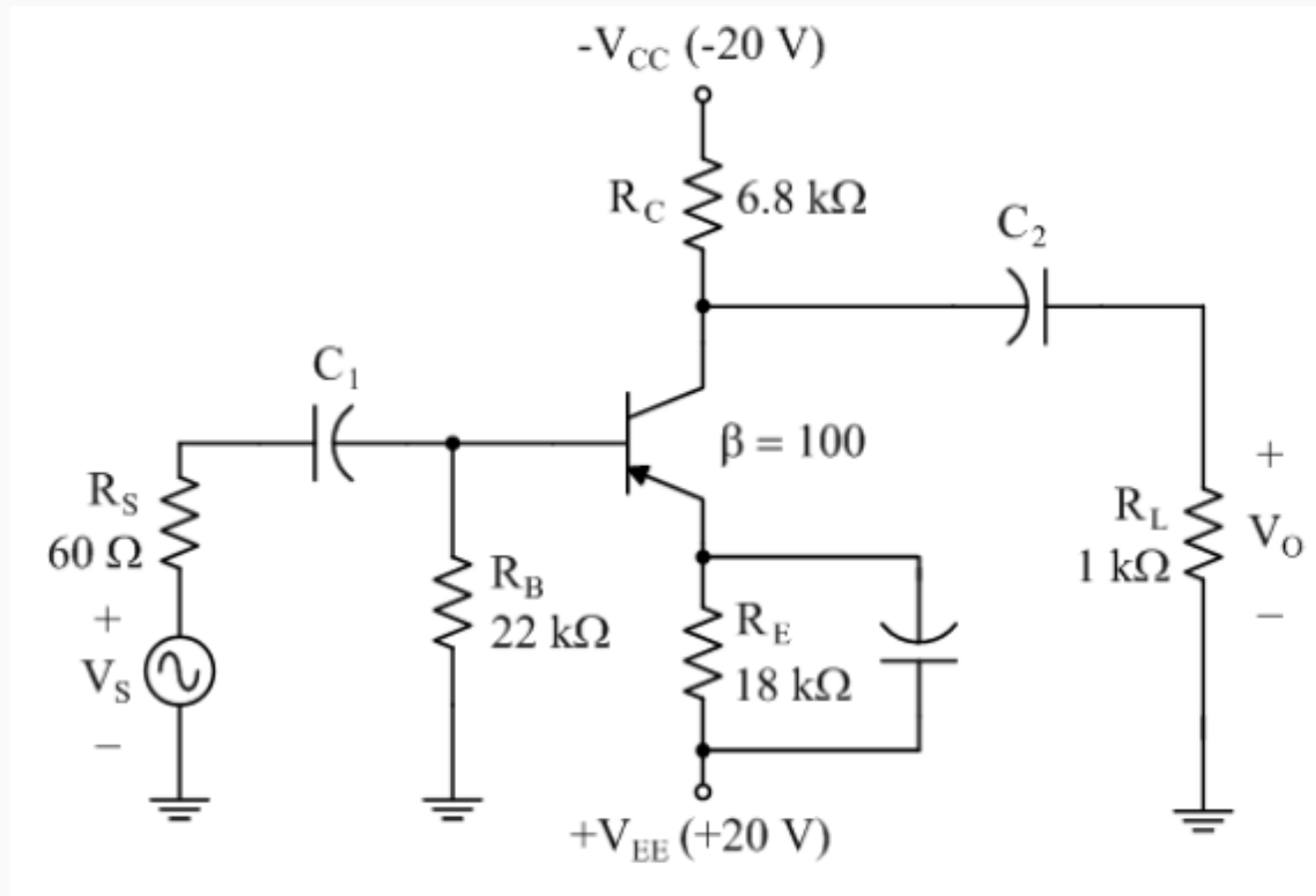
## Example Fixed Bias with 2 supply

Determine  $I_{BQ}$ ,  $I_{CQ}$ ,  $V_{CEQ}$ ,  $V_B$ ,  $V_C$ ,  $V_E$ . Given  $\beta = h_{FE} = 100$  and  $V_{EB} = 0.7V$ .

[Ans:  $I_{BQ} = 10.49\mu A$ ,  $I_{CQ} = 1.05mA$ ,  $V_{CEQ} = -13.96V$ ,  $V_B = 0.2V$ ,  $V_C = -12.86V$  and  $V_E = 0.93V$ ]



# Solution

step 1 : open all capacitors and draw the DC equivalent circuit.

step 2 :

E - B Loop KVL

$$20 - I_E R_E - V_{EB} - I_B R_B = 0$$

using relation  $I_E = (1 + \beta) I_B$

$$20 - (1 + \beta) I_B R_E - V_{EB} - I_B R_B = 0$$

$$I_B = \frac{20 - V_{EB}}{R_B + R_E (1 + \beta)} = \frac{20 - 0.7}{22k + 18k(1 + 100)} = \underline{10.49 \mu A}$$

using relation  $I_E \approx I_C$

$$I_E \approx I_C = (1 + 100) \times 10.49 \mu = \underline{1.06 \text{ mA}}$$

step 3

E - C Loop KVL

$$V_{EE} - I_E R_E - V_{EC} - I_C R_C + V_{CC} = 0$$

$$20 - 18k(1.06) - V_{EC} - 6.8k(1.06) + 20 = 0$$

$$V_{EC} = 20 - 18k(1.06) - 6.8k(1.06) + 20$$

$$V_{EC} = V_{ECQ} = \underline{13.73V}$$

$$\therefore V_{CE} = V_{CEQ} = \underline{-13.73V}$$

We know  $\Rightarrow V_{EB} = V_E - V_B$  and  $V_E = -I_E R_E + V_{EE}$


Therefore  $V_E = -I_E R_E + V_{EE} = (-1.06m)18k + 20 = \underline{0.92V}$

$$\therefore V_B = V_E - V_{EB} = 0.92 - 0.7 = \underline{0.22V}$$

$$\text{and } V_C = V_E - V_{EC} = 0.92 - 13.73 = \underline{-12.81V}$$
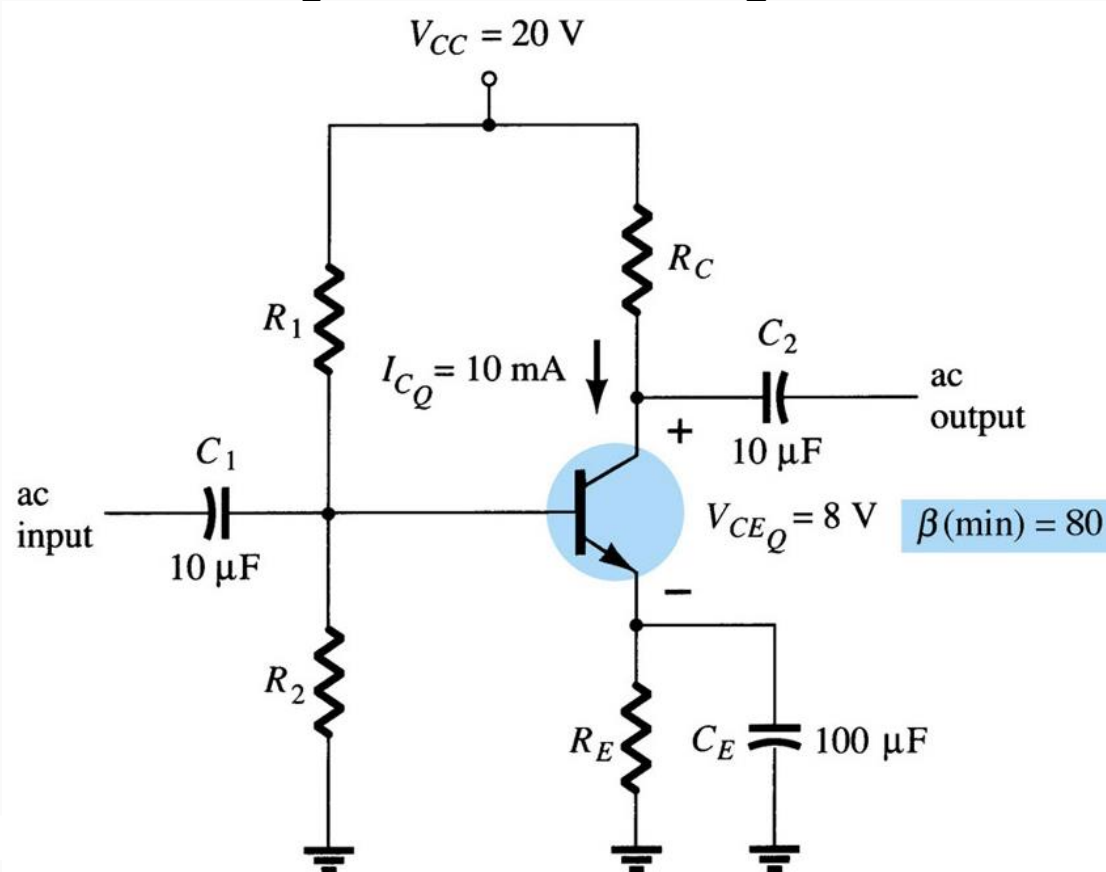
## Exercise : Design

Determine all the resistors  $R_E$ ,  $R_C$ ,  $R_2$  and  $R_1$  values in designing the fixed bias with emitter-stabilized circuit as below. Given  $\beta_{\min} = h_{FE(\min)} = 80$  and  $V_{BE} = 0.7 \text{ V}$ ,  $V_{CEQ} = 8 \text{ V}$  and  $I_{CQ} = 10 \text{ mA}$ . Assume  $V_E = (1/10)V_{CC}$  and  $\beta R_E = 10R_2$ .  
 [Ans:  $R_E = 197.53 \Omega$ ,  $R_C = 1 \text{ k}\Omega$ ,  $R_1 = 10.12 \text{ k}\Omega$ ,  $R_2 = 1.58 \text{ k}\Omega$ ]







## Exercise

Calculate the value for  $R_C$ ,  $R_B$ ,  $V_{CE}$  and  $\beta$  for a fixed bias circuit if  $V_{CC} = 24V$ ,  $I_B = 20\mu A$  dan  $I_C = 3mA$ . Transistor must properly biased to achieve maximum symmetrical output swing for the voltage and current. Given  $V_{BE} = 0.7V$ .



## Example

# Transistor Specification & Data Sheet

Answer the following questions by referring to the partial transistor data sheet for transistor 2N3904.

- a) What is the maximum collector to emitter voltage?
- b) How much continuous collector current can the 2N3904 handle?
- c) How much power can 2N3904 dissipate if the ambient temperature is 25° C?
- d) What is the minimum and maximum  $\beta$ ?

# Data Sheet for BJT

2N3904 / MMBT3904 / PZT3904 — NPN General-Purpose Amplifier

## Absolute Maximum Ratings<sup>(1), (2)</sup>

Stresses exceeding the absolute maximum ratings may damage the device. The device may not function or be operable above the recommended operating conditions and stressing the parts to these levels is not recommended. In addition, extended exposure to stresses above the recommended operating conditions may affect device reliability. The absolute maximum ratings are stress ratings only. Values are at  $T_A = 25^\circ\text{C}$  unless otherwise noted.

Symbol	Parameter	Value	Unit
$V_{CEO}$	Collector-Emitter Voltage	40	V
$V_{CBO}$	Collector-Base Voltage	60	V
$V_{EBO}$	Emitter-Base Voltage	6.0	V
$I_C$	Collector Current - Continuous	200	mA
$T_J, T_{STG}$	Operating and Storage Junction Temperature Range	-55 to 150	$^\circ\text{C}$

### Notes:

1. These ratings are based on a maximum junction temperature of  $150^\circ\text{C}$ .
2. These are steady-state limits. Fairchild Semiconductor should be consulted on applications involving pulsed or low-duty cycle operations.

## Thermal Characteristics

Values are at  $T_A = 25^\circ\text{C}$  unless otherwise noted.

Symbol	Parameter	Maximum			Unit
		2N3904	MMBT3904 <sup>(3)</sup>	PZT3904 <sup>(4)</sup>	
$P_D$	Total Device Dissipation	625	350	1,000	mW
	Derate Above $25^\circ\text{C}$	5.0	2.8	8.0	mW/ $^\circ\text{C}$
$R_{\theta JC}$	Thermal Resistance, Junction to Case	83.3			$^\circ\text{C}/\text{W}$
$R_{\theta JA}$	Thermal Resistance, Junction to Ambient	200	357	125	$^\circ\text{C}/\text{W}$

### Notes:

3. Device is mounted on FR-4 PCB 1.6 inch X 1.6 inch X 0.06 inch.
4. Device is mounted on FR-4 PCB 36 mm X 18 mm X 1.5 mm, mounting pad for the collector lead minimum  $6\text{ cm}^2$ .

# Data Sheet for BJT

## Electrical Characteristics

Values are at  $T_A = 25^\circ\text{C}$  unless otherwise noted.

Symbol	Parameter	Conditions	Min.	Max.	Unit
OFF CHARACTERISTICS					
$V_{(BR)CEO}$	Collector-Emitter Breakdown Voltage	$I_C = 1.0\text{ mA}, I_B = 0$	40		V
$V_{(BR)CBO}$	Collector-Base Breakdown Voltage	$I_C = 10\text{ }\mu\text{A}, I_E = 0$	60		V
$V_{(BR)EBO}$	Emitter-Base Breakdown Voltage	$I_E = 10\text{ }\mu\text{A}, I_C = 0$	6.0		V
$I_{BL}$	Base Cut-Off Current	$V_{CE} = 30\text{ V}, V_{EB} = 3\text{ V}$		50	nA
$I_{CEX}$	Collector Cut-Off Current	$V_{CE} = 30\text{ V}, V_{EB} = 3\text{ V}$		50	nA
ON CHARACTERISTICS <sup>(5)</sup>					
$h_{FE}$	DC Current Gain	$I_C = 0.1\text{ mA}, V_{CE} = 1.0\text{ V}$	40		
		$I_C = 1.0\text{ mA}, V_{CE} = 1.0\text{ V}$	70		
		$I_C = 10\text{ mA}, V_{CE} = 1.0\text{ V}$	100	300	
		$I_C = 50\text{ mA}, V_{CE} = 1.0\text{ V}$	60		
		$I_C = 100\text{ mA}, V_{CE} = 1.0\text{ V}$	30		
$V_{CE(sat)}$	Collector-Emitter Saturation Voltage	$I_C = 10\text{ mA}, I_B = 1.0\text{ mA}$		0.2	V
		$I_C = 50\text{ mA}, I_B = 5.0\text{ mA}$		0.3	
$V_{BE(sat)}$	Base-Emitter Saturation Voltage	$I_C = 10\text{ mA}, I_B = 1.0\text{ mA}$	0.65	0.85	V
		$I_C = 50\text{ mA}, I_B = 5.0\text{ mA}$		0.95	
SMALL SIGNAL CHARACTERISTICS					
$f_T$	Current Gain - Bandwidth Product	$I_C = 10\text{ mA}, V_{CE} = 20\text{ V},$ $f = 100\text{ MHz}$	300		MHz
$C_{obo}$	Output Capacitance	$V_{CB} = 5.0\text{ V}, I_E = 0,$ $f = 100\text{ kHz}$		4.0	pF
$C_{ibo}$	Input Capacitance	$V_{EB} = 0.5\text{ V}, I_C = 0,$ $f = 100\text{ kHz}$		8.0	pF
NF	Noise Figure	$I_C = 100\text{ }\mu\text{A}, V_{CE} = 5.0\text{ V},$ $R_S = 1.0\text{ k}\Omega,$ $f = 10\text{ Hz to }15.7\text{ kHz}$		5.0	dB
SWITCHING CHARACTERISTICS					
$t_d$	Delay Time	$V_{CC} = 3.0\text{ V}, V_{BE} = 0.5\text{ V}$		35	ns
$t_r$	Rise Time	$I_C = 10\text{ mA}, I_{B1} = 1.0\text{ mA}$		35	ns
$t_s$	Storage Time	$V_{CC} = 3.0\text{ V}, I_C = 10\text{ mA},$		200	ns
$t_f$	Fall Time	$I_{B1} = I_{B2} = 1.0\text{ mA}$		50	ns

### Note:

5. Pulse test: pulse width  $\leq 300\text{ }\mu\text{s}$ , duty cycle  $\leq 2.0\%$ .

2N3904 / MMBT3904 / PZT3904 — NPN General-Purpose Amplifier