

SEEE 1223

DIGITAL ELECTRONICS

CHAPTER 7: LATCHES AND FLIP FLOPS

DR. MOHD SAIFUL AZIMI BIN MAHMUD

P19a-04-03-30

School of Electrical Engineering

Faculty of Engineering


Universiti Teknologi Malaysia

019-7112948



azimi@utm.my



COMBINATIONAL VS SEQUENTIAL LOGIC

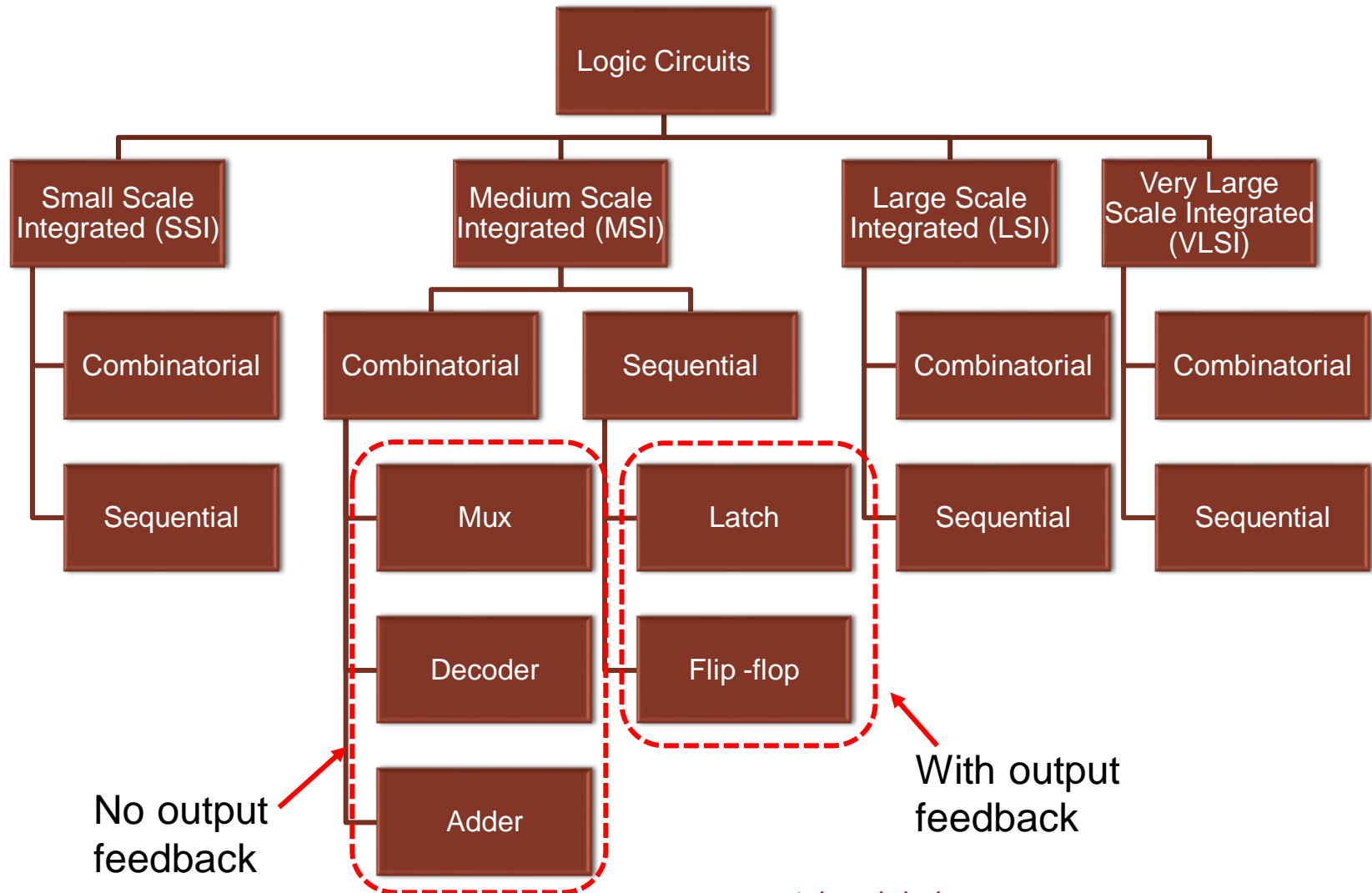

COMBINATIONAL VS SEQUENTIAL LOGIC

  


LATCHES

LATCHES

INTRODUCTION



- **Latch** is a type of **temporary storage device** that has **two stable states (bistable)**.
- It is a basic form of memory, i.e store value of **0** and **1** in a latch.
- Latches are similar to flip-flops because they are **bistable** devices that can reside in either of two states using a feedback arrangement. In which the outputs are connected back to the opposite inputs.
- Latches however, are considered unstable in modern circuits and rarely used.
- Flip-flops are the dominant sequential circuit element and are present in almost all digital system.

 

LATCHES

SR LATCH

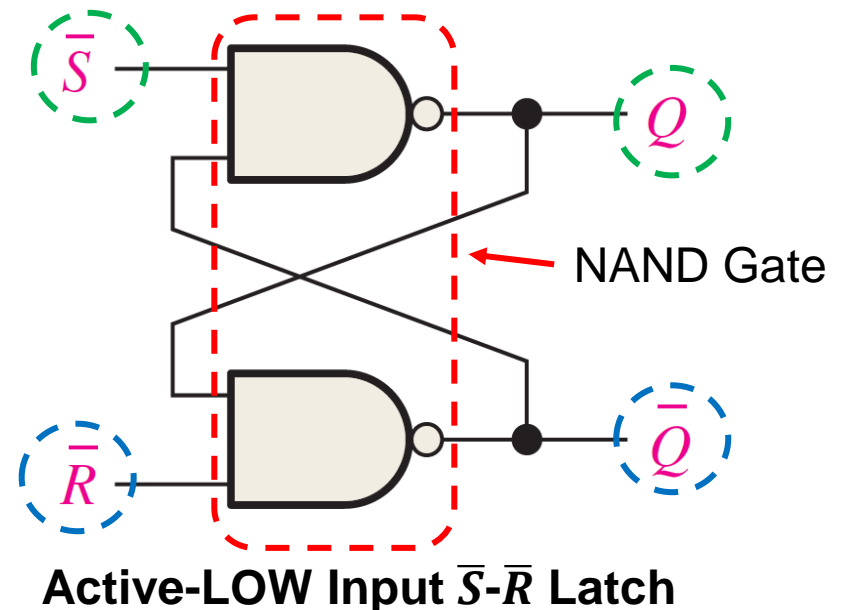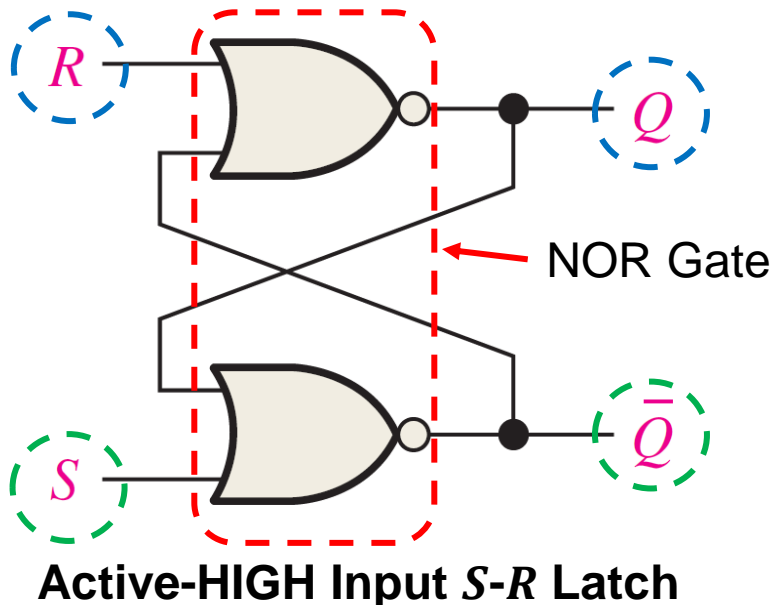
- The **SR Latch (Set-Reset Latch)** is the most basic type, which can be constructed using NOR or NAND gates.
- An **Active-HIGH input SR Latch** is formed with **two cross-couple NOR gate**.
- An **Active-LOW input $\bar{S}\bar{R}$ Latch** is formed with **two cross-couple NAND gate**.



LATCHES

ACTIVE-HIGH SR LATCH

 - The Active-High SR Latch has **two inputs S** and **R**, which will let us control the outputs **Q** and **\bar{Q}** .



- Here **Q** and **\bar{Q}** **feed back** into the circuit. They are not the only outputs, they also are the inputs.
- To figure out how **Q** and **\bar{Q}** change, we have to look at not only the inputs **S** and **R**, but also the current values of **Q** and **\bar{Q}** are:

$$Q_{next} = \overline{(R + \overline{Q_{current}})}$$

$$\overline{Q_{next}} = \overline{(S + Q_{current})}$$

LATCHES


ACTIVE-HIGH SR LATCH: STORING A VALUE: $SR = 00$

- What if $S = 0$ and $R = 0$?
- The equations on the right reduce to:

$$Q_{next} = \overline{(R + \overline{Q_{current}})}$$
$$= \overline{(0 + \overline{Q_{current}})} = Q_{current}$$

$$\overline{Q_{next}} = \overline{(S + Q_{current})}$$
$$= \overline{(0 + Q_{current})} = \overline{Q_{current}}$$

 - So when $SR = 00$, then $Q_{next} = Q_{current}$. Whatever value of $Q_{current}$ has, Q_{next} keeps.
- This is exactly what how the values are **stored** inside the latch.



LATCHES

ACTIVE-HIGH SR LATCH: SETTING THE LATCH: $SR = 10$

- What if $S = 1$ and $R = 0$?
- Since $S = 1$, $\overline{Q_{next}}$ is 0, regardless of $Q_{current}$:

$$\overline{Q_{next}} = \overline{(S + Q_{current})} = \overline{(1 + Q_{current})} = \overline{1} = 0$$

- Then, this new value of \overline{Q} goes into the top NOR gate, along with $R = 0$.

$$Q_{next} = \overline{(R + \overline{Q_{current}})} = \overline{(0 + 0)} = 1$$

- So when $SR = 10$, then $\overline{Q_{next}} = 0$ and $Q_{next} = 1$.
- This is how you **set** the latch to 1. The S input stands for **“SET”**.
- Notice that it can take up to **two steps (two gate delays)** from the time S becomes 1 to the time Q_{next} becomes 1.
- But once Q_{next} becomes 1, the outputs will stop changing. This is a **stable state**.

LATCHES

ACTIVE-HIGH SR LATCH: RESETTING THE LATCH: **SR = 01**

- What if **S = 0** and **R = 1**?
- Since $R = 1$, Q_{next} is 0, regardless of $Q_{current}$:

$$Q_{next} = \overline{(1 + Q_{current})} = \overline{1} = 0$$

- Then, this new value of Q goes into the bottom NOR gate, along with $S = 0$.

$$\overline{Q_{next}} = \overline{(S + Q_{current})} = \overline{(0 + 0)} = 1$$

- So when $SR = 01$, then $Q_{next} = 0$ and $\overline{Q_{next}} = 1$.
- This is how you **reset**, or **clear**, the latch to 0. The R input stands for “**reset**”.
- Again, it can take two gate delays before a change in R propagates to the output $\overline{Q_{next}}$.

LATCHES

ACTIVE-HIGH SR LATCH: WHAT ABOUT: $SR = 11$

- Both Q_{next} and $\overline{Q_{next}}$ will become **0**.
- This contradicts the assumption that Q and \bar{Q} are always complements.
- Another problem is what happens if we then make $S = 0$ and $R = 0$ together.

$$Q_{next} = \overline{(0 + 0)} = 1$$

$$\overline{Q_{next}} = \overline{(0 + 0)} = 1$$

- But these new values go back into the NOR gates, and in the next step we get:


$$Q_{next} = \overline{(0 + 1)} = 0$$

$$\overline{Q_{next}} = \overline{(0 + 1)} = 0$$

- The circuit enters an **infinite loop**, where Q and \bar{Q} cycle between 0 and 1 forever.
- This is actually the worst case, but the moral is don't ever set $SR = 11!$

LATCHES


ACTIVE-HIGH SR LATCH

 

Active-High SR Latch Logic Circuit

Active-High SR Latch Truth Table

Inputs		Outputs		Action
S	R	$Q(next)$	$\overline{Q}(next)$	
0	0	Q	\overline{Q}	NO CHANGE
0	1	0	1	RESET
1	0	1	0	SET
1	1	0	0	FORBIDDEN

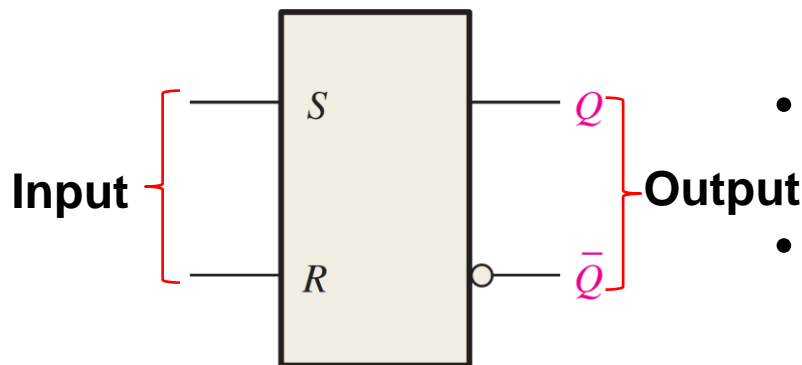


Active-High SR Latch Logic Symbol

- When $S = 0$ and $R = 0$, Q and \overline{Q} maintains the previous value.
- When $S = 0$ and $R = 1$, the latch is **RESET** ($Q = 0$).
- When $S = 1$ and $R = 0$, the latch is **SET** ($Q = 1$).
- When $S = 1$ and $R = 1$, both Q and \overline{Q} are **0**, which is **invalid**.

LATCHES

ACTIVE-HIGH SR LATCH

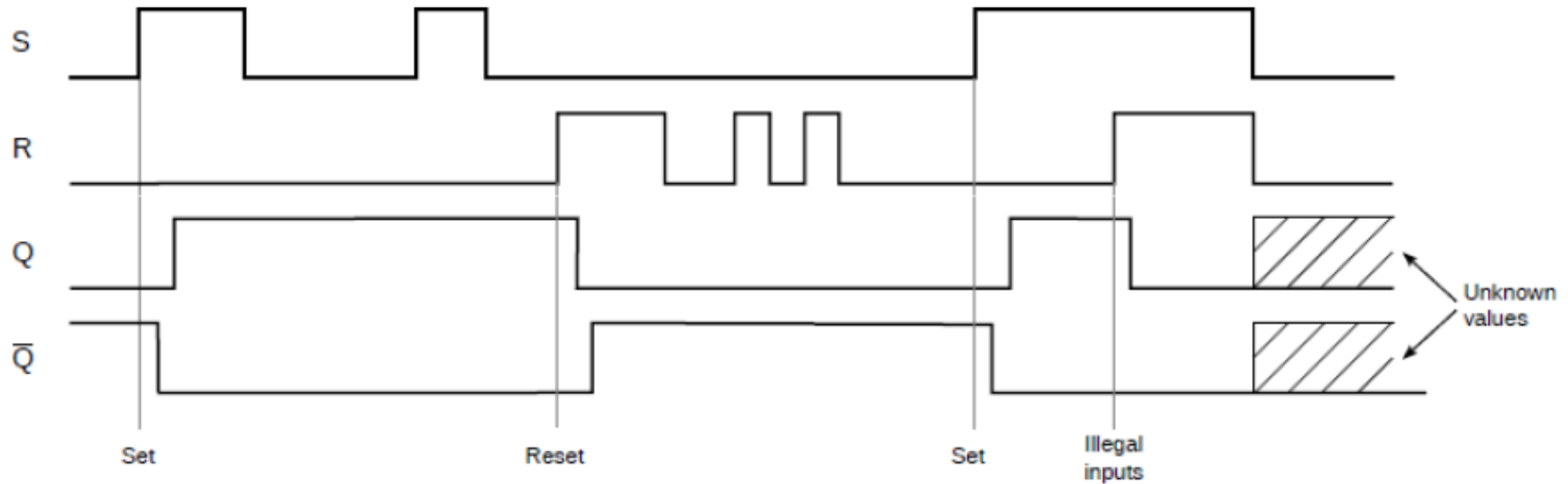


Timing Diagram for SR Latch (with propagation delay)

LATCHES


ACTIVE-LOW SR LATCH ($\overline{S}\overline{R}$ LATCH)

- To get an **Active-Low SR Latch ($\overline{S}\overline{R}$ Latch)**, NAND gates are used.

 $\overline{S}\overline{R}$ Latch Logic Circuit



 $\overline{S}\overline{R}$ Latch Logic Symbol



$\overline{S}\overline{R}$ Latch Truth Table

Inputs		Outputs		Action
\overline{S}	\overline{R}	$Q(next)$	$\overline{Q}(next)$	
0	0	1	1	FORBIDDEN
0	1	1	0	SET
1	0	0	1	RESET
1	1	Q	\overline{Q}	NO CHANGE


- When $S = 0$ and $R = 1$, the latch is **SET ($Q = 1$)**.
- When $S = 1$ and $R = 0$, the latch is **RESET ($Q = 0$)**.
- When $S = 1$ and $R = 1$, Q and \overline{Q} **maintains the previous value**.
- When $S = 0$ and $R = 0$, **both Q and \overline{Q} are 1**, which is invalid.

LATCHES

GATED SR LATCH

- **Gated SR Latch** is a SR Latch with control input, **C/EN** to enable or disable S and R inputs.


Gated SR Latch Logic Circuit

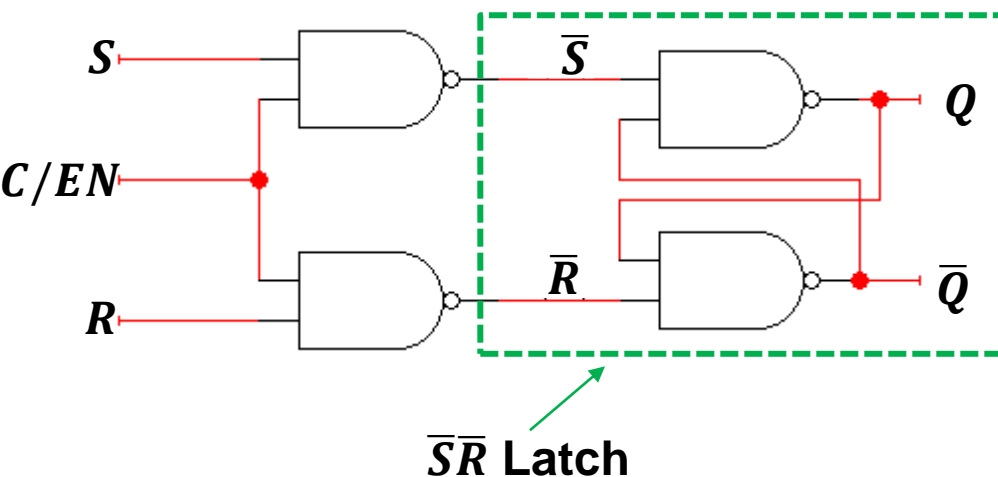

Gated SR Latch Truth Table

EN	S	R	\bar{S}	\bar{R}	Q_{next}
0	X	X	1	1	NO CHANGE
1	0	0	1	1	NO CHANGE
1	0	1	1	0	0 (RESET)
1	1	0	0	1	1 (SET)
1	1	1	0	0	FORBIDDEN

Gated SR Latch Logic Symbol

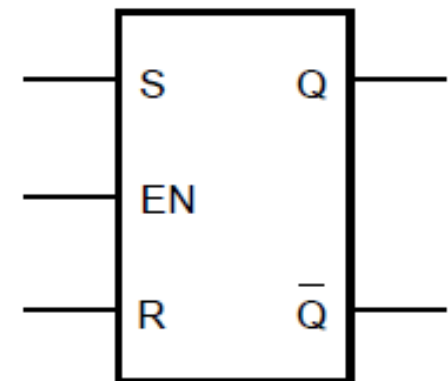


- The additional NAND gates are simply used to generate the correct inputs for the $\bar{S}\bar{R}$ Latch.
- The control input acts just like an enable.

LATCHES

GATED SR LATCH

 Example


Draw the output Q for the gated SR Latch with Q is initially LOW.



LATCHES

GATED D LATCH

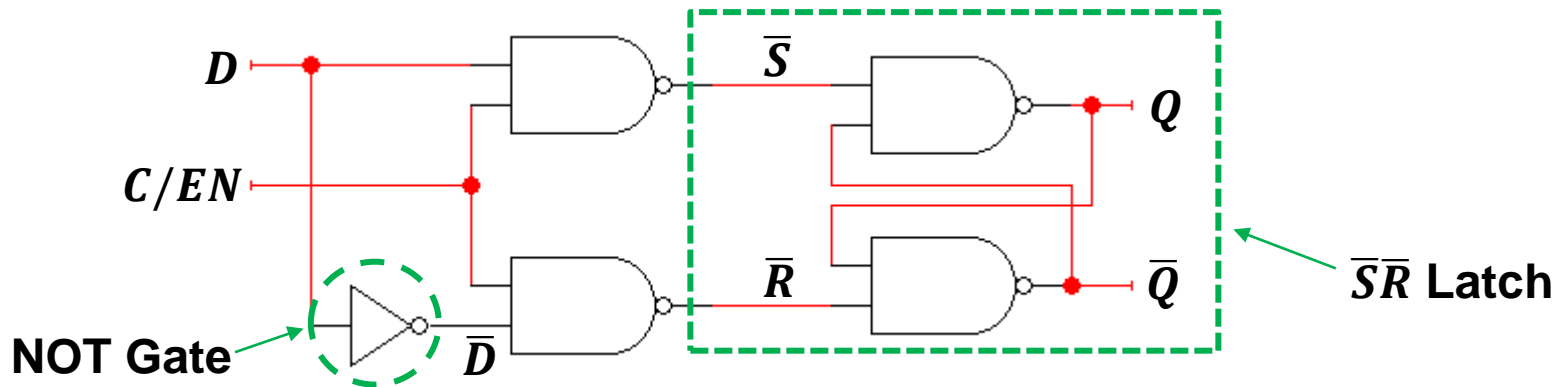- **Gated D Latch** is based on an $\bar{S}\bar{R}$ Latch. The additional gates generate the \bar{S} and \bar{R} signals, based on inputs **D (“data”)** and **EN (“enable”)**.
 - When $EN = 0$, \bar{S} and \bar{R} are both 1, so the state Q does not change.
 - When $EN = 1$, the latch output Q will equal the input D.
- No more messing with one input for set and another input for reset!




- Also, this latch has no **“bad”** input combinations to avoid. Any of the four possible assignments to C and D are valid.

LATCHES

GATED D LATCH

Example


Draw the output Q for the Gated D Latch.

 

LATCHES

GATED JK LATCH

 - **Gated JK Latch** is another way to improve the gated SR Latch.
- The input of **J** and **K** performs exactly the same as **S** and **R**, with the **exception** of the condition of **$JK = 11$** .
- When J and K are both HIGH ($JK = 11$), the output **toggles** (switch from 0 to 1 or vice versa).




Gated JK Latch Logic Circuit

LATCHES


GATED JK LATCH

Gated JK Latch Symbol

 

Gated JK Latch Truth Table

EN	J	K	Q_{next}	Action
0	X	X	Q	NO CHANGE
1	0	0	Q	NO CHANGE
1	0	1	0	0 (RESET)
1	1	0	1	1 (SET)
1	1	1	\bar{Q}	TOGGLE

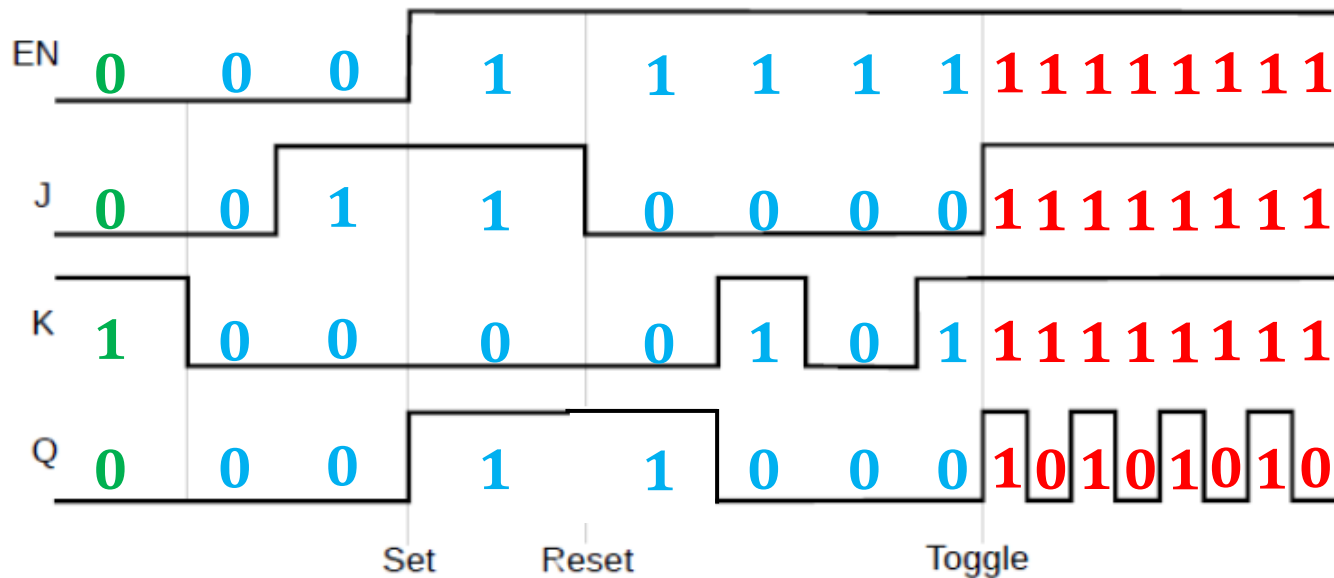


FLIP-FLOPS

FLIP-FLOPS

INTRODUCTION

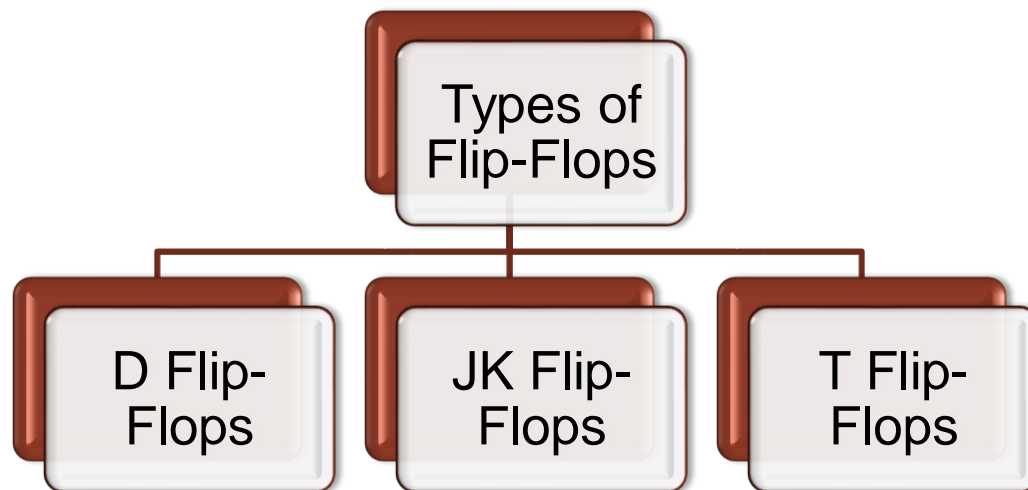
- **Flip-flops** are synchronous bistable devices.
- The term **synchronous** means that the output changes state only at a specified point on the triggering input called the **clock (CLK)**.
- This **CLK** is designated as a control input, C (in latches); that is, changes in the output occur in synchronization with the **clock**.




FLIP-FLOPS

EDGE TRIGGER

- An **edge-triggered flip-flops** change state either at the **positive edge** (rising edge) or **negative edge** (falling edge) of the clock pulse.
- It is **sensitive to its inputs only at this transition of the clock**.
- Clock inputs of flip-flops are symbolized by a triangle in logic symbols.
- **Positive edge** triggered no bubble at CLK input.
- **Negative edge** triggered has bubble at CLK input.

 

Positive edge triggered device

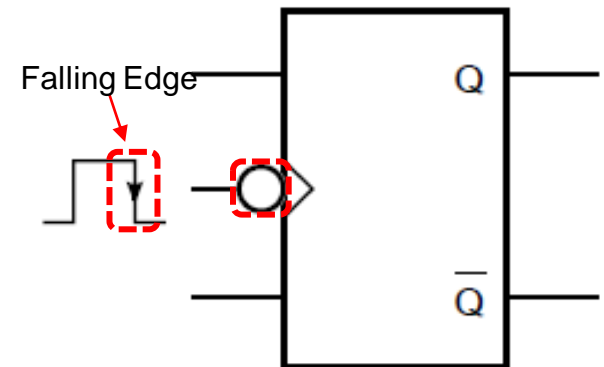


Negative edge triggered device

FLIP-FLOPS

D FLIP-FLOP

- **D flip-flop** is useful when a single data bit (**1 or 0**) is to be stored.
- It works almost the same as the D latch.
- When a clock pulse arrives, the input is transferred to the output.
- The D flip-flop can be either positive edge or negative edge triggered.
- The positive edge triggered D flip-flop, the input only valid or seen during the clock rising edge.

 Logic Symbol of Positive edge triggered D flip-flop



Characteristic Table of Positive edge triggered D flip-flop


<i>CLK</i>	<i>D</i>	<i>Q_{next}</i>	<i>Action</i>
0	X	Q	NO CHANGE
1	X	Q	NO CHANGE
↑	0	0	0 (RESET)
↑	1	1	1 (SET)

FLIP-FLOPS

D FLIP-FLOP


 
Example

Draw the output waveform of the positive edge triggered and negative edge triggered of the D flip-flop.



FLIP-FLOPS


D LATCH VS D FLIP-FLOP

 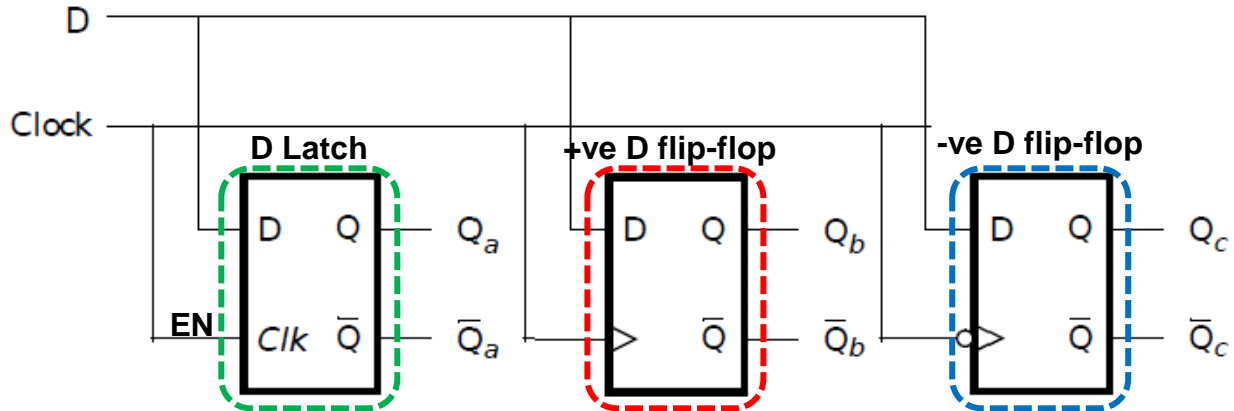

FLIP-FLOPS

T FLIP-FLOP

 - **T (toggle) flip-flop** has two inputs: a clock and a T input.
- When T is **0**, clock pulses have no effect on the output.
- When T is **1**, when a clock pulse arrives, the **output toggles**.



Logic Symbol of
Positive edge triggered
T flip-flop

Characteristic Table of Positive
edge triggered T flip-flop


<i>CLK</i>	<i>T</i>	<i>Q_{next}</i>	<i>Action</i>
0	X	<i>Q</i>	NO CHANGE
1	X	<i>Q</i>	NO CHANGE
↑	0	<i>Q</i>	NO CHANGE
↑	1	\bar{Q}	TOGGLE

FLIP-FLOPS

T FLIP-FLOP

 Example

Draw the output waveform of the positive edge triggered of the T flip-flop.




*NC: Not Change, T: Toggle

FLIP-FLOPS

JK FLIP-FLOP

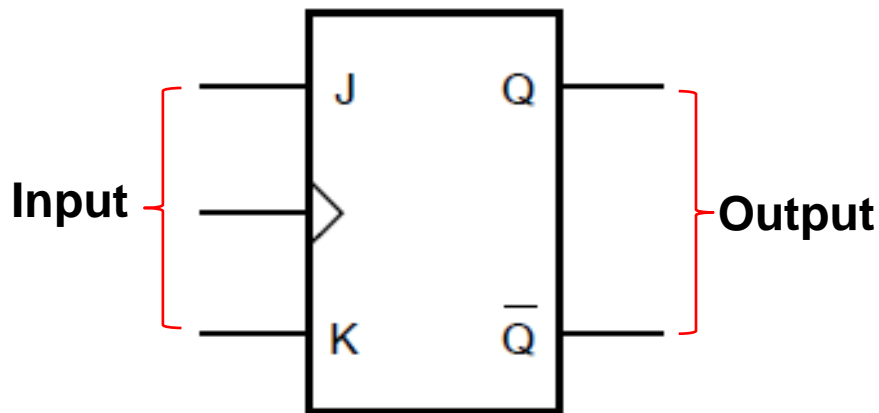- **JK flip-flop** is versatile and is widely used type of flip-flop.
- It is identical to JK Latch where the output is toggled or inverted when $JK = 11$. But the input is changes during a clock edge.



Logic Symbol of Positive edge triggered JK flip-flop

Characteristic Table of Positive edge triggered JK flip-flop


<i>CLK</i>	<i>J</i>	<i>K</i>	<i>Q_{next}</i>	<i>Action</i>
0	X	X	<i>Q</i>	NO CHANGE
1	X	X	<i>Q</i>	NO CHANGE
↑	0	0	<i>Q</i>	NO CHANGE
↑	0	1	0	RESET
↑	1	0	1	SET
↑	1	1	\bar{Q}	TOGGLE

FLIP-FLOPS

JK FLIP-FLOP

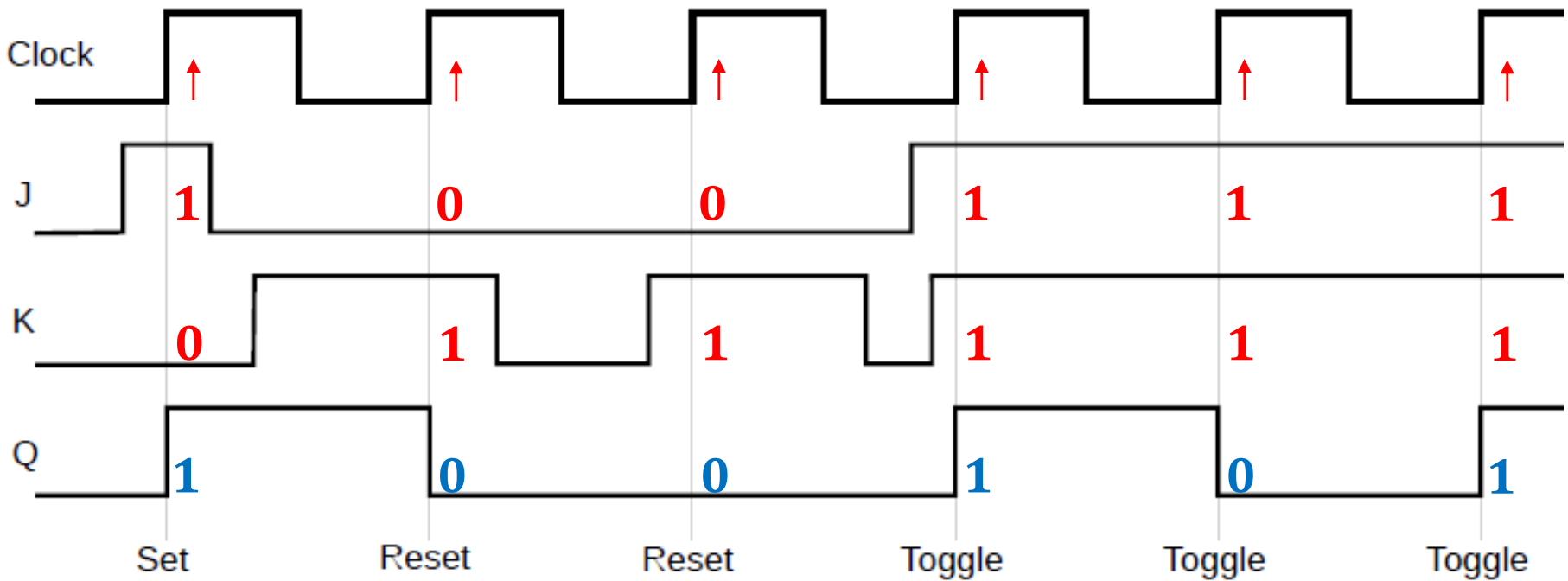Example



Draw the output waveform of the positive edge triggered of the JK flip-flop.



FLIP-FLOPS

JK FLIP-FLOP

 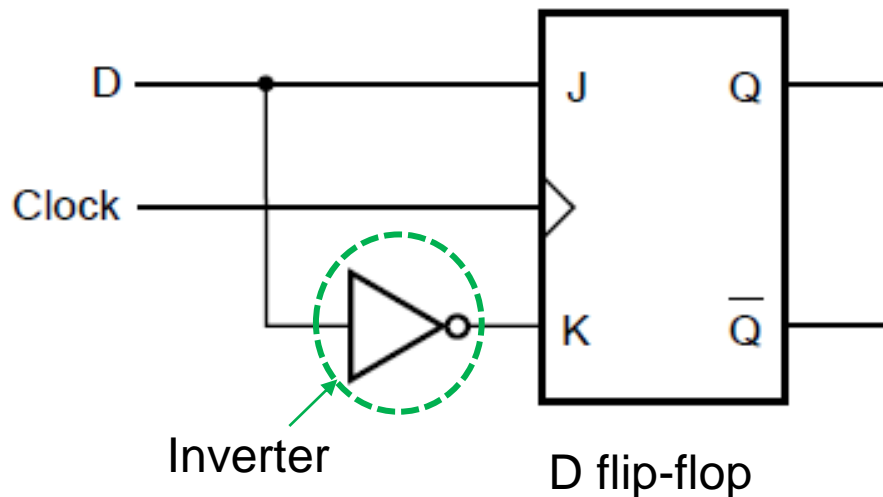- We have seen three types of flip-flops. These flip-flops can be implemented using JK flip-flop.
- To implement a **D flip-flop**, an inverter is placed between J and K inputs.




- To implement a **T flip-flop**, connect both inputs of J and K together.

FLIP-FLOPS

ASYNCHRONOUS FLIP-FLOP

- Previously, we had seen **synchronous flip-flop** such as D, T and JK flip flops.
- **Synchronous flip-flop**: Input transferred on the triggered edge of the clock (data transfer synchronously with the clock).
- **Asynchronous flip-flop**: Input effect flip-flop state (output) independent of the clock.
- The asynchronous flip-flops normally labeled by **preset** (\overline{PRE}), direct SET and **clear** (\overline{CLR}), direct RESET.

 


\overline{PRE}	\overline{CLR}	FF State	Mode
0	1	SET	Asynchronous
1	0	RESET	Asynchronous
1	1	JK	Synchronous

FLIP-FLOPS

ASYNCHRONOUS FLIP-FLOP

 Example of characteristic table for asynchronous JK flip-flop.



\overline{PRE}	\overline{CLR}	J	K	$Clock$	Q_{next}
1	1	0	0	↑	Q
1	1	0	1	↑	0
1	1	1	0	↑	1
1	1	1	1	↑	\overline{Q}
1	1	X	X	0,1	Q
0	1	X	X	X	1
1	0	X	X	X	0
0	0	X	X	X	NA


FLIP-FLOPS

ASYNCHRONOUS FLIP-FLOP

Example

Draw the output waveform for asynchronous JK flip-flop given an input timing diagram as below:

CLK pulse	\overline{PRE}	\overline{CLR}	J	K	FF State	Comment
1, 2, 3	0	1	1	1	SET	JK input - don't care
4,5,6,7	1	1	1	1	TOGGLE	Synchronous mode
8,9	1	0	1	1	RESET	JK input - don't care

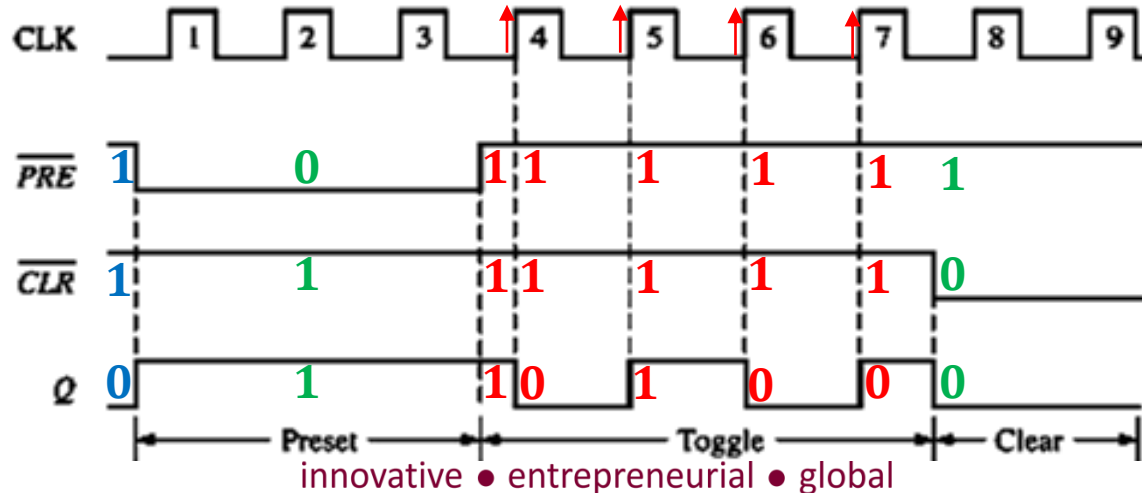


FLIP-FLOPS

FLIP FLOPS IC: 74x74 (DUAL D FLIP FLOP)

- **74x74** contains **two identical D flip-flops** that are independent of each other except sharing VCC and ground.
- The flip-flops are **positive edge triggered** and have active-low asynchronous preset and clear output.

74x74 IC Connection Diagram

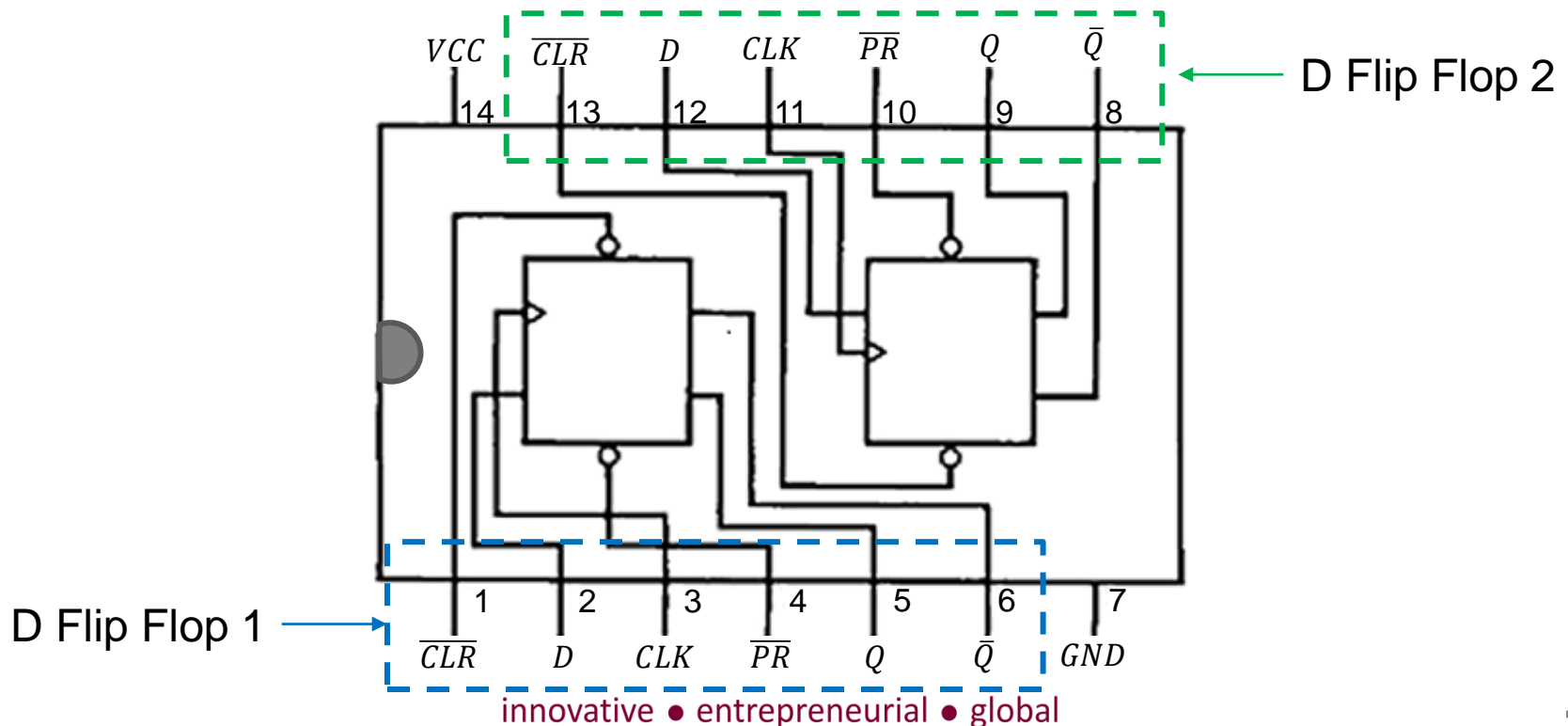


FLIP-FLOPS

FLIP FLOPS IC: 74x76 (DUAL JK FLIP FLOP)

- **74x76** contains **two identical JK flip-flops** that are independent of each other except sharing VCC and ground.
- The flip-flops are **negative edge triggered** and have active-low asynchronous preset and clear output.

74x76 IC Connection Diagram

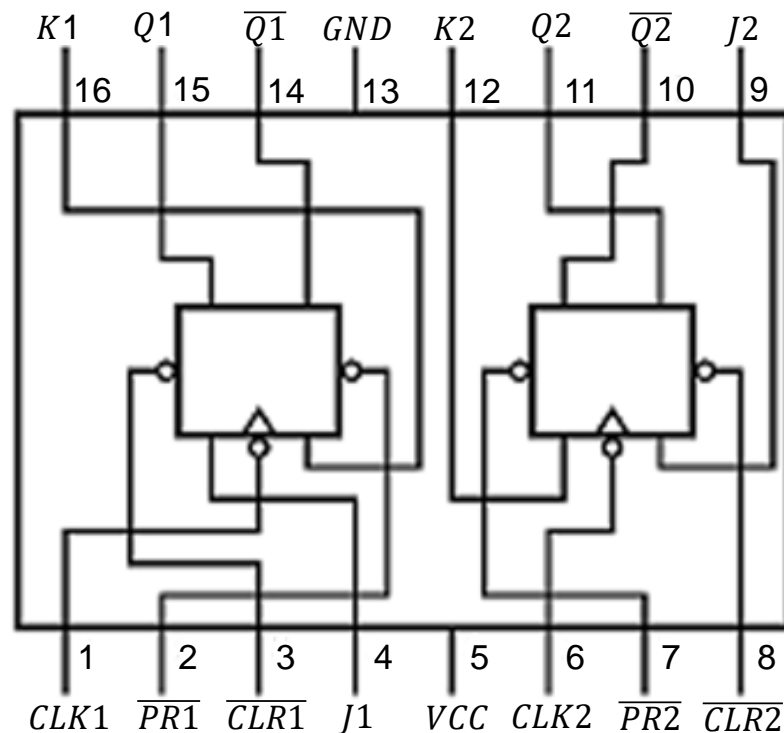

FLIP-FLOPS

FLIP FLOPS IC: 74x76 (DUAL JK FLIP FLOP)

Example

Given input waveforms that are applied to one of the JK flip-flop in 74x76. Determine the 1Q output waveform.

