

SEEE 1223

DIGITAL ELECTRONICS

CHAPTER 9:

PROGRAMMABLE LOGIC

DR. MOHD SAIFUL AZIMI BIN MAHMUD

P19a-04-03-30

School of Electrical Engineering

Faculty of Engineering

Universiti Teknologi Malaysia

019-7112948

azimi@utm.my




MEMORY: RAM & ROM

MEMORY

INTRODUCTION

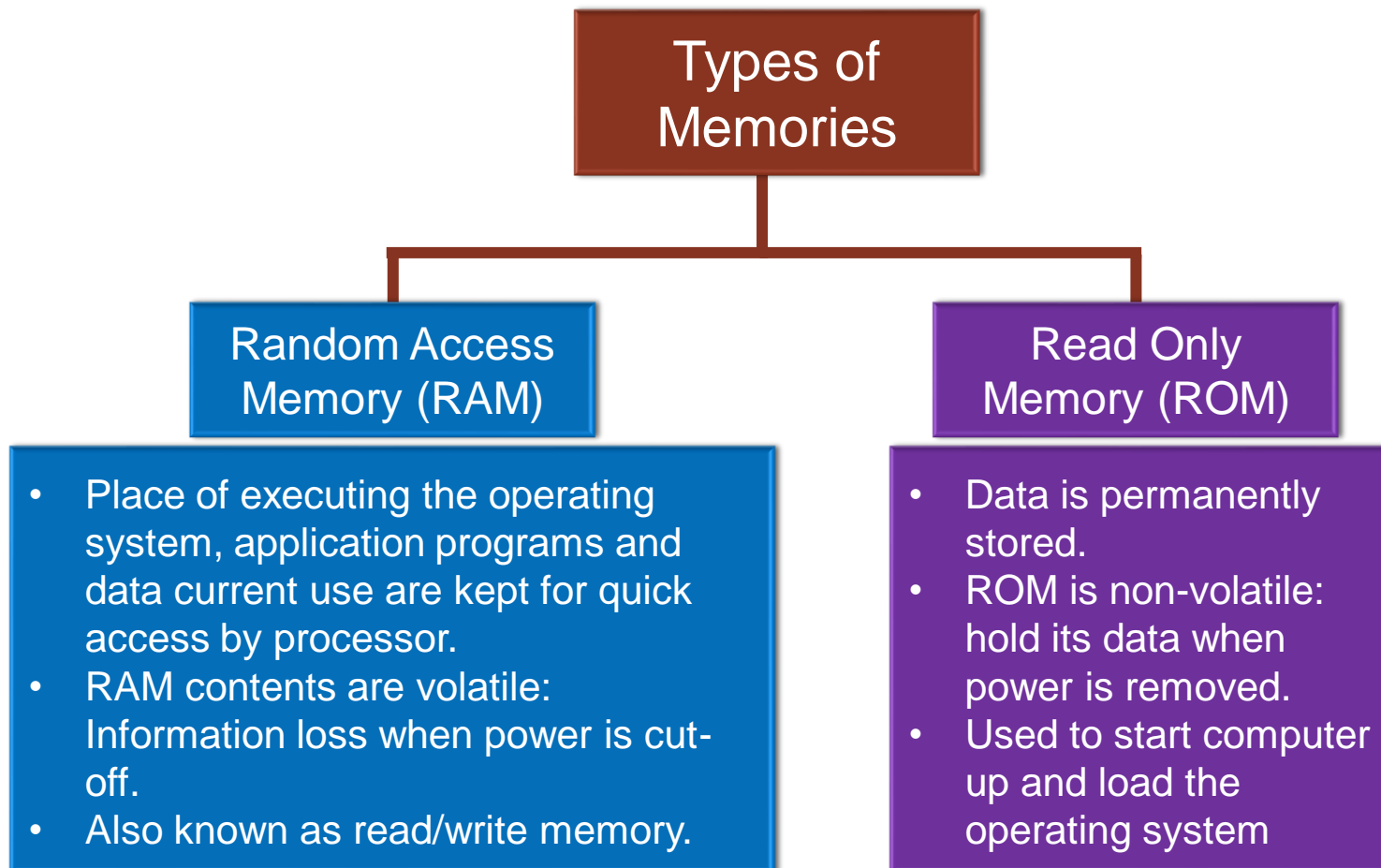- **Memories** are devices to which information is transferred for **storage** and from which information is available for **processing**.



MEMORY

RAM

- Integrated circuit RAM devices are available in two variations:
 1. **Static RAM (SRAM)**
 - Consist of internal latches that store the binary information.
 - Stored information remains valid as long as power is applied to the unit.
 - Faster.
 - High power consumption.
 - Expensive.
 2. **Dynamic RAM (DRAM)**
 - Stores binary information in the form of electric charges on capacitors provided by MOS transistors.
 - The charge of capacitors tend to decay with time, thus need to periodically recharge by refreshing the dynamic memory every few milliseconds.
 - Reduce power consumption.
 - Large number of memory words per chip.

MEMORY

ROM

- Various types of ROM:

1. Mask Programmed ROM (MROM)



- Programmed using a mask during fabrication by manufacturer.
- Advantages: high speed, high density, low unit costs.
- Disadvantage: contents are permanent.

2. Programmable ROM (PROM)

- Contents are in the form fuses which are blown during programming.
- Once blown, the fuses cannot be restored.
- PROM is one time programmable (OTP): cannot be updated and reused after initial programming.

MEMORY

ROM

 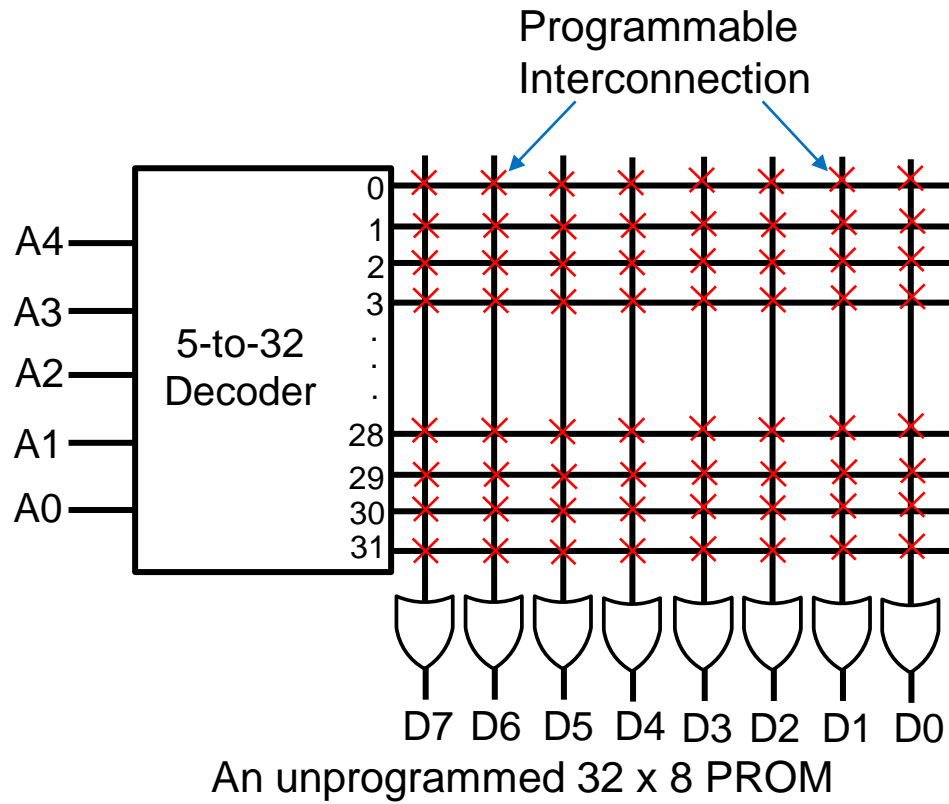

MEMORY

ROM

- Various types of ROM (cont.):

3. Erasable Programmable ROM (EPROM)

- Can be erased and reprogrammed many times.
- The whole chip is erased by exposure to approximately 20 minutes of intense UV light.

4. Electrically-Erasable Programmable ROM (EEPROM)

- Can be erased and reprogrammed without requiring special burning equipment.
- High costs.
- Allows only one memory word to be written or erased at any one time.

5. Flash Memory

- High speed and high density.
- Erases many locations simultaneously.
- Can only tolerate about 10000 erase operations before the device fails.

MEMORY


ROM

Example

Given the truth table of 8 x 4 ROM as follows. Find the number of programmable interconnections & implements the ROM circuit.

A2	A1	A0	D3	D2	D1	D0
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

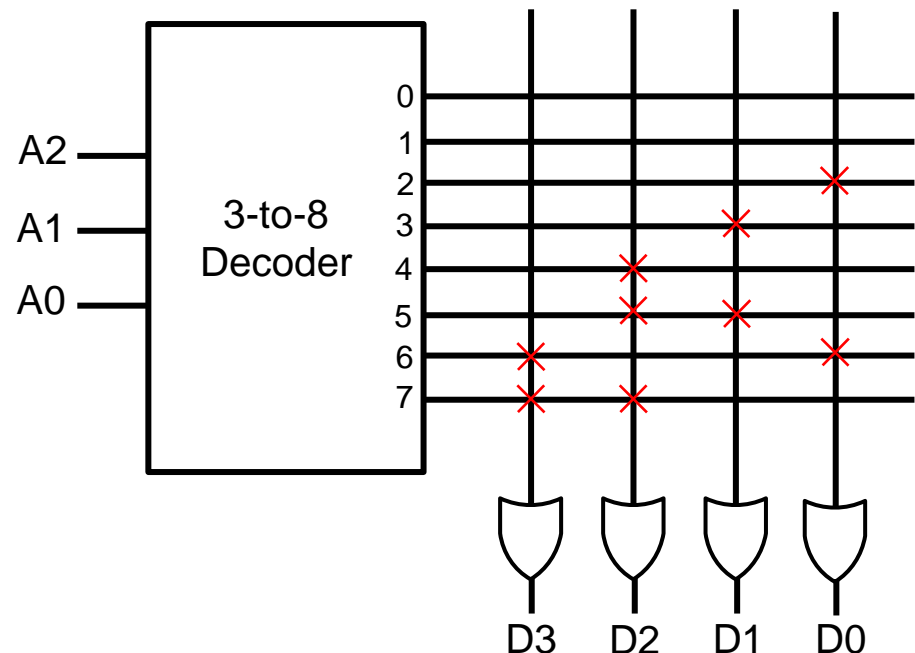Number of programmable interconnection:
 $= 8 \times 4 = 32$



PROGRAMMABLE LOGIC DEVICE: PLA & PAL


PROGRAMMABLE LOGIC DEVICE (PLD)

INTRODUCTION

- **PLD** consists of general purpose logic resources that can be connected according to the engineer's design.
- It must be programmed first before be used in circuit.
- **Advantages:** Fewer parts needed, reduce inventory cost, number of interconnections are decreases as more logic integrated into each chip, higher reliability.
- **Disadvantages:** Longer propagation delay, high power consumption.
- Example of PLD are:
 - **ROM**
 - **PLA**
 - **PAL**
 - **GAL**

PROGRAMMABLE LOGIC DEVICE (PLD)

INTRODUCTION

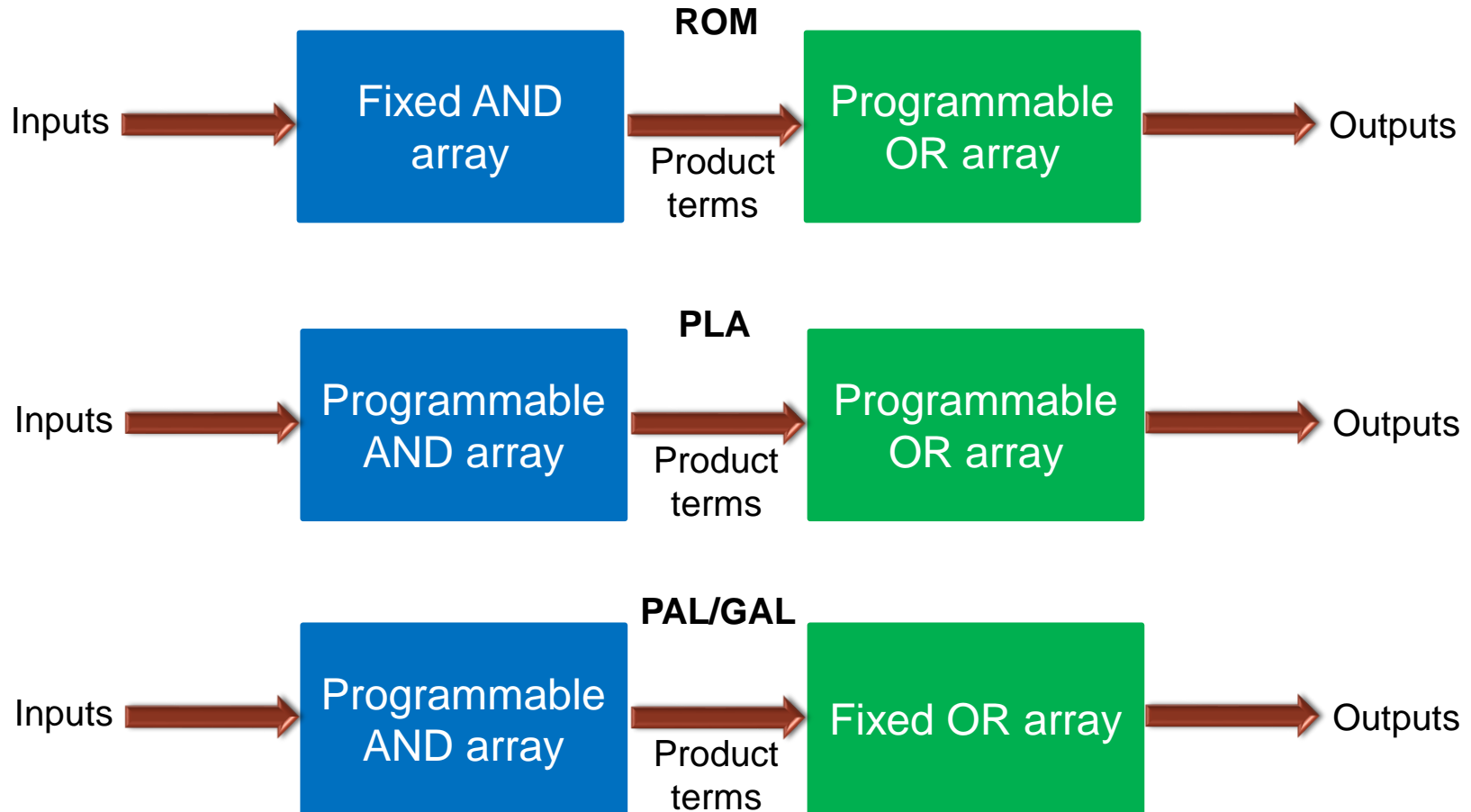

Three configurations of SPLDs
innovative • entrepreneurial • global


PROGRAMMABLE LOGIC DEVICE (PLD)

PLA

- **Programmable Logic Array (PLA)** consists of programmable AND and OR arrays.
 - ❖ **Advantageous when**
 - Relatively few unique minterm combinations.
 - Many minterms are shared among the output functions.
 - ❖ **Drawbacks**
 - Expensive to manufacture.
 - Poor speed performance: Thus PAL (Programmable Array Logic) and GAL (Generic Array Logic) were introduced.

PROGRAMMABLE LOGIC DEVICE (PLD)

PLA

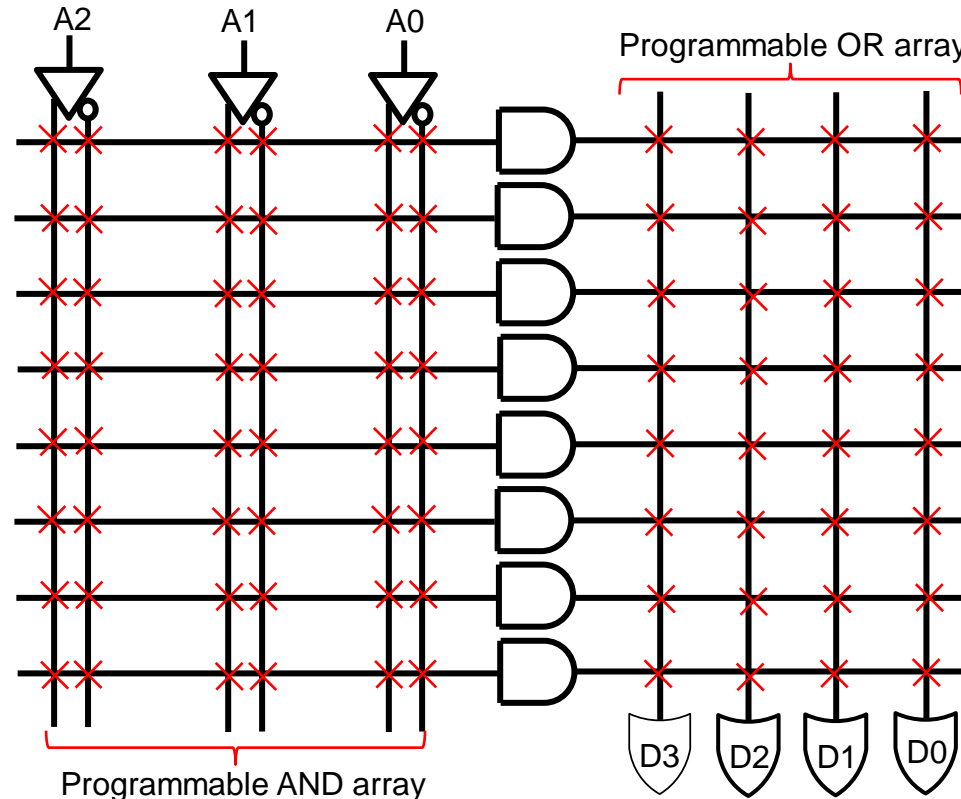

× Programmable Interconnection

PROGRAMMABLE LOGIC DEVICE (PLD)

PLA

Example


Implement the following logic function using PLA.

$$W = A + \bar{B}\bar{C}$$

$$X = A\bar{C} + AB$$

$$Y = \bar{B}\bar{C} + AB$$

$$Z = \bar{B}\bar{C} + A$$

 

PROGRAMMABLE LOGIC DEVICE (PLD)

PAL

- **Programmable Array Logic (PAL)** provides an array of programmable AND gates, but the OR connections are fixed.
- Unlike PLA, product term cannot be shared among gates.
 - ❖ **Advantageous when**
 - Cheaper and faster.


GAL

- **Generic Array Logic (GAL)** has the same basic structure as PAL (Programmable AND Gates, OR connections are fixed), but being EEPROM-based: Can be erased and reprogrammed.
 - ❖ **GAL improves upon PAL in three aspects.**
 - Can be erased.
 - Can be programmed while installed in circuit.
 - Has programmable output stage or macrocells that has feedback to enable product term to be expanded and complementary output.

PROGRAMMABLE LOGIC DEVICE (PLD)

PAL/GAL

PAL/GAL general configuration

 

- × Programmable Interconnection
- Fixed Interconnection